



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)


COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai





FUNDAMENTALS OF ELECTRICAL ENGINEERING

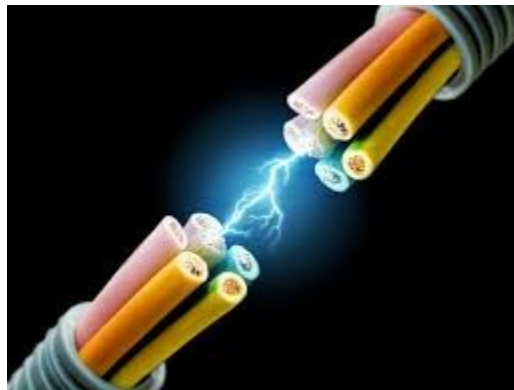

LOAD (POWER CONSUMED)

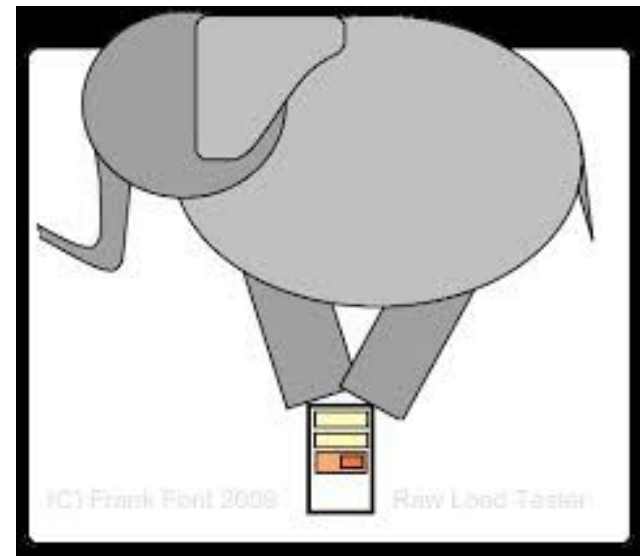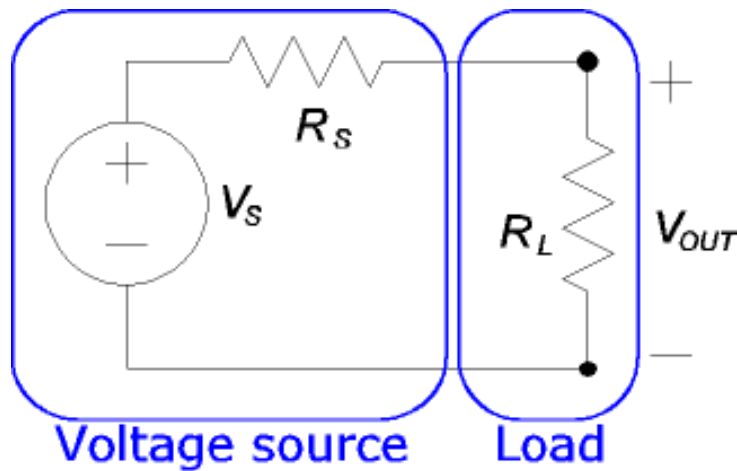- It is a any electric load on a circuit that does work.
- A device connected to the **output of a circuit**
 - **Example:** Power windows, light bulbs, motors.



CIRCUIT

- Source:

A Voltage or a Current source which delivers Electrical energy

- Sink:

A Element which consumes Electrical energy

- Circuit:

Consist of a source and a sink connected with some wires forming a closed loop

CIRCUIT DEFINITIONS

- **Node:**

Any point where 2 or more circuit elements are connected together

- **Branch:**

A circuit element between **two nodes**

- **Loop:**

Collection of branches that form a **closed path** returning to the same node without intersecting


Would This Work?




Would This Work?



Simple Circuits

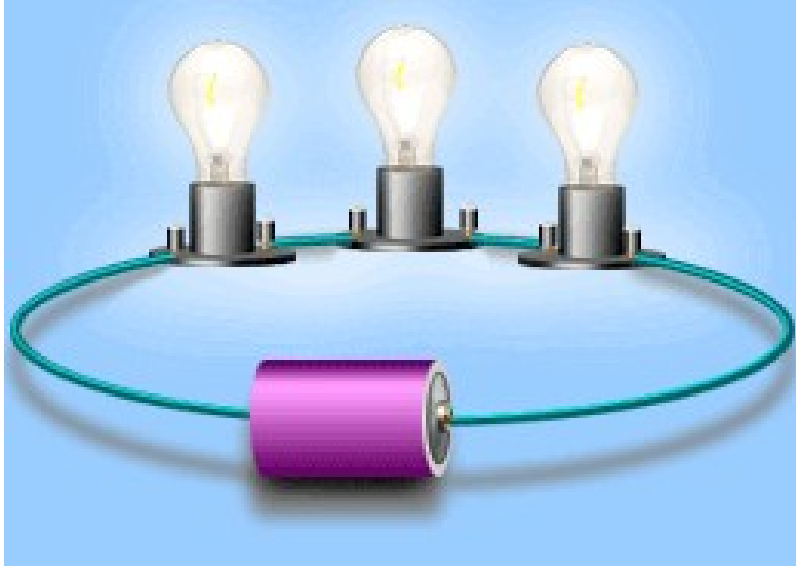

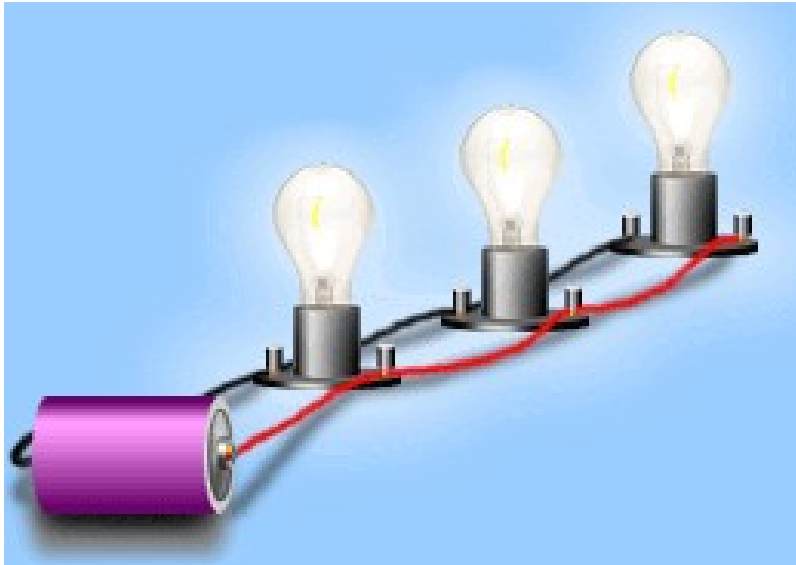- Series circuit
 - All in a row
 - **1 path** for electricity
 - 1 light goes out and the circuit is broken




- Parallel circuit
 - **Many paths** for electricity
 - 1 light goes out and the others stay on

DIFFERENT TYPES OF CIRCUIT


SERIES CIRCUIT

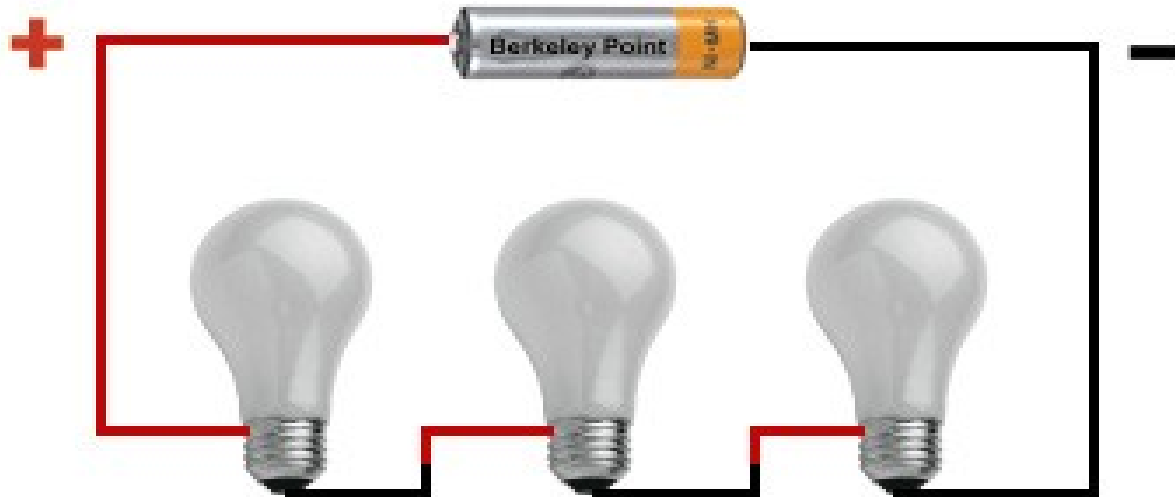- One pathway for current to flow.
- Example: Old Christmas lights




PARALLEL CIRCUIT

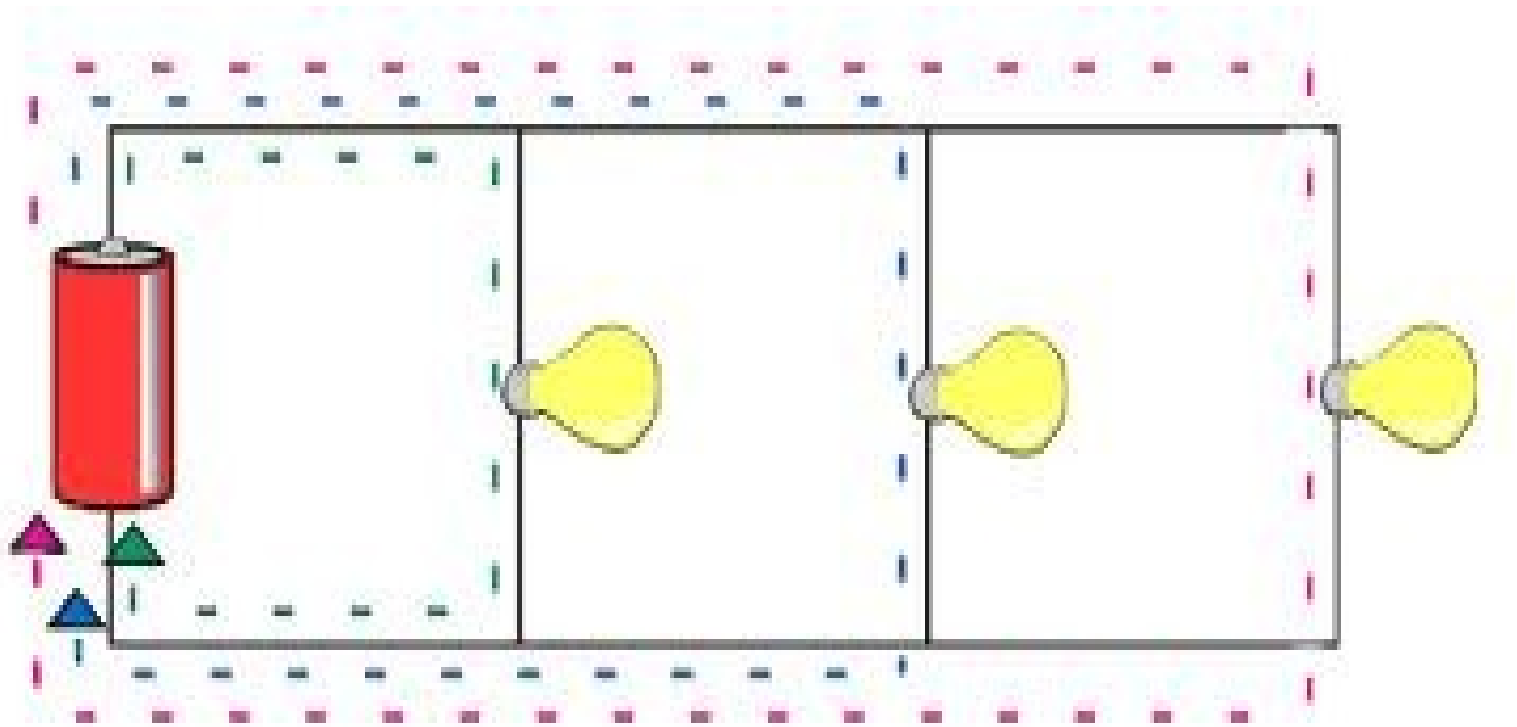- More than one path way for current to flow.
- Used in most **electrical vehicle** circuits.




SERIES RESISTANCE CIRCUIT

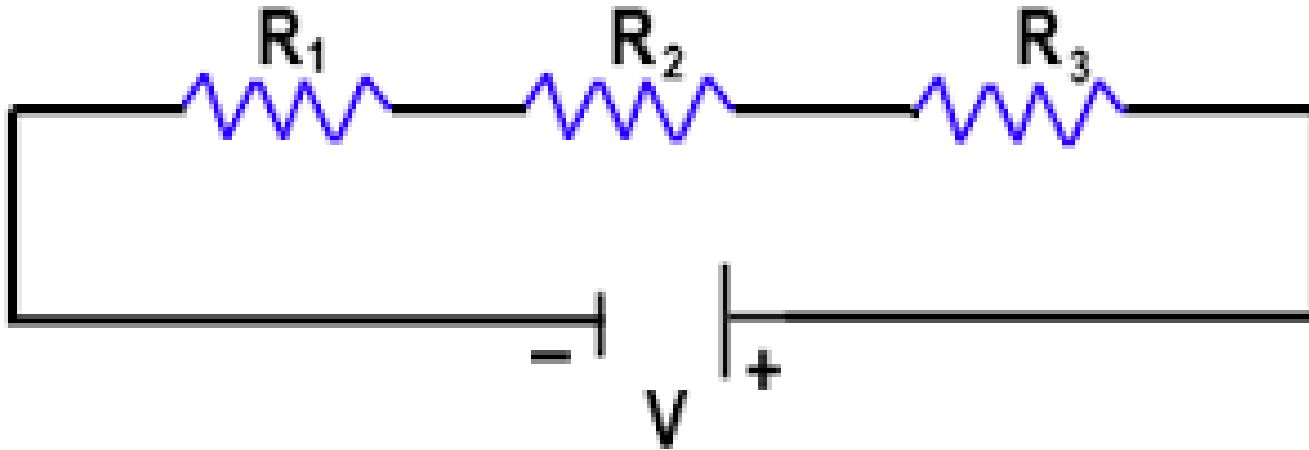

$$R_{\text{total}} = R_1 + R_2 + R_3 \dots$$

PARALLEL RESISTANCE CIRCUIT

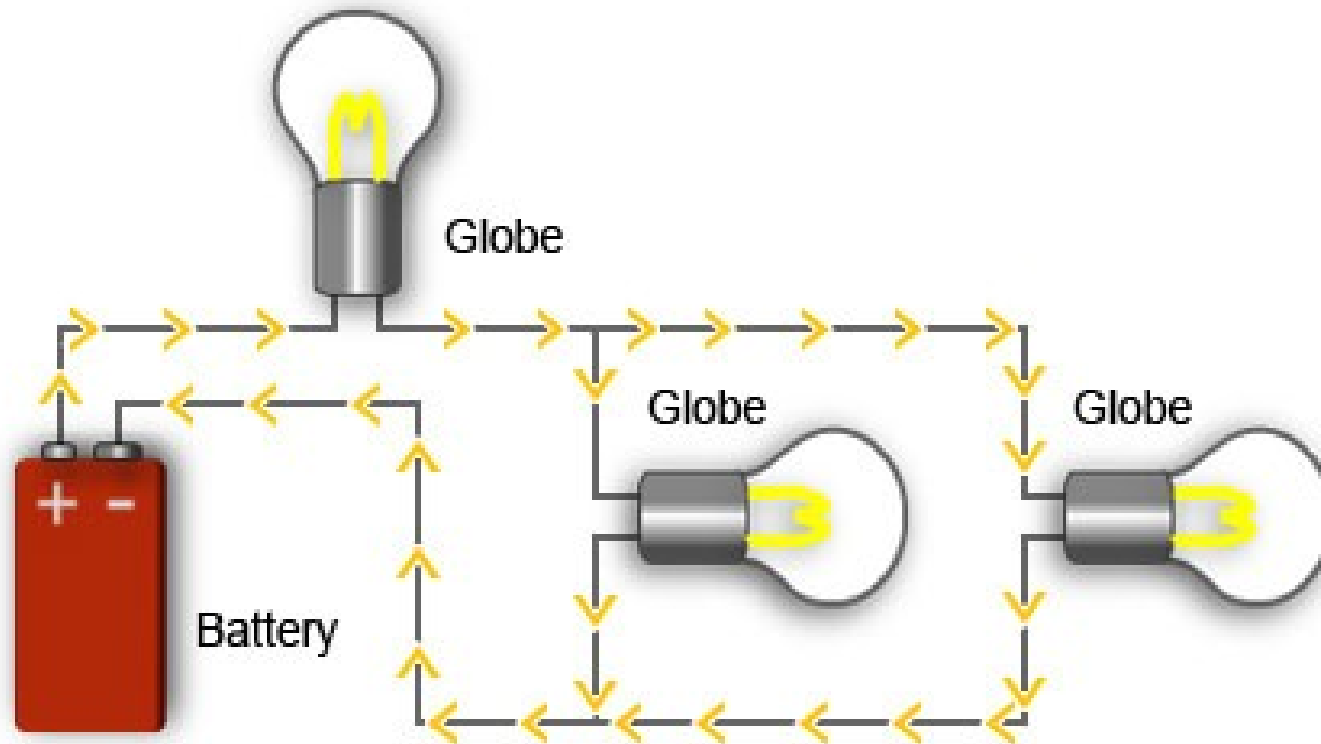


$$\frac{1}{R_{\text{TOT}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots \text{etc.}$$

$$R_{\text{TOT}} = \frac{R_1 \times R_2}{(R_1 + R_2)}$$


EXAMPLE

- Three nodes

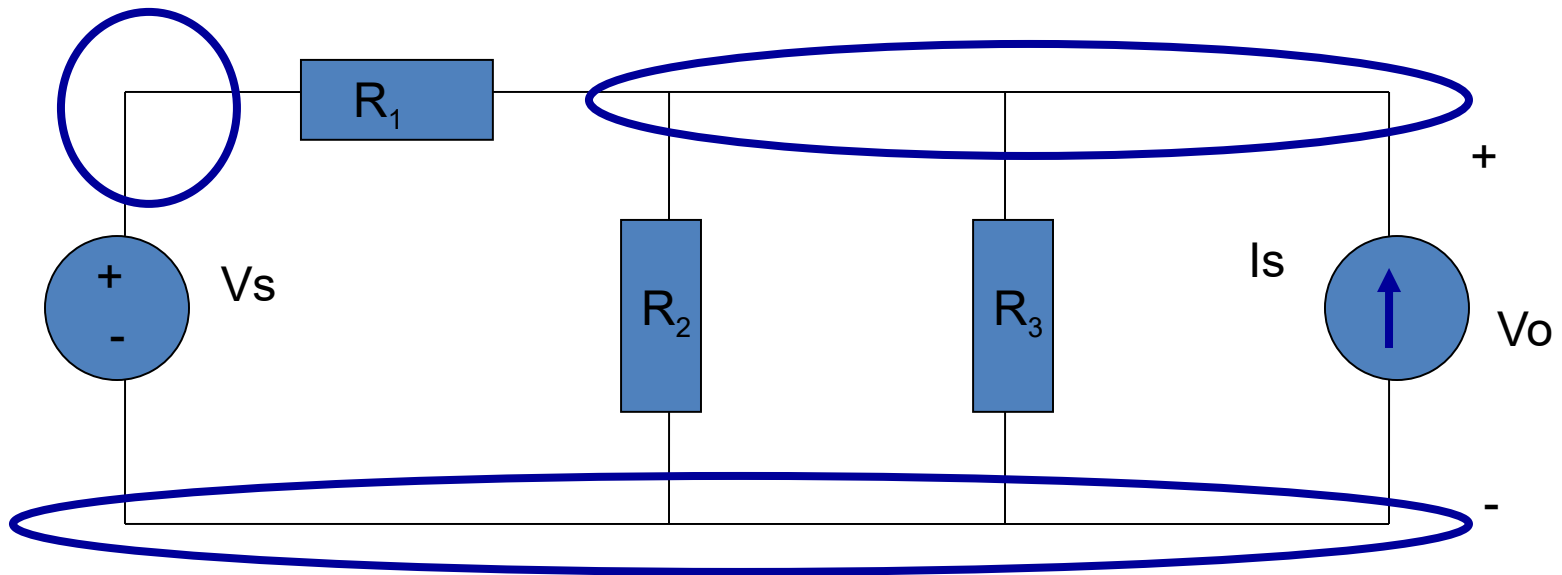


EXAMPLE

- 5 Branches

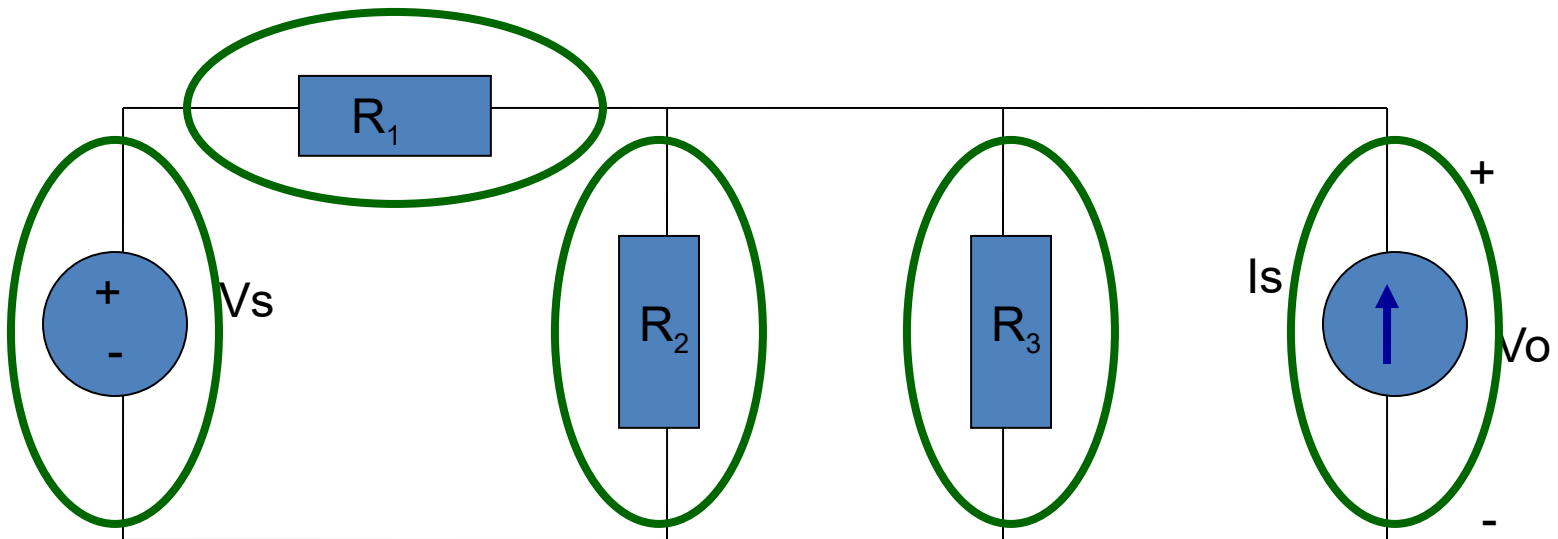

Example

- Three Loops, if starting at node A

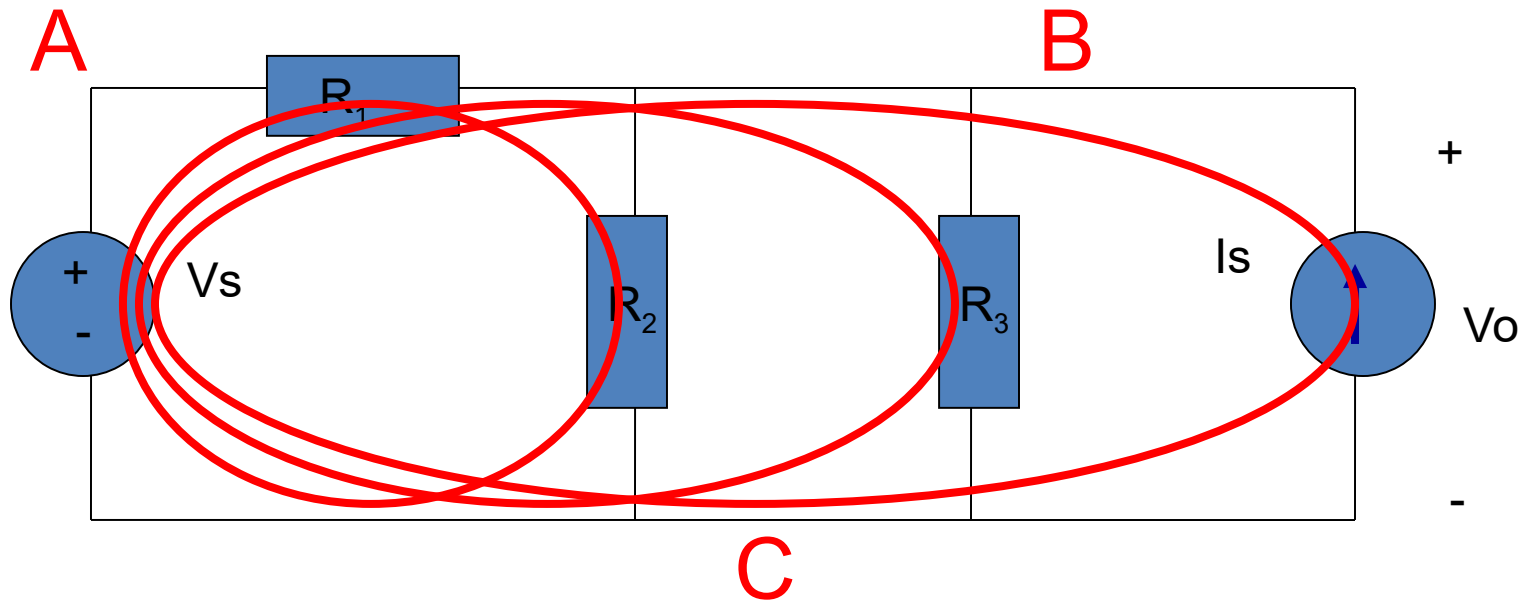

AC FUNDAMENTALS

PARAMETER VALUES:


- Instantaneous (e, i)
- Peak (V_m, I_m)
- Average (V_{ave}, I_{ave})
- RMS (V, I or V_{rms}, I_{rms})

Parameters V and I are in sine wave.

ROOT MEAN SQUARE (RMS)

Definition:

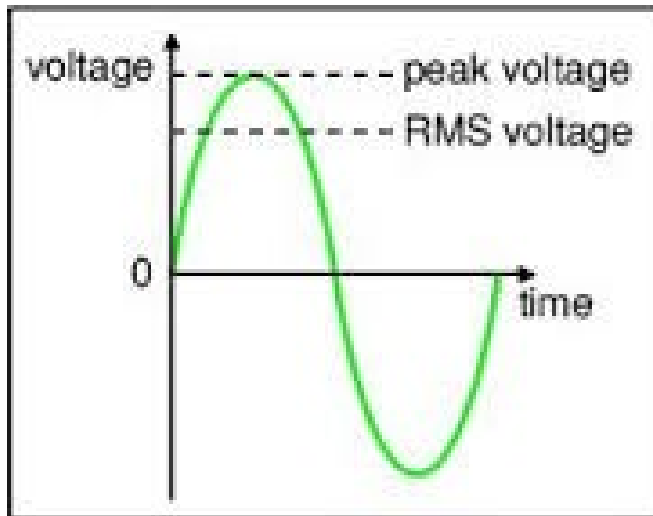The RMS value of a set of values (or a continuous-time waveform) is the **square root** of the arithmetic mean of the squares of the original values.



$$rms = \frac{V_{peak}}{\sqrt{2}} \text{ (for an undistorted sine wave)}$$
$$rms = \frac{V_{peak}}{\sqrt{3}} \text{ (for an undistorted triangle wave)}$$
$$rms = \frac{V_{peak}}{1} \text{ (for a symmetrical square wave)}$$

POWER

- The instantaneous **power** dissipated in a component is a **product of** the instantaneous **voltage** and the instantaneous **current**

$$p = vi$$

- In a **resistive circuit** the voltage and current are in **phase** – calculation of **p is straightforward**
- In **reactive circuits**, there will normally be some phase **shift between v and i** , and calculating the power becomes more complicated

1. POWER IN RESISTOR

- Suppose a voltage $v = V_p \sin \omega t$ is applied across a resistance R . The resultant current i will be

$$i = \frac{v}{R} = \frac{V_p \sin \omega t}{R} = I_p \sin \omega t$$

- The result power p will be


$$p = vi = V_p \sin \omega t \times I_p \sin \omega t = V_p I_p (\sin^2 \omega t) = V_p I_p \left(\frac{1 - \cos 2\omega t}{2} \right)$$

- The average value of $(1 - \cos 2\omega t)$ is 1, so

$$\text{Average Power } P = \frac{1}{2} V_p I_p = \frac{V_p}{\sqrt{2}} \times \frac{I_p}{\sqrt{2}} = VI$$

where V and I are the **RMS voltage and current**

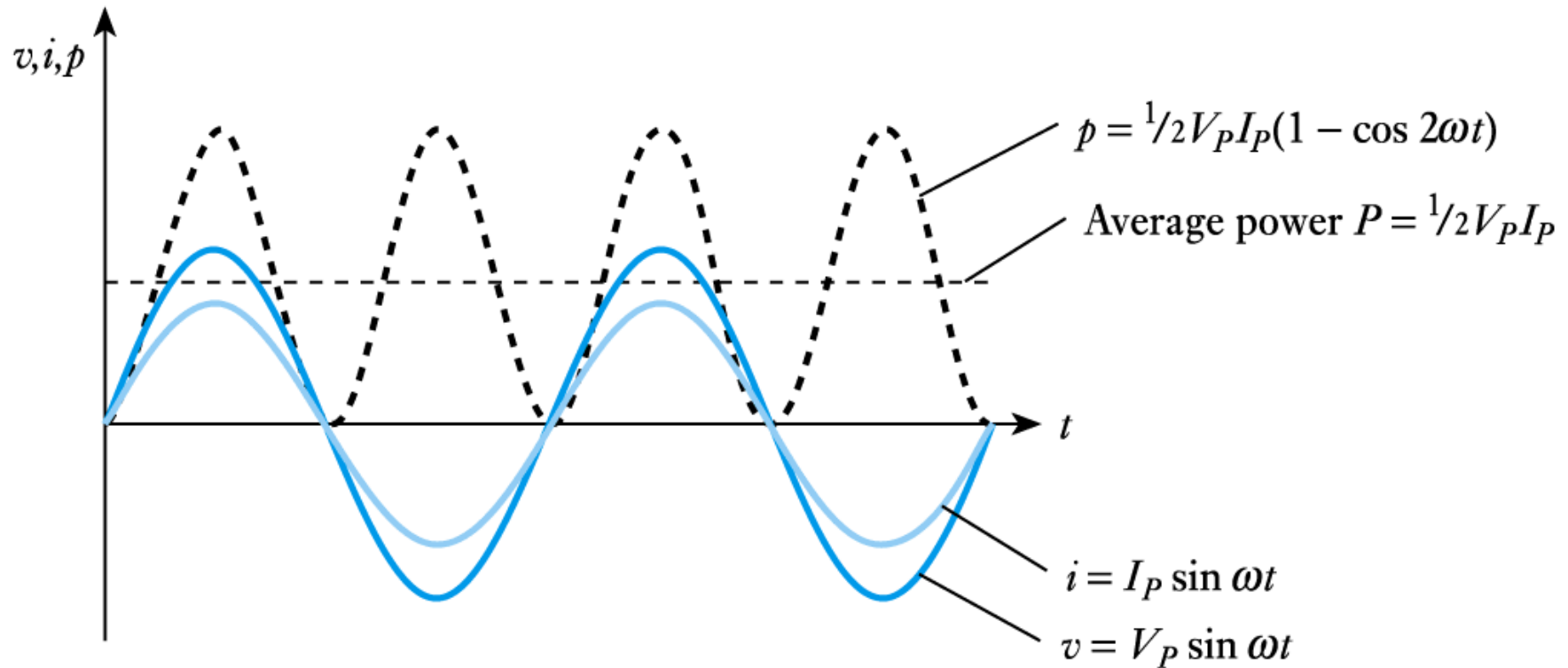
RELATIONSHIP BETWEEN V , I AND P IN A RESISTOR



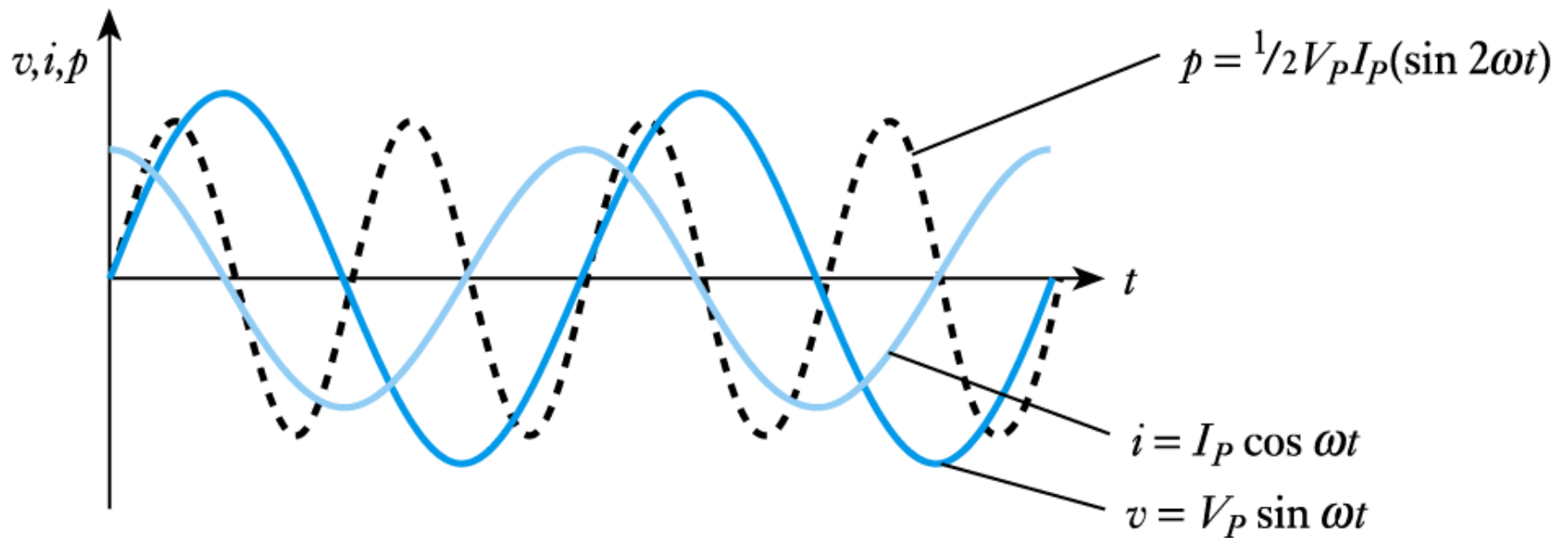2.POWER IN CAPACITORS

- For capacitors we know that the current leads the voltage by 90° .
- Therefore, if a voltage $v = V_p \sin \omega t$ is applied across a capacitance C , the current will be given by $i = I_p \cos \omega t$
- Then
$$\begin{aligned} p &= vi \\ &= V_P \sin \omega t \times I_P \cos \omega t \\ &= V_P I_P (\sin \omega t \times \cos \omega t) \\ &= V_P I_P \left(\frac{\sin 2\omega t}{2} \right) \end{aligned}$$

RELATIONSHIP BETWEEN V , I AND P IN A CAPACITOR




3.POWER IN INDUCTORS

- For inductors we know that the **current lags the voltage by 90°** .
- Therefore, if a voltage $v = V_p \sin \omega t$ is applied across an inductance L , the current will be given by $i = -I_p \cos \omega t$


- Then
$$\begin{aligned} p &= vi \\ &= V_p \sin \omega t \times -I_p \cos \omega t \\ &= -V_p I_p (\sin \omega t \times \cos \omega t) \\ &= -V_p I_p \left(\frac{\sin 2\omega t}{2} \right) \end{aligned}$$

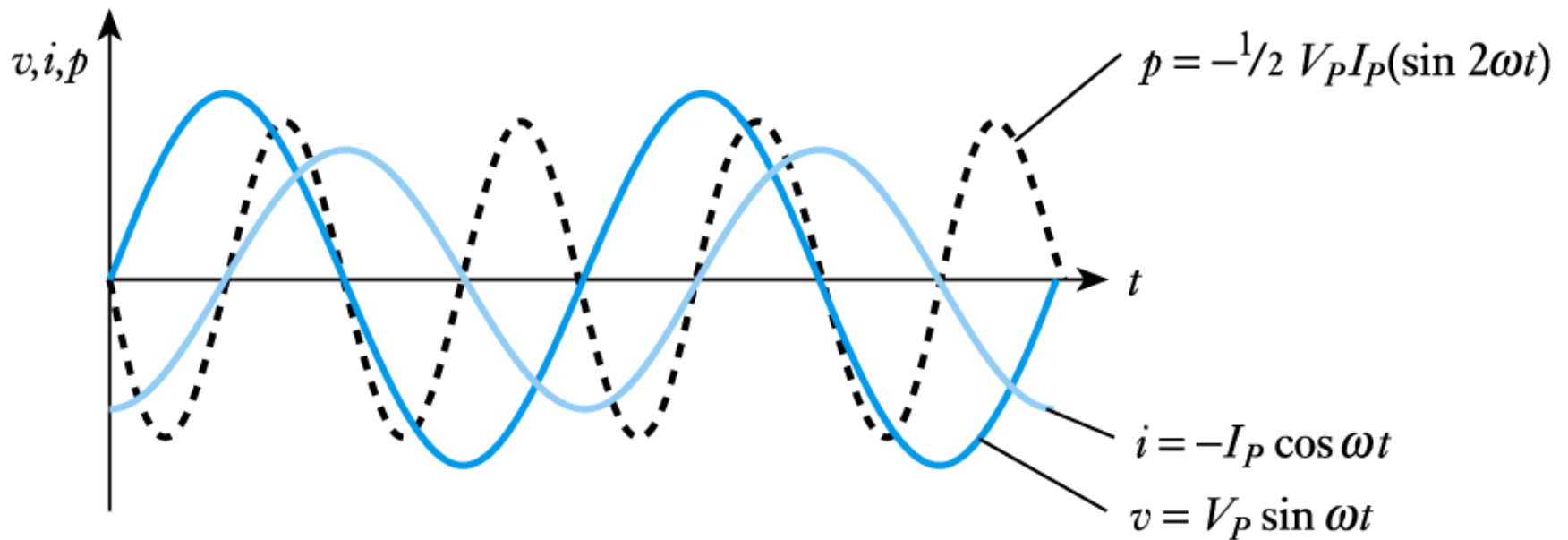RELATIONSHIP BETWEEN V , I AND P IN AN INDUCTOR



ACTIVE AND REACTIVE POWER

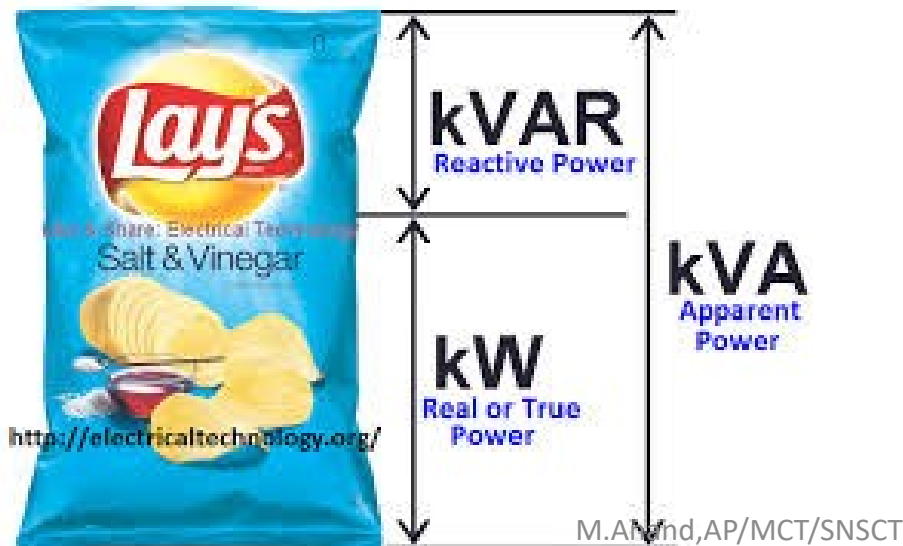- When a circuit has resistive and reactive parts, the resultant power has 2 parts:
 - The first is *dissipated* in the resistive element. This is the **active power, P**
 - The second is *stored and returned* by the reactive element. This is the **reactive power, Q** , which has units of **volt amperes reactive** or **var**



POWERS AND UNITS

Active Power $P = VI \cos \phi$ watts


Reactive Power $Q = VI \sin \phi$ var

Apparent Power $S = VI$ VA

$$S^2 = P^2 + Q^2$$

POWER TRIANGLE

The Power Triangle:

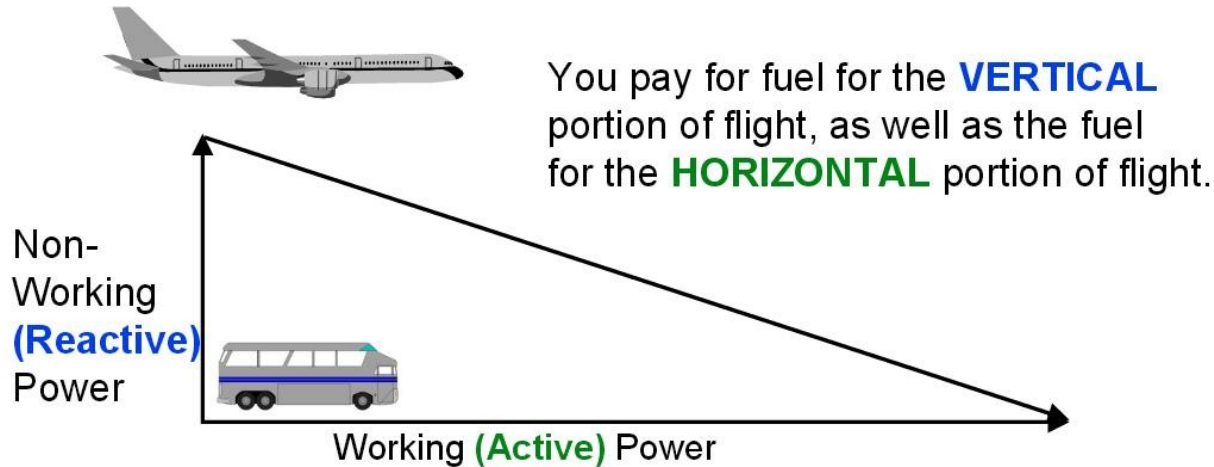

- Power Factor is the ratio of **Active Power** to **Total Power**:

$$\begin{aligned} \text{Power Factor} &= \frac{\text{Active (Real) Power}}{\text{Total Power}} \\ &= \frac{\text{kW}}{\text{kVA}} \\ &= \text{Cosine } (\theta) \end{aligned}$$

A small right-angled triangle is shown to the left of the equations. The horizontal base is labeled 'Active Power (kW)'. The vertical side is labeled 'Reactive Power'. The hypotenuse is labeled 'Total Power (kVA)'. The angle between the base and the hypotenuse is labeled with the Greek letter phi (ϕ).

- Power Factor is a measure of efficiency (Output/Input)

POWER FACTOR

Definition:

It is the ratio of the **real power** flowing to the load, to the **apparent power** in the circuit (or) the cosine angle of voltage and current

- **Real power** is the capacity of the circuit for performing work in a particular time.
- **Apparent power** is the product of the current and voltage of the circuit

THANK YOU...