



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution

*Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai*



DEPARTMENT OF MECHATRONICS

16MC302 – INDUSTRIAL ELECTRONICS & APPLICATION *III YEAR V SEM*

UNIT 1 – INTRODUCTION TO POWER ELECTRONICS

TOPIC – TRIAC

Mr. M.Anand., M.E.,(Ph.D.,)

ASSISTANT PROFESSOR,

DEPARTMENT OF MECHATRONICS,

SNSCT, Coimbatore.





APPLICATION








TRIAC

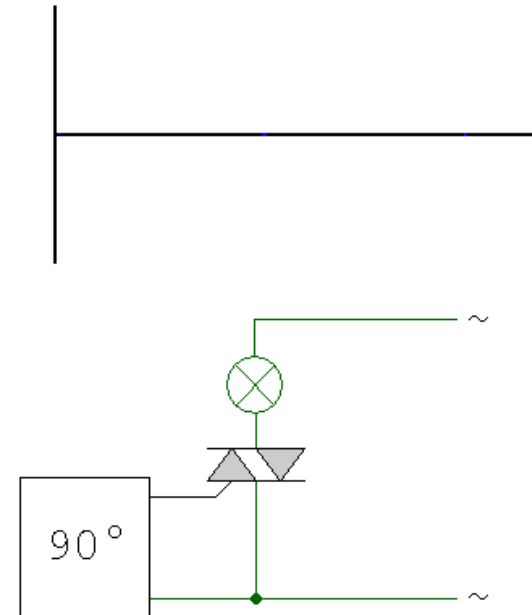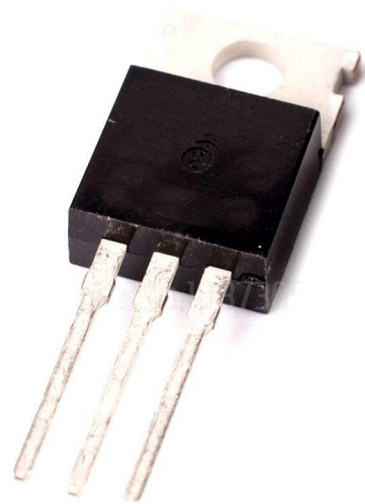TRIAC (triode for alternating current) is a generic trademark for a three terminal electronic component that conducts current in either direction when triggered..






SYMBOL

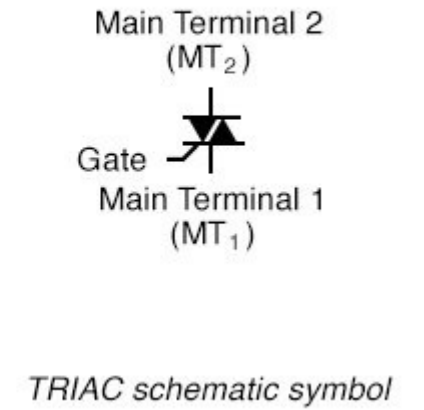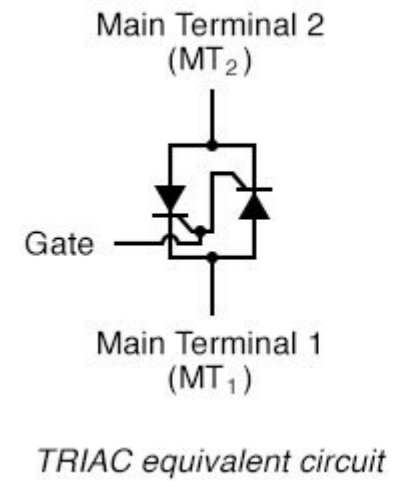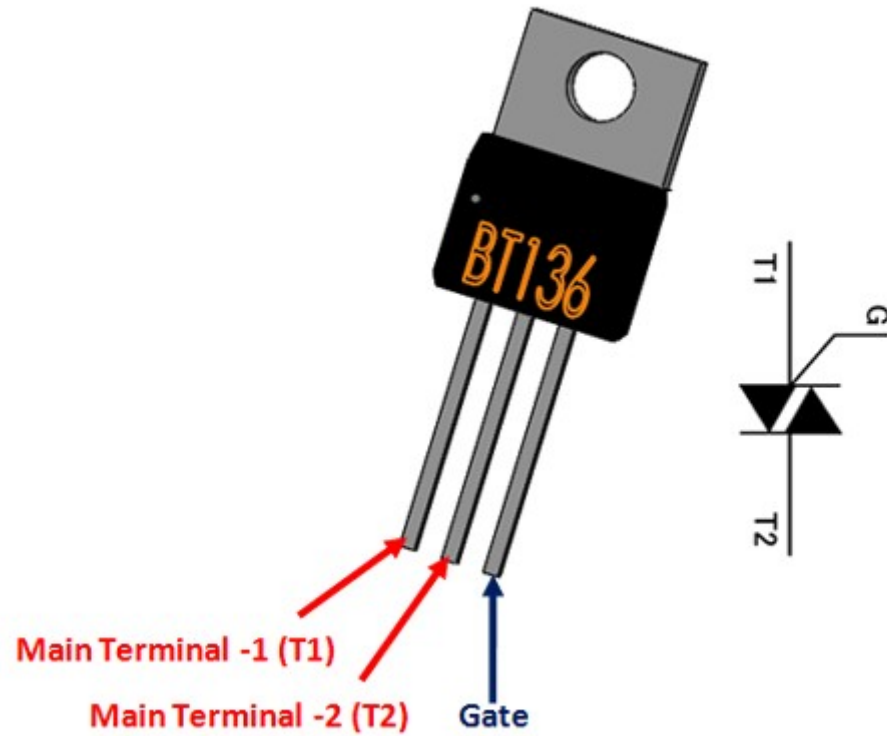




LAYER

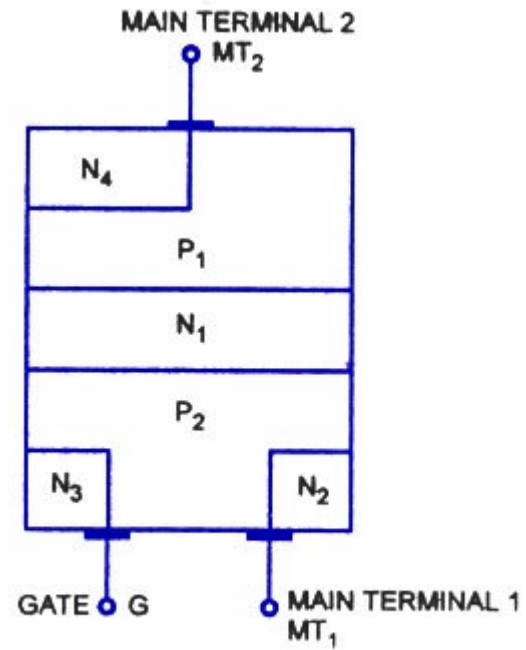


Basic Structure

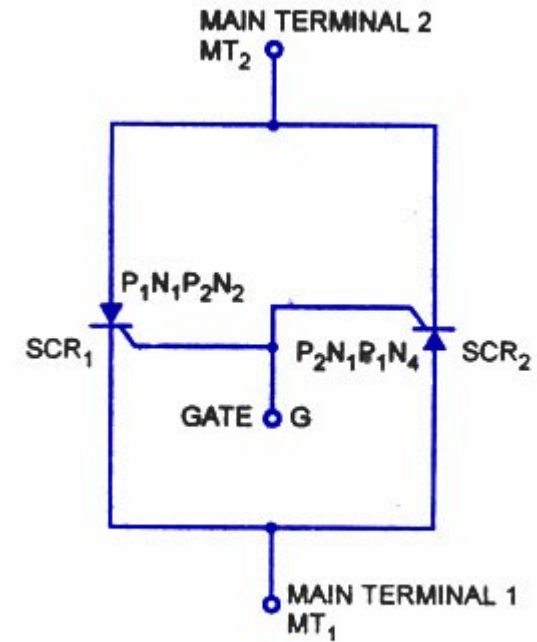

Electrical Equivalent Circuit



CIRCUIT DIAGRAM


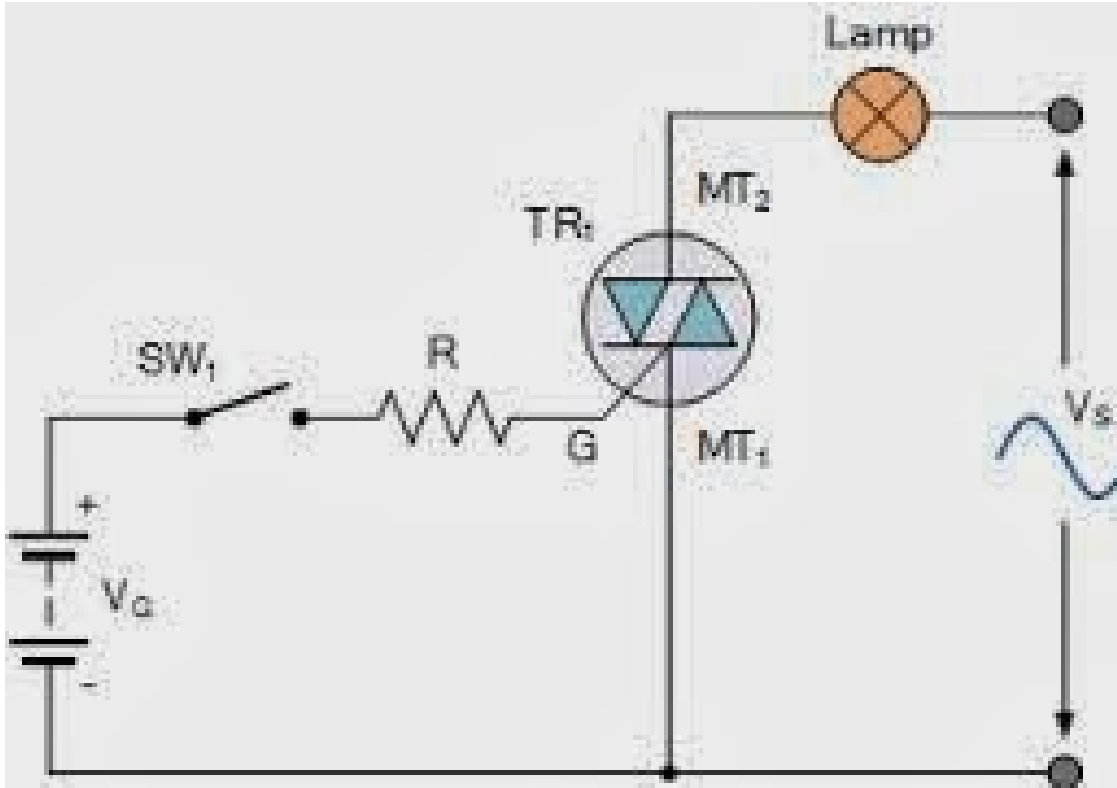


https://www.youtube.com/watch?v=-A_Mi-Xncqg






CHARACTERISTIC DIAGRAM

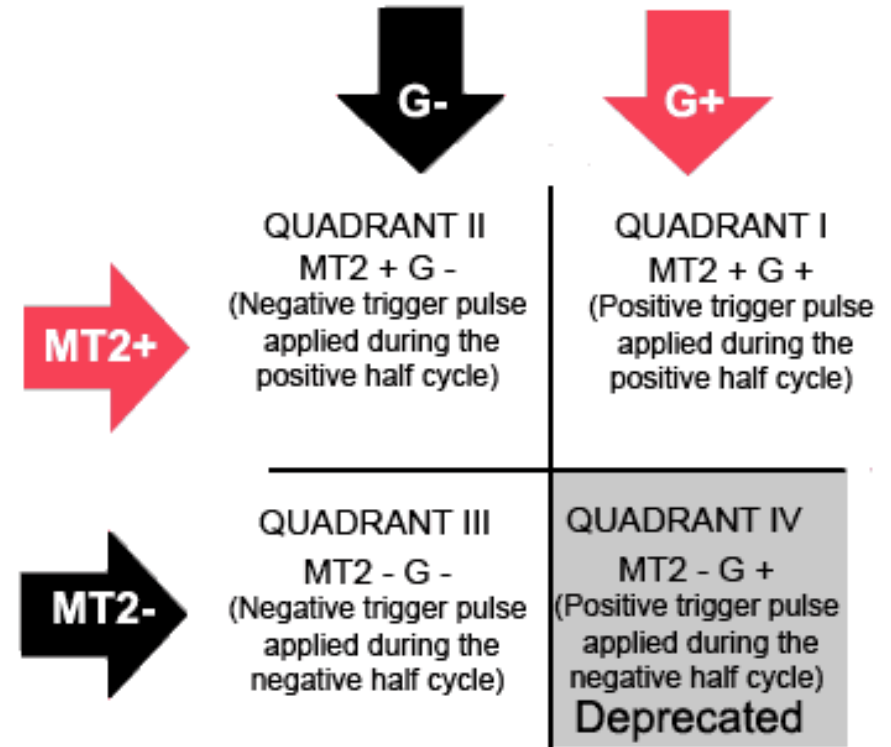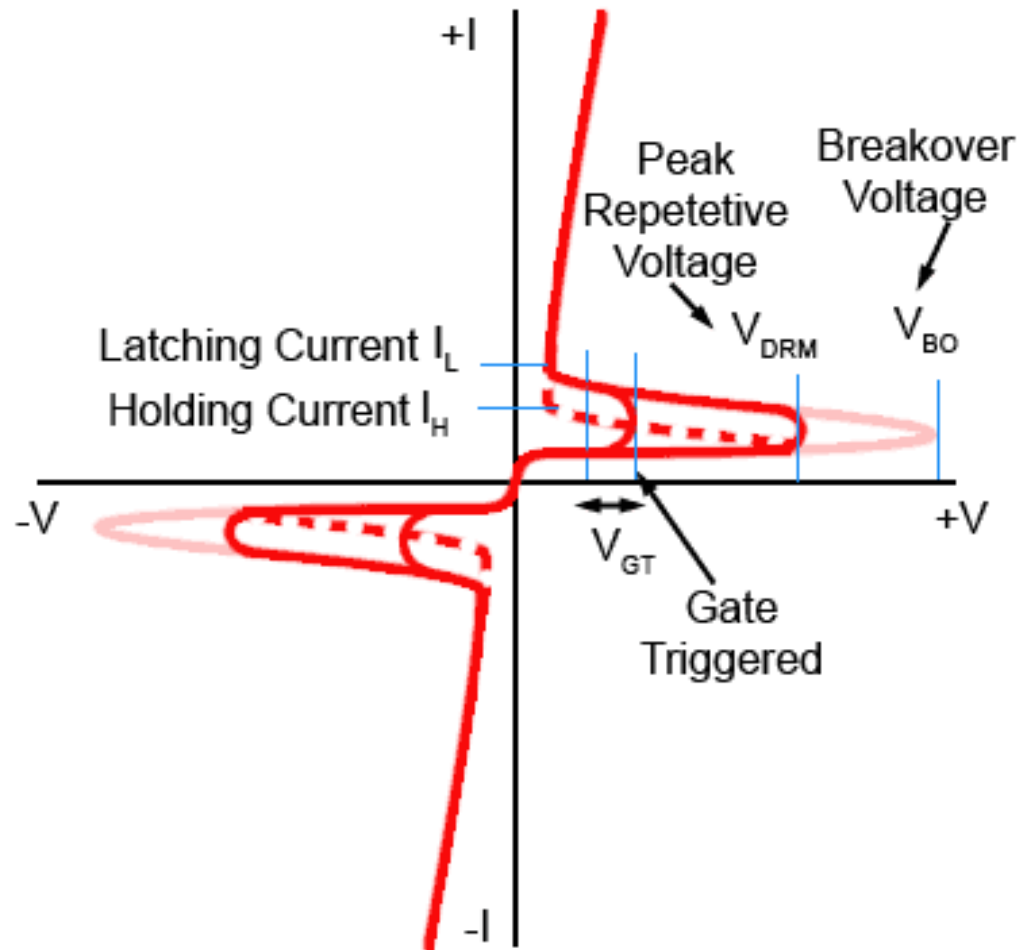



MODE OF OPERATION:

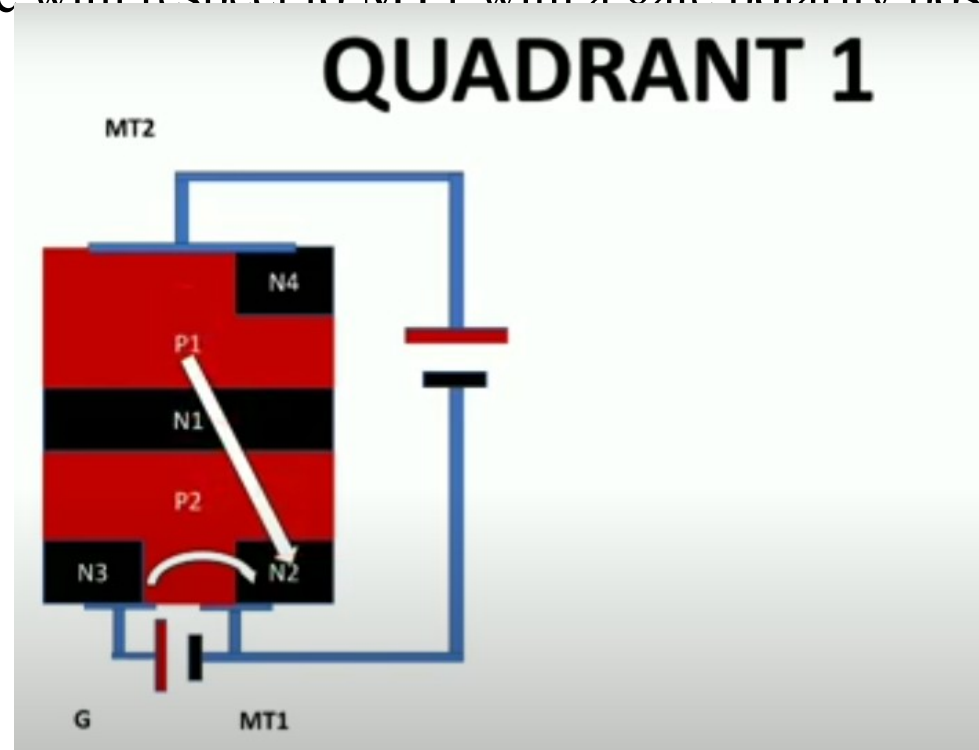
1. MT2 is positive with respect to MT1 with a gate polarity positive with respect to MT1.





MODE OF OPERATION:

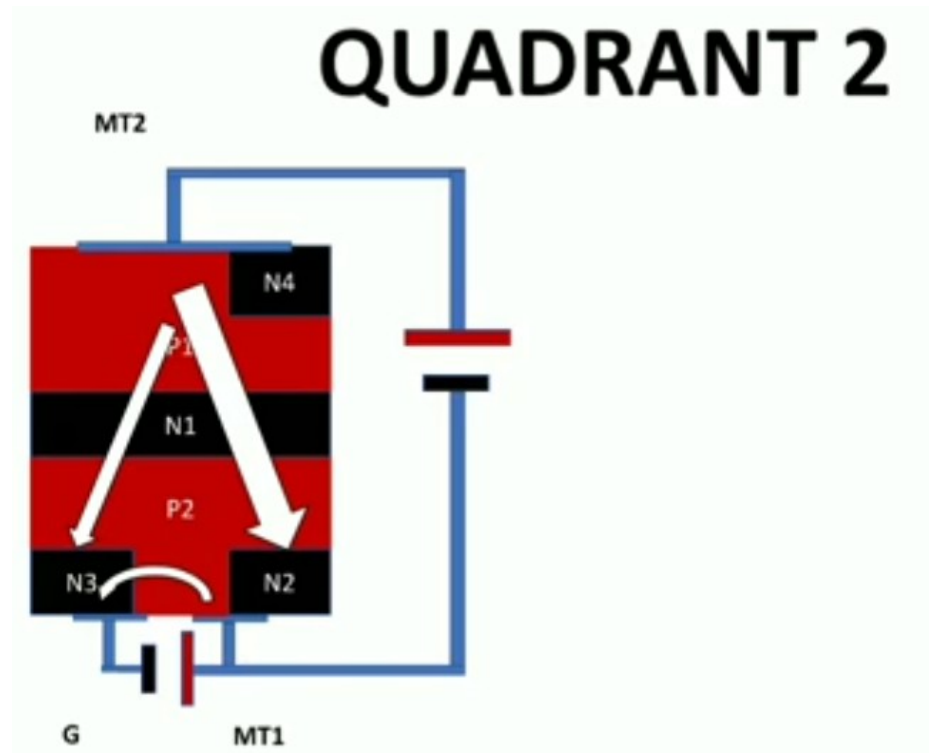
1. MT2 is positive with respect to MT1 with a gate polarity negative with respect to MT1.





MODE OF OPERATION:


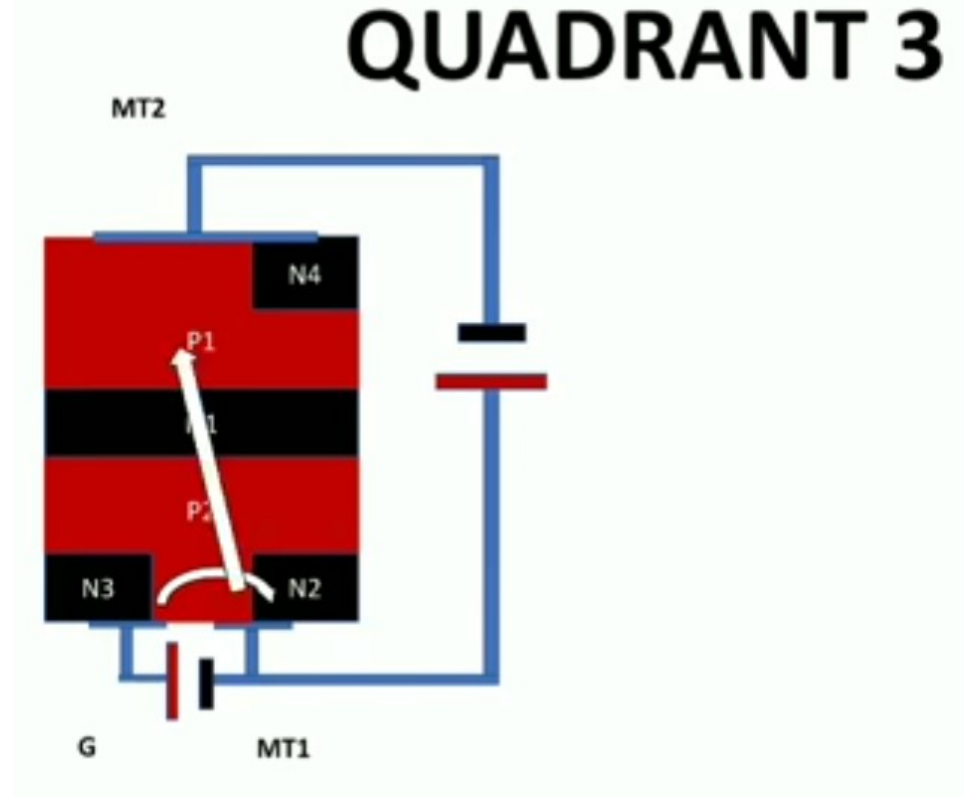
1. MT2 is negative with respect to MT1 with a gate polarity negative with respect to MT1.





MODE OF OPERATION:

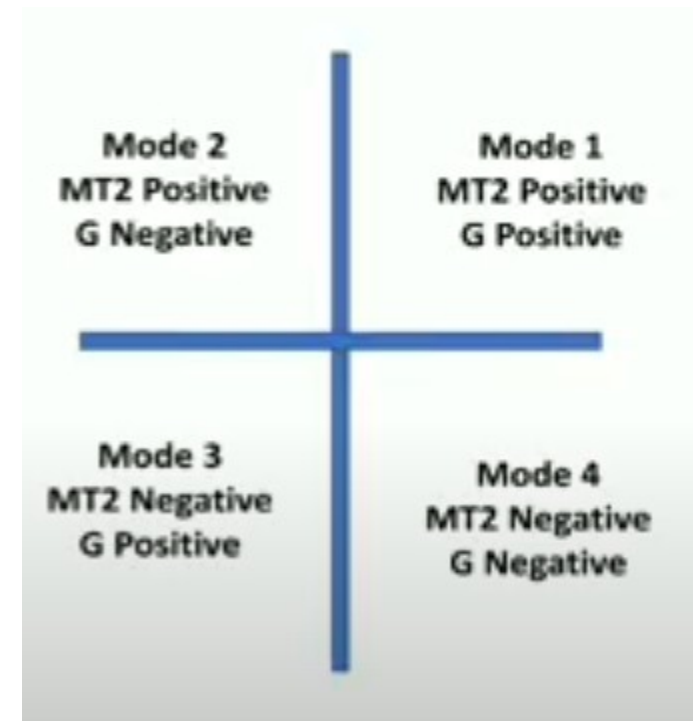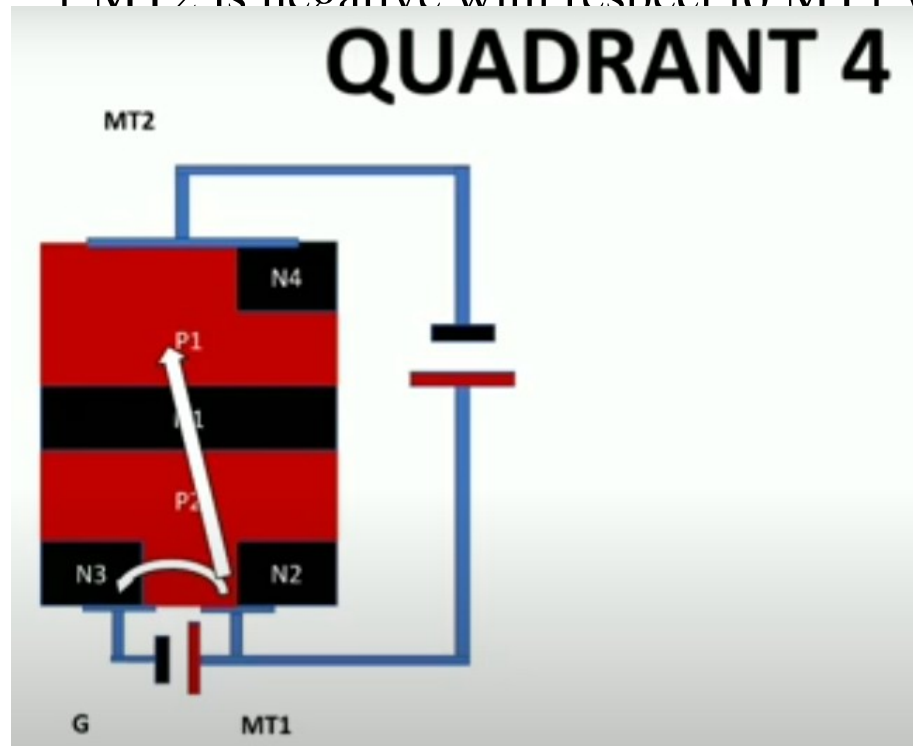1 MT2 is negative with respect to MT1 with a gate polarity positive with respect to MT1.





Advantage:

- The TRIAC need single fuse for protection.
- It can be triggered with positive or negative polarities of gate pulses.
- A safe breakdown in either direction is possible but for SCR protection should be given with parallel diode.
- It needs only a single heat sink of slightly larger size where as for SCR two heat sinks should be required of smaller size.
- When the voltage is reduced to zero the TRIAC turns OFF.

Disadvantages:

- It can be triggered in any direction so we need to be careful about triggering circuit.
- As compared to SCR (silicon controlled rectifier) it has low ratings.
- The TRIACs are not much reliable as compared to SCR.
- This is not suitable for DC applications.
- The dv/dt rating is very low as compared to SCR.
- It has a very high switching delay.



ASSESSMENT

Can we adjust the illumination of the bulb....? Justify.





References

1. <https://components101.com/articles/triac-symbol-working-and-application-circuits>
2. <https://www.electrical4u.com/triac/>
3. https://www.electronics-notes.com/articles/electronic_components/scr/what-is-a-triac.php
4. <https://www.youtube.com/watch?v=rIMexAWE6Cc>
5. <https://www.youtube.com/watch?v=qGQdbUiTd54>

