

SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF MECHATRONICS

16MC302 - INDUSTRIAL ELECTRONCIS & APPLICATION

III YEAR V SEM

UNIT 1 – INTRODUCTION TO POWER ELECTRONICS

TOPIC - SCR

Mr. M.Anand., M.E.,(Ph.D.,)

ASSISTANT PROFESSOR,

DEPARTMENT OF MECHATRONICS,

SNSCT, Coimbatore.



<u>Revision</u>





Differentiate Power Electronics Switch and Solid state swith.

Why Power Electronics Switch?

4 Type of Conversion process.









SCR



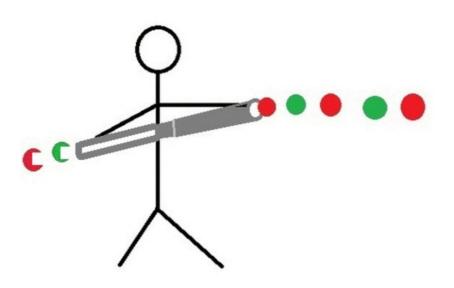The Silicon Controlled Rectifier (SCR) is the most important and mostly used member of the thyristor family. SCR can be used for different applications like rectification, regulation of power and inversion, etc. Like a diode, SCR is a unidirectional device that allows the current in one direction and opposes in another direction.




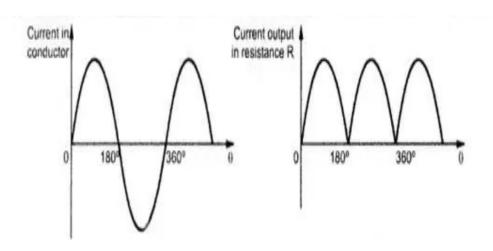



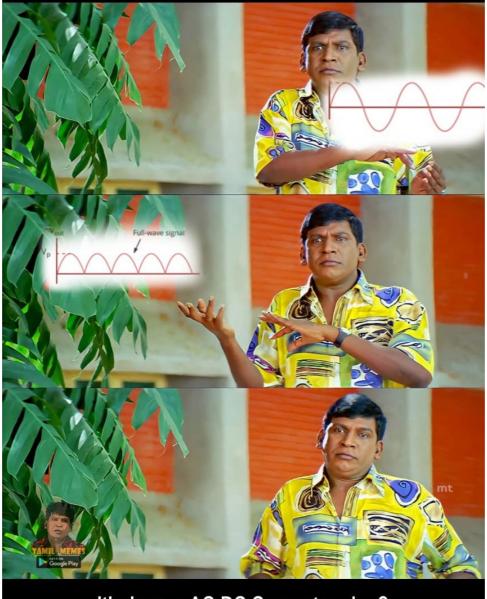Intha Waveform Direction ah intha side maathuthu...






09/03/2024






SYMBOL

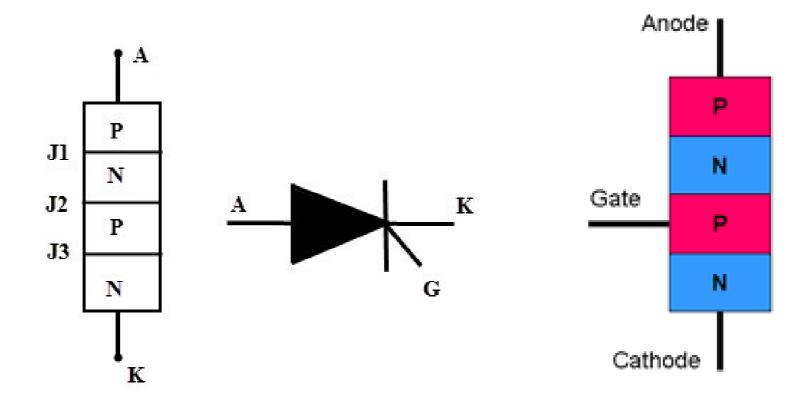








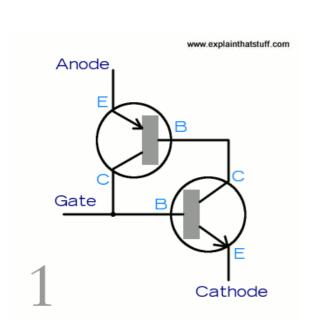

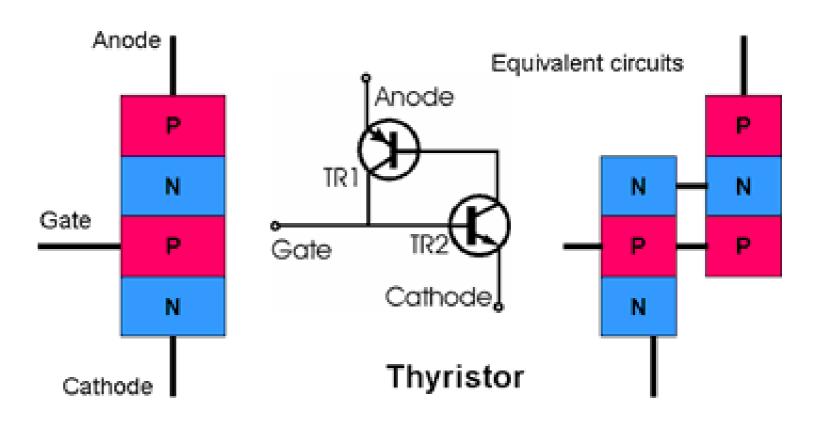




CIRCUIT DIAGRAM





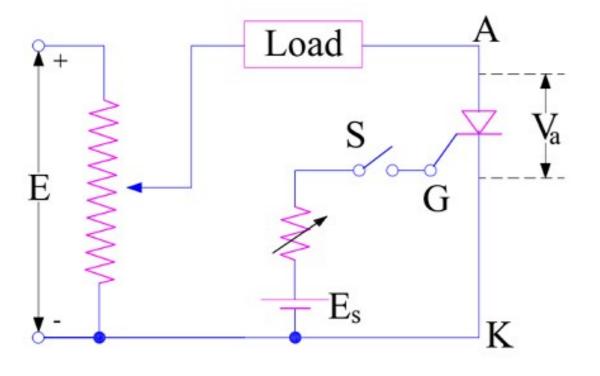









https://www.youtube.com/watch?v=xefULD5GEpo



How SCR works:




Forward Blocking mode




Reverse Blocking mode




Forward Conduction mode

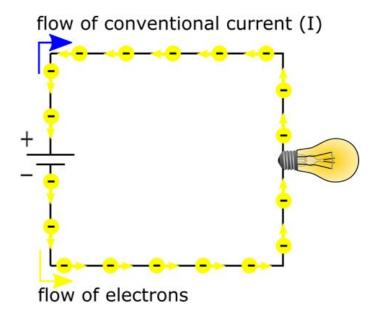


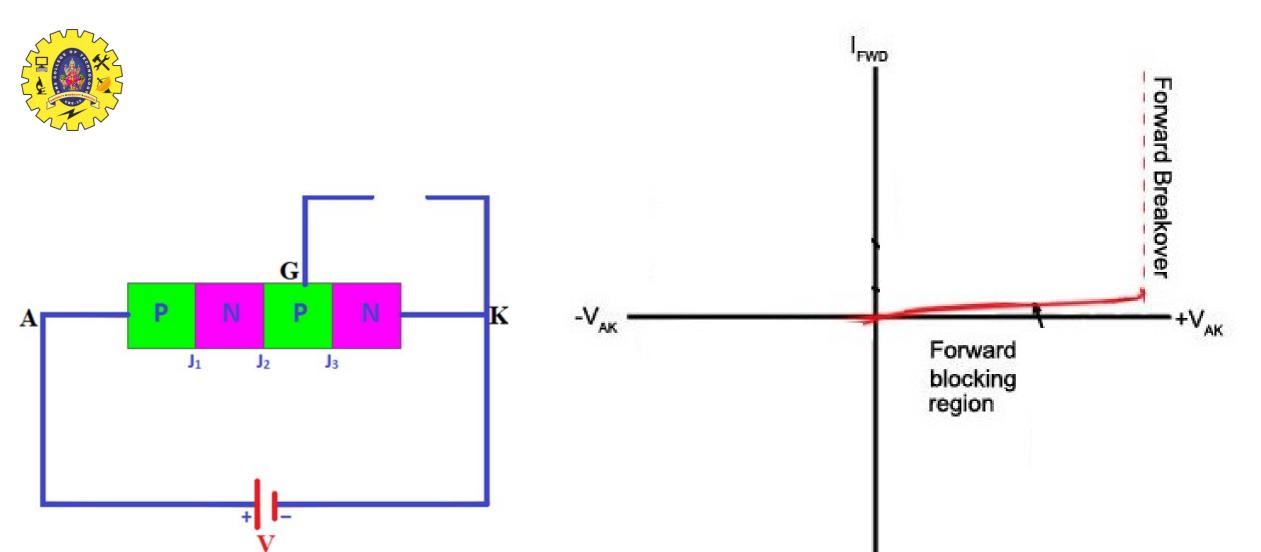


Forward Blocking Mode of SCR




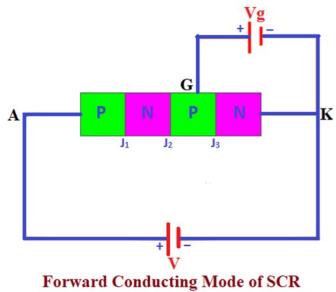

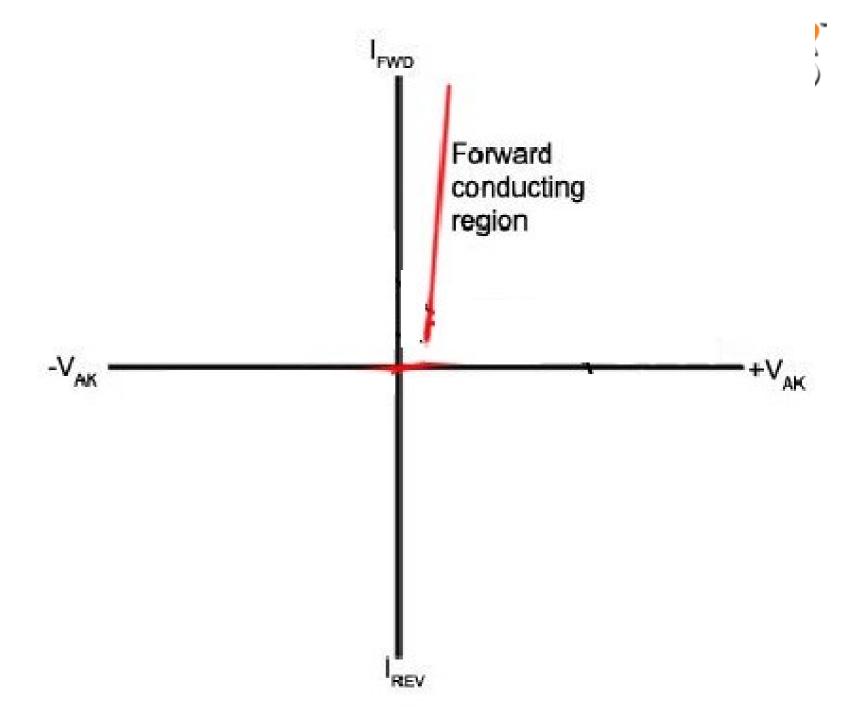



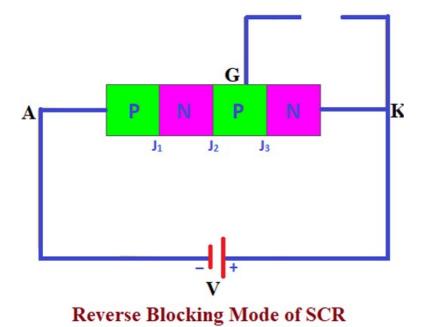

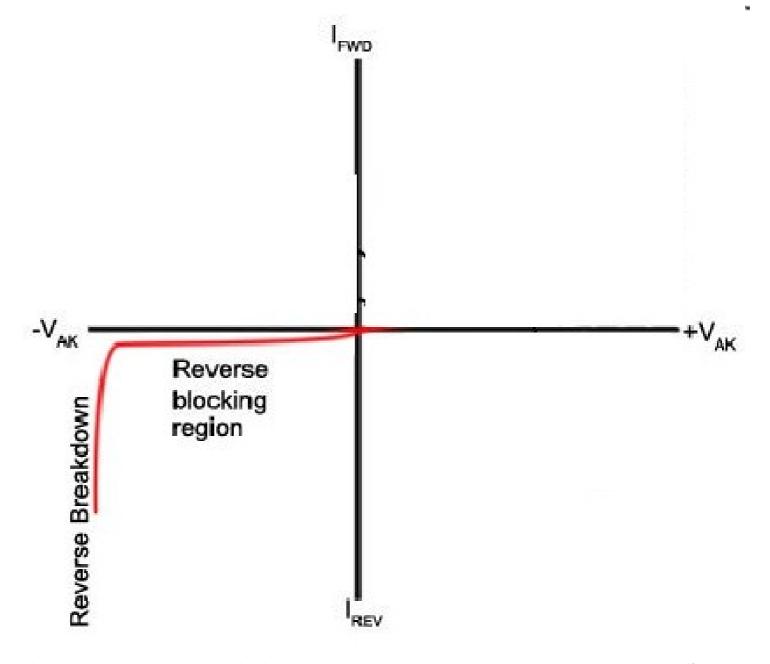




Thyristor Operating modes



Thyristors have three modes:

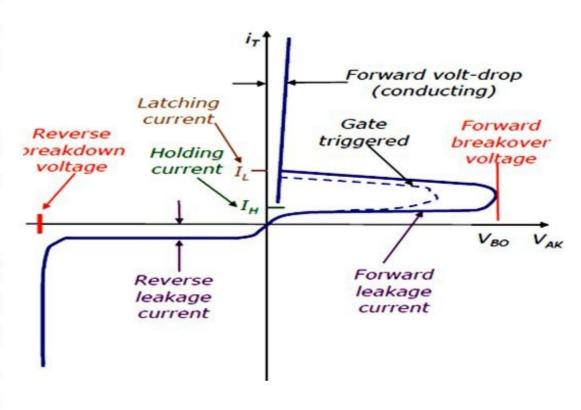- Forward blocking mode:
 Only leakage current flows,
 so thyristor is not conducting.
- Forward conducting mode: large forward current flows through the thyristor.
- Reverse blocking mode:
 When cathode voltage is
 increased to reverse
 breakdown voltage ,
 Avalanche breakdown
 occurs and large current
 flows.







Advantages of Silicon Controlled Rectifier

- ✓ As compared with electromechanical or mechanical switch, SCR has no moving parts. Hence, with a high efficiency it can deliver noiseless operation.
- ✓ The switching speed is very high as it can perform 1 nano operations per second.
- ✓ These can be operated at high voltage and current ratings with a small gate current.
- ✓ More suitable for AC operations because at every zero position of the AC cycle the SCR will automatically switch OFF.
- ✓ Small in size, hence easy to mount and trouble free service.



Application











ASSESSMENT



Find the Difference and justify it.

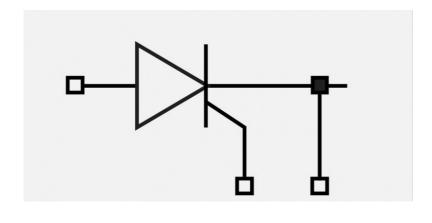

A

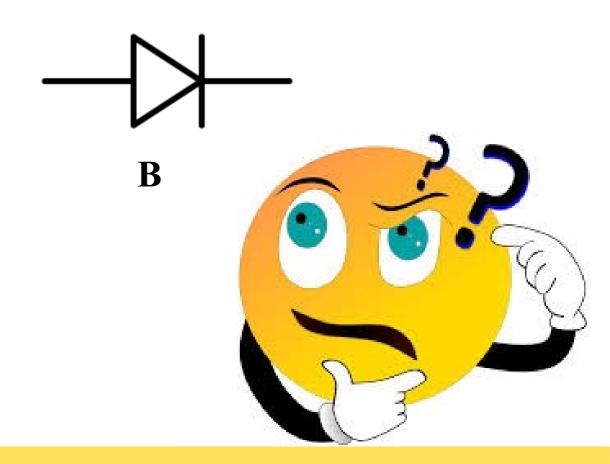





<u>References</u>

- 1. https://components101.com/articles/scr-introduction-working-and-applications-in-power-electronics
- 2. https://www.electrical4u.com/thyristor-silicon-controlled-rectifier-scr/
- 3. https://www.allaboutcircuits.com/textbook/semiconductors/chpt-7/silicon-controlled-rectifie-r-scr
- 4. https://www.youtube.com/watch?v=9h7_vDUE908
- 5. https://www.youtube.com/watch?v=npRk_P5A5

