



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF MECHATRONICS ENGINEERING**

### **19MCT201 - DESIGN OF DIGITAL CIRCUITS**

**II YEAR - III SEM**


### **UNIT 4 – DESIGN OF SEQUENTIAL CIRCUITS**

**TOPIC 1– Register**



# Shift registers


## Bidirectional Shift Register

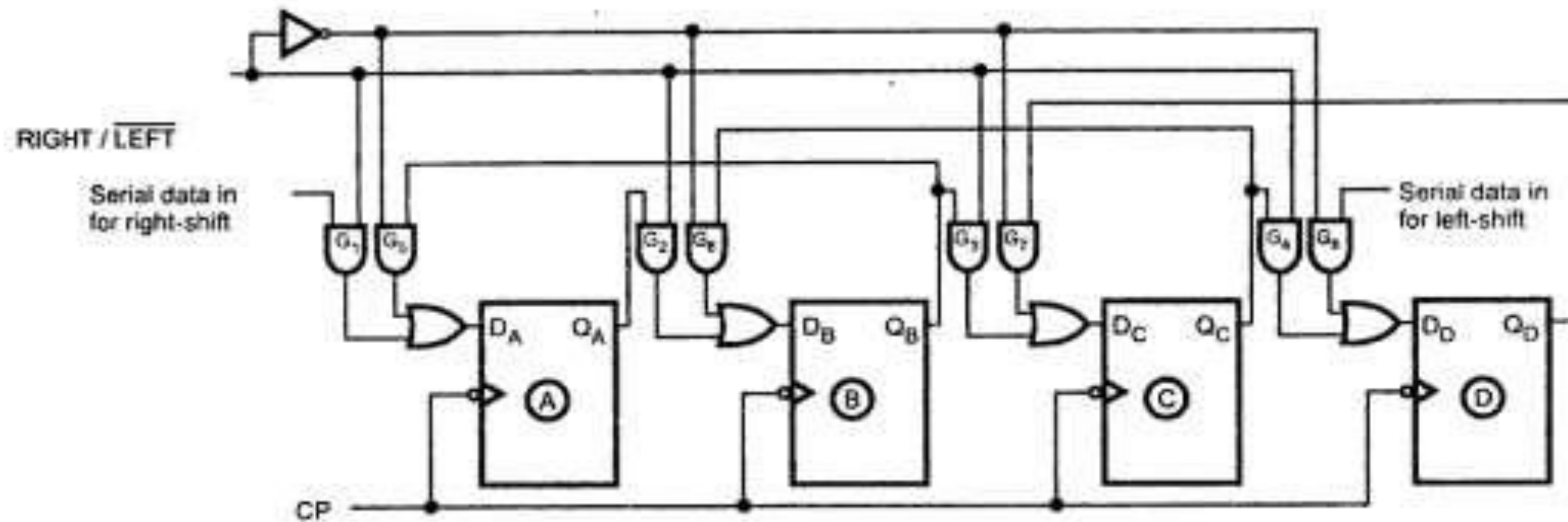


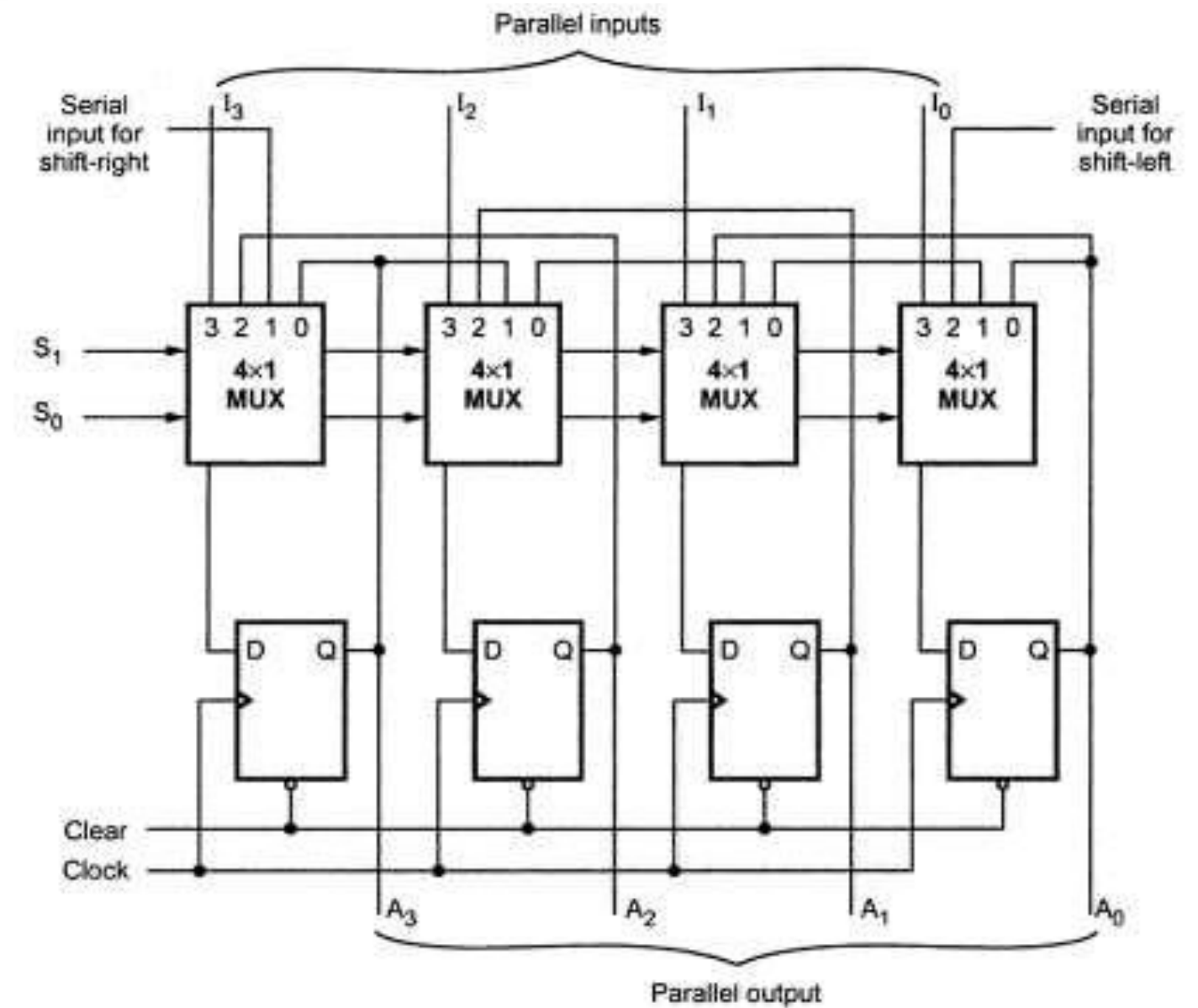
# Universal shift register

A register capable of shifting in one direction only is a unidirectional shift register. A register capable of shifting in both directions is a bidirectional shift register. If the register has both shifts (right shift and left shift) and parallel load capabilities, it is referred to as **Universal shift register**.





# Ring counters

Fig. shows the logic diagram for four-bit ring counter. As shown in the Fig. the Q output of each stage is connected to the D input of the next stage and the output of last stage is fed back to the input of first stage. The  $\overline{\text{CLR}}$  followed by  $\overline{\text{PRE}}$  makes the output of first stage to '1' and remaining outputs are zero, i.e.  $Q_A$  is one and  $Q_B, Q_C, Q_D$  are zero.

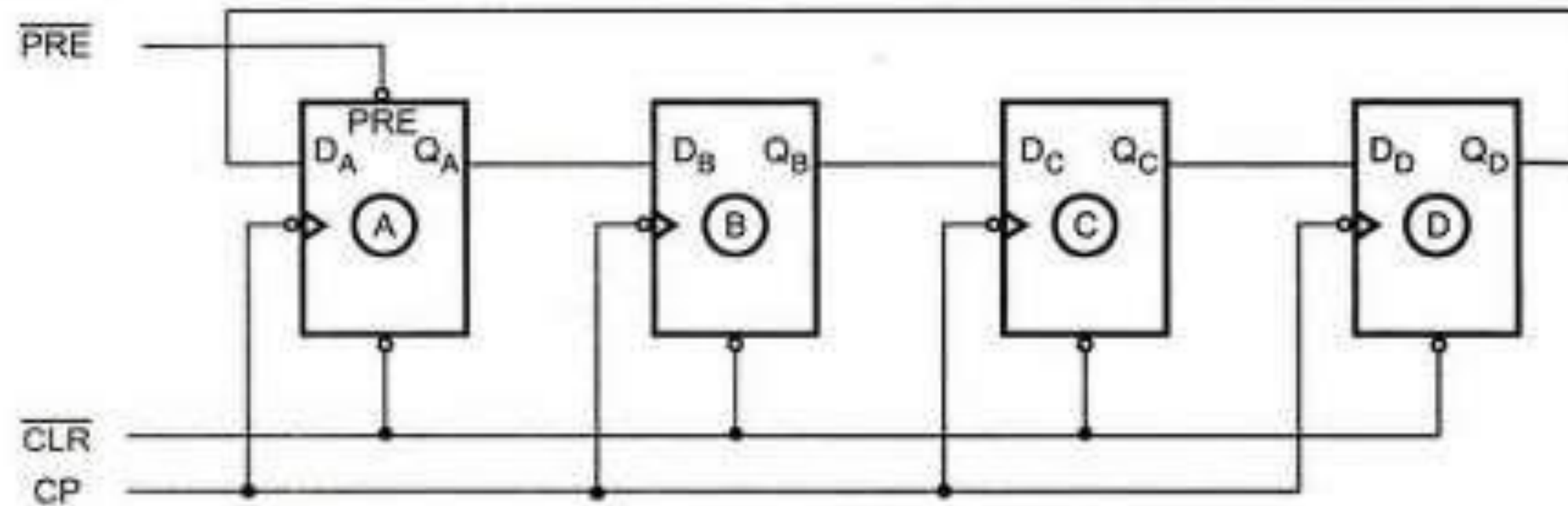


Fig. Four-bit ring counter





# ASSESSMENT - 1

Mux relates with us....

## Question 1

**Which combinational circuit is renowned for selecting a single input from multiple inputs & directing the binary information to output line?**

- ▶ a) Data Selector
- ▶ b) Data distributor
- ▶ c) Both data selector and data distributor
- ▶ d) DeMultiplexer

## Question 2

**Which is the major functioning responsibility of the multiplexing combinational circuit?**

- ▶ a) Decoding the binary information
- ▶ b) Generation of all minterms in an output function with OR-gate
- ▶ c) Generation of selected path between multiple sources and a single destination
- ▶ d) Encoding of binary information



# References

- <https://brilliant.org/wiki/de-morgans-laws/>
- <https://circuitglobe.com/demorgans-theorem.html>
- <https://www.electrical4u.com/>