

SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



19EET103 / ELECTRIC CIRCUITS AND ELECTRON DEVICES


AC CIRCUITS

INDUCTIVE ELEMENTS






Inductive AC circuit

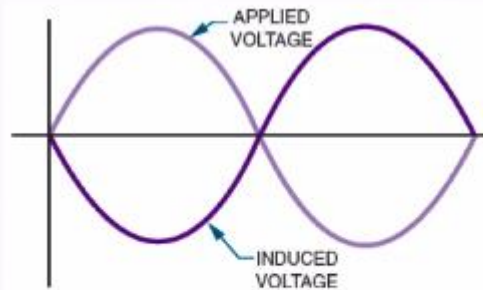

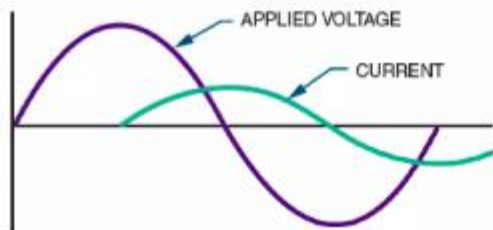The applied voltage and the induced voltage are 180 degrees out of phase with each other in an inductive circuit.



The current lags the applied voltage in an AC inductive circuit.






- Inductive reactance

- Opposition to current flow offered by an inductor in an AC circuit
- Expressed by the symbol X_L
- Measured in ohms





Applications of Inductive Circuits

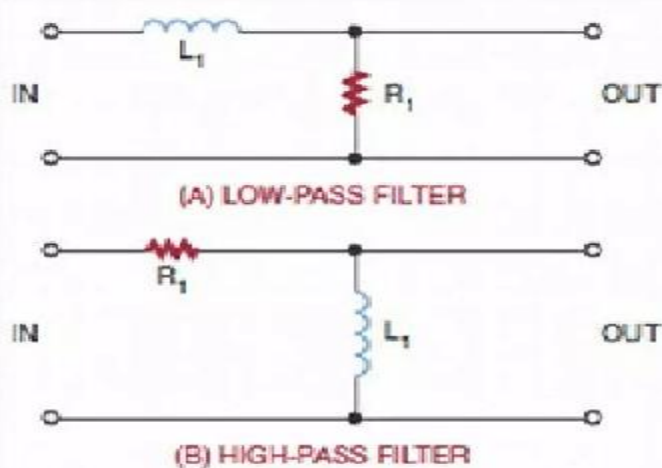



Summary


- In a pure inductive circuit, the current lags the applied voltage by 90 degrees
- Inductive reactance is the opposition to current flow offered by an inductor in an AC circuit
- Inductive reactance can be calculated by the formula:

$$X_L = 2\pi fL$$





RECAP....

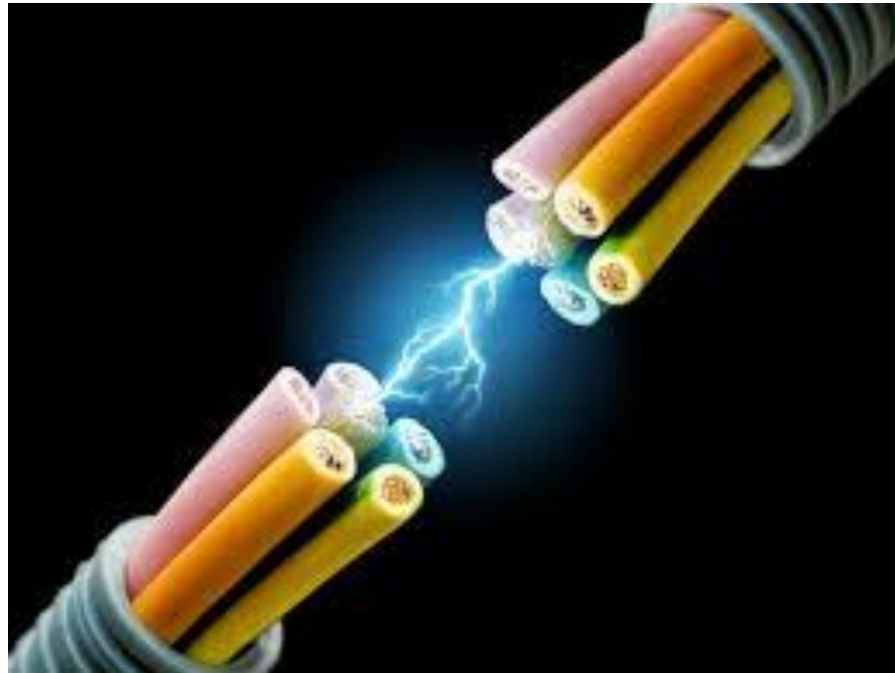

...THANK YOU