



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai




19EET103 / ELECTRIC CIRCUITS AND ELECTRON DEVICES AC CIRCUITS

IMPEDEDANCE , POWER & POWER FACTOR



TOPIC OUTLINE

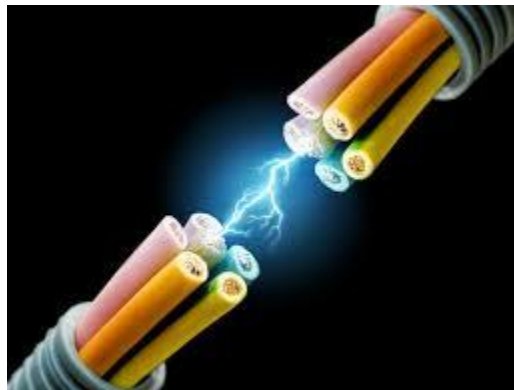- AC fundamentals
 - Peak and RMS
 - Power
- Real and Reactive Power
 - Power factor






AC FUNDAMENTALS

PARAMETER VALUES:

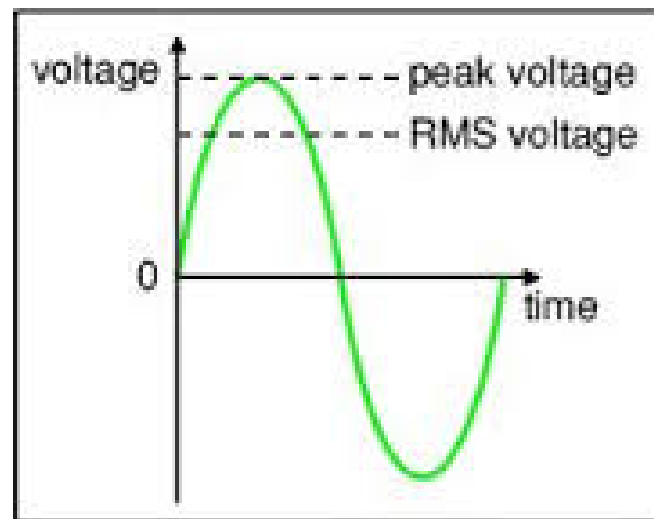- Instantaneous (v , i)
- Peak (V_m , I_m)
- Average (V_{ave} , I_{ave})
- RMS (V , I or V_{rms} , I_{rms})




Parameters V and I are in sine wave.





AC FUNDAMENTALS

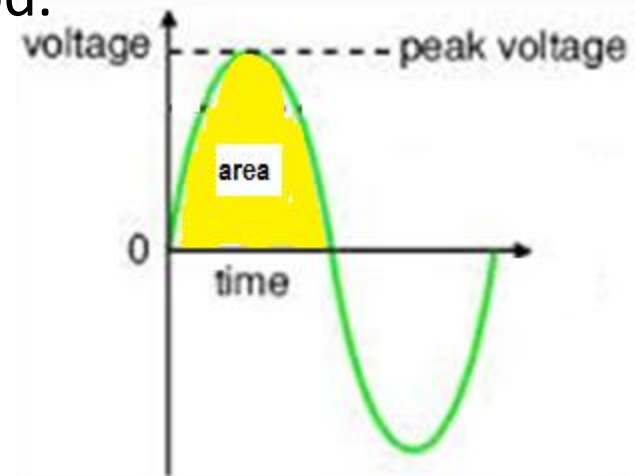
- **Peak (V_m , I_m)** : It is the maximum value
- **Instantaneous (v , i)** : The values at any instant. It may be voltage or current.
- **Average (V_{ave} , I_{ave})**: Average value is the sum of instantaneous power in one period.
- It is also said to be as area under the curve divided by time.
- Average power - for half cycle is shown
- - for full cycle is ZERO





ROOT MEAN SQUARE (RMS)

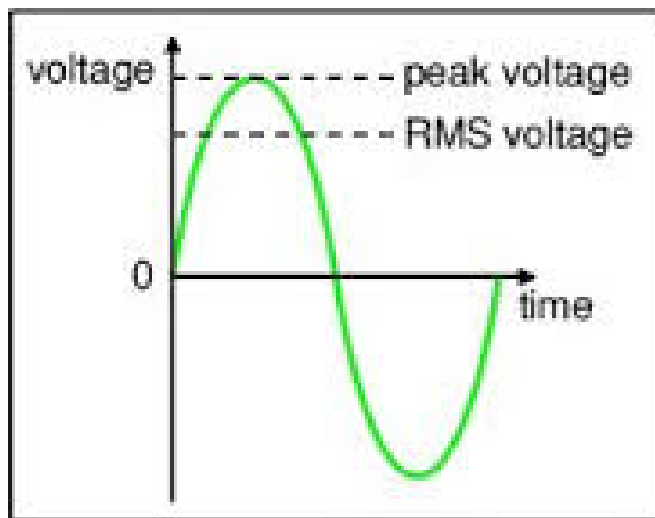The RMS value of a set of values (or a continuous-time waveform) is the **square root** of the arithmetic mean of the squares of the original values.



$$rms = \frac{V_{peak}}{\sqrt{2}} \text{ (for an undistorted sine wave)}$$

$$rms = \frac{V_{peak}}{\sqrt{3}} \text{ (for an undistorted triangle wave)}$$

$$rms = \frac{V_{peak}}{1} \text{ (for a symmetrical square wave)}$$



RMS


RMS value for I and V is given

$$I = I_p \sin \omega t$$

$$V = V_p \sin \omega t$$

Where,

ωt = radians per second

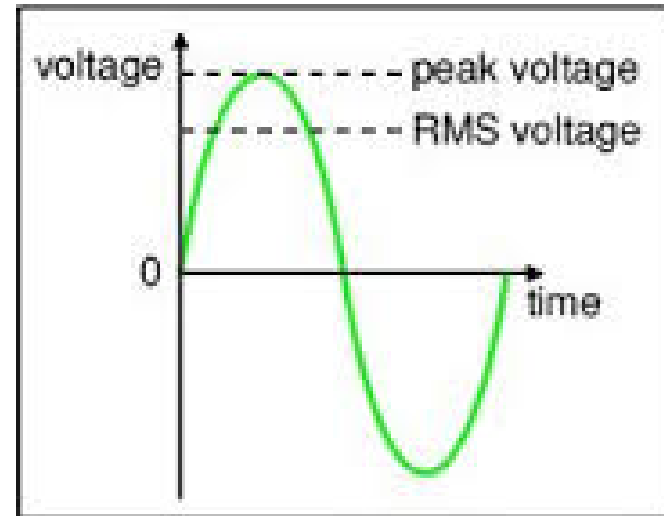



Impedance

3.Impedance

$$Z = \frac{v}{i} = \frac{V_m \angle 0}{I_m \angle 90} = \frac{V_m \angle 0}{V_m \omega C \angle 90} = \frac{1}{\omega C} \angle -90 = \frac{-j}{\omega C} = -j X_c$$

The quantity $\frac{1}{\omega C}$ is called capacitive reactance, is denoted by X_c and is measures in ohms

**** **Significance of operator- j** : The operator- j is used in rectangular form. It is used to indicate clock wise rotation of phasor through 90 degrees . Mathematically $-j = -\angle -1$





POWER

- The **power** dissipated in a component is a **product of** the instantaneous **voltage** and the instantaneous **current**

$$p = vi$$

- In a **resistive circuit** the voltage and current are in **phase** – calculation of **p is straightforward**
- In **reactive circuits**, there will normally be some **phase shift between v and i** , and calculating the power becomes more complicated







POWER

LOAD (POWER CONSUMED)

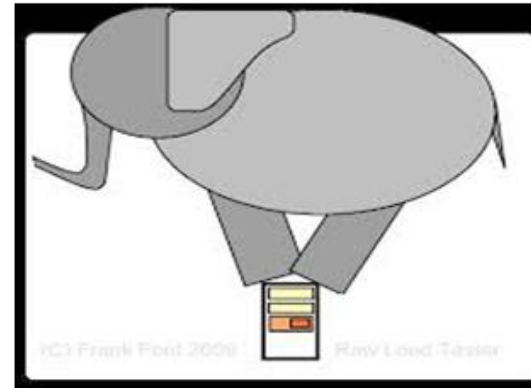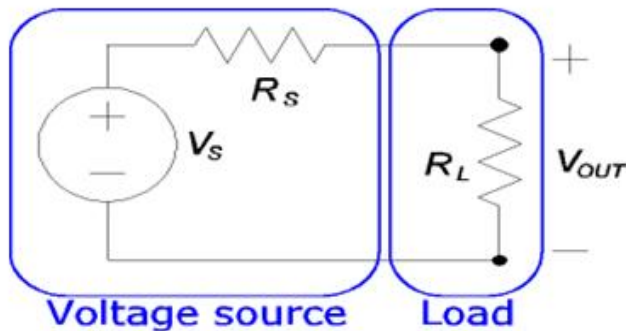- It is a any electric load on a circuit that does work.
 - A device connected to the **output of a circuit**
- **Example:** Power windows, light bulbs, motors.





POWER

- **Real power** is the capacity of the circuit performing work in a particular time.
- It is the product of V , I and cosine angle of voltage and current
- **Apparent power** is the product of the current and voltage of the circuit
- **Reactive power** is the product of V , I and sine angle of voltage and current



POWER

Real Power

$$P = VI \cos \phi \quad \text{watts or kW}$$


Reactive Power

$$Q = VI \sin \phi \quad \text{var or kVAR}$$

Apparent Power

$$S = VI \quad \text{VA or kVA}$$

$$S^2 = P^2 + Q^2$$

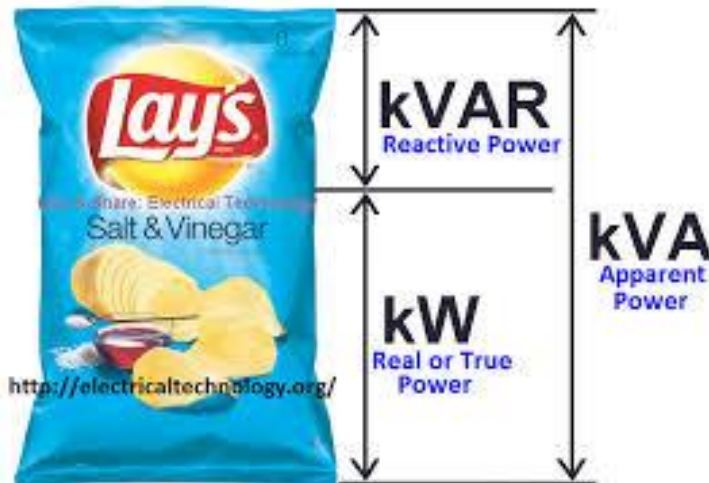



REAL AND REACTIVE POWER


If a circuit has resistive and reactive parts, the resultant power has 2 parts:

- The first is *dissipated* in the resistive element. This is the **real power, P**
- The second is *stored and returned* by the reactive element. This is the **reactive power, Q** , which has units of **volt amperes reactive** or **var**





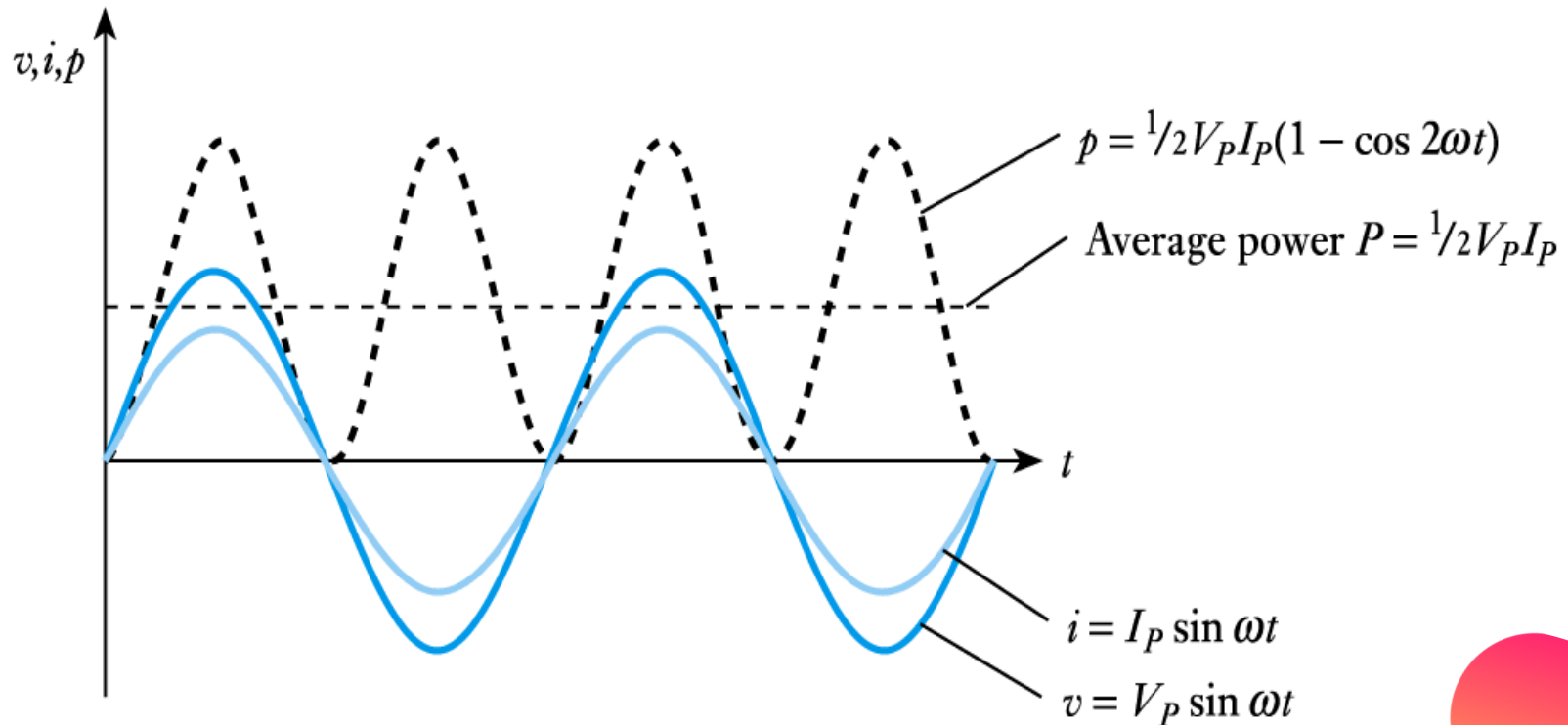RELATIONSHIP BETWEEN V , I AND P IN A RESISTOR





POWER FACTOR


- Power Factor is the ratio of **Active Power** to **Total Power**:

$$\begin{aligned} \text{Power Factor} &= \frac{\text{Active (Real) Power}}{\text{Total Power}} \\ &= \frac{\text{kW}}{\text{kVA}} \\ &= \text{Cosine } (\theta) \end{aligned}$$

- Power Factor is a measure of efficiency (Output/Input)



RECAP....

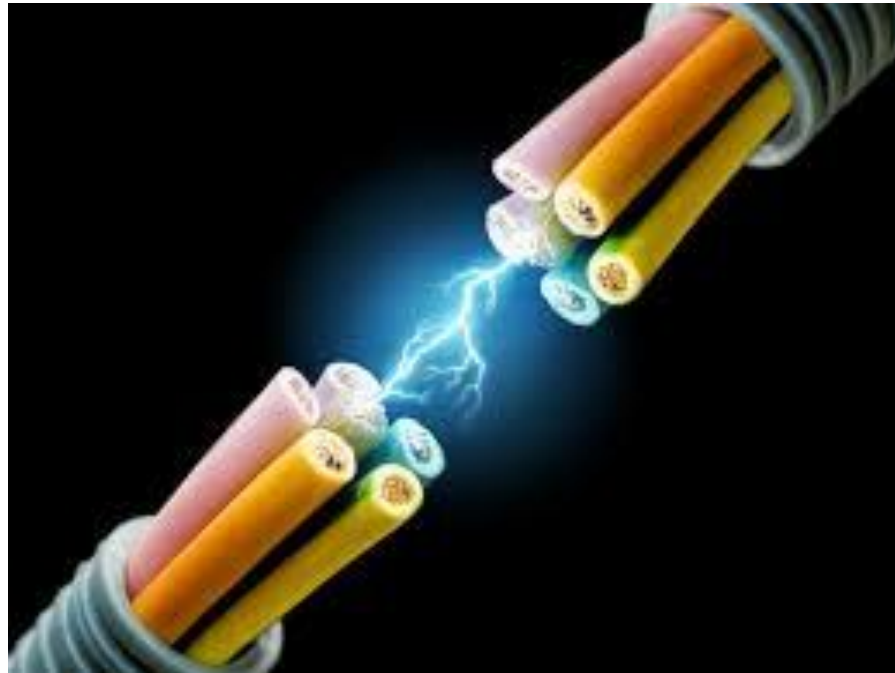

...THANK YOU