



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



23EET104 / ANALOG ELECTRONICS CIRCUITS I YEAR / II SEMESTER


UNIT-IV: MULTIVIBRATOR

INTRODUCTION, TYPES





What we study?

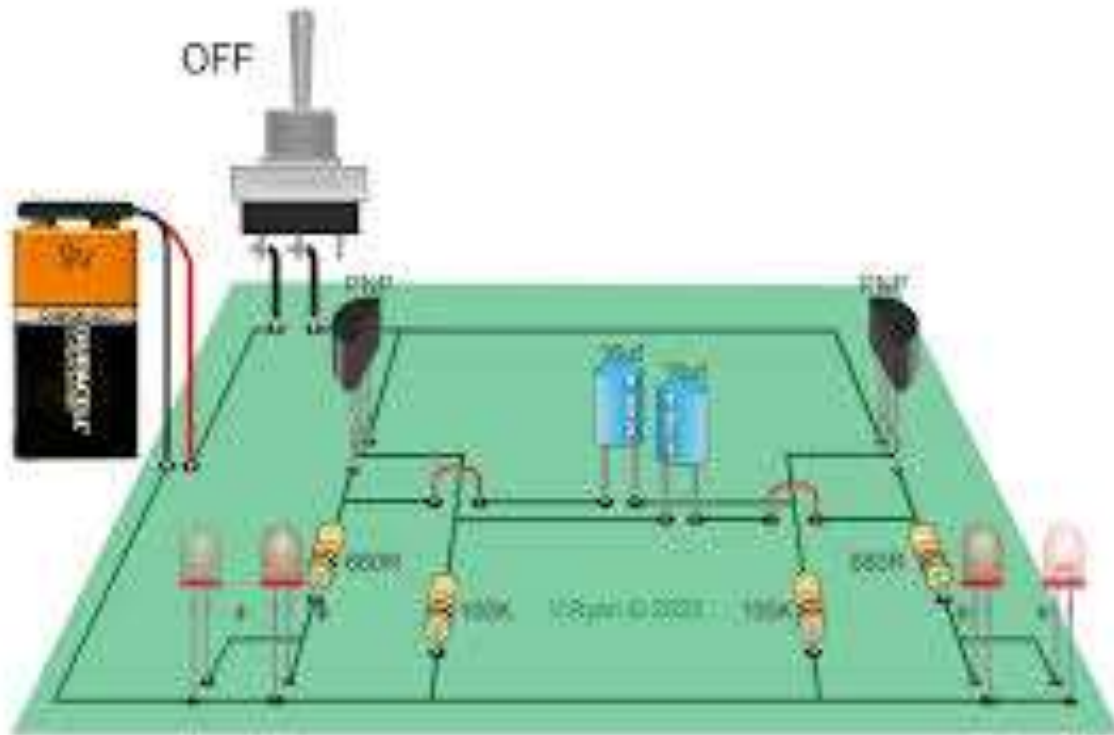

1. Define multivibrator
2. Classification of Basic multivibrator
3. Understand the Basic Concept of multivibrator
- ∴ Get Knowledge About the Condition for Oscillator
5. Application of multivibrator





What we study?

- **A multivibrator is an electronic circuit that is used to implement two state systems like oscillators, timers and flip-flops.**
- It is characterized by two amplifying devices (transistors or other devices) cross-coupled by resistors or capacitors

Invention of Multivibrator

Henri Abraham and Eugene Bloch described the first multivibrator circuit in 1920, also called a plate-coupled multivibrator.

It was made from vacuum tubes and its harmonics are being used to calibrate a wavemeter .





CLASSIFICATION OF MULTIVIBRATOR




There are three types of multivibrator circuits depending on the circuit operation:

Astable – neither state is stable.


Monostable - one of the states is stable, but the other is not.

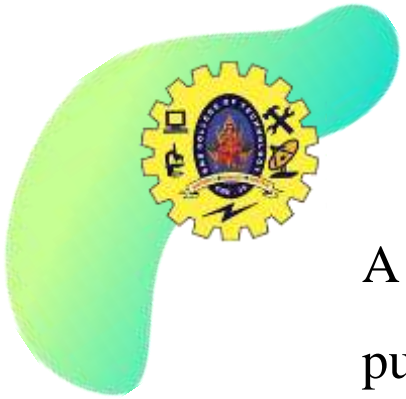Bistable – it remains in either state indefinitely.



ASTABLE MULTIVIBRATOR


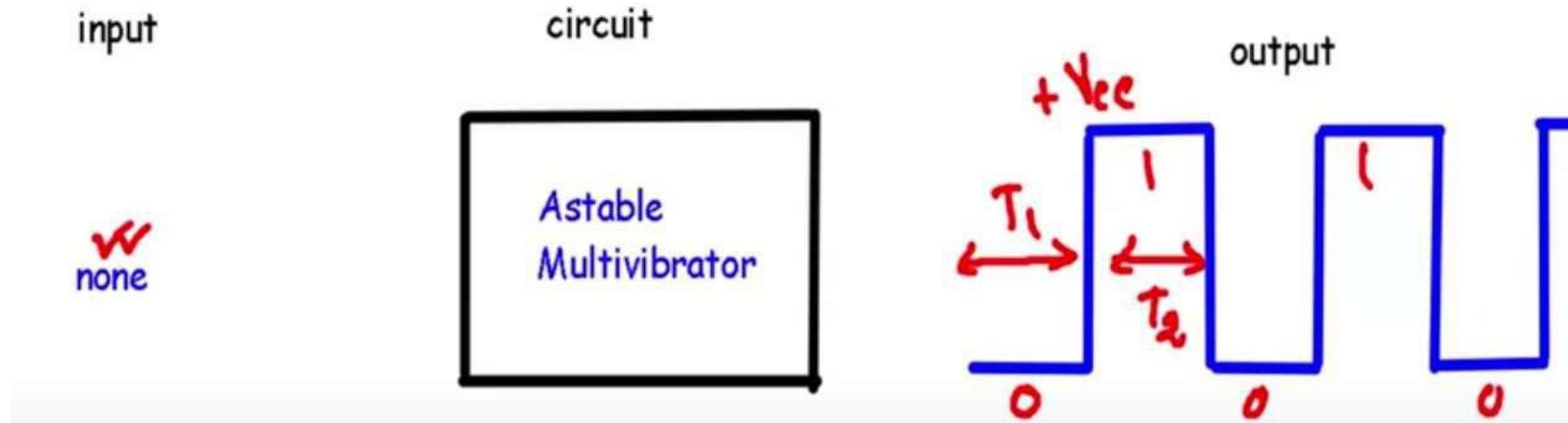
A Multivibrator that generates square waveform without using external triggering pulse is known as Astable multivibrator. It also known as **Free-running Multivibrator**.






ASTABLE MULTIVIBRATOR

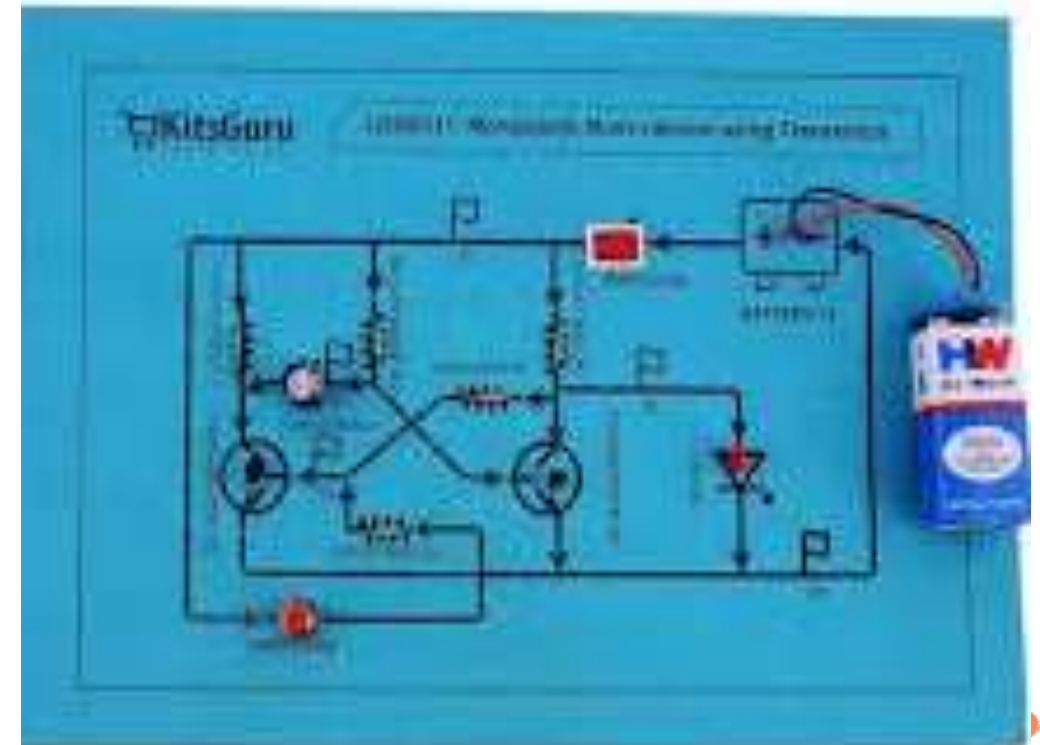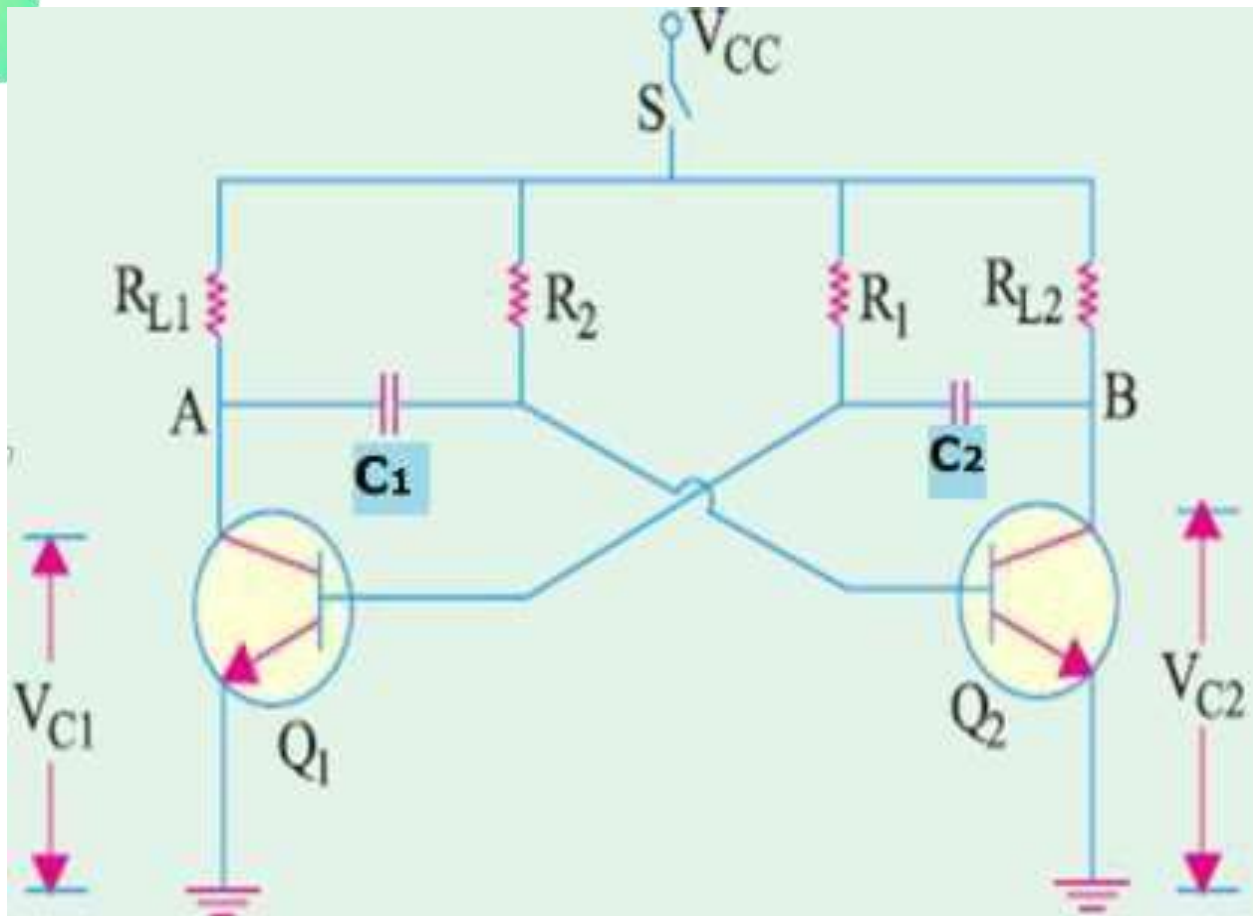This astable circuit consists of two transistors, a cross coupled Feedback network, and two capacitors and four resistors.





ASTABLE MULTIVIBRATOR

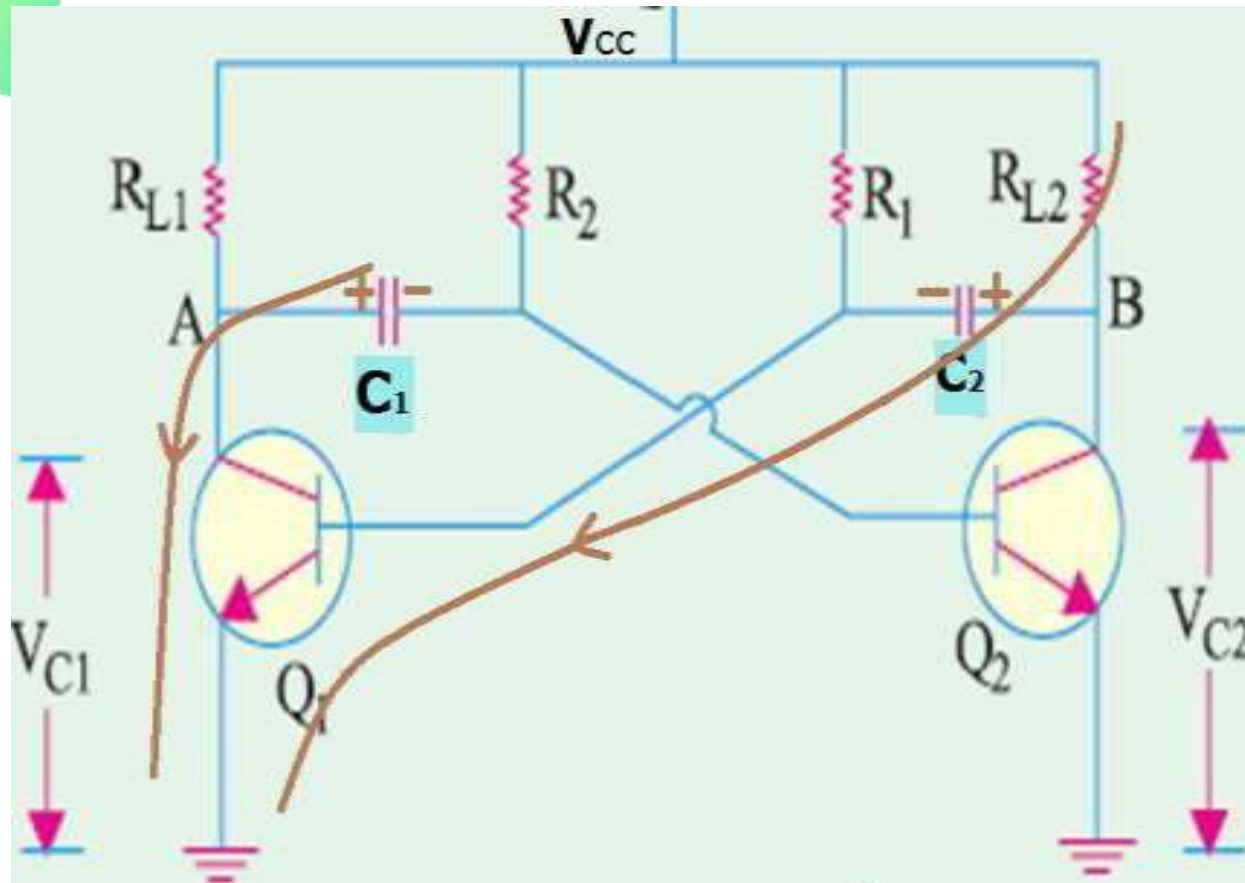


Consider **Q1 is ON** and **Q2 is OFF**:

V_{CC} drops across R_L1 .


Hence, $V_{C1} = 0$ and point A is at ground potential and $V_{C2} = V_{CC}$.

C_1 discharging and C_2 charging.

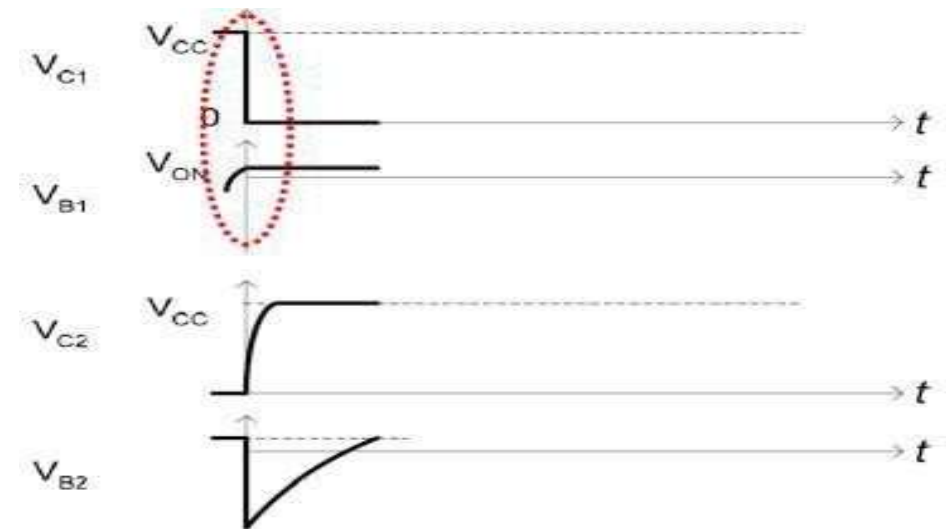



ASTABLE MULTIVIBRATOR

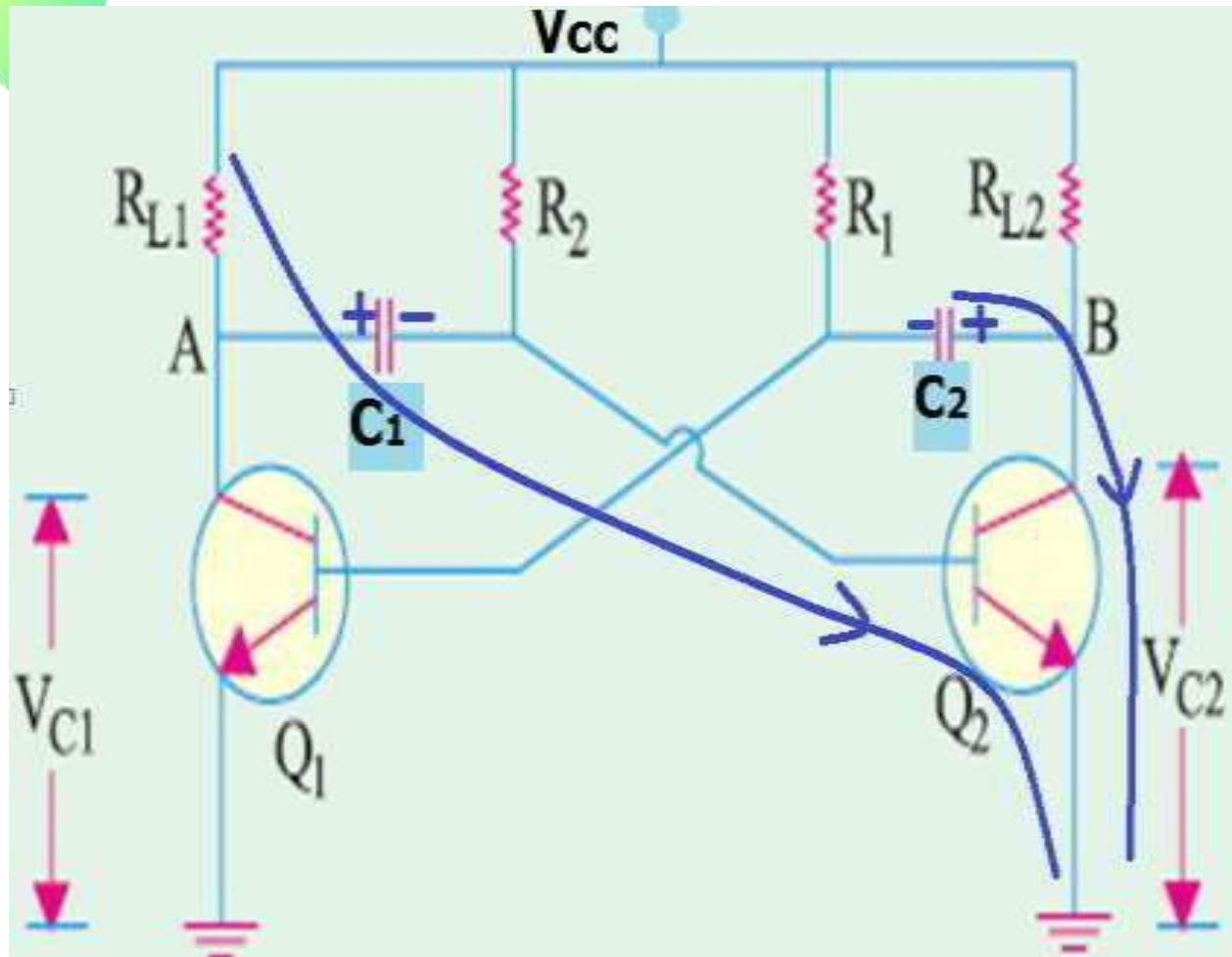


Consider **Q2 is ON** and **Q1 is OFF**:

V_{CC} drops across R_{L2} .



Hence, $V_{C2} = 0$ and point B is at ground potential and $V_{C1} = V_{CC}$.

C_2 discharging and C_1 charging.

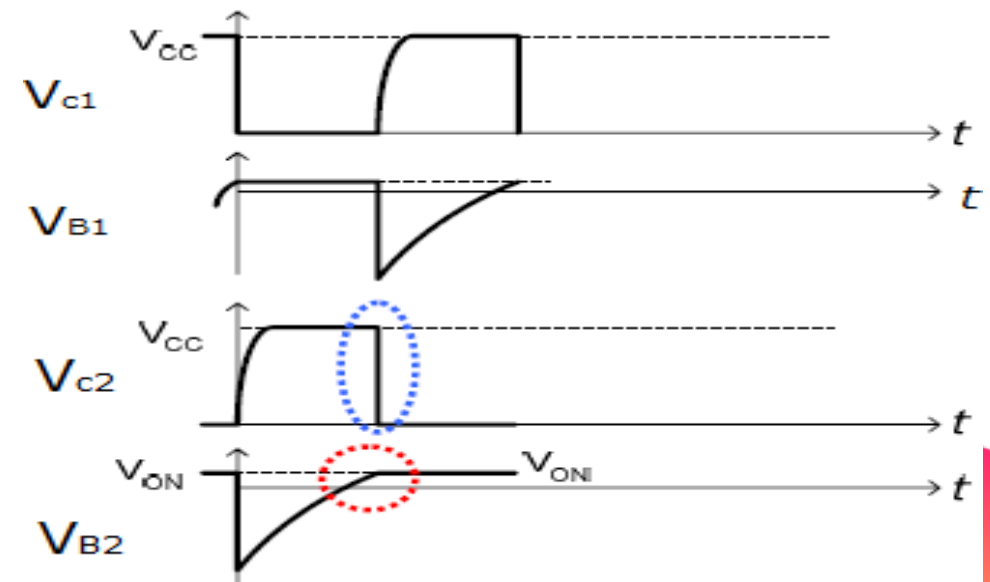



ASTABLE MULTIVIBRATOR

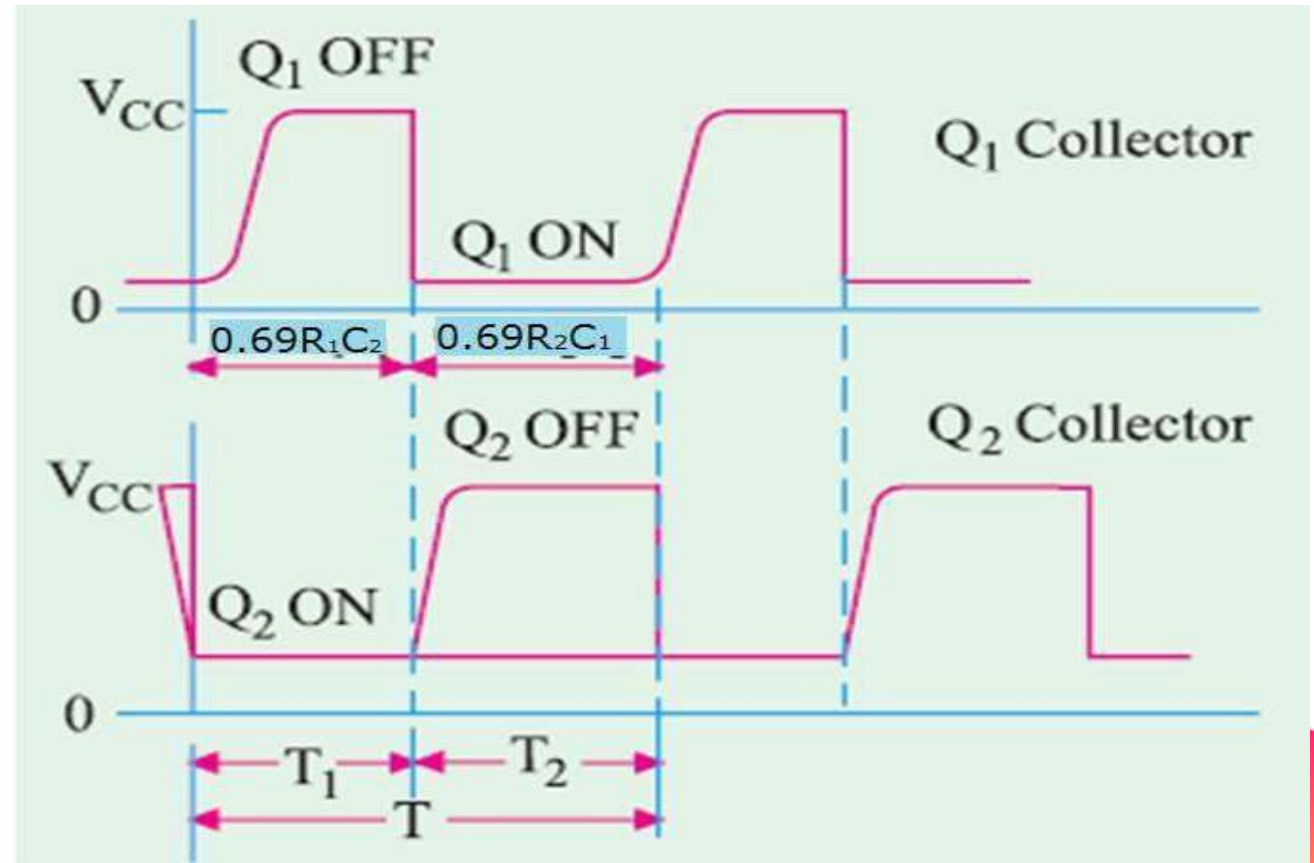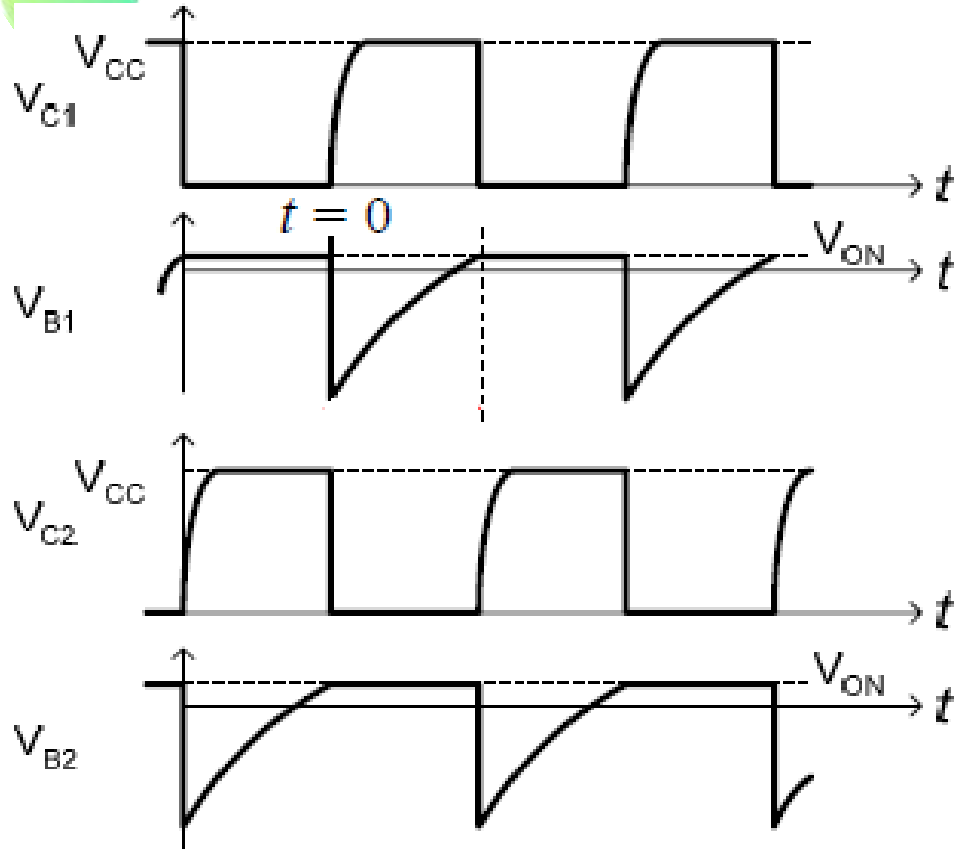



Frequency of Oscillation, Application




It can be proved that off-time for Q_1 is $T_1 = 0.69 R_1 C_2$ and that for Q_2 is $T_2 = 0.69 R_2 C_1$.

Hence, total time-period of the wave is $T = T_1 + T_2 = 0.69 (R_1 C_2 + R_2 C_1)$

If $R_1 = R_2 = R$ and $C_1 = C_2 = C$ i.e. the two stages are symmetrical, then $T = 1.38 RC$

It is given by the reciprocal of time period,
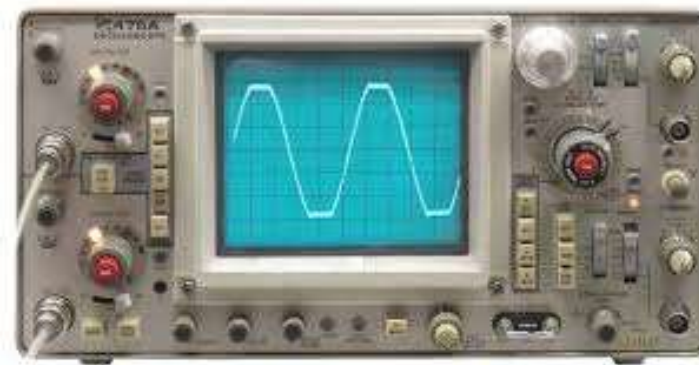
$$f = \frac{1}{T} = \frac{1}{1.38 RC} = \frac{0.7}{RC}$$





APPLICATION

Application

- Used in applications where **low clock frequency - clock pulse train is required.**
- **Relaxation oscillators**, which are parts of **vehicle indicator lights**, early oscilloscopes and television receivers.
- **Timing signals.**



...THANK YOU

