



# SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



## 23EET104 / ANALOG ELECTRONICS CIRCUITS I YEAR / II SEMESTER




### UNIT-IV: DIFFERENTIAL AMPLIFIER AND MULTIVIBRATOR

# DIFFERENTIAL AMPLIFIER





# Transistor operation - Recall

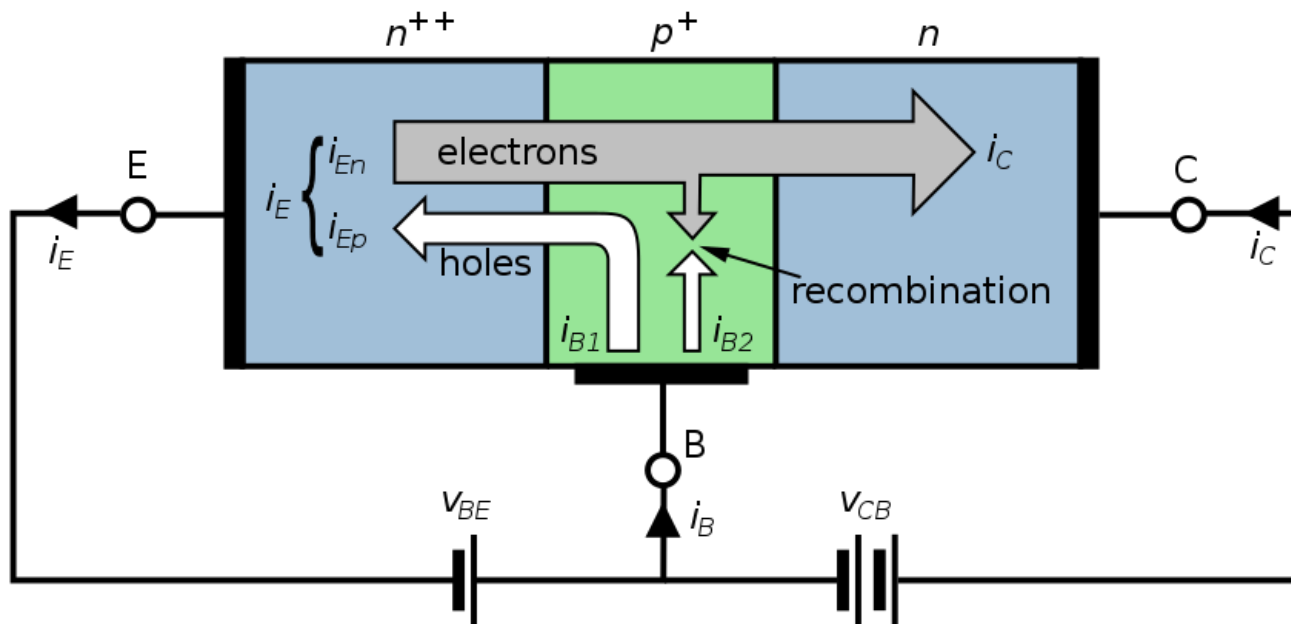



# Introduction




- The function of differential amplifier is to *amplify the difference of two signals*.
- The need for differential amplifier in many physical measurements arises where response from d.c to many megahertz is required. It is also the *basic input stage of an integrated amplifier*.





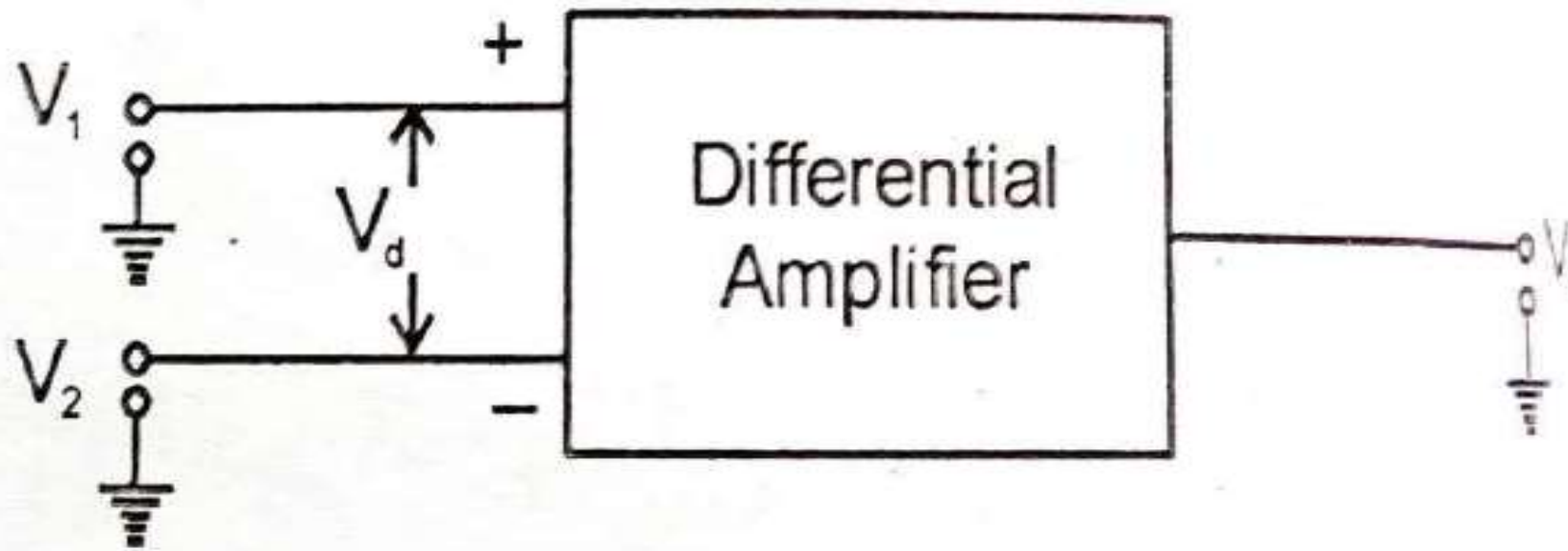
## **Block diagram of differential amplifier**


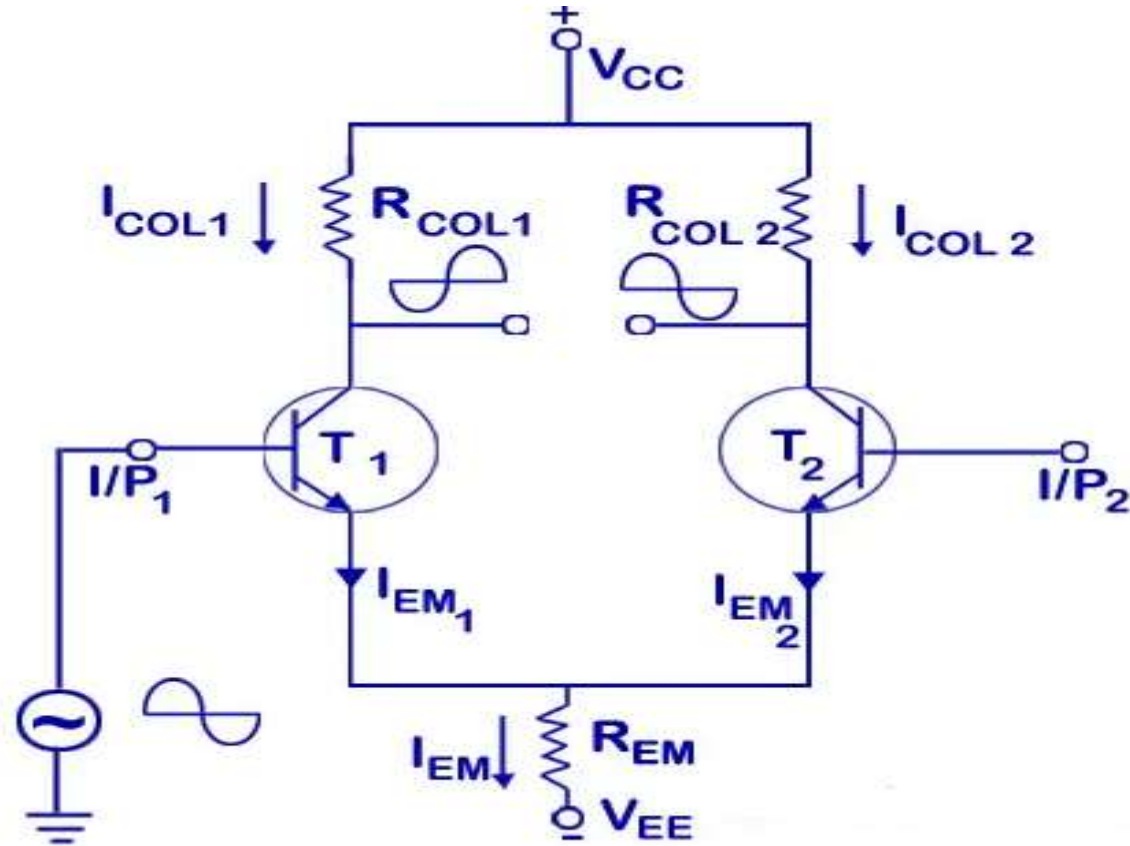
# Circuit Diagram of Differential Amplifier



# Operation

- The output signal in a differential amplifier is proportional to the difference between the two input signals.

$$V_o \propto (V_1 - V_2)$$

Where,

$V_1$  &  $V_2$  – Two input signals

$V_o$  – Single ended output



# Differential mode Gain

Differential Gain ( $A_d$ ):

$$V_o = A_d (V_1 - V_2)$$

Where,  $A_d$  is the **constant of proportionality**.

$A_d$  is the gain with which differential amplifier amplifies the difference of two input signals.

Hence it is known as '*differential gain of the differential amplifier*'.

$$A_d = \frac{V_o}{V_d} = -g_m R_C$$

$V_1 - V_2$  = Difference of two voltage

# Common mode Gain

## Common Mode Gain ( $A_c$ ):

An average of the two input signals is called common mode signal denoted as  $V_c$ .

$$V_c = \frac{V_1 + V_2}{2}$$

Hence, the differential amplifier also produces the output voltage proportional to common mode signals.

$$V_o = A_c V_c$$

Where  $A_c = -R_c / R_E$ , is the common mode gain.

Therefore, there exists some finite output for  $V_1 = V_2$  due to common mode gain  $A_c$ .

Hence the total output of any differential amplifier can be given as,

$$V_o = A_d V_d + A_c V_c$$



# CMRR

## Common Mode Rejection Ratio (CMRR):

- The ability of a differential amplifier to reject a common mode signal is defined by a ratio called '*Common Mode Rejection Ratio*' denoted as CMRR.
- **CMRR** is defined as the *ratio of the differential voltage gain  $A_d$  to common mode gain  $A_c$*  and is expressed in dB.


$$CMRR = A_d/A_c = g_m R_E$$

$$CMRR = 20 \log \left| \frac{A_d}{A_c} \right| dB$$



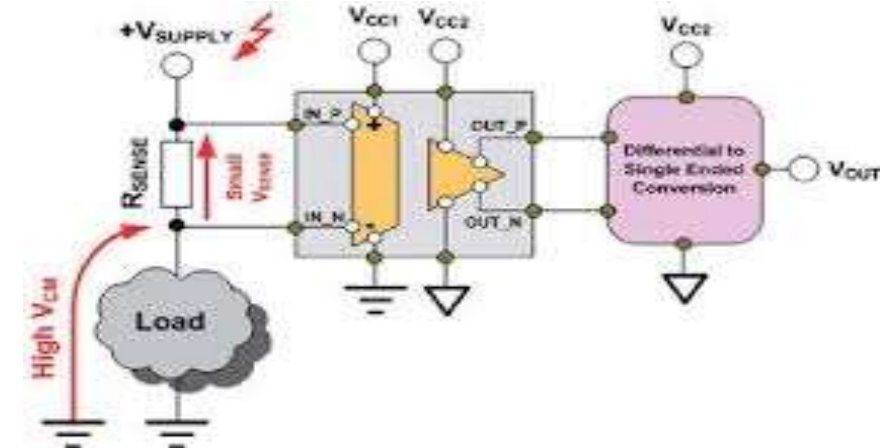
# Advantages & Applications

- Differential amplifiers are pervasive in analog electronics
  - Low frequency amplifiers
  - High frequency amplifiers
  - Operational amplifiers – the first stage is a differential amplifier
  - Analog modulators
  - Logic gates
- Advantages
  - Large input resistance
  - High gain
  - Differential input
  - Good bias stability
  - Excellent device parameter tracking in IC implementation
- Examples
  - Bipolar 741 op-amp (mature, well-practiced, cheap)
  - CMOS or BiCMOS op-amp designs (more recent, popular)





# RECAP....

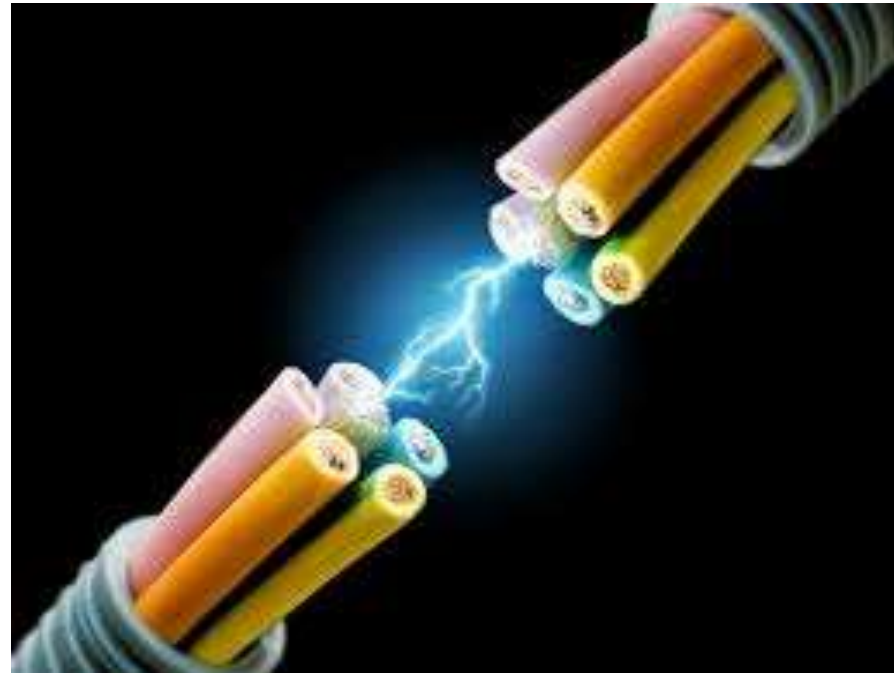

# ...THANK YOU

