



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35


Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



23EET104 / ANALOG ELECTRONICS CIRCUITS I YEAR / II SEMESTER

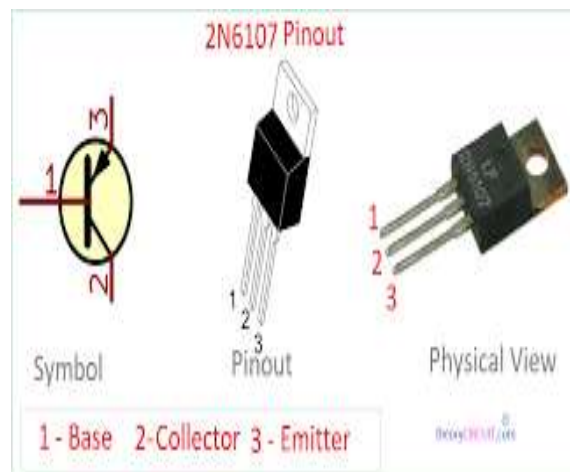UNIT-V: FEEDBACK AMPLIFIER AND OSCILLATOR



RC PHASE SHIFT OSCILLATOR





Introduction to RC Phase Shift Oscillators

Oscillators produce continuous waveforms autonomously.

Used in clocks, radios, and signal generators.

Main types: sinusoidal and non-sinusoidal oscillators.




by Senthil Kumar R.





What is an RC Phase Shift Oscillator?

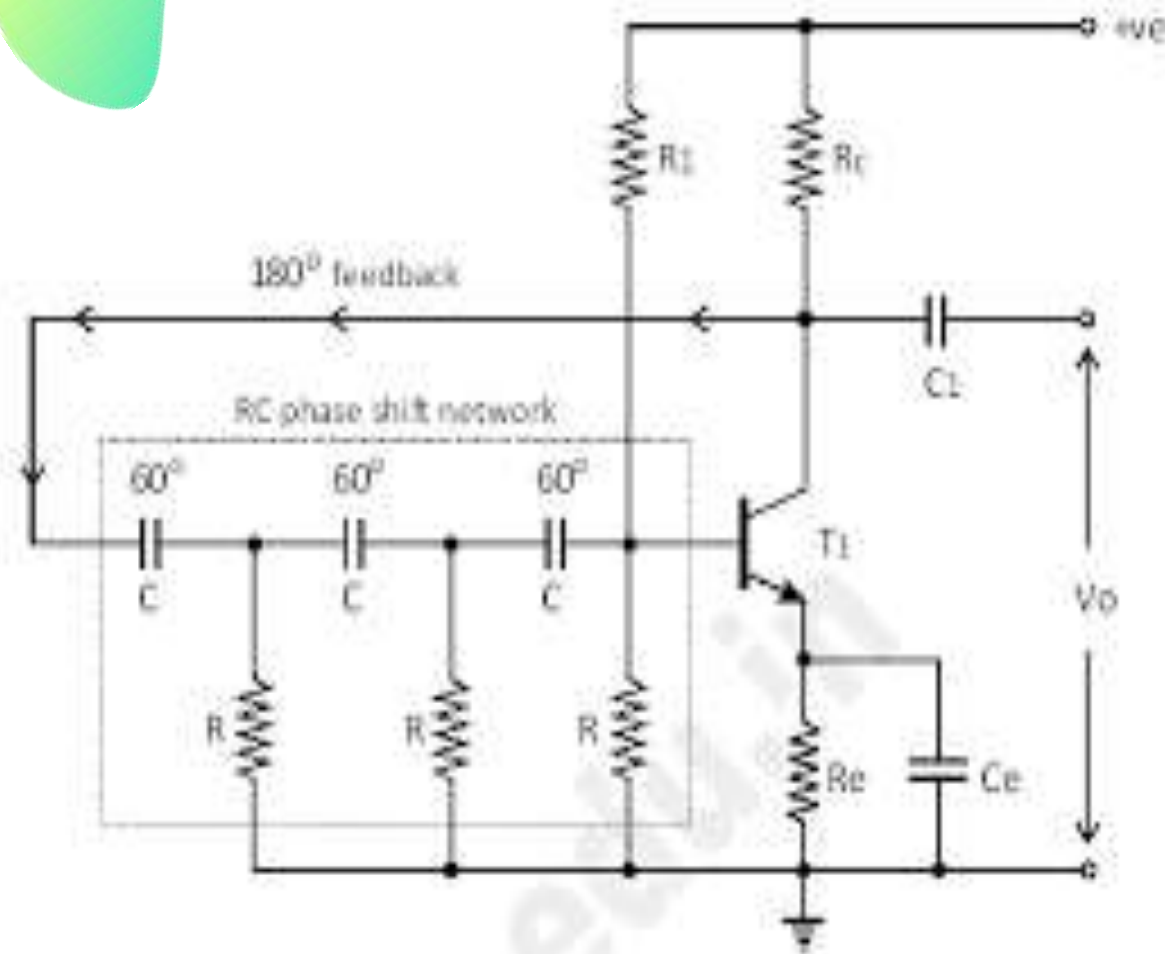

Sinusoidal Oscillator
with positive feedback
Generates smooth sine wave
outputs

RC phase shift network
Provides 180° phase shift via
resistor-capacitor sections

Transistor Amplifier

Common-emitter or op-amp adds 180° phase shift



Basic Circuit Diagram

Amplifier

Transistor or operational amplifier

RC Network


Three cascaded resistor-capacitor sections


Power Supply

Provides necessary voltage and current

Output

Continuous sinusoidal waveform

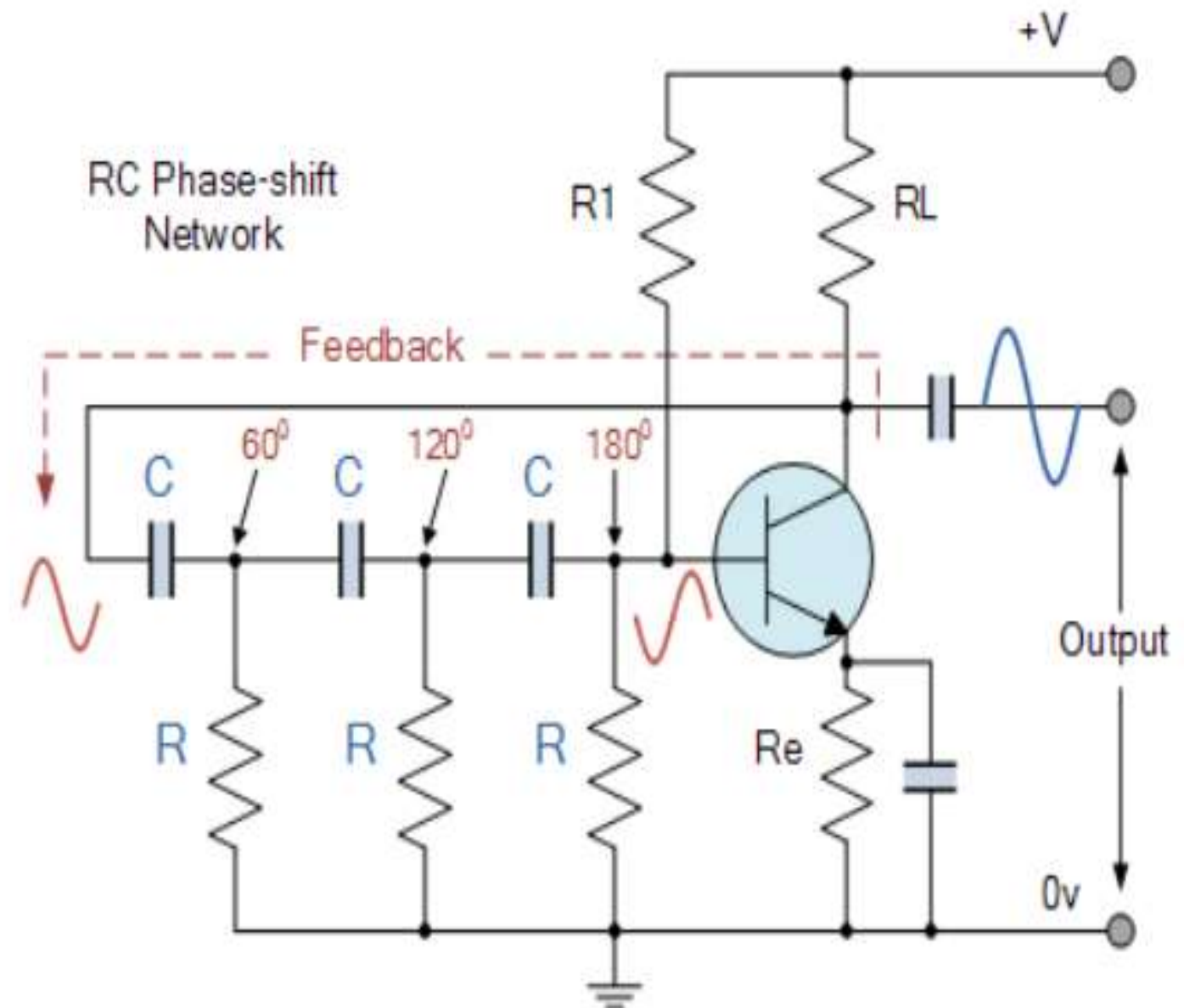

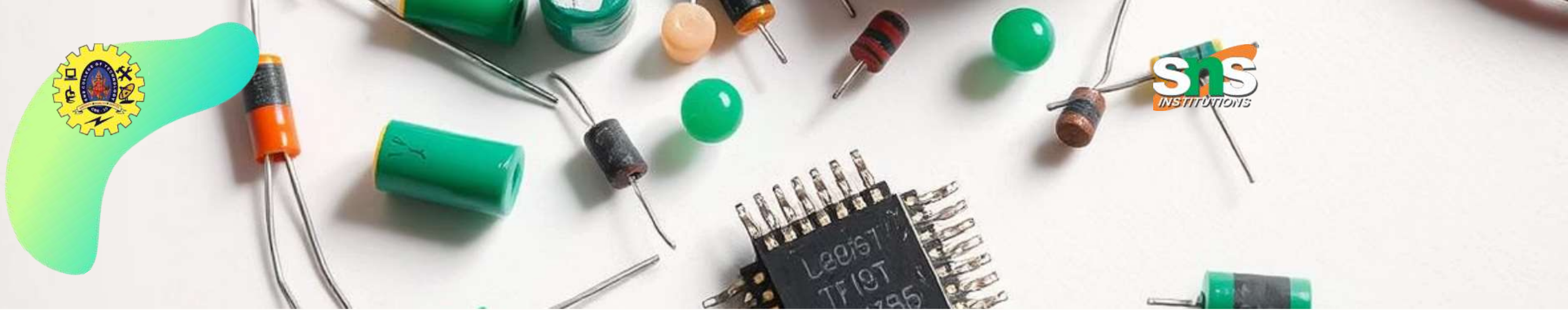

Components Used



Resistors (R)

Set phase shift and control gain



Capacitors (C)

Work with resistors in phase shift network



Amplifier

BJT or operational amplifier for gain



Power Supply

Supplies energy for oscillation



Working Principle

- The primary component of an RC phase shift oscillator is a phase shift network consisting of a series of resistors and capacitors.
- This network generates a phase shift of 180 degrees at the desired oscillation frequency, which is then combined with an additional 180 degrees of phase shift from an amplifier to create a total of 360 degrees phase shift.
- When the total phase shift is equal to an integer multiple of 360 degrees
- Hence a stable oscillation is achieved.



Frequency of Oscillation

Formula

$$f = 1 / (2\pi RC\sqrt{6}) \text{ for 3 RC stages}$$

R

Resistance controls frequency

C


Capacitance adjusts oscillation rate

Frequency

Dependent on R and C values

$$F - F_{y3} - E_2 = +EaFa) =$$
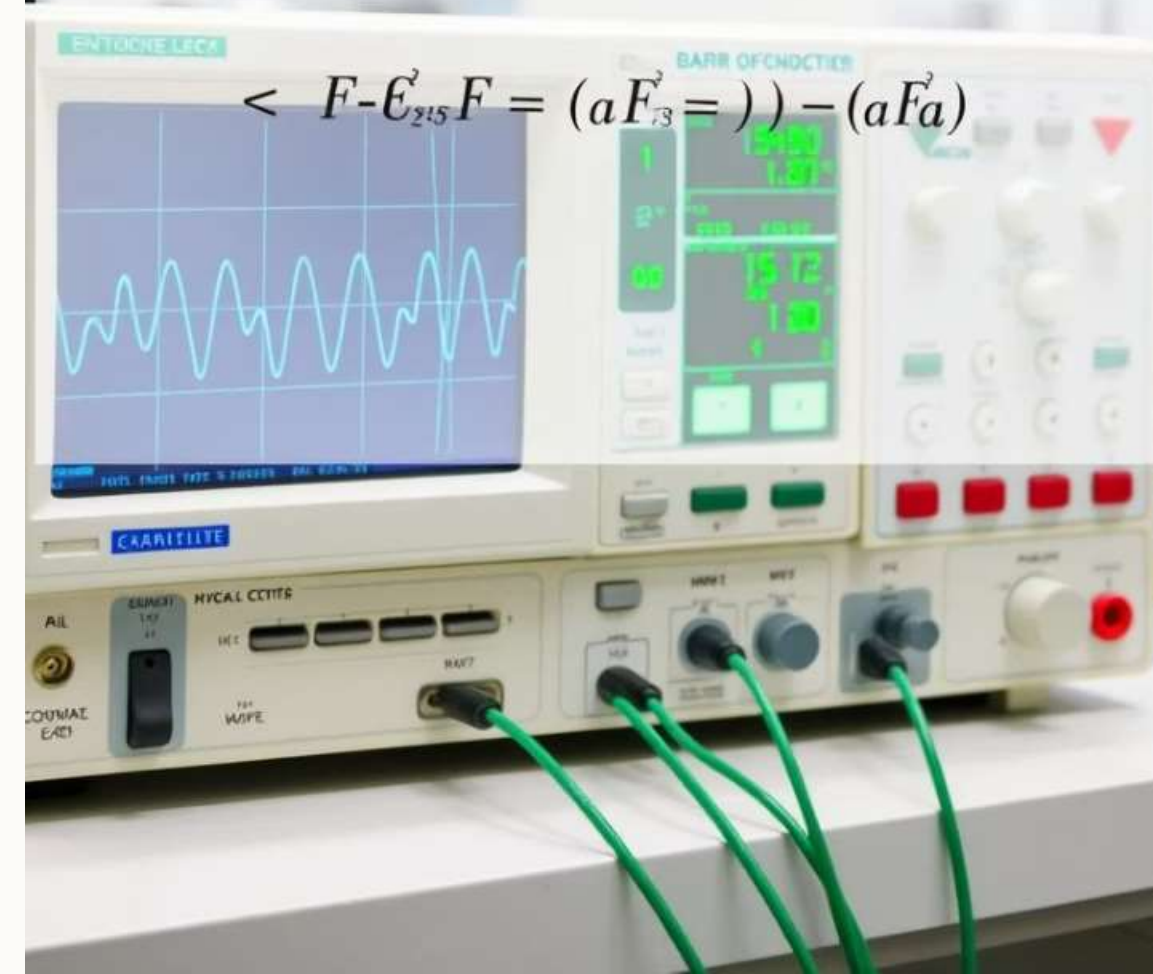
$$< F - E_{215} F = (aF_{13} =) - (aFa)$$





Barkhausen Criteria

1

Loop Gain ≥ 1

2

Total Phase Shift = 360°


3

RC Network Phase Shift = 180°

4

Amplifier Phase Shift = 180°

Barkhausen Criterion for Oscillator

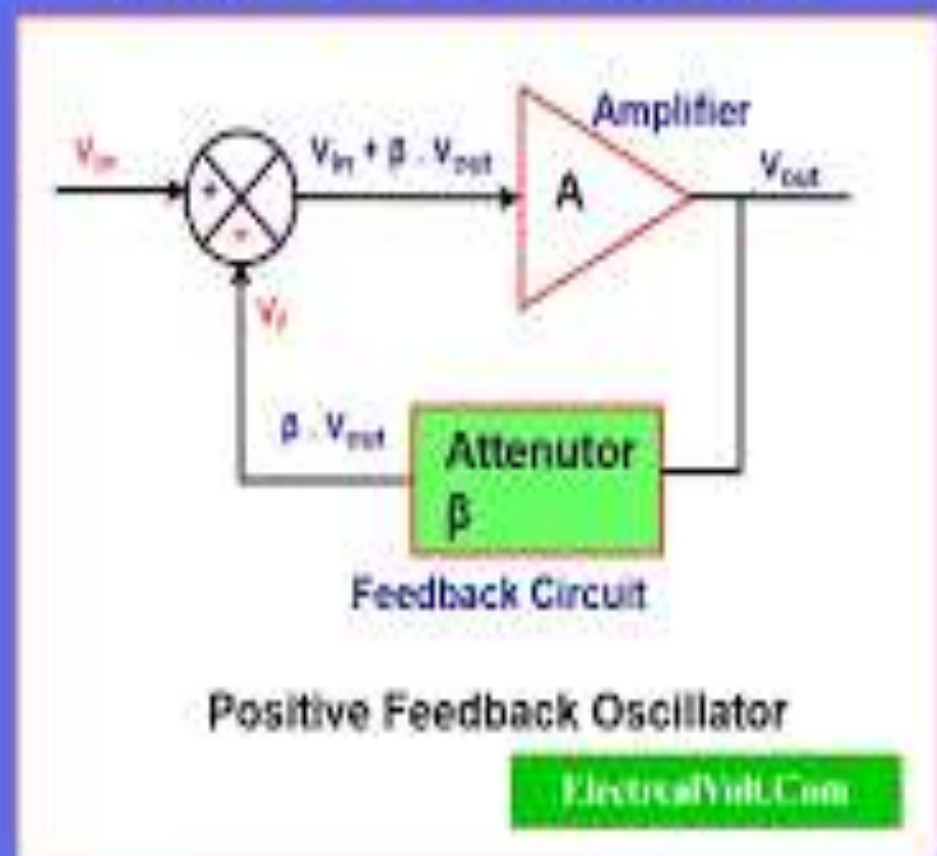




Advantages & Disadvantages

Advantages

- Simple, low cost design
- Good frequency stability

Disadvantages

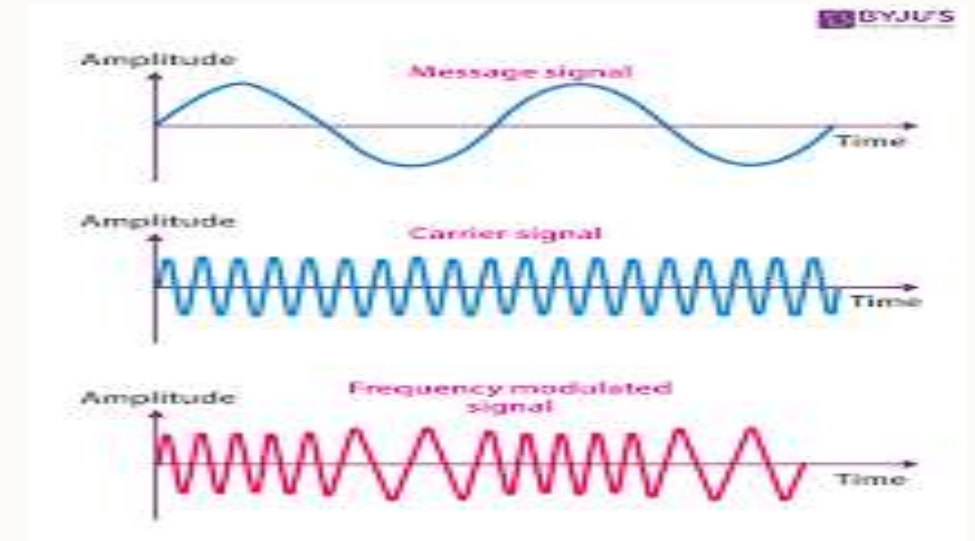- Limited to low frequencies
- Amplitude varies with temp/supply






Applications

Audio Frequency Generation

Sine Wave Generators

Function Generators

Signal Modulation Systems

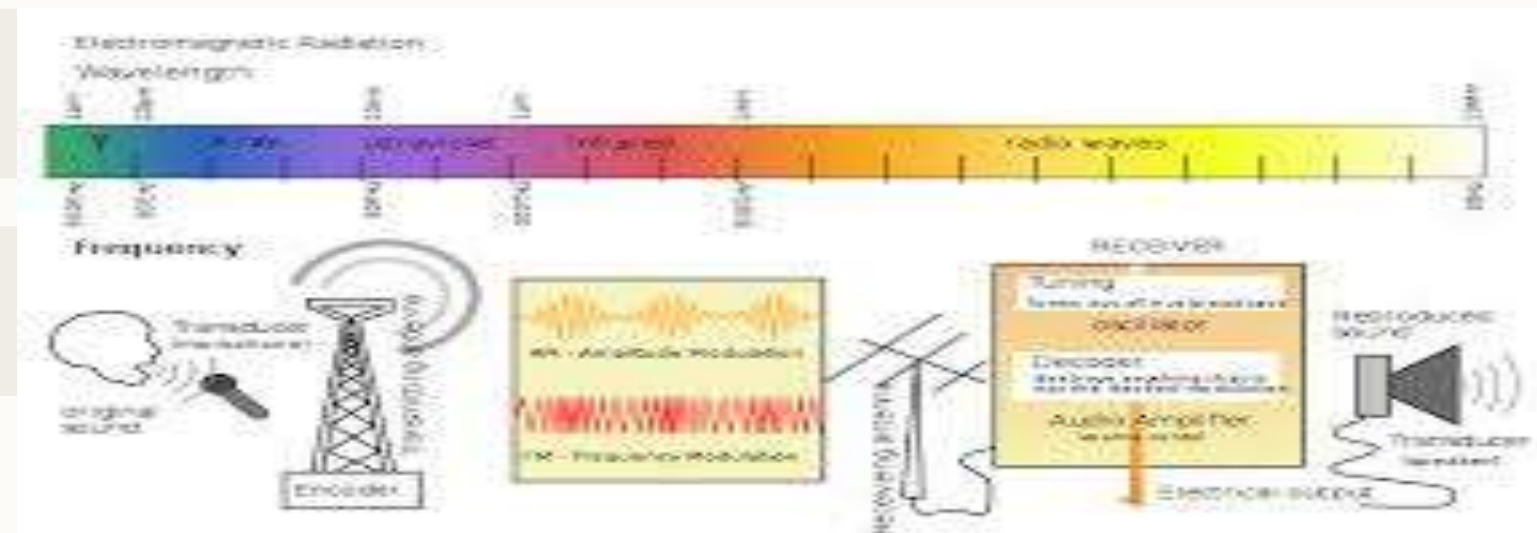



Conclusion

- Low-Frequency Sine Wave Source

- Easy Implementation

- Uses basic resistors, capacitors, and amplifiers

- Relies on Phase Shift & Feedback

- Positive feedback sustains oscillation

