



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35


Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



23EET104 / ANALOG ELECTRONICS CIRCUITS I YEAR / II SEMESTER

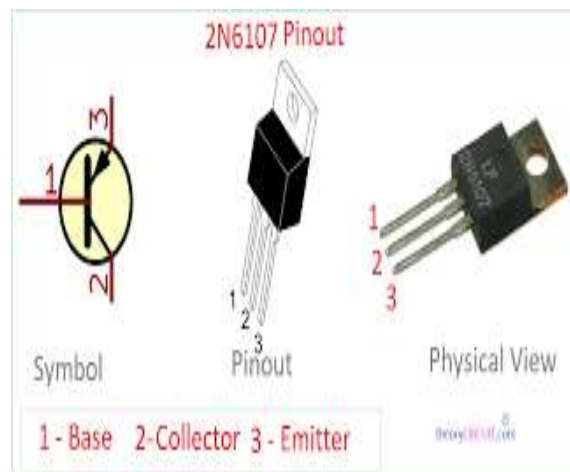UNIT-V: FEEDBACK AMPLIFIER AND OSCILLATOR



CRYSTAL OSCILLATOR






Understanding Crystal Oscillators

This presentation explores crystal oscillators, vital for stable frequencies in electronics. We cover principles, circuits, advantages, types, and applications.



by Senthil Kumar R.

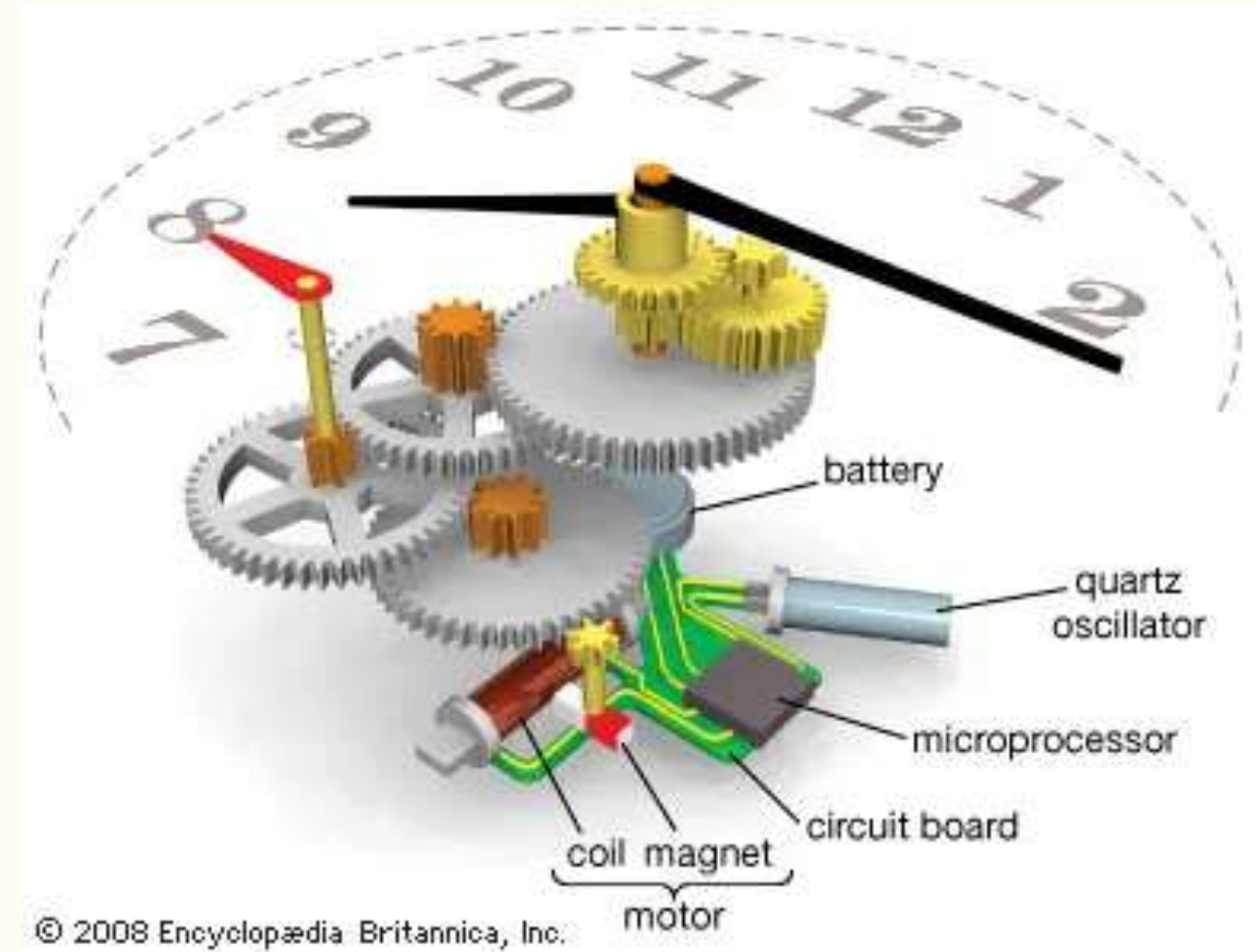



What is a Crystal Oscillator?

Definition

A **crystal oscillator** uses a **piezoelectric crystal** for frequency generation.

Key Features


- Stable and precise frequency
- Long-term reliability
- Common in clocks, microcontrollers, comm devices





Piezoelectric Effect

Direct Piezoelectric Effect Principle

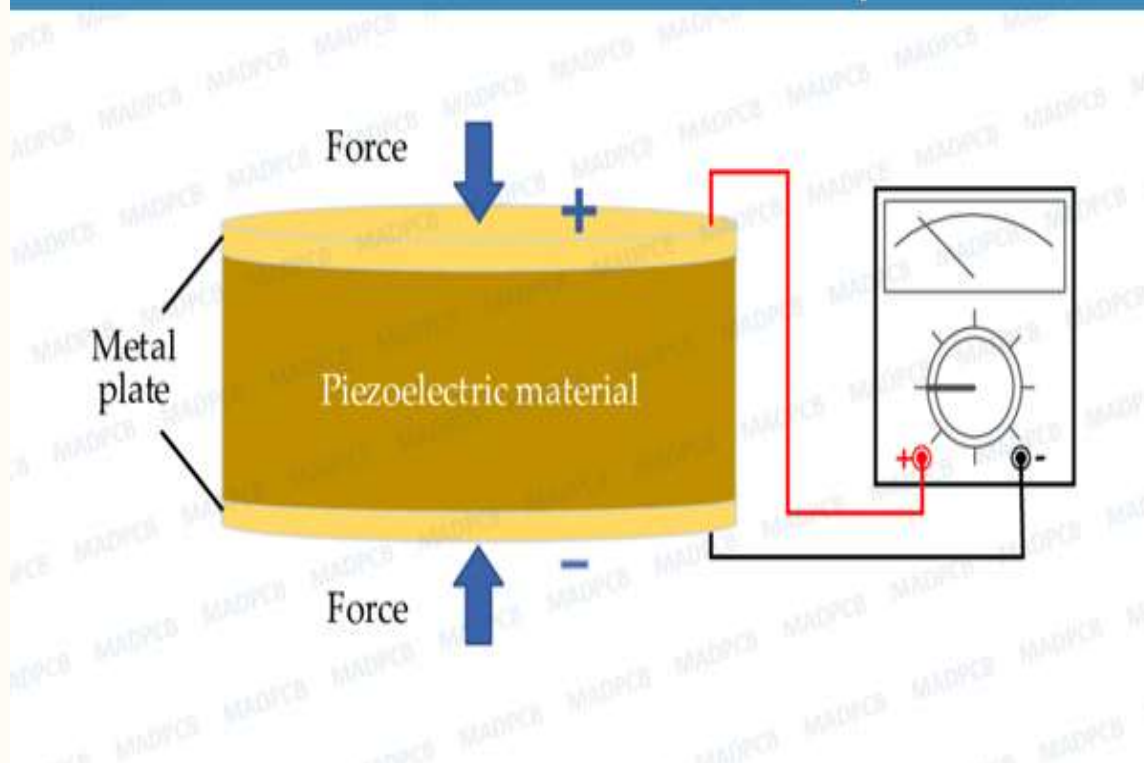

Voltage Application

Voltage causes crystal to mechanically vibrate at resonant frequency.

Mechanical Stress


Mechanical stress generates electric charge in crystal.

High Q Resonance

Crystal acts like a high-Q tuned LC circuit.



Equivalent Circuit of a Crystal

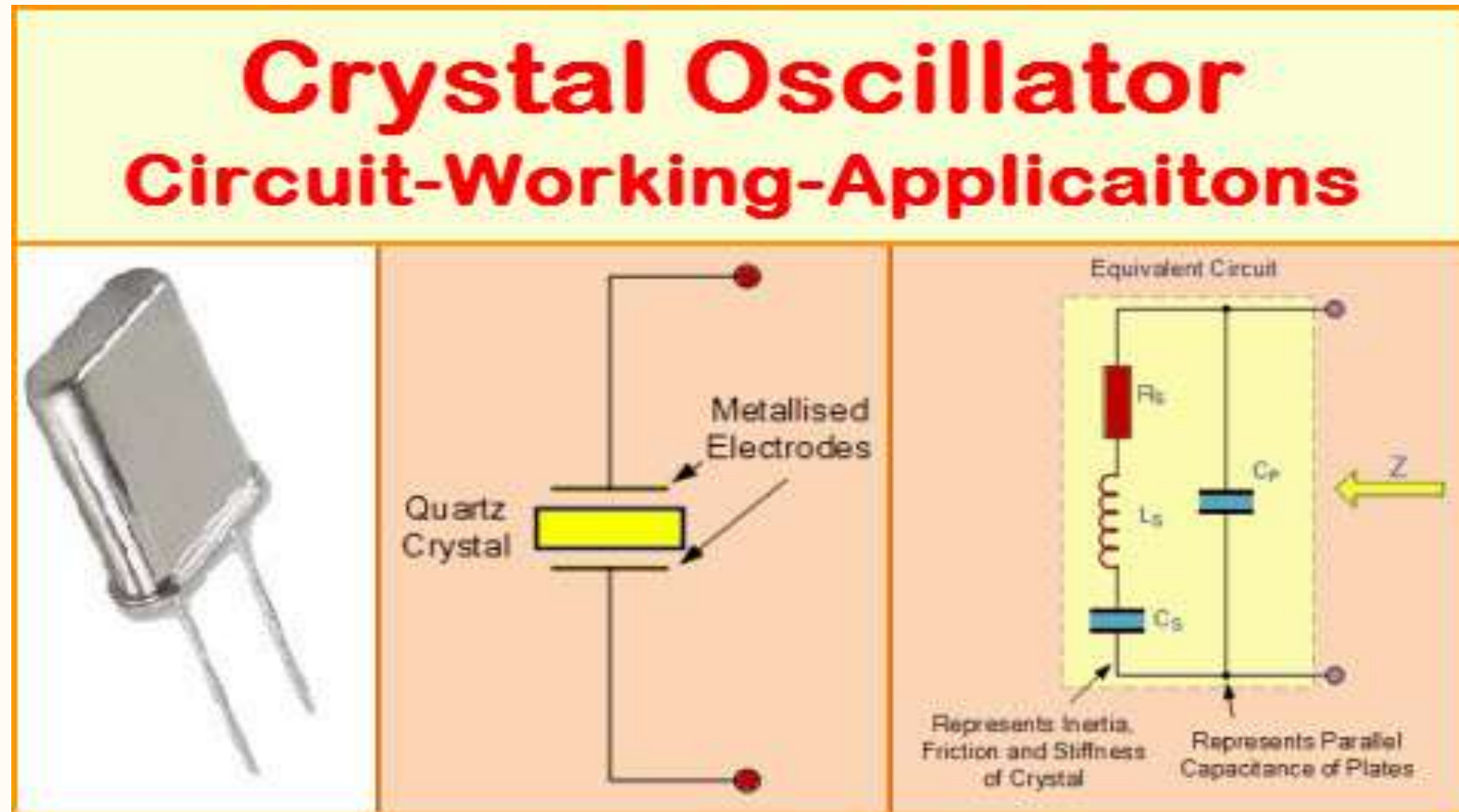


Represents the crystal's electrical behavior as a series RLC circuit in parallel with capacitance C_0 .




Crystal Oscillator Circuit

Key Components

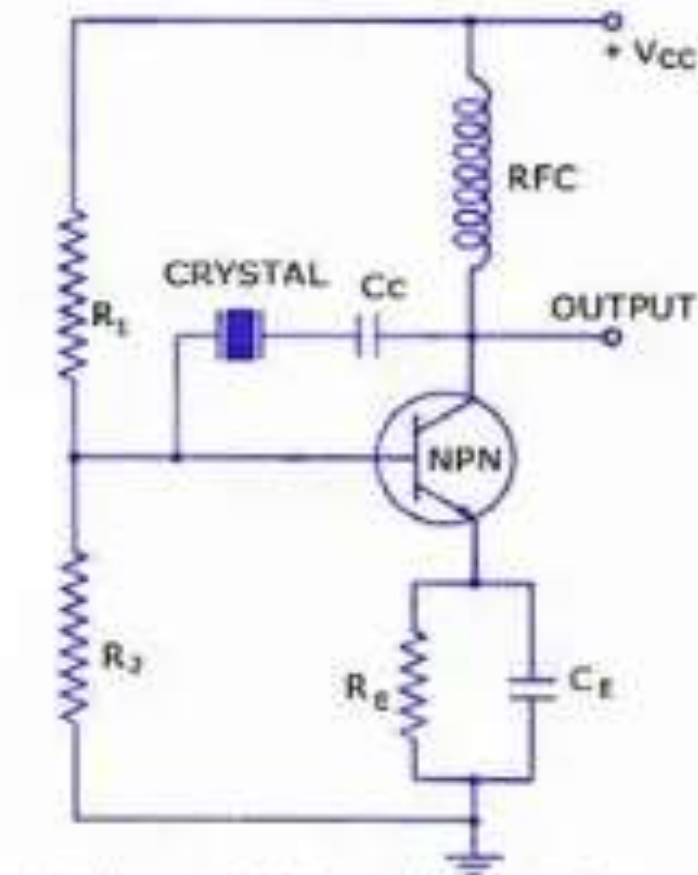- Crystal (XTAL)
- Capacitors and resistors
- Transistor or logic inverter
- Feedback network



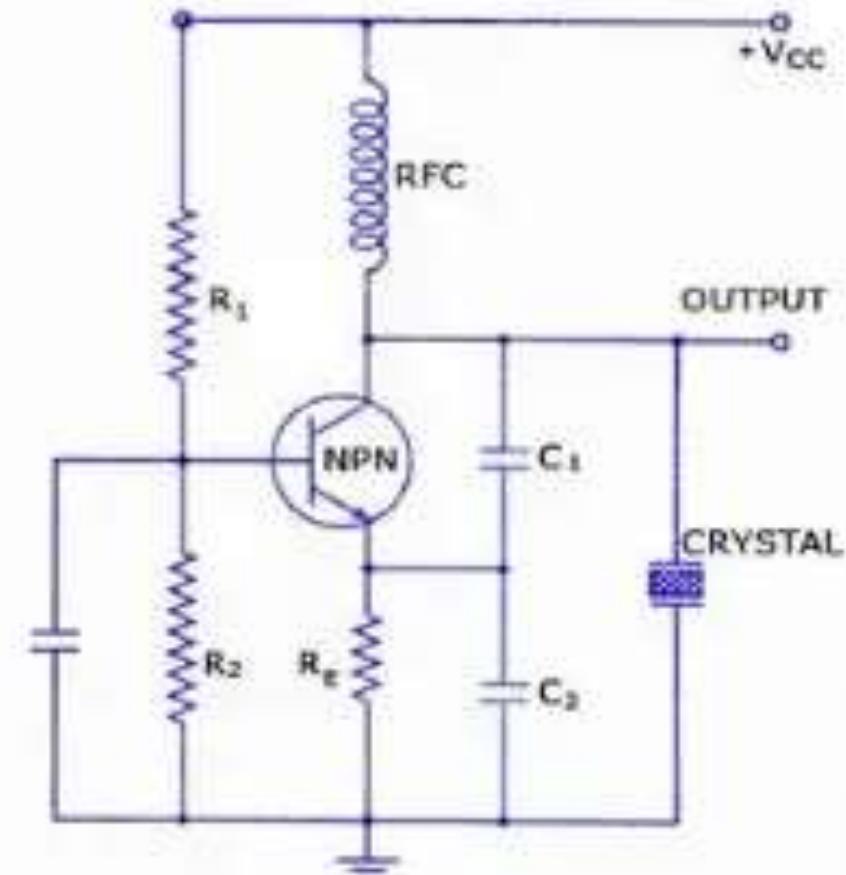Oscillator With Crystal Operating in Series Resonance



Oscillator With Crystal Operating in Parallel Resonance




Principle of Operation

A crystal oscillator uses a piezoelectric crystal, like quartz, to generate a stable and precise electrical signal at a specific frequency.


This is achieved by applying voltage to the crystal, causing it to vibrate at its natural resonant frequency, which is then converted into an electrical signal.

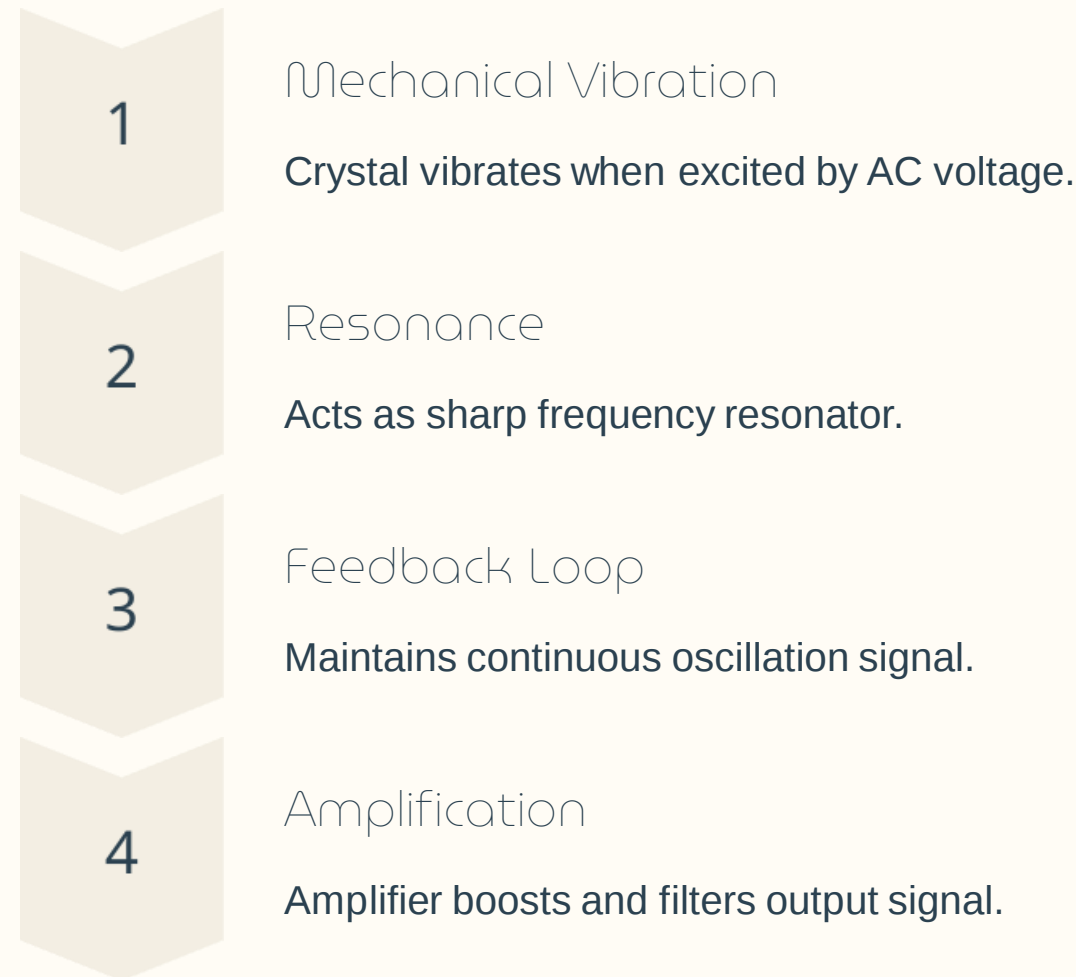The crystal's vibrations are sustained by a feedback loop that amplifies and feeds back the signal to the crystal, sustains oscillation.






Frequency Stability

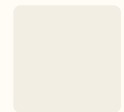

High Q-Factor

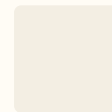Ensures low signal loss and sharp resonance.




Temperature Sensitivity

Low drift with temperature changes.



Aging Effects

Minimal frequency shift over years.

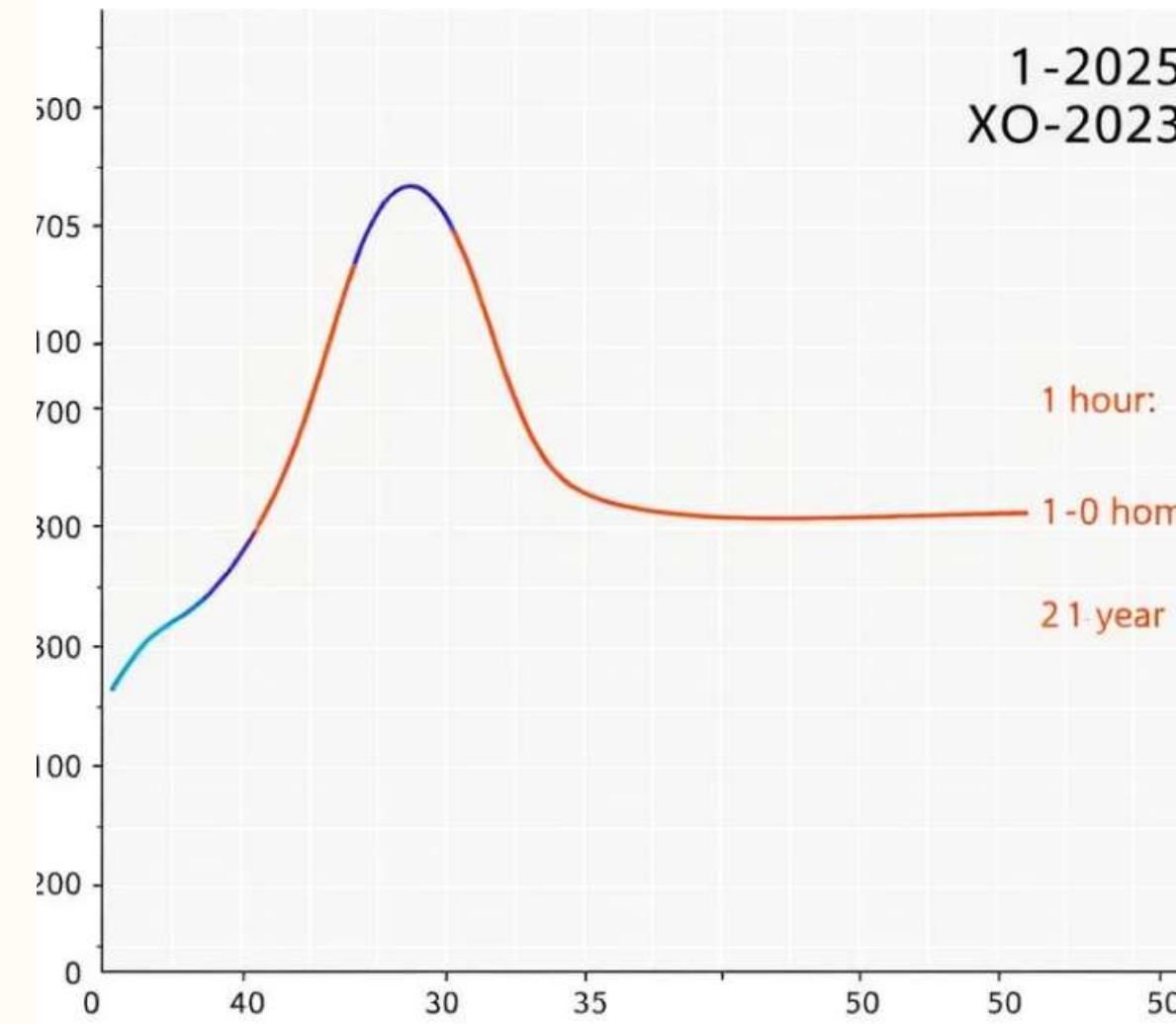




Advantages and Disadvantages

Advantages

- High frequency accuracy
- Very low phase noise
- Long-term stability

Disadvantages

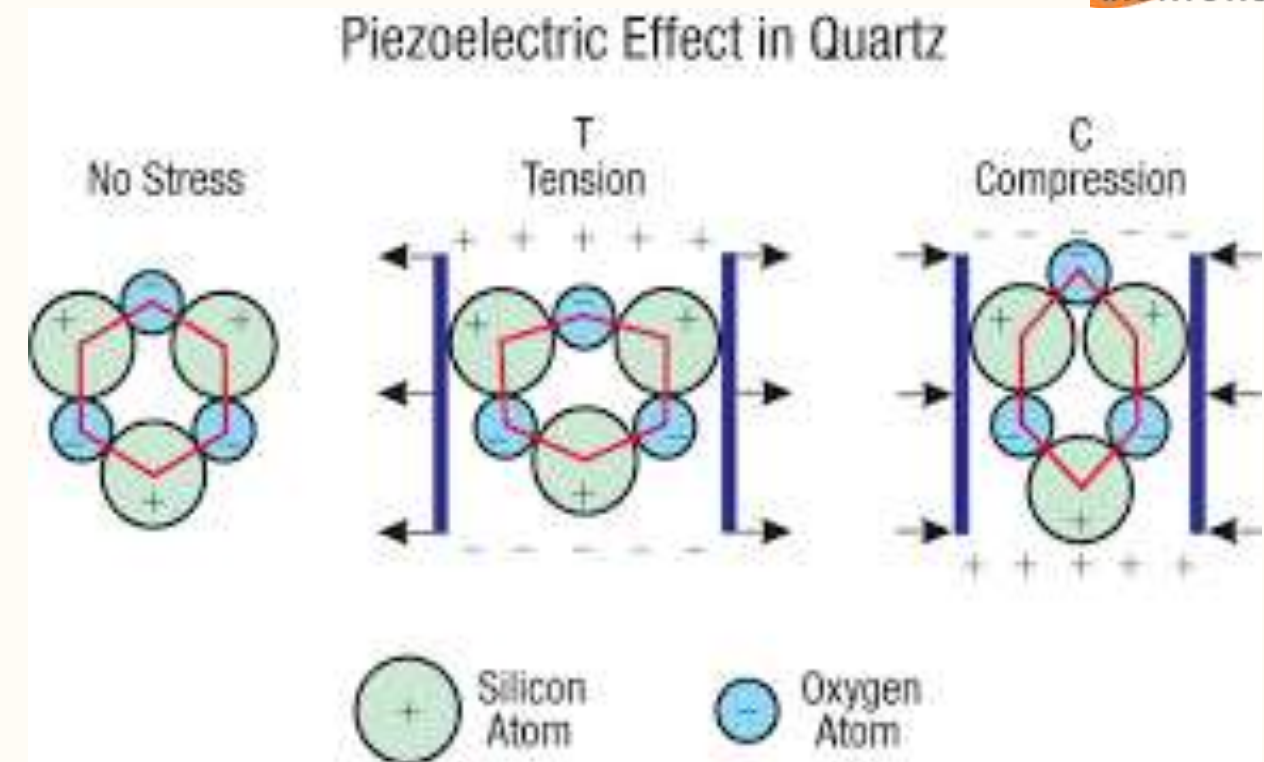
- Fixed frequency, limited tuning
- Mechanical shock sensitive
- Higher cost than RC/LC oscillators



Piezo Electric in QUARTZ



Crystal oscillator

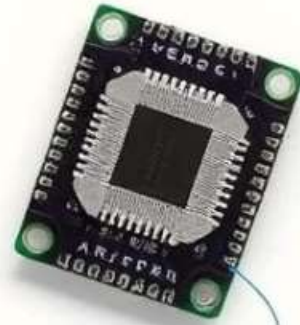


Microcontroller



Applications of Crystal Oscillators



Watches &
Clocks

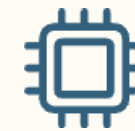

Microcontrollers



Communication
Systems



GPS Devices



Communication



Crystal oscillator

Digital oscillator

23EET104 / AEC / R.SENTHIL KUMAR / EEE



Types and Conclusion

1

Pierce Oscillator

Simple, popular design using inverter and crystal.

2

Colpitts Oscillator

Uses capacitive voltage divider and crystal.

3

Butler Oscillator

Stable oscillator with feedback from crystal.

4

OCXO & TCXO

Temperature compensated and oven-controlled for ultra stability.

Crystal oscillators deliver precise, stable frequencies vital to modern electronics.