

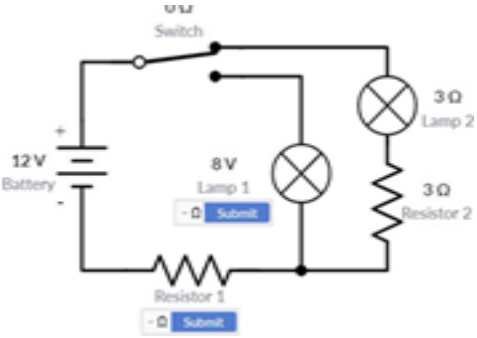

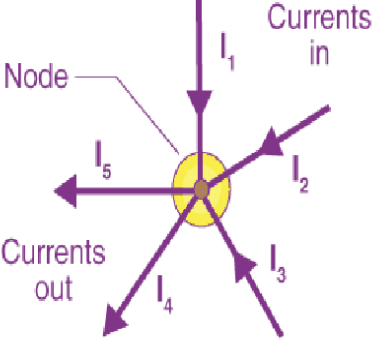
DEPARTMENT OF EEE

Course Code & Name : 23EET101- Basic Electrical and Electronics Engineering

Course Faculty : Ms.R.Revathi

Puzzles / In Class Activities

Find / Write the Answers:

Action	Electrical Circuits
 <p>The current is 1500ma ,If the switch is operated on opposite direction what will be the current.</p>	<p>----- (mA)</p>
	
 <p>Observe the given circuit picture and find the equation.</p>	

