



# SNS COLLEGE OF TECHNOLOGY

Coimbatore-35  
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade (III Cycle)  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

### 19ECB302-VLSI DESIGN

III YEAR/ V SEMESTER

### UNIT 1 –MOS TRANSISTOR PRINCIPLE

### TOPIC 8 –STICK DIAGRAM

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT



## OUTLINE



- INTRODUCTION
- CMOS INVERTER
- MAPPING:STICK DIAGRAM -> CMOS TRANSISTOR CIRCUIT
- NMOS INVERTER-STICK DIAGRAM
- STATIC CMOS NAND GATE
- STATIC CMOS NOR GATE
- STATIC CMOS EXAMPLES-2 STYLES
- ACTIVITY
- EULER PATH
- YOUTUBE VIDEO
- ASSESSMENT

30 July 2024


STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT




## STICK DIAGRAMS-INTRODUCTION



- Intermediate representation between circuit diagram and layout
- Symbolic design is "Stickş" layout.
- Metal-wire
- VDD-power supply
- POLY-Polysilicon (Gate)
- NDIFF-N diffusion(Source)
- PDIFF-P diffusion(Drain)
- VSS-Ground
- A,B-Input
- Y-Output

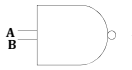SYMBOL   $W_p = 5u$   
 $W_n = 2.5u$

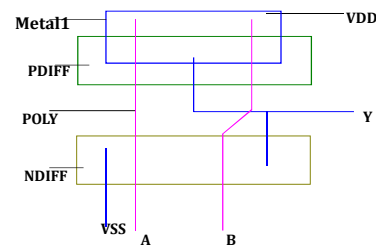




Symbol and Stick Diagram of 2 inputs NAND gate

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT



## CMOS INVERTER STICK DIAGRAM

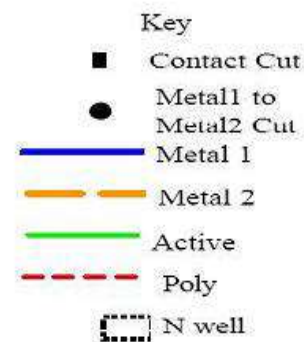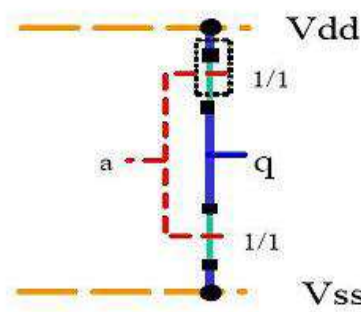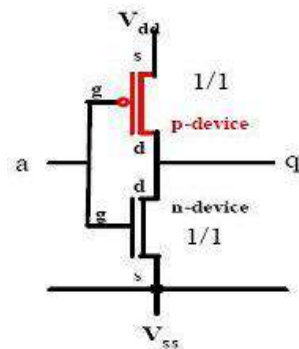


30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT


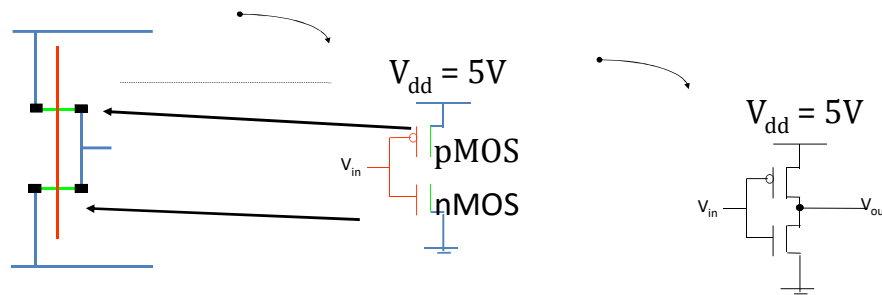
## MAPPING:STICK DIAGRAM -> CMOS TRANSISTOR CIRCUIT




30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.V.S.Nishok/Assistant Professor/ECE/SNSCT



## NMOS INVERTER COLOURED STICK DIAGRAM

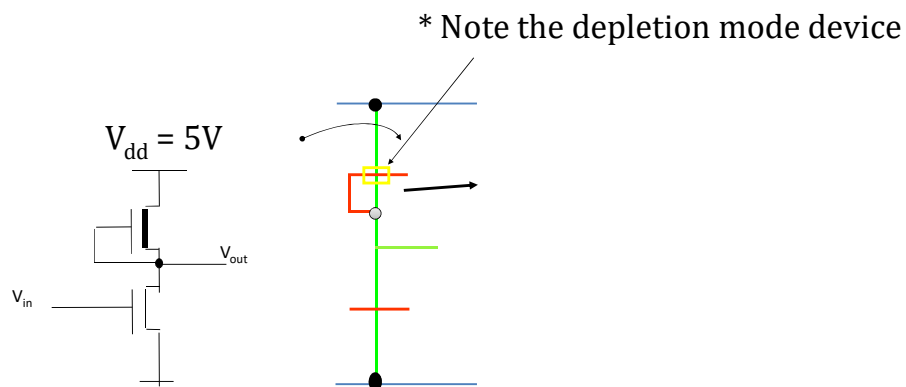


30 July 2024


STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.V.S.Nishok/Assistant Professor/ECE/SNSCT



## STATIC CMOS NAND GATE

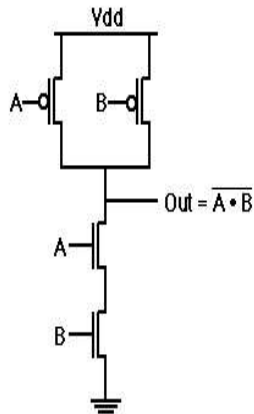

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

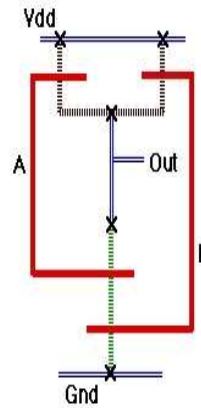


--Pull Down:  
Connect to  
ground If A=1  
**AND** B=1  
--Pull Up:  
Connect to VDD  
If A=0 **OR** B=0

30 July 2024


STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT



## STATIC CMOS NOR GATE

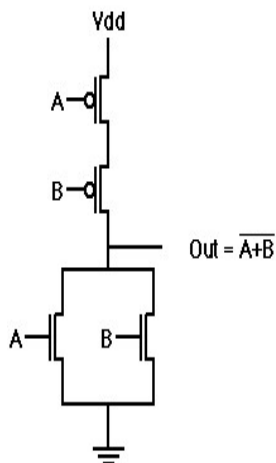

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

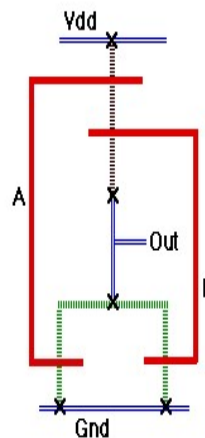



--Pull Down:  
Connect to  
ground If A=1 **OR**  
B=1  
--Pull Up:  
Connect to VDD  
If A=0 **AND** B=0

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT


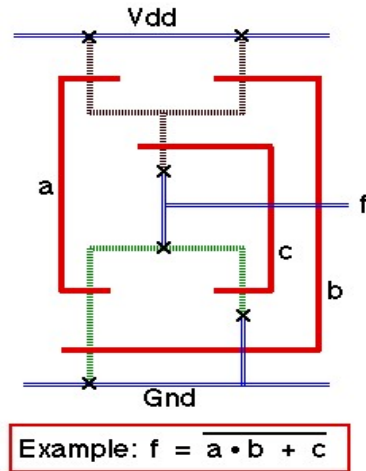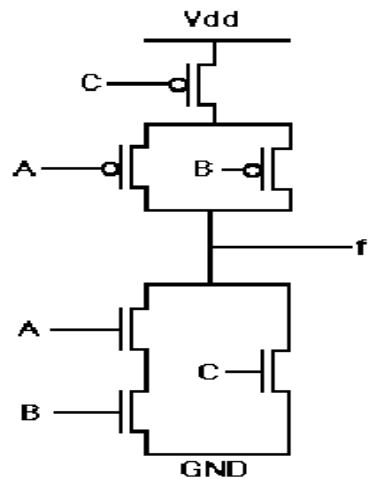
## STATIC CMOS DESIGN EXAMPLE STICK DIAGRAM





30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT


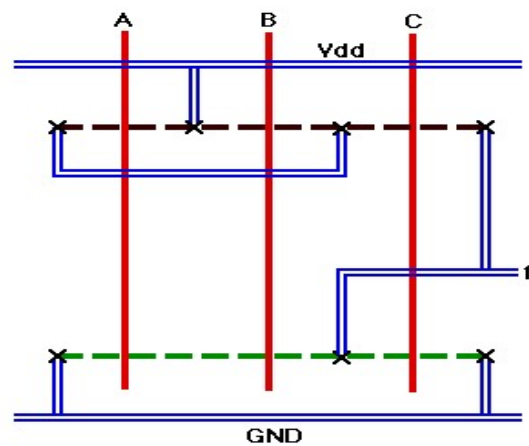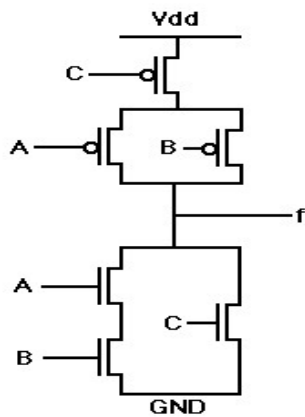
## STICK DIAGRAM 2 (DIFFERENT LAYOUT STYLE TO PREVIOUS BUT SAME FUNCTION BEING IMPLEMENTED)



Example:  $f = \overline{(A \cdot B)} + C$

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT



## COMPLEX LOGIC GATES LAYOUT



EX:  $F = AB + E + CD$


### Euler paths

Circuit to graph (convert)

- 1) Vertices are source/Drain connections
- 2) Edges are transistors

Find p and n Euler paths

$$F = (AB) + E + (CD)$$

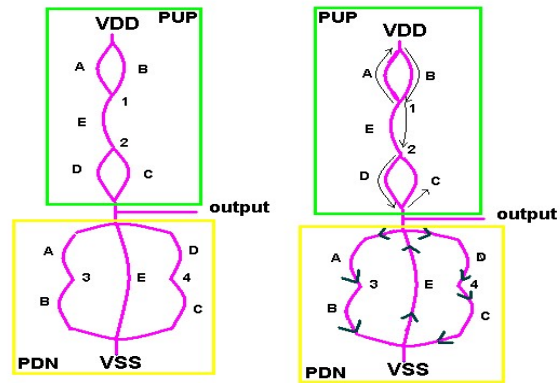


EULER PATH = {A,B,E,D,C}

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT



## CLASS ROOM ACTIVITY

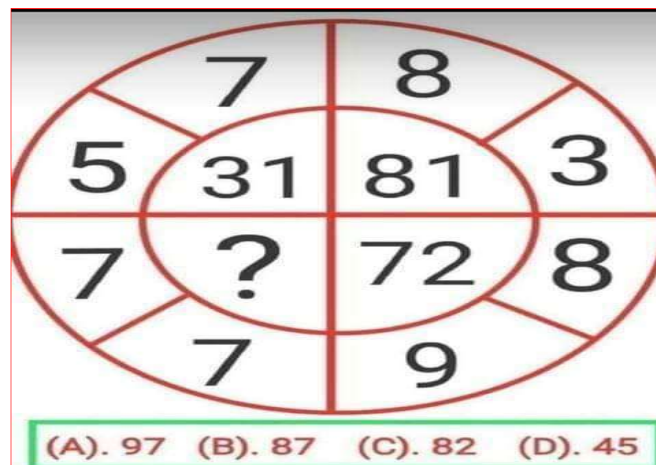

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT




## EULER PATH



EULER PATH = {A,B,E,D,C}

— METAL 1  
— POLY  
— ACTIVE

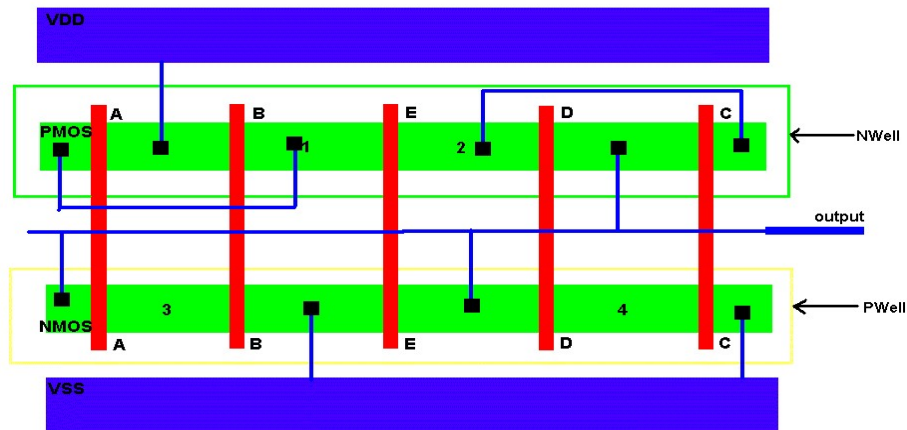

30 July 2024


STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT


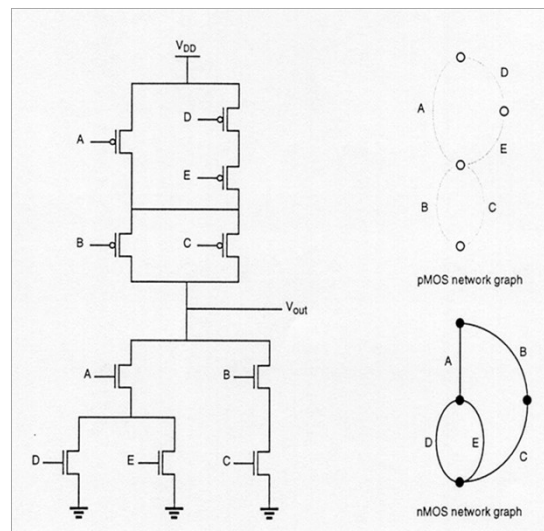
## PMOS & NMOS



- This notation indicates only the relative positioning of the various design components.
- The absolute coordinates of these elements are determined automatically by the editor using a compactor.
- The compactor translates the design rules into a set of constraints on the component positions, and solve a constrained optimization problem that attempts to minimize the area or cost function.




30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT



## EULER GRAPH-STICK DIAGRAM COMPARISON

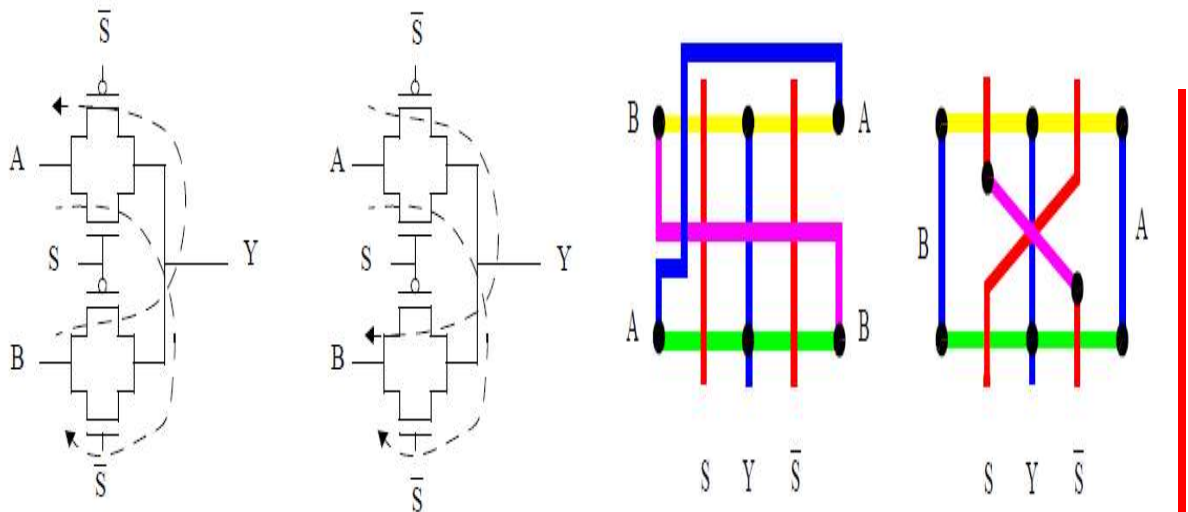

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT



## YOUTUBE VIDEO LINK



STICK DIAGRAM - simplified (VLSI)

<https://www.youtube.com/watch?v=wqRGa5sOUmc&t=212s>

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT






## ASSESSMENT- CMOS INVERTER COLOURED STICK DIAGRAM



 - 1.DRAW THE CMOS INVERTER STICK DIAGRAM
- 2.DRAW THE CMOS NAND GATE



3.TELL ME THE COLOR CODING NAME ????????

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT



## ADVANTAGE & DISADVANTAGE



- ADVANTAGE** :Designer does not have to worry about design rules, because the compactor ensures that the final layout is physically correct.
- DISADVANTAGE** : The outcome of the compaction phase is often unpredictable. The resulting layout can be less dense than what is obtained with the manual approach.It does not show exact placement, transistor sizes, wire lengths, wire widths, tub boundaries.

To easy remember

.ns  
Dot-NAND,  
n-NMOS,S-  
Series

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT



## SUMMARY & THANK YOU

30 July 2024

STICK DIAGRAM /19ECB302-VLSI DESIGN/Dr.VS.Nishok/Assistant Professor/ECE/SNSCT