



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++'
Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECT201-ELECTRONIC CIRCUITS

UNIT 1 BJT AND FET BIASING

TOPIC 1 : OPERATING POINT



OPEARTING POINT



Q-point: It is point on load line which represents DC value of V_{CE} and I_C in absence of signal. Best position is mid-point on load line, $V_{CE} = \frac{1}{2} V_{CC}$

- ▶ For transistor amplifiers the resulting dc current and voltage establish an operating point on the characteristics that define the region that will be employed for amplification of the applied signal.
- ▶ Since the operating point is a fixed point on the characteristics, it is also called the quiescent point (abbreviated Q-point).
- ▶ By definition, quiescent means quiet, still, inactive. Figure shows a general output device characteristic with four operating points indicated.




NEED OF OPERATING POINT

- ▶ Temperature causes the device parameters such as the transistor current gain (β) and the transistor leakage current (I_{CEO}) to change.
- ▶ Higher temperatures result in increased leakage currents in the device, thereby changing the operating condition set by the biasing network. The result is that the network design must also provide a degree of *temperature stability so that temperature changes result* in minimum changes in the operating point.
- ▶ This maintenance of the operating point can be specified by a *stability factor, S* .




DC LOAD LINE

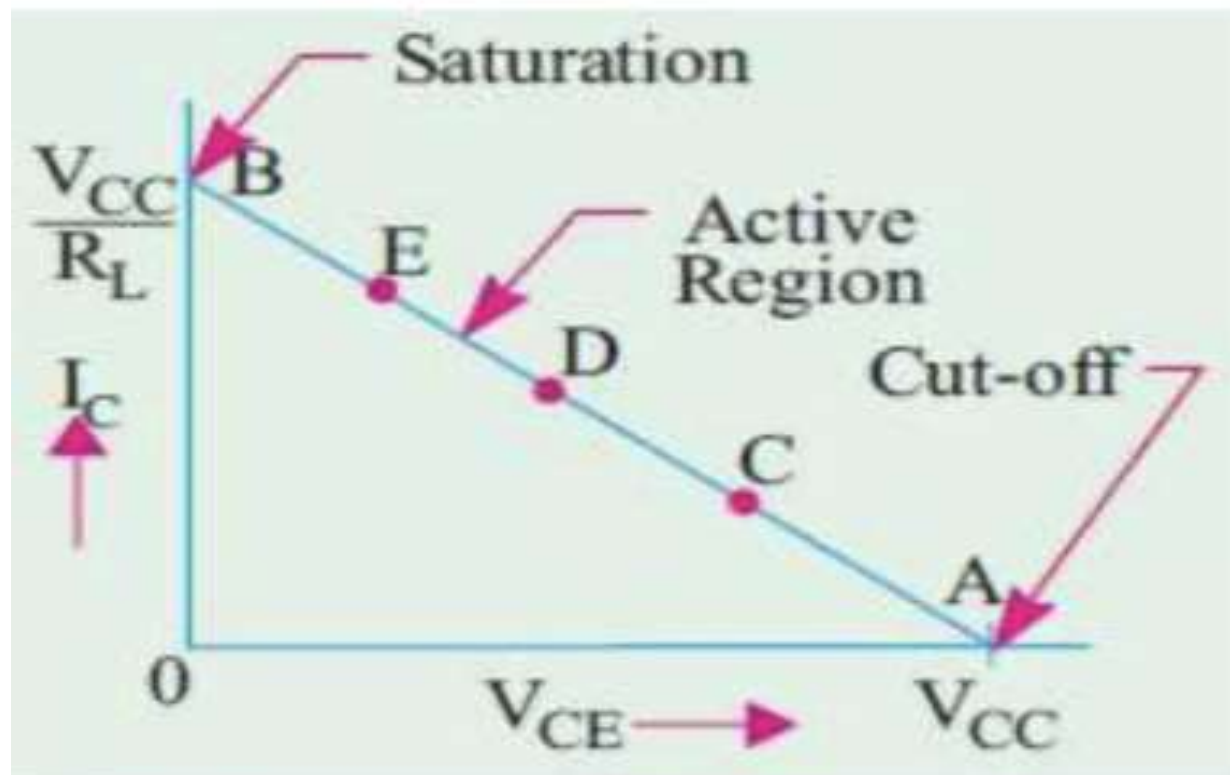- ▶ Load line: locus of operating point on o/p characteristics of transistor
- ▶ A line on which operating point moves according to input ac signal






▶ 3

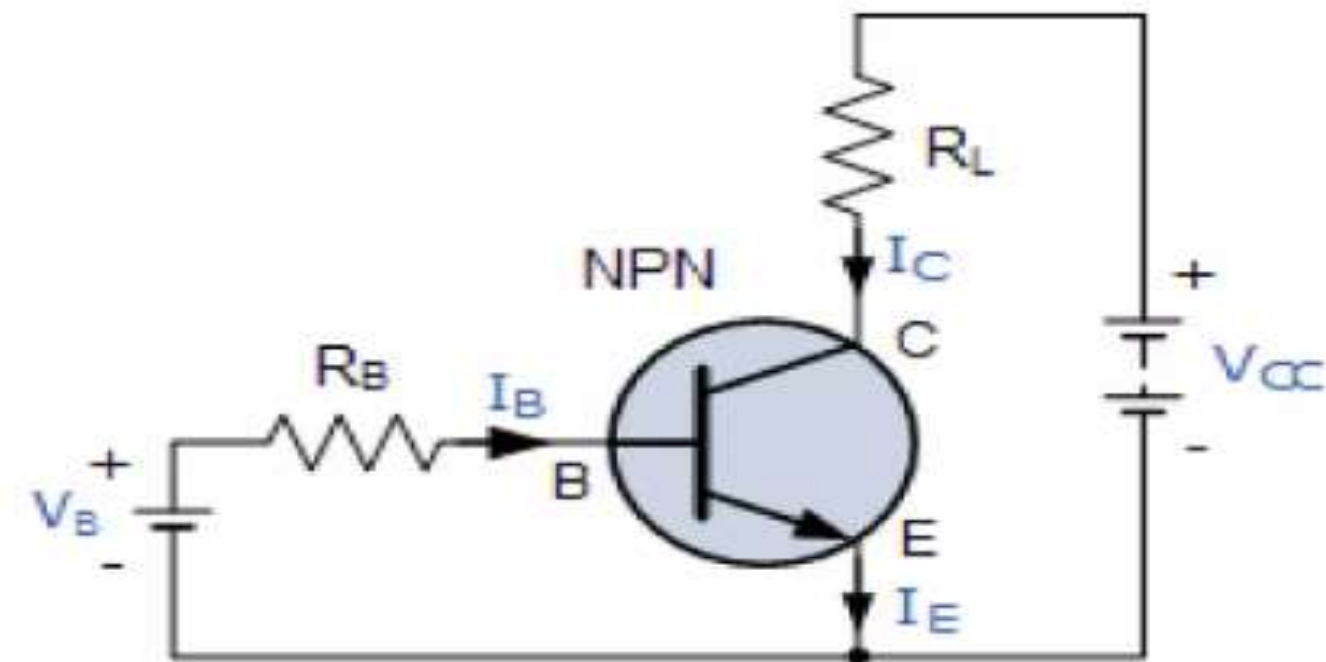

$$V_{CC} = I_C R_L + V_{CE} \quad \therefore \quad I_C = \frac{V_{CC}}{R_L} - \frac{V_{CE}}{R_L}$$




OPEARTING REGION

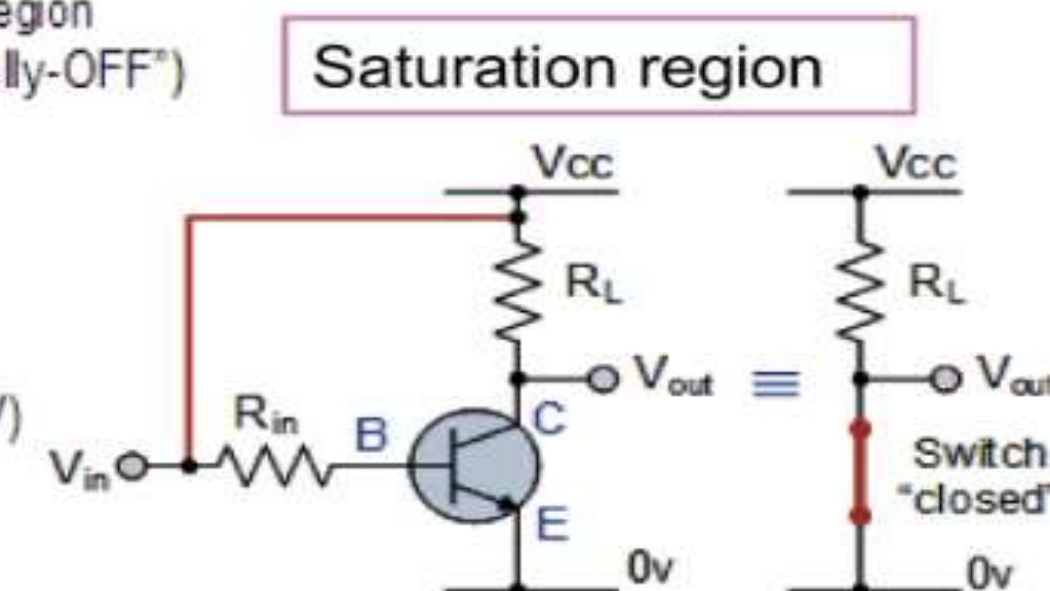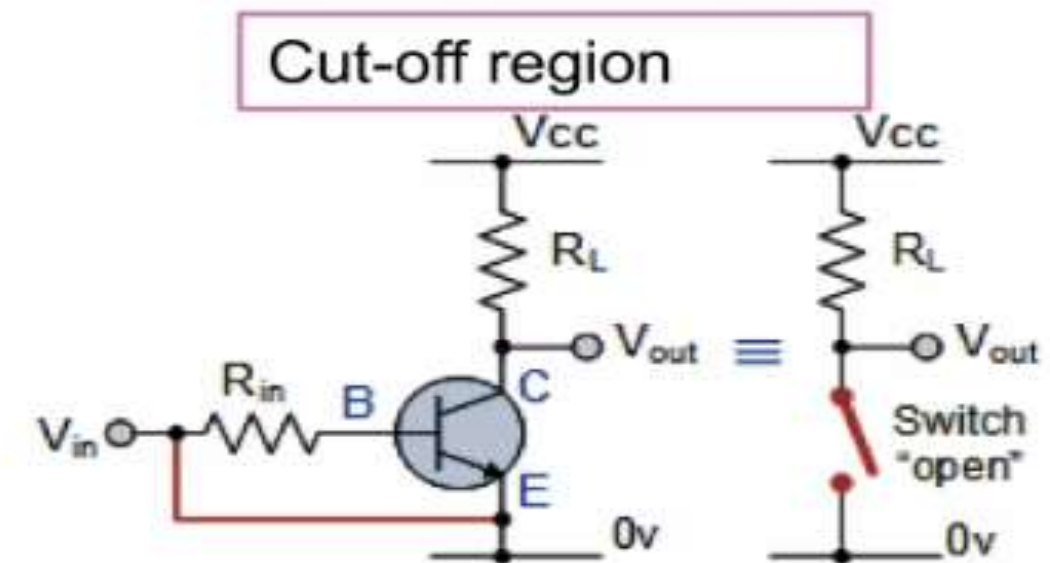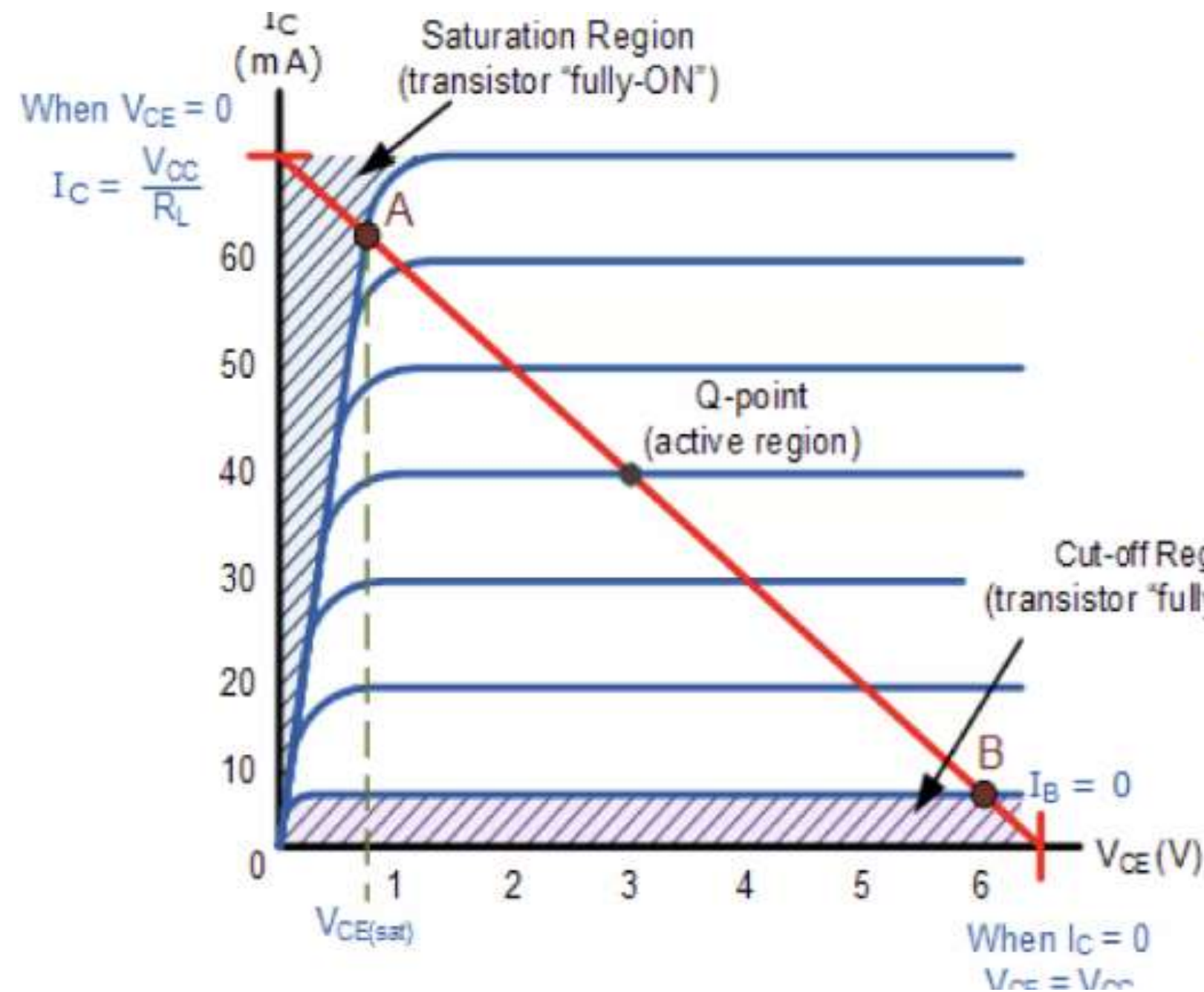



SELECTION OF OPERATING POINT

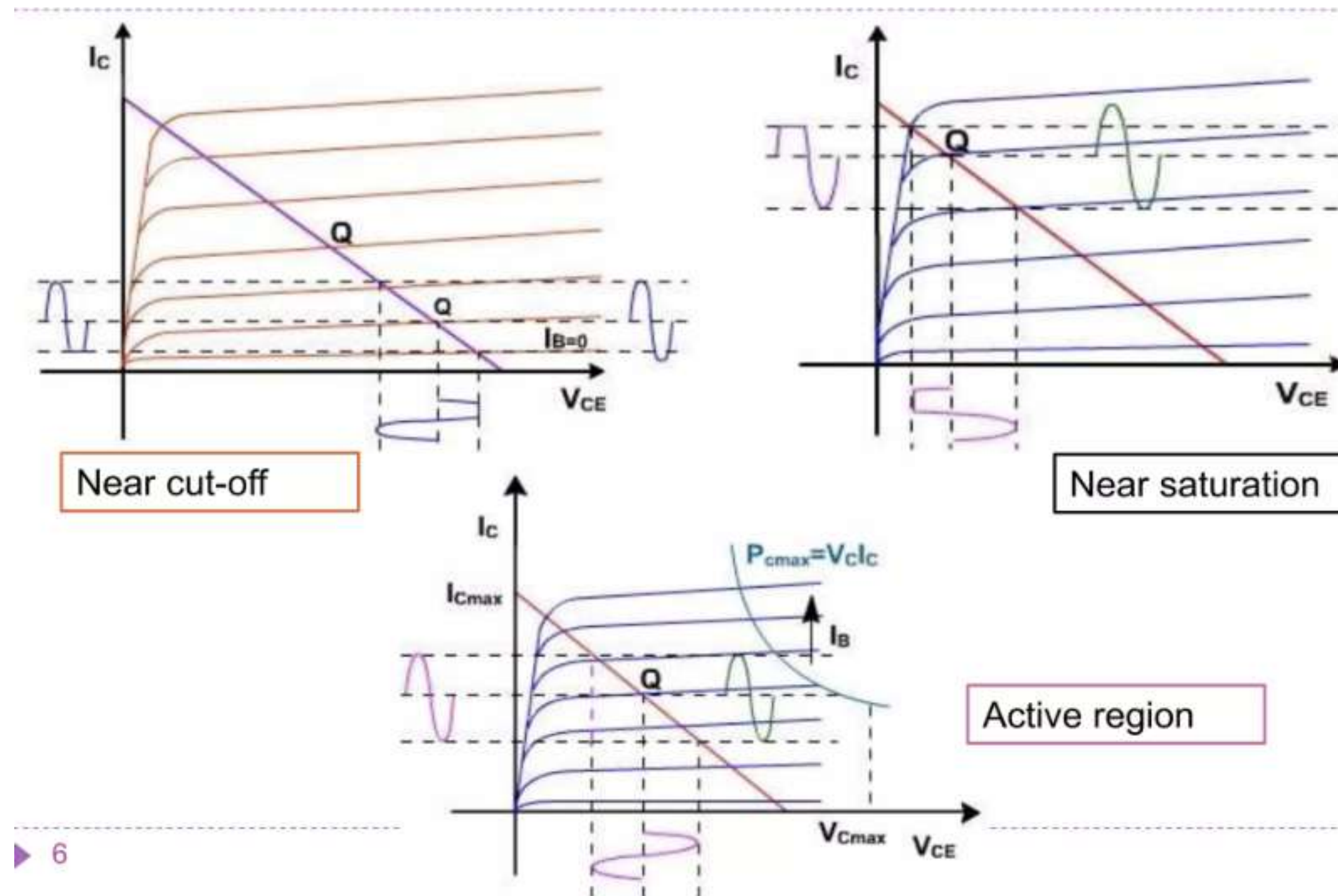

► 6



EXAMPLE

1. For CE configuration $V_{cc} = 10\text{ v}$, $R_c = 8\text{ k}$. Draw DC load line. Find Q-point for zero signal if base current is $15\mu\text{A}$, $\beta=40$
 - ▶ $I_c = 1.25\text{mA}$,
 - ▶ Zero signal $I_c = \beta I_B = 0.6\text{mA}$, $V_{CE} = 5.2\text{v}$
2. In transistor ckt $R_c = 5\text{ k}$, quiescent current is 1.2mA . Determine Q-point when $V_{cc} = 12\text{ v}$. how will point change when R_c is changed from 5 k to 7.5 k
 - ▶ Operating pt 1: $(6\text{ v}, 1.2\text{mA})$
 - ▶ Operating pt 2: $(3\text{ v}, 1.2\text{mA})$



Assessment



Define operating Point

Q-point: It is point on load line which represents DC value of V_{CE} and I_C in absence of signal. Best position is mid-point on load line, $V_{CE} = \frac{1}{2} V_{CC}$

