



## Topic 1.2 : Bias stability

### Variation of Q-point (or) Factors Affecting stability of Q-point

- \* The biasing circuit should be designed to fix the operating point (or) Q-point at the centre of the active region.
- \* But only fixing of the operating point is not sufficient.
- \* While designing the biasing circuit, care should be taken so that the Q-point will not shift into an undesirable region (ie cutoff or saturation).
- \* Designing the bias circuit to stabilize the Q-point is taken as bias stability.

### Temperature

#### 1) $I_{C0}$

- \* The flow of current in the circuit produces heat at the junctions.
- \* This heat increases the temperature at the junctions.
- \* We know that the minority carriers are temperature dependent.
- \* They increase with temperature.
- \* The increase in the minority carriers increases the leakage current  $I_{C0}$ .

$$\therefore I_{C0} = (1 + \beta) I_{CBO}$$

- \*  $I_{CBO}$  doubles for every  $10^\circ\text{C}$  rise in temperature.



# SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech&B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU




- \* Increase in  $I_{CEO}$  is turn Increase in the collector current.

$$\therefore I_C = \beta I_B + I_{CEO}$$

- \* The increase in  $I_C$  further raises the temperature at the collector junction & the same cycle repeats.
- \* The excessive increase in  $I_C$  shifts the Q-point into the saturation region, changing the operating condition set by biasing circuit.
- \* The power dissipation at collector base junction is

$$P_D = V_C I_C$$

- \* The increase in the  $I_C$  increases the power dissipated at the collector junction.
- \* This in turn further increase the temperature of the junction & hence increase the  $I_C$ .
- \* The power is cumulative.
- \* The excess heat produced at the collector base junction may even burn & destroy the transistor.
- \* This situation is called Thermal runaway of the transistor.
- \* For any Transistor the maximum power dissipation is always a fixed value.
- \* This known as maximum power dissipation rating of a Transistor.

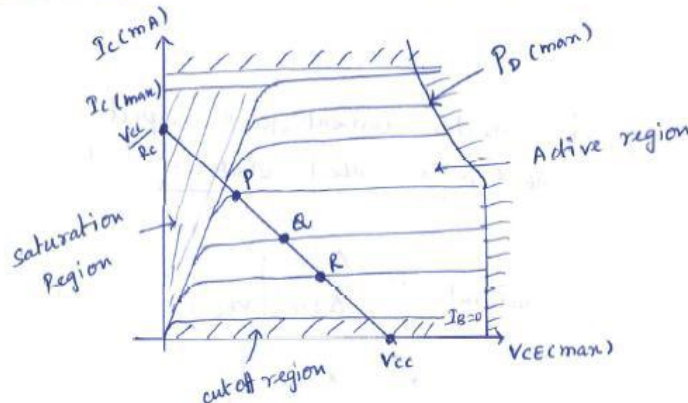

- \* The hyperbola give the maximum power dissipation for Transistor.
- \* If this limit is crossed the device will fail.

## 2) $V_{BE}$

- \*  $V_{BE}$  changes with temperature at the rate of  $2.5 \text{ mV}/^\circ\text{C}$
- \*  $I_B$  depends upon  $V_{BE}$
- \*  $I_B$  depends on  $V_{BE}$  &  $I_C$  depends on  $I_B$ ,  $I_C$  depends on  $V_{BE}$ .
- \*  $\therefore I_C$  changes with temperature due to changes in  $V_{BE}$
- \* The change in  $I_C$  changes the Q-point.



3)  $\beta_{dc}$

\* It's also temperature dependent.

\* As  $\beta_{dc}$  varies,  $I_c$  also varies, since  $I_c = \beta I_B$

\* The change in  $I_c$  change the Q-point.


Transistor current gain  $\beta_{FE} \approx \beta$

\* There are changes in the Transistor parameters among different units of the same type, same number.

\* If we take 2 transistor units of same type & use them in the circuit, there is change in the  $\beta$  value in actual practice.

\* The biasing circuit is designed according to the required  $\beta$  value.

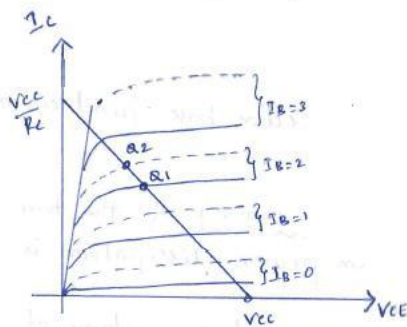\* But due to change in  $\beta$  from unit to unit, the Q-point may shift.



\* This fig: shows the CE o/p characteristics for 2 Transistor of the same type.

\* The dashed characteristics are for a Transistor whose  $\beta$  is much larger than that of the Transistor represented by solid curves.

## Stability Factors

S:

\* The rate of change of collector current ( $I_c$ ) with respect to collector leakage current ( $I_{co}$ ) at constant  $V_{BE}$  &  $\beta$  is called stability factor.

$$S = \left. \frac{\partial I_c}{\partial I_{co}} \right|_{V_{BE} \text{ \& \& } \beta \text{ constant}} = \left. \frac{\Delta I_c}{\Delta I_{co}} \right|_{V_{BE} \text{ \& \& } \beta \text{ constant}}$$

$$= \left. \frac{\Delta I_{c2} - \Delta I_{c1}}{\Delta I_{co2} - \Delta I_{co1}} \right|_{V_{BE} \text{ \& \& } \beta \text{ constant}}$$

S':

\* The rate of change of collector current ( $I_c$ ) with respect to  $V_{BE}$  at constant  $I_{co}$  &  $\beta$  is called stability factor S'.

$$S' = \left. \frac{\partial I_c}{\partial V_{BE}} \right|_{I_{co} \text{ \& \& } \beta \text{ constant}} = \left. \frac{\Delta I_c}{\Delta V_{BE}} \right|_{I_{co} \text{ \& \& } \beta \text{ constant}} = \left. \frac{\Delta I_{c2} - \Delta I_{c1}}{\Delta V_{BE2} - \Delta V_{BE1}} \right|_{I_{co} \text{ \& \& } \beta \text{ constant}}$$





# SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech&B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU



$S''$ :

\* The rate of change of collector current ( $I_c$ ) with respect to  $\beta$  at constant  $I_{c0}$  &  $V_{BE}$  is called stability factor  $S''$ .

$$S'' = \left. \frac{\Delta I_c}{\Delta \beta} \right|_{I_{c0} \text{ \& \& } V_{BE} \text{ constant}} = \left. \frac{\Delta I_c}{\Delta \beta} \right|_{I_{c0} \text{ \& \& } V_{BE} \text{ constant}}$$
$$= \left. \frac{\Delta I_{c2} - \Delta I_{c1}}{\Delta \beta_2 - \Delta \beta_1} \right|_{I_{c0} \text{ \& \& } V_{BE} \text{ constant}}$$

# The total change in collector current over a specified temperature range is obtained by expressing this change as the sum of individual changes due to 3 stability factors.

$$\Delta I_c = S \Delta I_{c0} + S' \Delta V_{BE} + S'' \Delta \beta$$