




## Topic 1.3 : Fixed Bias configuration

Different types of Biasing circuits / various biasing Methods for BJT

1. Fixed Bias
2. Collector to Base Bias / Biasing with Feedback Resistor
3. Self Bias or Voltage Divider Bias

1. Fixed Bias / Base Bias

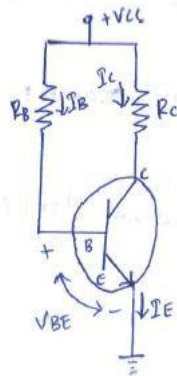

Dc Analysis:

\* For Dc  $f = 0$

$$X_c = \frac{1}{2\pi f C} = \frac{1}{0} = \infty$$

collector current ( $I_c$ ):

\* Apply KVL to the Base-Emitter circuit

$$V_{cc} - I_B R_B - V_{BE} = 0$$

$$I_B R_B = V_{cc} - V_{BE}$$

$$I_B = \frac{V_{cc} - V_{BE}}{R_B}$$

\* When  $V_{cc}$  &  $R_B$  are selected for a circuit  $I_B$  is fixed. Hence, the circuit is called Fixed bias circuit.

$$I_c = \beta I_B = \beta \left( \frac{V_{cc} - V_{BE}}{R_B} \right)$$



## Collector Emitter Voltage ( $V_{CE}$ )

- \* Apply KVL to the collector-emitter circuit

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

## Load line Analysis

- \* Apply KVL to the collector-emitter circuit

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$I_C R_C = -V_{CE} + V_{CC}$$

$$I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C}$$

- \* This eqn represents dc load line with slope of  $-\frac{1}{R_C}$  & y-intercept of  $\frac{V_{CC}}{R_C}$ .

- \* When  $I_C = 0$  i.e. the transistor is in cutoff region


$$V_{CE} = V_{CC}$$

- \* When  $V_{CE} = 0$  i.e. the transistor is in saturation region

$$I_C = \frac{V_{CC}}{R_C}$$

- \* Thus the 2 end points are  $(V_{CC}, 0)$  &  $(0, \frac{V_{CC}}{R_C})$

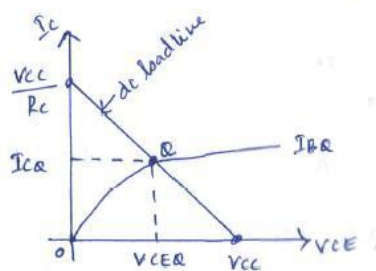- \* By joining this 2 end points dc load line is drawn.



- \* The saturation current for the circuit is  $I_{C \text{ sat}} = \frac{V_{CC}}{R_C}$ .

## Stability factors

S:

$$S = \left. \frac{\partial I_C}{\partial I_{C0}} \right|_{V_{BE} + \beta \text{ constant}} \quad (\text{or}) \quad \left. \frac{\Delta I_C}{\Delta I_{C0}} \right|_{V_{BE} + \beta \text{ constant}}$$

- \* We know that

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

- \* No collector current present in this equation. So  $\frac{\partial I_B}{\partial I_C} = 0 \rightarrow 0$



# SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech&B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU



\* We know  $I_c$

$$I_c = \beta I_B + (1 + \beta) I_{CO}$$

\* differentiate  $I_c$  with respect to  $I_c$  we get

$$\frac{\partial I_c}{\partial I_c} = \beta \frac{\partial I_B}{\partial I_c} + (1 + \beta) \frac{\partial I_{CO}}{\partial I_c}$$

$$\therefore \frac{\partial I_c}{\partial I_{CO}} = S$$

$$1 = \beta \frac{\partial I_B}{\partial I_c} + (1 + \beta) \times \frac{1}{S}$$

$$1 - \beta \frac{\partial I_B}{\partial I_c} = \frac{1 + \beta}{S}$$

$$S = \frac{1 + \beta}{1 - \beta \frac{\partial I_B}{\partial I_c}} \quad \text{--- (2)}$$

\* Substitute (1) in (2)

$$S = \frac{1 + \beta}{1 - \beta(0)}$$

$$S = 1 + \beta$$

S':

$$S' = \left. \frac{\partial I_c}{\partial V_{BE}} \right|_{I_{CO} \text{ \& } \beta \text{ constant}} \quad (\text{or}) \quad \left. \frac{\Delta I_c}{\Delta V_{BE}} \right|_{I_{CO} \text{ \& } \beta \text{ constant}}$$

\* W.K.T

$$I_c = \beta I_B + (1 + \beta) I_{CO}$$

\* substitute  $I_B$  in  $I_c$

$$I_c = \beta \left( \frac{V_{CC} - V_{BE}}{R_B} \right) + (1 + \beta) I_{CO}$$

$$I_c = \frac{\beta V_{CC}}{R_B} - \frac{\beta V_{BE}}{R_B} + (1 + \beta) I_{CO} \quad \text{--- (3)}$$

\* differentiate w.r. to  $V_{BE}$

$$\frac{\partial I_c}{\partial V_{BE}} = 0 - \frac{\beta}{R_B} + 0$$

$$S' = -\frac{\beta}{R_B}$$



# SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech&B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU



## Relation between $s$ & $s'$

$$s = 1 + \beta \quad s' = \frac{-\beta}{R_B}$$

In  $s'$  Multiply numerator & denominator by  $(1 + \beta)$  we get

$$s' = \frac{-\beta(1 + \beta)}{R_B(1 + \beta)} = \frac{-\beta s}{R_B(1 + \beta)} \quad \because s = 1 + \beta$$

$s''$ :

$$s'' = \left. \frac{\partial I_C}{\partial \beta} \right|_{V_{BE} + I_{CO} \text{ constant}} = \left. \frac{\Delta I_C}{\Delta \beta} \right|_{V_{BE} + I_{CO} \text{ constant}}$$

From (3)

$$I_C = \frac{\beta V_{CC}}{R_B} - \frac{\beta V_{BE}}{R_B} + (1 + \beta) I_{CO}$$

differentiate w.r. to ' $\beta$ '

$$\frac{\partial I_C}{\partial \beta} = \frac{V_{CC}}{R_B} - \frac{V_{BE}}{R_B} + I_{CO}$$

$$= I_B + I_{CO}$$

$$= I_B + 0$$

$$\frac{\partial I_C}{\partial \beta} = \frac{I_C}{\beta}$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\because I_B \gg I_{CO}$$

$$\therefore I_B = \frac{I_C}{\beta}$$

$$s'' = \frac{\partial I_C}{\partial \beta} = \frac{I_C}{\beta}$$

## Relation b/w $s$ & $s''$

$$s = 1 + \beta \quad s'' = \frac{I_C}{\beta}$$

In  $s''$  Multiply Numerator & denominator by  $(1 + \beta)$  we get-

$$s'' = \frac{I_C(1 + \beta)}{\beta(1 + \beta)} = \frac{I_C s}{\beta(1 + \beta)} \quad \because s = 1 + \beta$$

Advantages:

- \* Simple circuit which uses very few components.
- \* The operating point can be fixed anywhere in the active region of the characteristics by simply changing the value of  $R_B$ . Thus it provides maximum flexibility in the design.



# SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech&B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU



## Disadvantages

1. Thermal stability is not provided by this circuit. so the operating point is not maintained.

$$I_C = \beta I_B + I_{CEO}$$

2. Since  $I_C = \beta I_B$  &  $I_B$  is already fixed;  $I_C$  depends on  $\beta$  which changes unit to unit & shifts the operating point.

# The stabilization of operating point is very poor in the fixed bias circuit. Because of this reason the fixed bias circuit need some modifications.

# In the modified circuit,  $R_B$  is connected b/w collector & base. Hence the circuit is called collector to base bias circuit.