



## Topic 1.6 : Bias Compensation

### Bias Compensation / Methods of stabilizing the Q-point

\* The compensation Techniques uses Temperature sensitive devices such as diodes, Transistors, Thermistors etc.. to maintain the operating point constant.

#### 1. Diode compensation Techniques

##### 1. Compensation for $V_{BE}$

a) Diode in Emitter circuit

b) Diode in Voltage Divider circuit

##### 2. Compensation for $I_{CO}$


#### 2. Thermistor Compensation Technique

#### 3. Sensistor compensation Technique

### 1. Diode Compensation Technique

#### 1. Compensation for $V_{BE}$

##### a) Diode in Emitter circuit

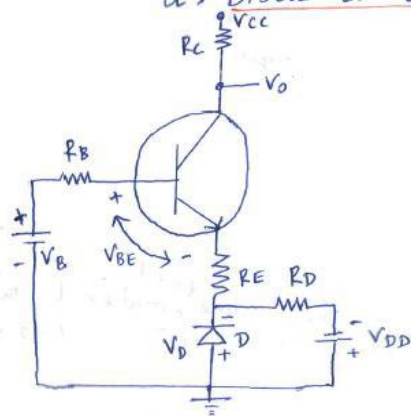

\* Here, separate supply  $V_{DD}$  is used to keep diode in Forward bias condition.

\* If the diode & Transistor are of same material, the voltage across the diode will have the same temperature coefficient ( $-2.5 \text{ mV}/^\circ\text{C}$ ) as the  $V_{BE}$ .

\* So the  $V_{BE}$  changes by  $\partial V_{BE}$  with change in temperature,  $V_D$  changes by  $\partial V_D$

$\partial V_D \approx \partial V_{BE}$ , the change tend to cancel each other.

\* We know,

$$V_{BE} = V_T - \left[ \frac{R_B + (1+\beta)R_E}{\beta} \right] I_C + \left[ \frac{(R_E + R_B)(1+\beta)}{\beta} \right] I_{CO}$$

$$\left[ \frac{R_B + (1+\beta)R_E}{\beta} \right] I_C = V_T - V_{BE} + \left[ \frac{(R_E + R_B)(1+\beta)}{\beta} \right] I_{CO}$$

$$I_C = \frac{\beta[V_T - V_{BE}] + \cancel{\left[ \frac{(R_E + R_B)(1+\beta)}{\beta} \right] I_{CO}}}{R_B + (1+\beta)R_E}$$




\* We modify the equation

$$I_c = \frac{\beta [V - (V_{BE} - V_D)] + (R_E + R_B)(1 + \beta) I_{CO}}{R_B + (1 + \beta) R_E}$$

\*  $I_c$  will be insensitive to variations in  $V_{BE}$ .

b) Diode in voltage divider circuit

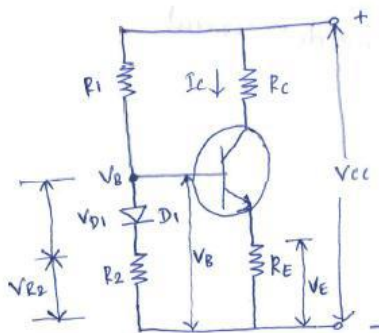

\* Here, the diode is connected in series with resistance  $R_E$  in the voltage divider circuit & it is in forward bias condition.

\* We derived for voltage divider bias

$$I_E = \frac{V_B - V_{BE}}{R_E}$$

$$\text{also } I_E = \frac{V_E}{R_E} \quad \& \quad I_C \approx I_E$$

$$I_C \approx \frac{V_B - V_{BE}}{R_E} \quad \text{--- (1)}$$

\* When  $V_{BE}$  changes with temperature  $I_C$  also changes.

\* The voltage at the base  $V_B$  is now

$$V_B = V_{R2} + V_D \quad \text{--- (2)}$$

\* Sub eqn (2) in (1)

$$(1) \Rightarrow I_C \approx \frac{V_{R2} + V_D - V_{BE}}{R_E}$$

\* If the diode & the Transistor are of the same <sup>type &</sup> material, the voltage across the diode will have the same temperature coefficient ( $-2.5 \text{ mV}/^\circ\text{C}$ ) as the  $V_{BE}$ .

\* So the  $V_{BE}$  changes by  $\partial V_{BE}$  with change in temperature,  $V_D$  changes by  $\partial V_D$  &  $\partial V_D \approx \partial V_{BE}$ , the changes tend to cancel each other.

\* The collector current as

$$I_C \approx \frac{V_{R2}}{R_E}$$

\* Which is unaffected due to change in  $V_{BE}$ .


\* The biasing is provided by  $R_1$ ,  $R_2$  &  $R_E$ .

\* The change in  $V_{BE}$  due to temperature are compensated by changes in the diode voltage which keeps  $I_C$  stable at Q-point.


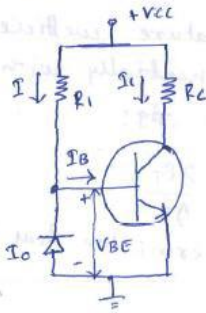
## 2. Compensation for $I_{CO}$ / Diode compensation for germanium Transist

\* In case of Ge, changes in  $I_{CO}$  with Temperature are comparatively larger than Si Transistor.



\* It plays more role in  $I_C$  stability than the change in  $V_{BE}$ .

\* It offers stabilization against variation in  $I_{CO}$ .

\* Here, the diode is kept in reverse bias condition.

\* In reverse bias condition the current flowing through diode is only the leakage current ( $I_0$ ).

\* If the diode & the Transistor are of the same type & material, the leakage current  $I_0$  of the diode will increase with temperature at the same rate as the collector leakage current  $I_{CO}$ .

$$I = \frac{V_{CC} - V_{BE}}{R_1} \quad \& \quad I = I_B + I_0$$

$$\therefore I_B = I - I_0 \quad \text{--- (1)}$$

\* For Ge Transistor  $V_{BE} = 0.2V$ , which is very small & neglecting change in  $V_{BE}$  with temperature.

\* We can write

$$I \approx \frac{V_{CC}}{R_1} \approx \text{constant}$$

\* We know

$$I_C = \beta I_B + (1 + \beta) I_{CO} \quad \text{--- (2)}$$

sub (1) in (2)

$$\begin{aligned} (2) \Rightarrow I_C &= \beta (I - I_0) + (1 + \beta) I_{CO} \\ &= \beta I - \beta I_0 + (1 + \beta) I_{CO} \end{aligned}$$

\* if  $\beta \gg 1$  we get

$$I_C = \beta I - \beta I_0 + \beta I_{CO}$$

\* We assume

$$I_0 = I_{CO} \text{ we get}$$

$$I_C = \beta I$$


\* As  $I$  is constant,  $I_C$  remains fairly constant.

\* We can say that changes by  $I_{CO}$  with temperature are compensated by diode & thus collector current remains fairly constant.





## 2. Thermistor Compensation Technique

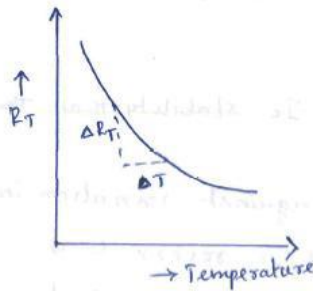


\* This method uses Temperature sensitive devices such as Thermistors rather than diode (or) Transistor

\* It has negative temperature coefficient. its resistance decreases exponentially with increasing Temperature: as shown in fig:

\* Slope of this curve =  $\frac{\partial R_T}{\partial T}$

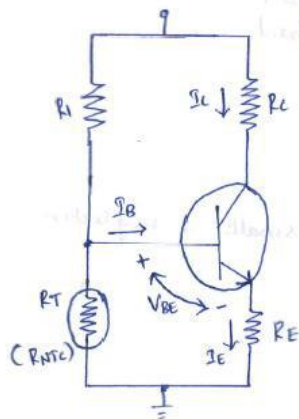\* The  $\frac{\partial R_T}{\partial T}$  is the temperature coefficient for Thermistor has negative temperature coefficient resistance (NTC).



In this figure:

\*  $R_2$  is replaced by Thermistor  $R_T$  in self bias circuit.

\* With increase in Temperature  $R_T$  decreases.


\* Hence the voltage drop across it also decreases.

\* The voltage drop is nothing but voltage at the base with respect to ground. Hence  $V_{BE}$  decreases which decrease  $I_B$ .

\* This behaviour will tend to offset the increase in  $I_C$  with Temperature

\* We know,

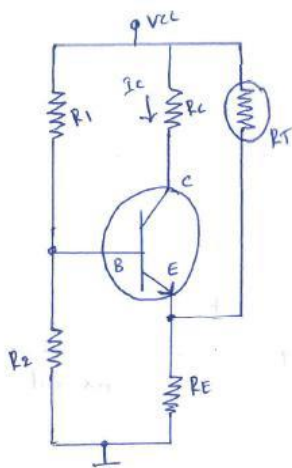$I_C = \beta I_B + (1 + \beta) I_{CBO}$  → In this equation, There is increase in  $I_{CBO}$  & decrease in  $I_B$  which keeps  $I_C$  almost constant.



In this Fig:

\* The Thermistor is connected b/w Emitter &  $V_{CC}$  to minimize the increase in  $I_C$  due to changes in  $I_{CBO}$ ,  $\beta$  (or)  $V_{BE}$  with Temperature.

\*  $I_C$  increases with Temperature &  $R_T$  decreases with increase in Temperature.

\* ∴ the current flow through  $R_E$  increases, which increase the voltage drop across it.

\* The Emitter-Base junction is forward biased.

(22)




- \* But due to increase in voltage drop across  $R_E$ , emitter is made more positive which decreases the forward bias voltage  $V_{BE}$ .
- \* Hence base current decreases.

\*  $I_C$  is given by

$$I_C = \beta I_B + (1 + \beta) I_{CBO}$$

- \* As  $I_{CBO}$  increases with Temperature,  $I_B$  decreases & hence  $I_C$  remains fairly constant.


### 3. Sensistor Compensation Technique

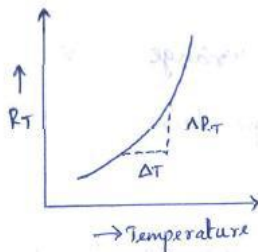

- \* This method uses temperature sensitive devices such as sensistor rather than diode or Transistor.
- \* It has a positive temperature coefficient, its resistance increases exponentially with increase temperature.

\* slope of this curve =  $\frac{\partial R_T}{\partial T}$

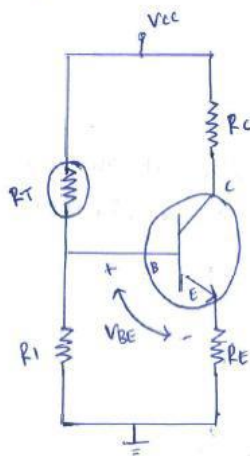- \*  $\frac{\partial R_T}{\partial T}$  is the temperature coefficient for sensistor & the slope is positive
- \* So we can say that sensistor have positive temperature coefficient of resistance (PTC)



In this fig:

- \*  $R_1$  is replaced by sensistor  $R_T$  in self bias circuit.
- \* Now  $R_T$  &  $R_2$  are 2 resistors of the potential divider
- \* As temperature increases,  $R_T$  increases which decrease the current flowing through it.
- \* Hence the current through  $R_2$  decreases which decrease the voltage drop across it.
- \* Voltage drop across  $R_2$  is the voltage b/w base & ground.
- \* So  $V_{BE}$  decreases which decreases  $I_B$ .

- \*  $I_C = \beta I_B + (1 + \beta) I_{CBO} \rightarrow$  When  $I_{CBO}$  increases with increase in Temperature,  $I_B$  decreases due to reduction in  $V_{BE}$ , maintaining  $I_C$  fairly constant.