



# SNS COLLEGE OF TECHNOLOGY

Coimbatore-35  
An Autonomous Institution

*Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai*



## DEPARTMENT OF MECHATRONICS

### INDUSTRIAL ELECTRONICS & APPLICATION

*III YEAR V SEM*

#### *UNIT 2 – PHASE CONTROLLED CONVERTER*

*TOPIC – Three phase controlled Rectifier*

Mr. M.Anand., M.E.,(Ph.D.,)

ASSISTANT PROFESSOR,

DEPARTMENT OF MECHATRONICS,

SNSCT, Coimbatore.





## APPLICATION






## Intro-Three Phase

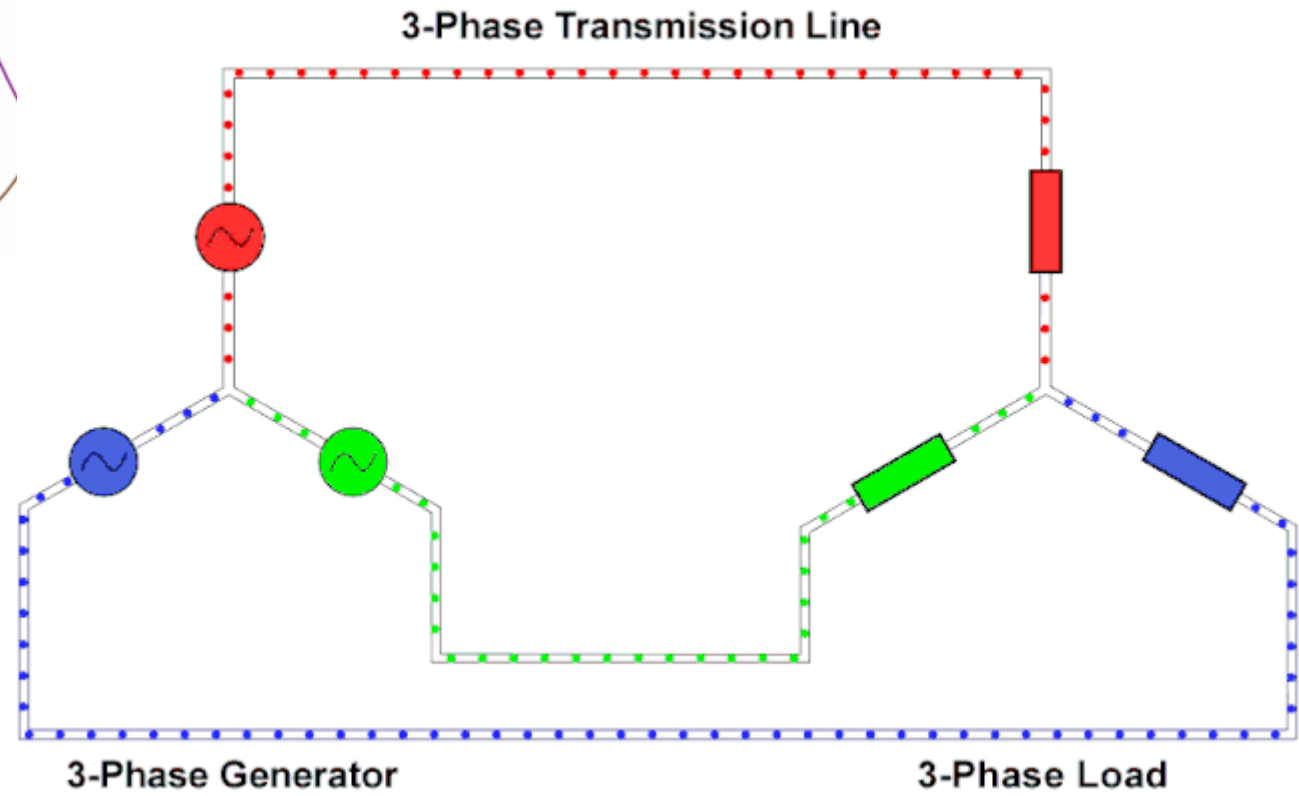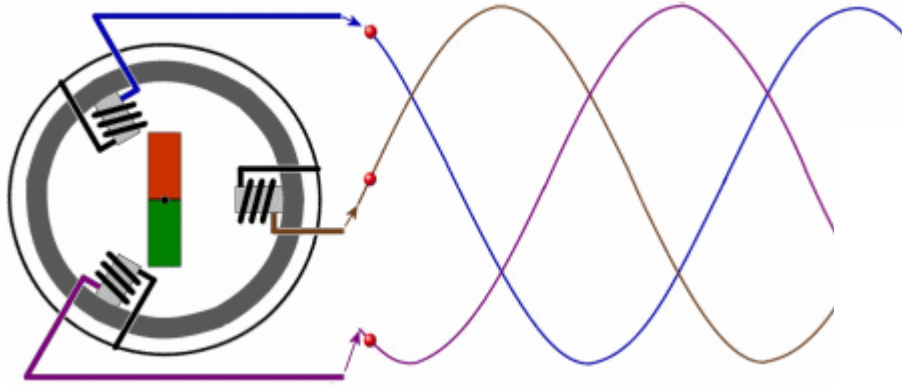



# Single phase controlled Converter

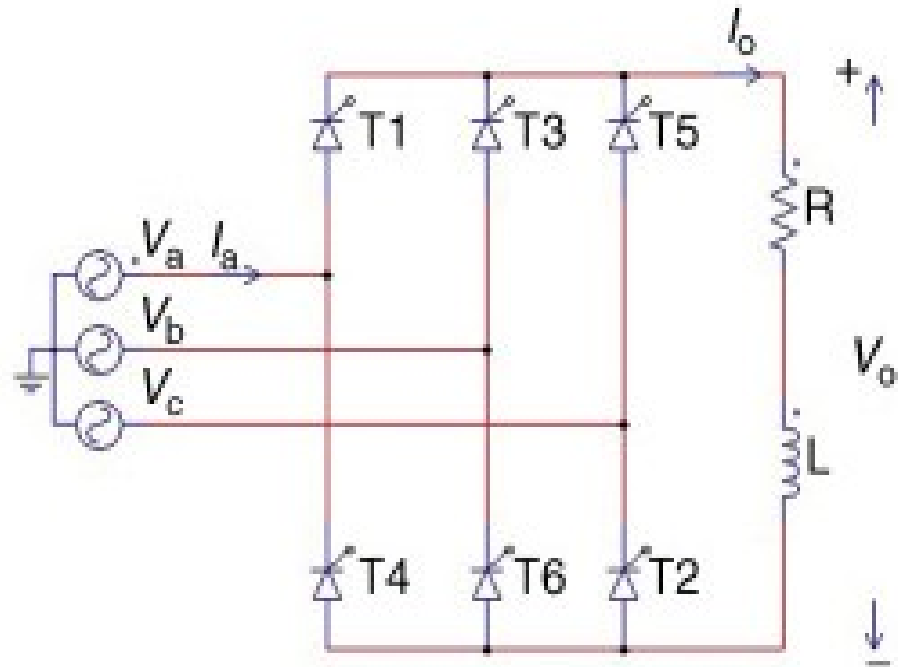

6 SCR



controlled converter

Input




Three phase AC

Output



controlled DC




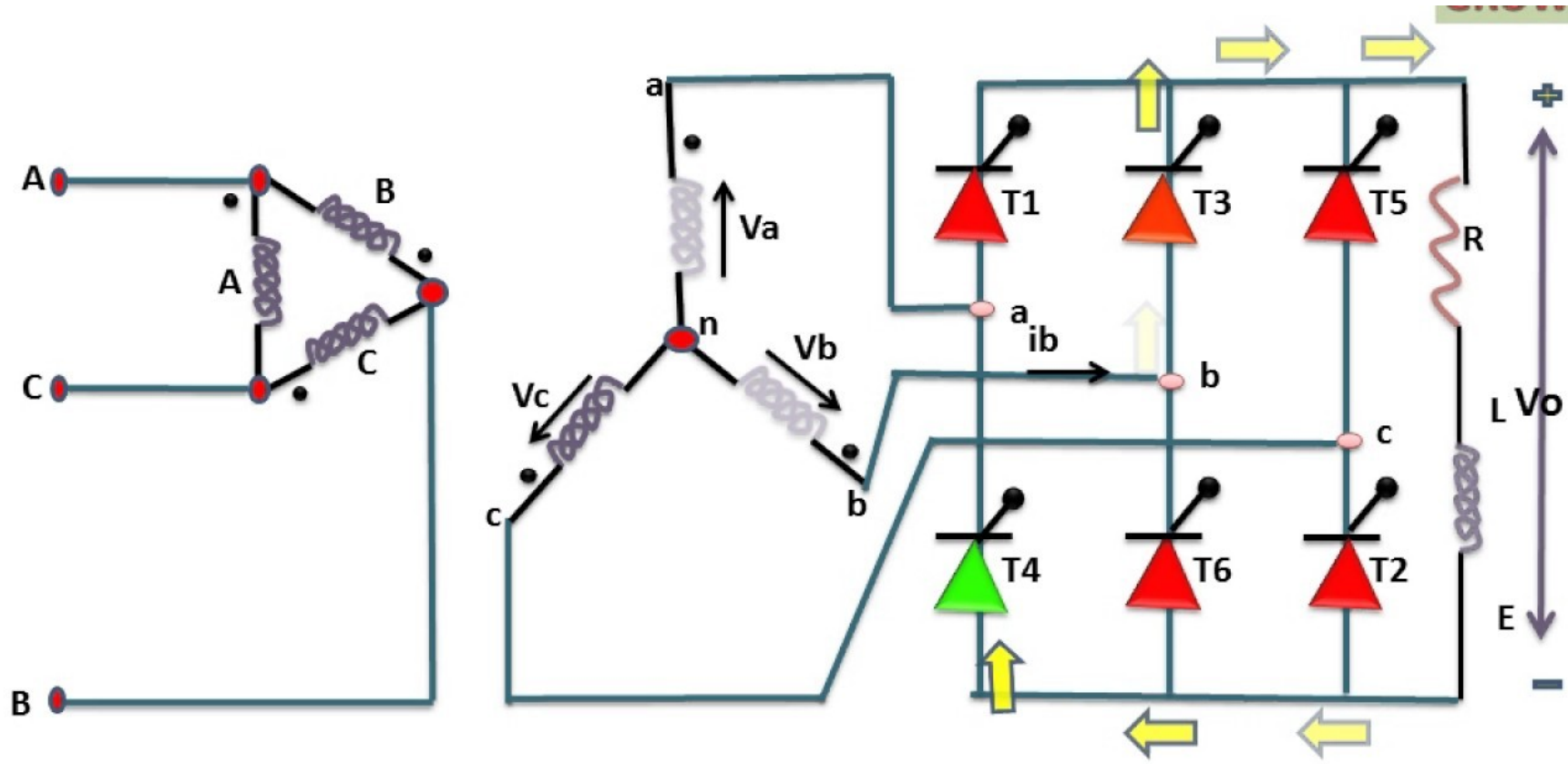


T1, T2 = Vac






## Output Waveform

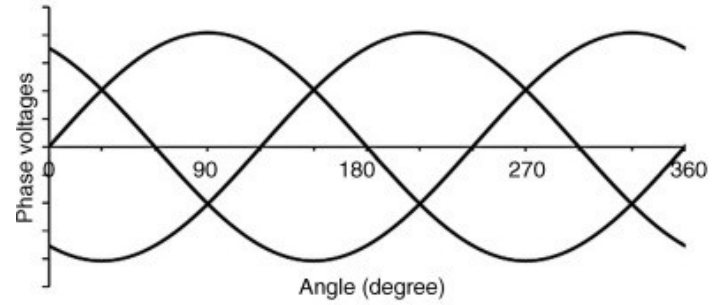

(a)

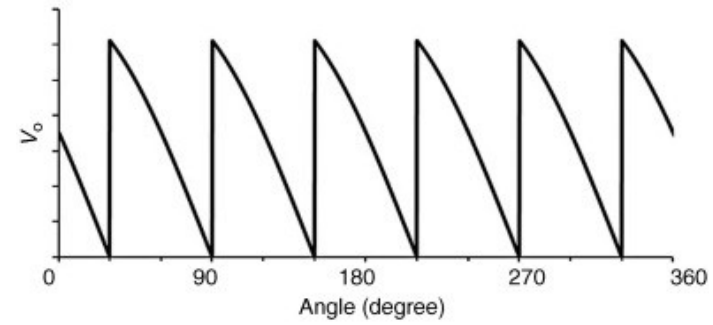


(b)

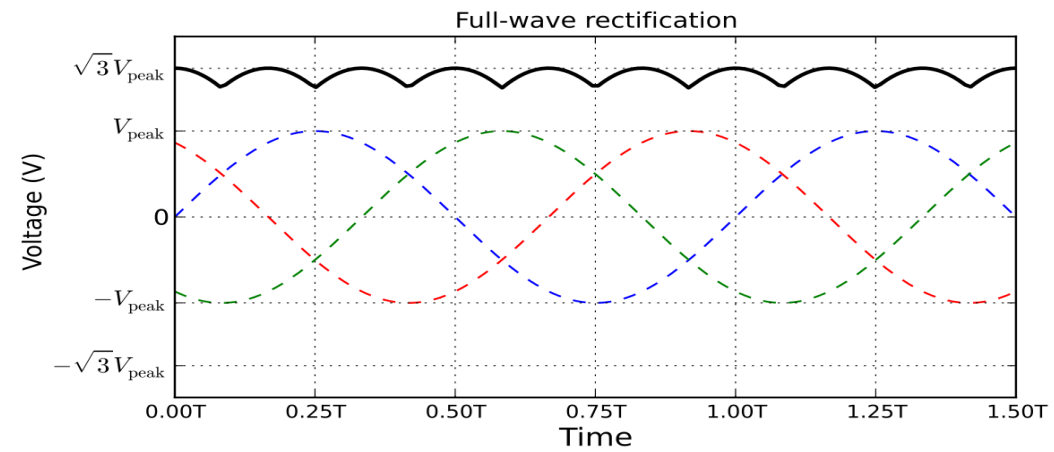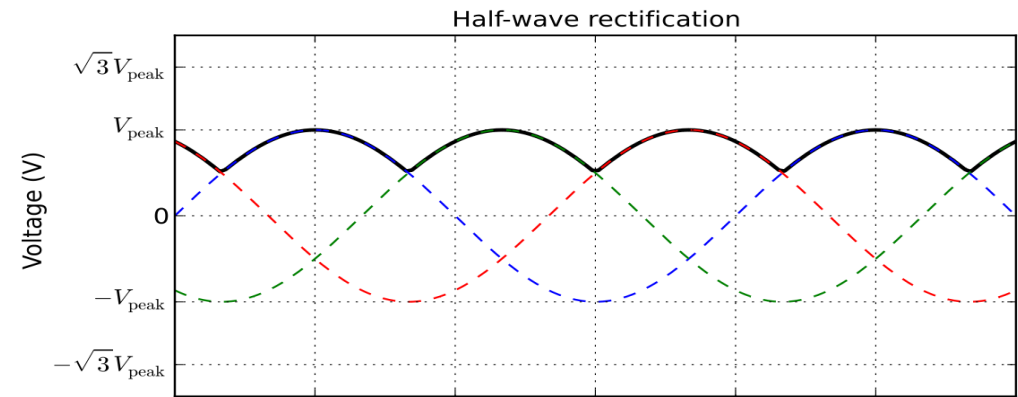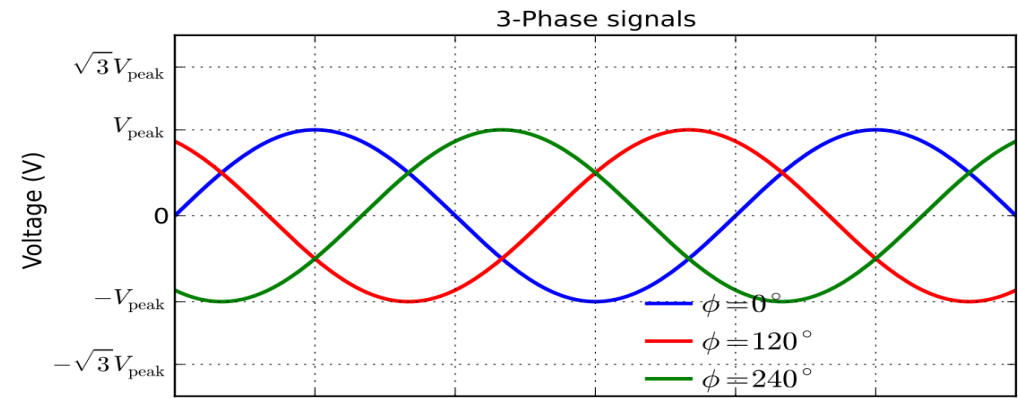



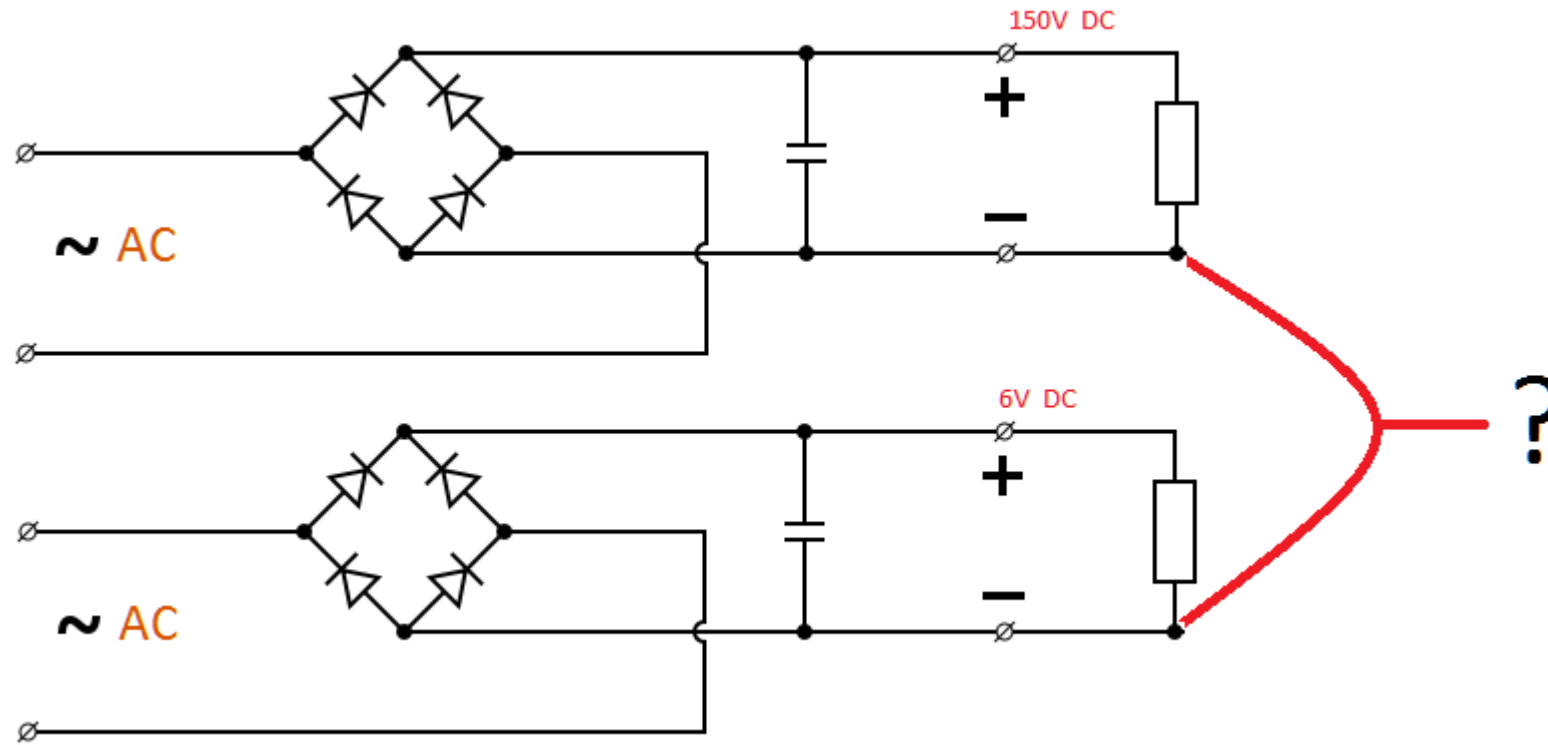**Assessment - If connect two negative in following circuit, what will happen? Why?**





## References

1. <https://www.electronics-tutorials.ws/power/single-phase-rectification.html>
2. [https://www.tutorialspoint.com/power\\_electronics/power\\_electronics\\_introduction.htm#:~:text=Power%20Electronics%20refers%20to%20the,efficiency%20and%20reliability%20is%20100%25](https://www.tutorialspoint.com/power_electronics/power_electronics_introduction.htm#:~:text=Power%20Electronics%20refers%20to%20the,efficiency%20and%20reliability%20is%20100%25)
3. <http://www.egr.unlv.edu/~eebag/EE-442-642%20Introduction%20F1>
4. <https://www.youtube.com/watch?v=djbJm-xWo2w>
5. <https://www.youtube.com/watch?v=jx5l2Fbil8U>

