



# **SNS COLLEGE OF TECHNOLOGY**

## **(AN AUTONOMOUS INSTITUTION)**

Approved by AICTE & Affiliated to Anna University  
Accredited by NBA & Accredited by NAAC with 'A+' Grade,  
Recognized by UGC saravanampatti (post), Coimbatore-641035.



## **Department of Biomedical Engineering**

**Course Name: 23BMT201 & Circuit Analysis**

**I Year : II Semester**

**Unit I – NETWORK THEOREMS FOR DC CIRCUITS**



**Topic : <sup>1</sup>Superposition Theorem**


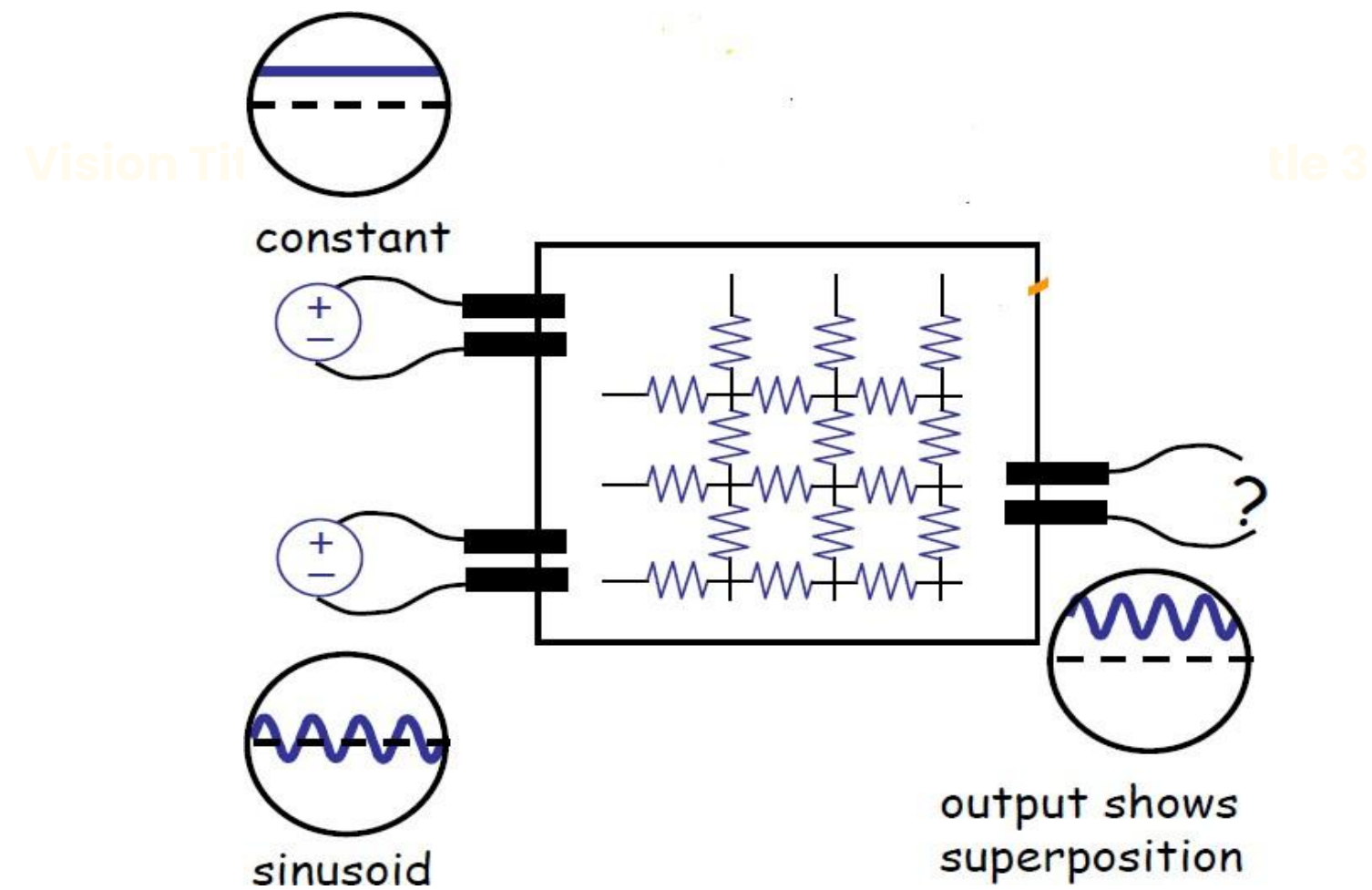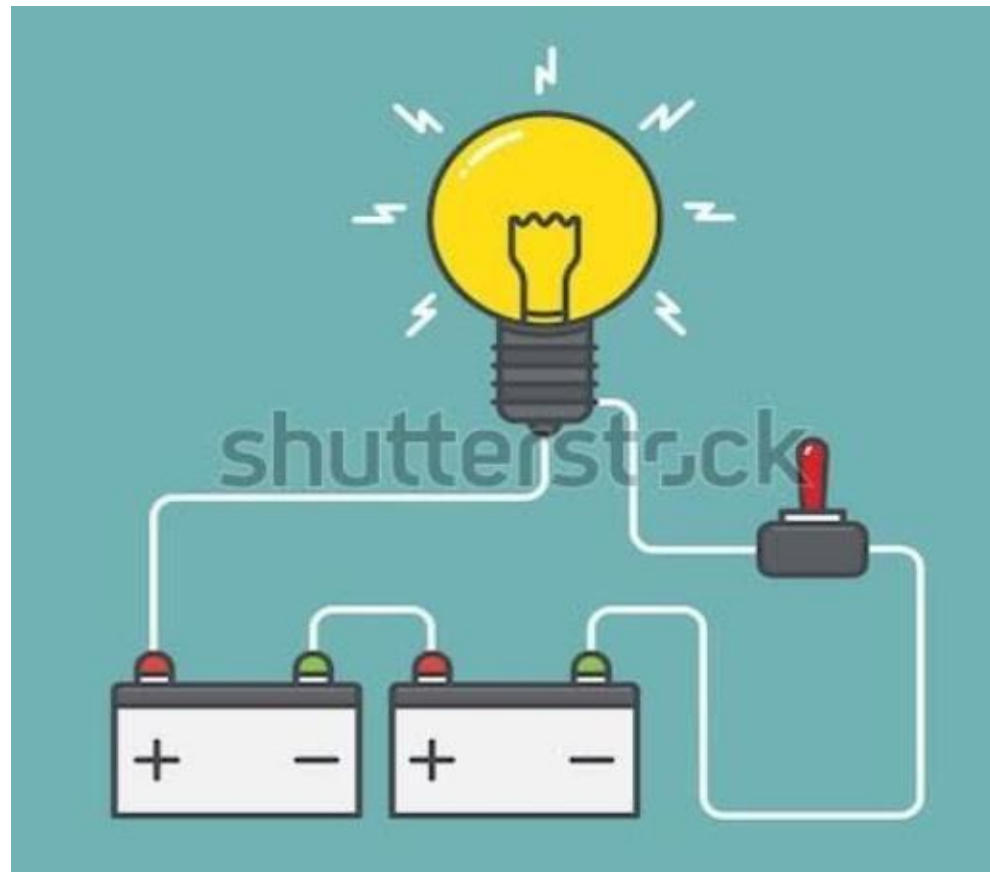
# Superposition Theorem



- Circuit with more than one energy/power supply units






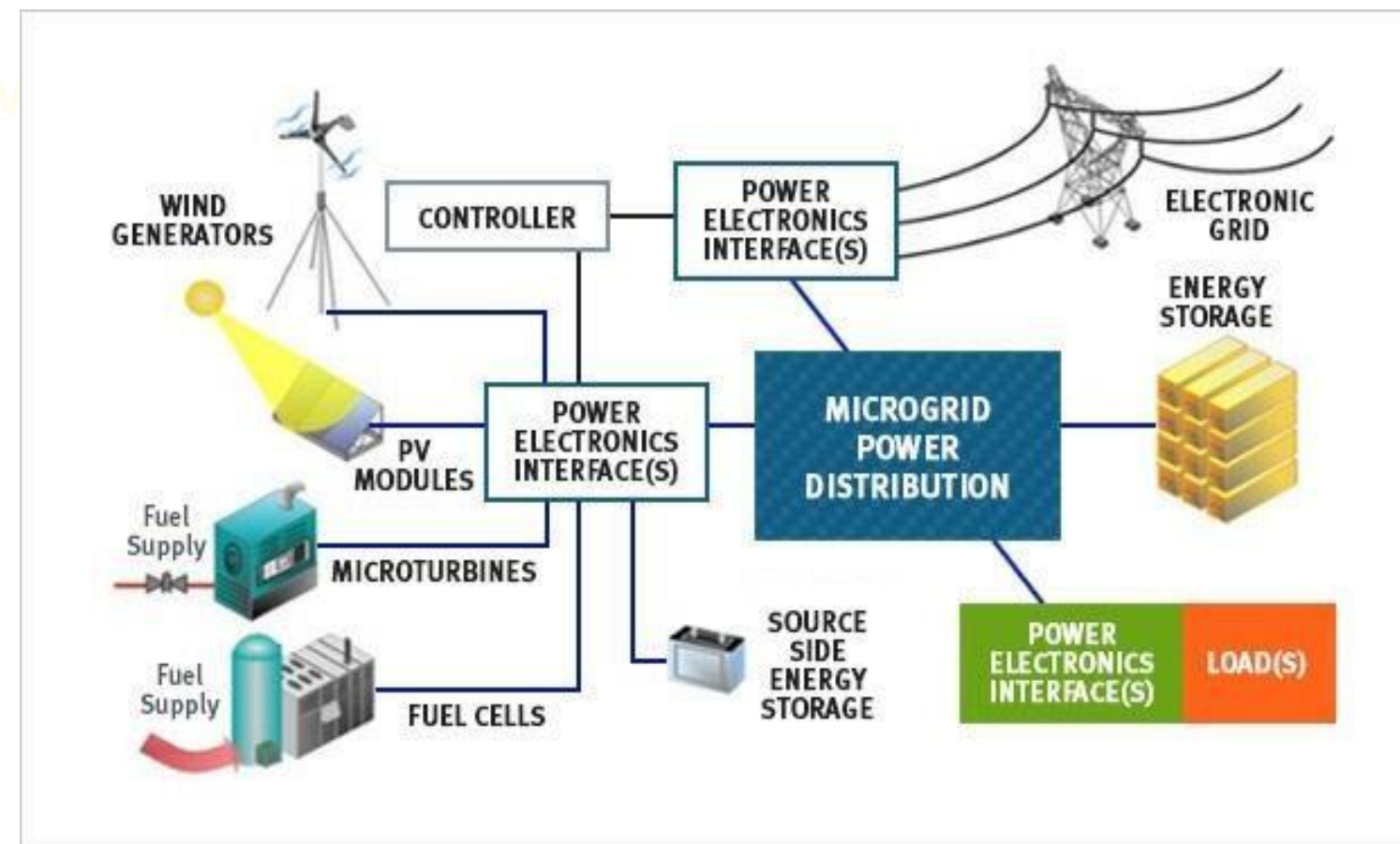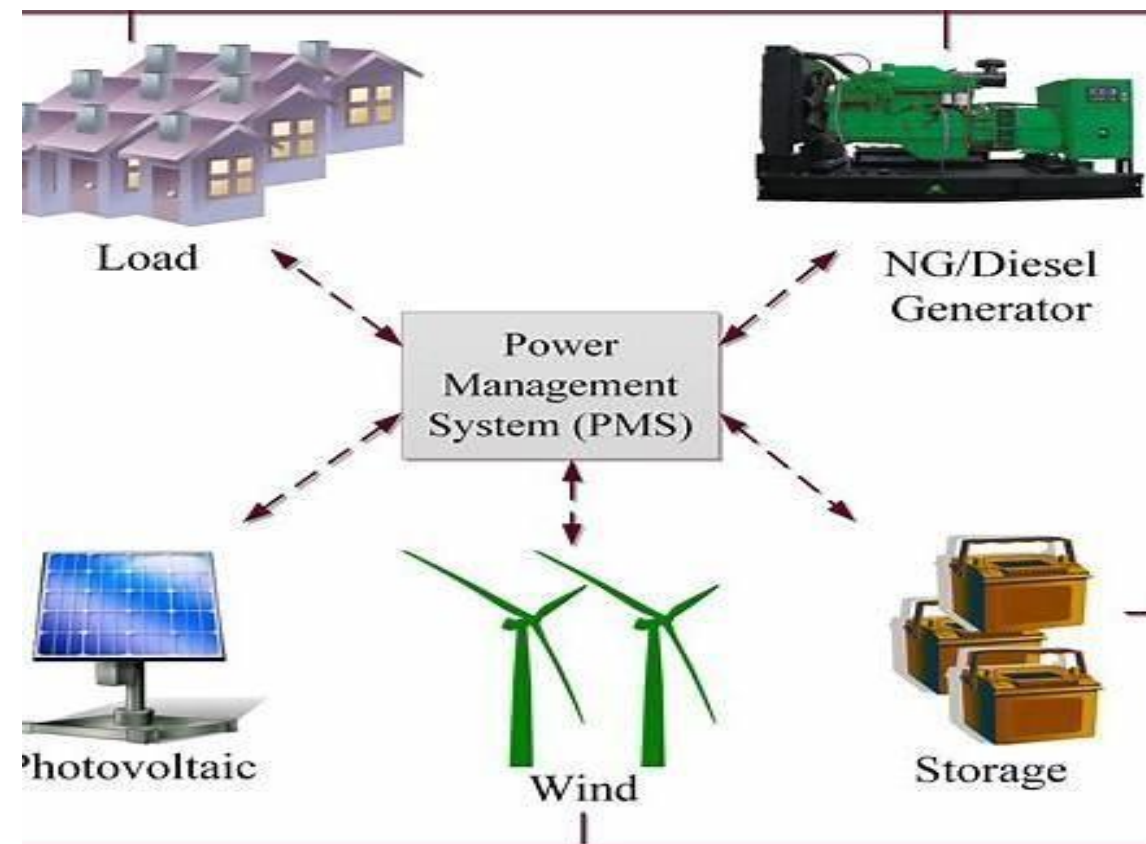
# Superposition Theorem



- System with more than one energy sources





# Superposition - Principle



- Helps us to analyze a linear circuit with more than one independent source.
- It is used to determine the value of some circuit variable (voltage across or current through a particular impedance)
- It is applied by calculating the contribution of each independent source separately.
- The output of a circuit is determined by summing the individual responses of each independent source.
- The idea of superposition rests on the linearity property (specifically, additive)


Vision Tit 2

Vision Title 3


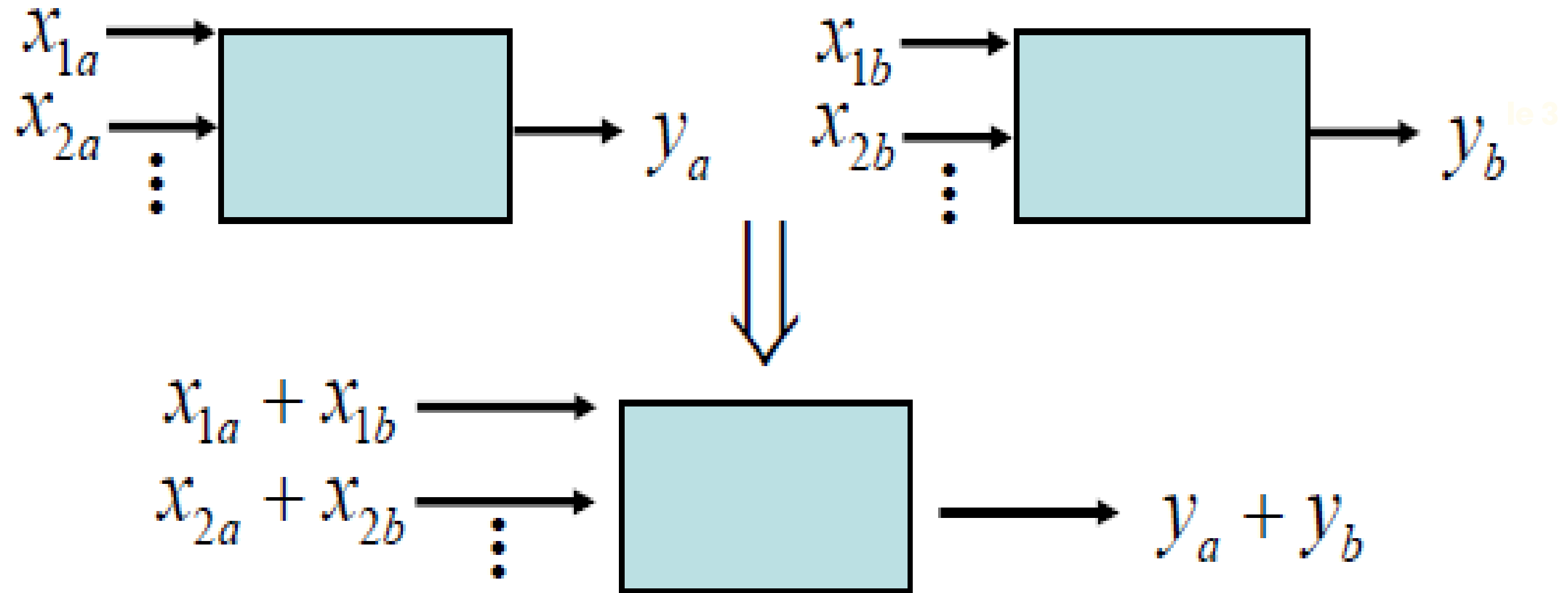
## Linearity – Additive Property


- The response to a sum of inputs is the sum of the responses to each input applied separately.




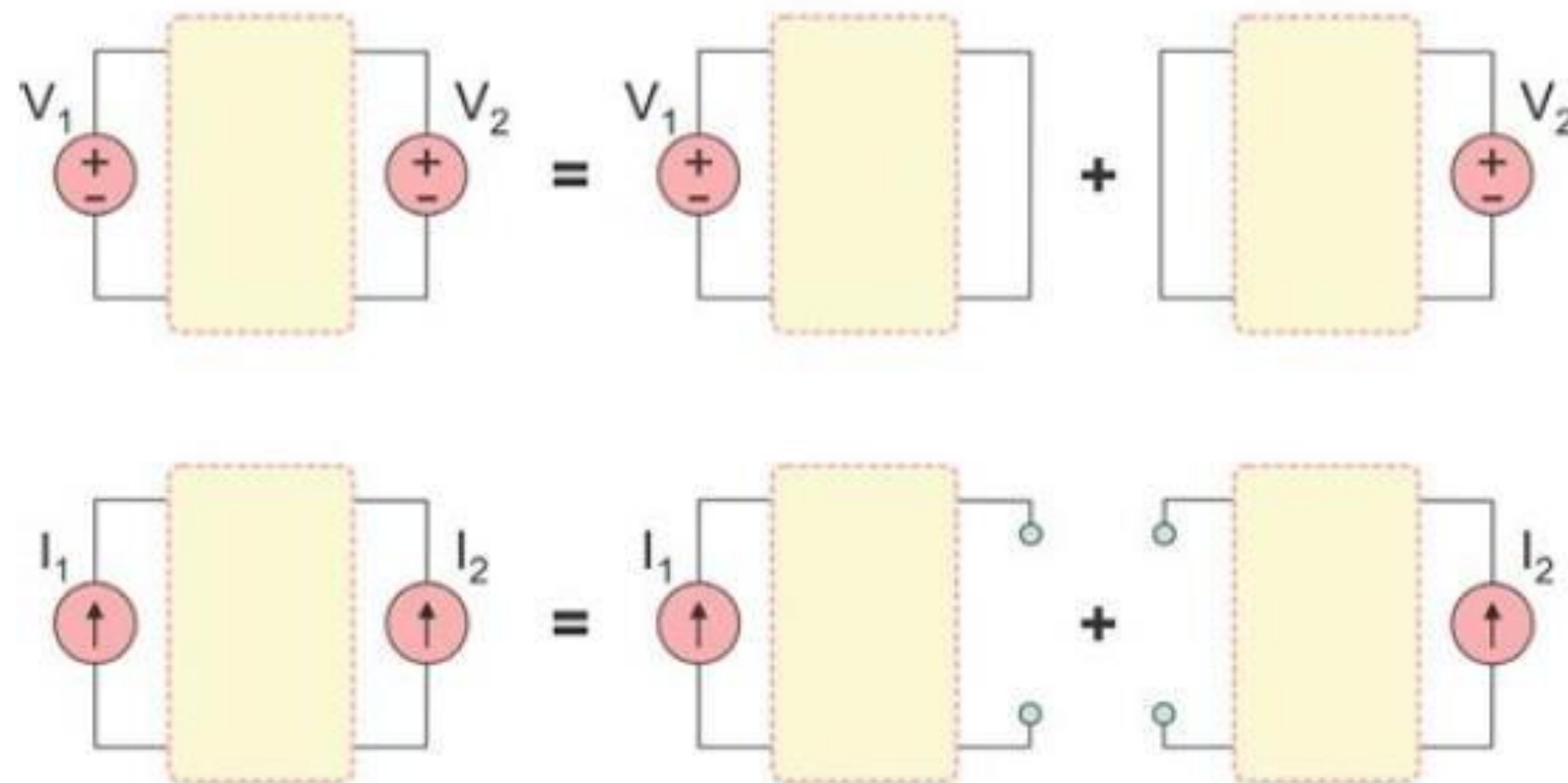
## Statement


- In any **linear bilateral network** containing two or more independent sources (voltage and/or current sources), **the resultant current / voltage** in any branch is the **algebraic sum of currents / voltages** caused by **each independent source** (with all other independent sources turned off).





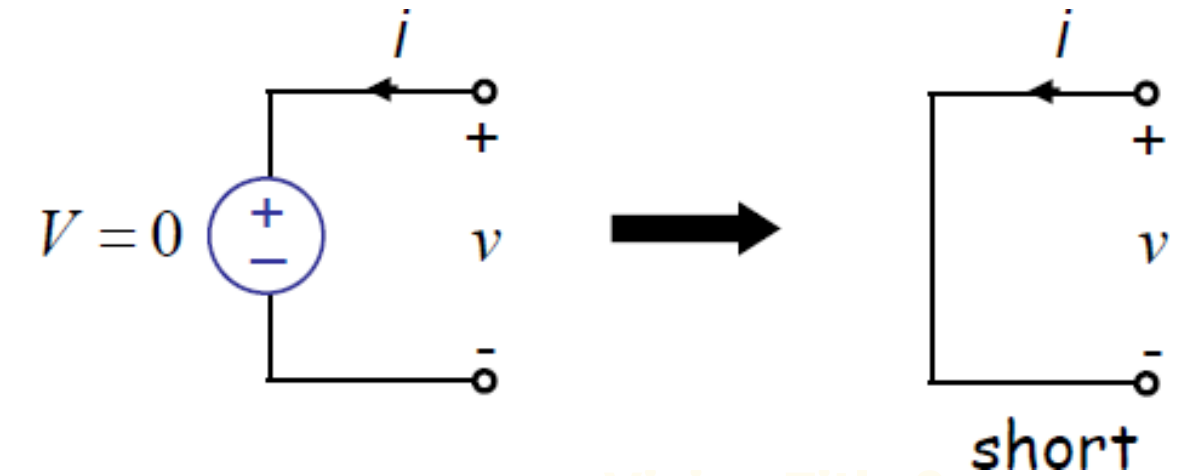
## Statement

- **To turn off a voltage source:** Replace by its internal resistance (for non-ideal source) or short circuit (for ideal source).
- **To turn off a current source:** Replace by its internal resistance (for non-ideal source) or open circuit (for ideal source).
- **The dependent sources should not be zeroed.** They remain the same for every particular solution with each independent source



Vision Tit 2

Vision Title 3

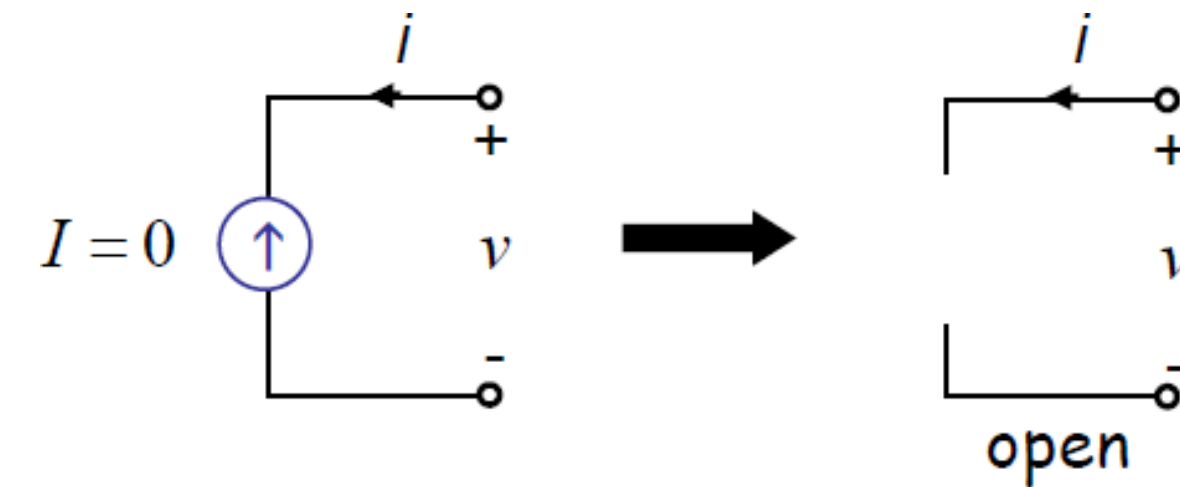



## Steps to Apply

- **Step-1:** Retain one source at a time in the circuit and replace all other sources with their internal resistances.
- **Step-2:** Determine the output (current or voltage) due to the single source acting alone using any circuit analysis techniques (mesh, node, transformations etc.).
- **Step-3:** Repeat steps 1 and 2 for every independent source.
- **Step-4:** Find the total contribution by adding algebraically all the contributions due to all the independent sources.