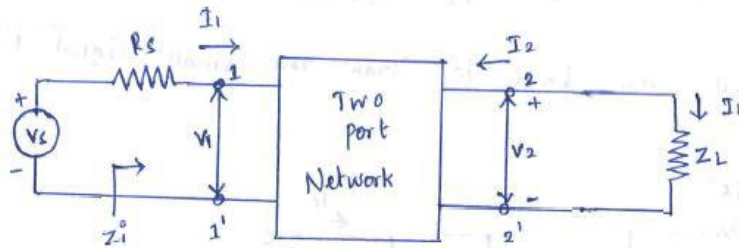





Topic 2.3 : Analysis of Transistor amplifier circuit using h parameters

Midband Analysis of BJT single stage Amplifiers

• 16 Mark



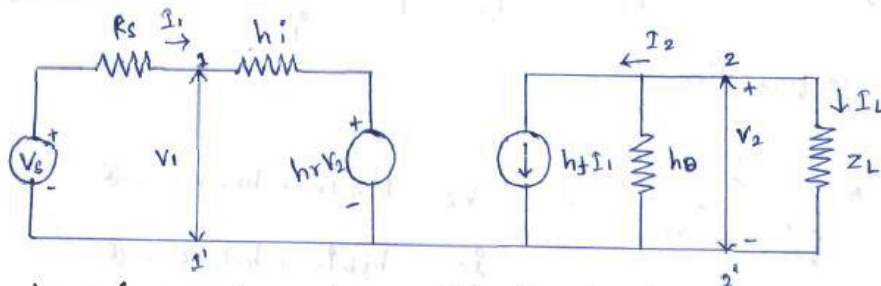A Transistor can be constructed by connecting an external load & signal source as indicated & biasing the transistor properly.



1. Current gain (or) Current Amplification (A_i)

It's the ratio of output current to input current.

$$A_i = \frac{I_L}{I_1} = \frac{-I_2}{I_1}$$

Here I_L & I_2 are equal in magnitude but opposite in sign

$$\text{i.e. } I_L = -I_2$$

From the circuit

$$I_2 = h_f I_1 + h_o V_2$$

Then

$$V_2 = I_L Z_L = -I_2 Z_L$$

Substitute V_2 in I_2



$$I_2 = h_f I_1 + h_o (-I_2 Z_L)$$

$$I_2 + h_o I_2 Z_L = h_f I_1$$

$$I_2 (1 + h_o Z_L) = h_f I_1$$

$$\frac{I_2}{I_1} = \frac{h_f}{1 + h_o Z_L}$$

$$\therefore A_I = \frac{-I_2}{I_1} = \frac{-h_f}{1 + h_o Z_L}$$

2. Input Impedance (Z_i)

$$Z_i = \frac{V_1}{I_1}$$

From input circuit

$$V_1 = h_i I_1 + h_r V_2$$

Substitute V_2 in Z_i

$$Z_i = \frac{h_i I_1 + h_r V_2}{I_1} = h_i + h_r \frac{V_2}{I_1} \quad \text{--- (1)}$$

$$\therefore V_2 = -I_2 Z_L$$

$$= -(-A_I I_1) Z_L$$

$$V_2 = A_I I_1 Z_L \quad \text{--- (2)}$$

Sub (2) in (1)

$$Z_i = h_i + h_r \frac{A_I I_1 Z_L}{I_1}$$

$$= h_i + h_r A_I Z_L$$

Sub A_I in Z_i

$$Z_i = h_i + h_r \left(\frac{-h_f}{1 + h_o Z_L} \right) Z_L$$

$$= h_i - \frac{h_r h_f \cdot Z_L}{1 + h_o Z_L} = h_i - \frac{(h_r h_f) Z_L}{Z_L (\frac{1}{Z_L} + h_o)}$$

$$= h_i - \frac{h_r h_f}{\frac{1}{Z_L} + h_o}$$

$$\therefore Y_L = \frac{1}{Z_L}$$

$$\boxed{Z_i = h_i - \frac{h_r h_f}{Y_L + h_o}} \quad \text{--- (3)} \rightarrow \text{The input impedance is the function of load impedance.}$$



3. Voltage gain (or) Voltage Amplification factor (A_v)

It's the ratio of output voltage to input voltage

$$A_v = \frac{V_2}{V_1}$$

$$V_2 = -I_2 Z_L = A_I I_1 Z_L$$

$$\therefore A_I = \frac{-I_2}{I_1}$$

Sub V_2 in A_v

$$A_v = \frac{A_I I_1 Z_L}{V_1}$$

$$\frac{I_1}{V_1} = \frac{1}{Z_i}$$

$$A_v = \frac{A_I Z_L}{Z_i}$$

4. Output Admittance (Y_o)

It's the ratio of output current (I_2) to the output voltage (V_2).

$$Y_o = \frac{I_2}{V_2} \text{ with } V_s = 0$$

$$I_2 = h_f I_1 + h_o V_2 \quad \text{--- (1)}$$

divide eqn (1) by V_2

$$Y_o \Leftarrow \frac{I_2}{V_2} = \frac{h_f I_1 + h_o V_2}{V_2} = \frac{h_f I_1}{V_2} + h_o \quad \text{--- (2)}$$

With $V_s = 0$ by Apply KVL to the above circuit

$$R_s I_1 + h_i I_1 + h_r V_2 = 0$$

$$I_1 (R_s + h_i) + h_r V_2 = 0$$

$$I_1 (R_s + h_i) = -h_r V_2$$

$$\frac{I_1}{V_2} = \frac{-h_r}{(R_s + h_i)}$$

$$Y_o = h_f \left(\frac{-h_r}{(R_s + h_i)} \right) + h_o$$

$$Y_o = h_o - \frac{h_f h_r}{(R_s + h_i)}$$

Output impedance is a function of source resistance. If the source impedance is resistive then Y_o is real.

(6)