



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**

**An Autonomous Institution**

Accredited by NBA – AICTE and Accredited by NAAC – UGC with  
'A++' Grade

Approved by AICTE, New Delhi & Affiliated to Anna University,  
Chennai



## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **23ECB222- Digital Principles and Computer Organization**

**II AIML / III SEMESTER**

**UNIT 2 – Combinational Circuits**

**Full Adder**



A combinational logic circuit that can add two binary digits (bits) and a carry bit, and produces a sum bit and a carry bit as output is known as a **full-adder**.

- The first two inputs are A and B and the third input is an input carry as C-IN.
- The output carry is designated as C-OUT and the normal output is designated as S which is SUM.

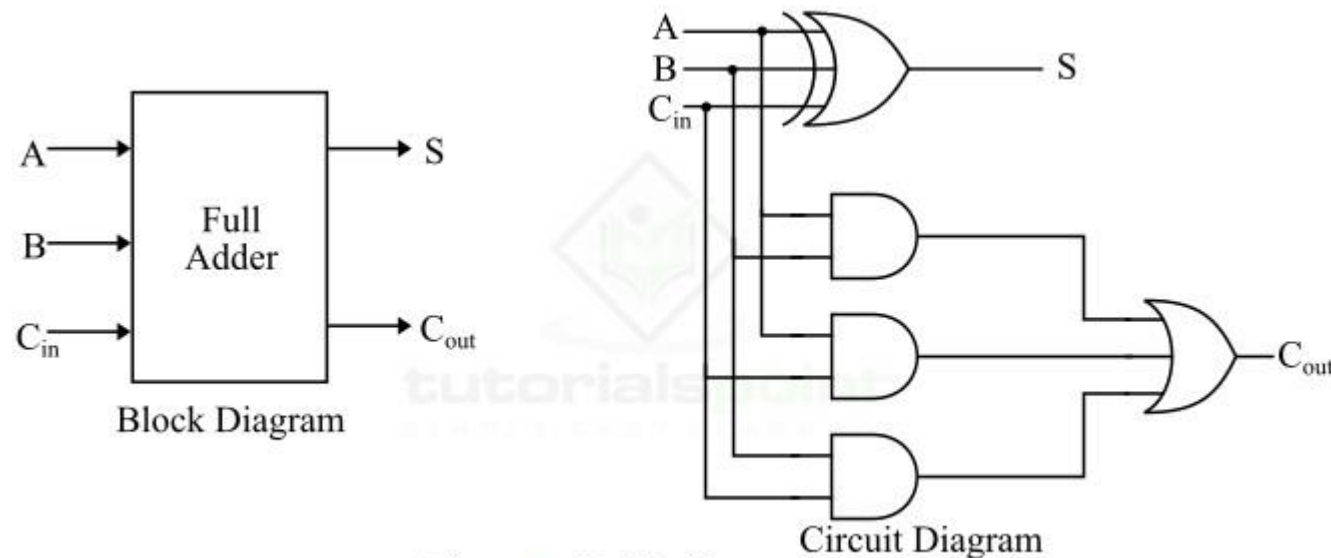


Figure 1 - Full Adder



## Truth table

Inputs			Outputs	
A	B	C-IN	Sum	C-Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



## K- Map for full adder

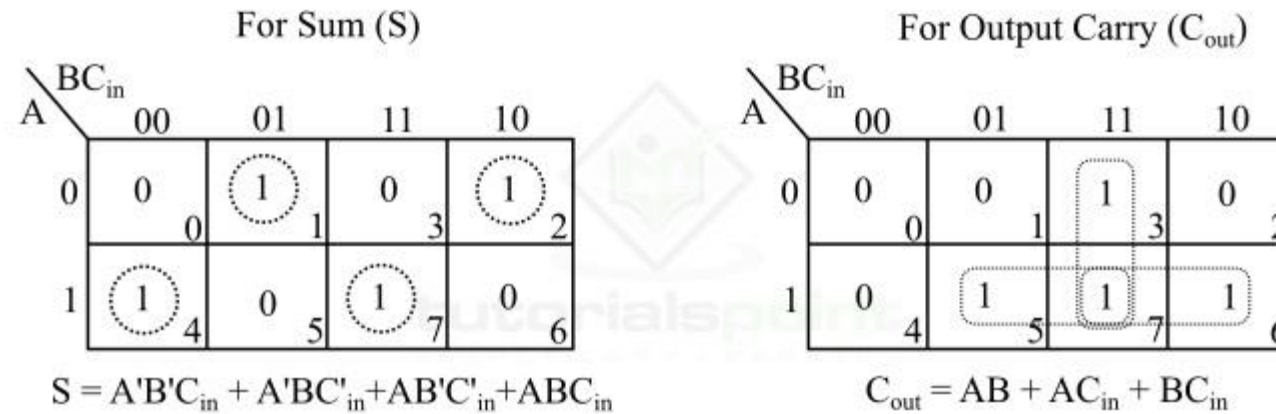


Figure 2 - K Map for Full Adder

$$\text{Sum, } S = A \oplus B \oplus C_{in} = A'B'C_{in} + A'BC'_{in} + AB'C'_{in} + ABC_{in}$$

$$\text{Carry, } C = AB + AC_{in} + BC_{in}$$



## Application of Half Adder in Digital Logic

- ALUs (arithmetic logic units) of CPUs of computers.
- It is used in calculators.
- It also helps in carrying out multiplication of binary numbers.
- It is used to realize critic digital circuits like multiplexers.
- To generate memory addresses.
- Full adders are also used in GPU (Graphical Processing Unit).



THANK YOU