



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' (III Cycle) Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**

### **23ECB201 – DIGITAL SYSTEMS DESIGN**

**II YEAR/ III SEMESTER**

#### **UNIT 2 – COMBINATIONAL CIRCUITS**


**TOPIC- HALF ADDER**


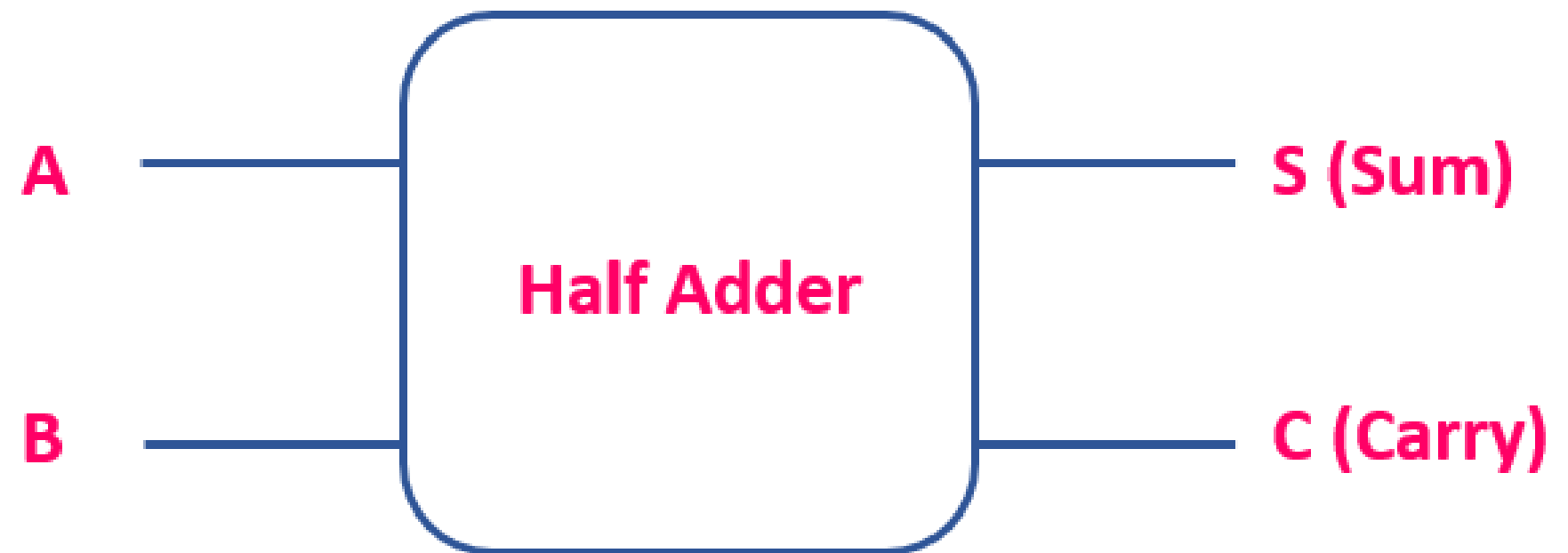
## HALF ADDER



- A half adder is a digital logic circuit that performs binary addition of two single-bit binary numbers.
- Half adder is a combinational arithmetic circuit that adds two numbers and produces a sum bit (s) and carry bit (c) both as output.
- The input variables are augend and addend bits and output variables are sum & carry bits.





## TRUTH TABLE



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

### Binary Addition

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$



## LOGICAL EXPRESSION



**FOR SUM**

A \ B	0	1
0	0	1
1	1	0

$$\text{Sum, } S = A \oplus B = AB' + A'B$$

**FOR CARRY**

A \ B	0	1
0	0	0
1	0	1


$$\text{Carry, } C = A \cdot B$$



## IMPLEMENTATION

$\text{Sum} = A \text{ XOR } B$

$\text{Carry} = A \text{ AND } B$

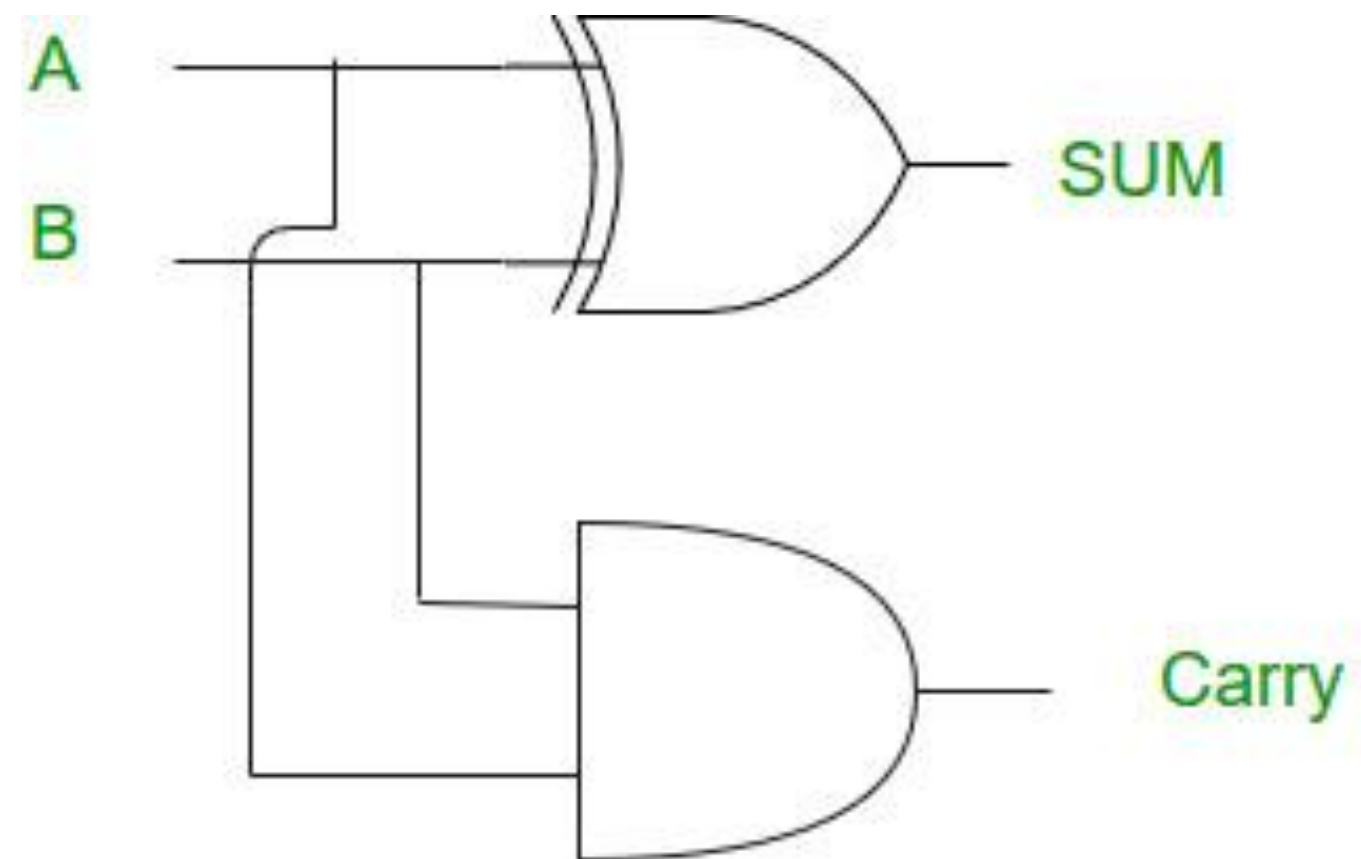



# APPLICATIONS OF HALF ADDER



1. Arithmetic circuits
2. Data handling
3. Address unraveling
4. Encoder and decoder circuits
5. Multiplexers and demultiplexers
6. Counters







# ADVANTAGES AND DISADVANTAGES



## ADVANTAGES

- Simplicity
- Speed

## DISADVANTAGES

- Limited Usefulness
- Lack of Convey Info
- Propagation Deferral





# ASSESSMENT QUESTIONS



1. Total number of inputs in a half adder is \_\_\_\_\_
  - a) 2
  - b) 3
  - c) 4
  - d) 1
2. In which operation carry is obtained?
  - a) Subtraction
  - b) Addition**
  - c) Multiplication
  - d) Both addition and subtraction
3. If A and B are the inputs of a half adder, the sum is given by \_\_\_\_\_
  - a) A AND B
  - b) A OR B
  - c) A XOR B**
  - d) A EX-NOR B







**THANK YOU**