



# SNS COLLEGE OF TECHNOLOGY

Coimbatore-35  
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

### 19ECB302–VLSI DESIGN

III YEAR/ V SEMESTER

### UNIT III-SEQUENTIAL LOGIC CIRCUITS

### TOPIC 1-STATIC LATCHES AND DYNAMIC REGISTERS



# OUTLINE



- **LATCH VERSUS REGISTER**
- **LATCH-BASED DESIGN**
  - MUX,
  - MASTER SLAVE REGISTER
- **ACTIVITY**
- **TIME,CLK BASED LATCHES**
- **PULSE-TRIGGERED LATCHES**
- **SUMMARY**

10/17/2024



# Introduction – Latches and Registers



## REGISTER

- Used to hold the system state. Clock pulse is applied to the registers. On the rising edge of the clock pulse, the next state bits are copied to the output of the registers .

## Two Types

1. **Positive edge triggered** – input is copied on positive edge of clock.
2. **Negative edge triggered** - input is copied on negative edge of clock.

## LATCH

- Level sensitive circuit which is used to pass the D input to the Q output when clock is high.

## SET UP TIME

- Time during which the data input is valid before the transition of the clock pulse.

## HOLD TIME

- Time during which the data input remains valid after the edge of the clock pulse.


## CONTAMINATION DELAY – Minimum Delay



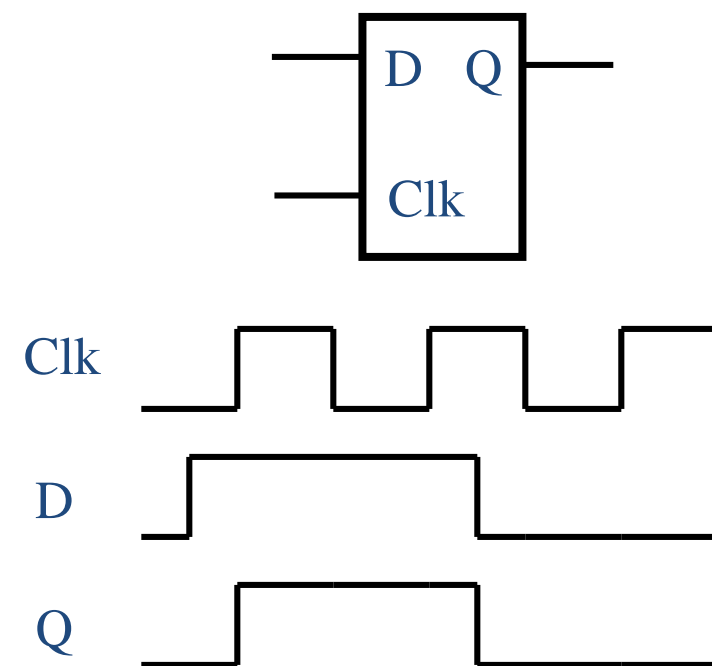
# LATCH VERSUS REGISTER



- Latch  
stores data when  
clock is low



 - Register  
stores data when  
clock rises







# LATCHES



### Positive Latch

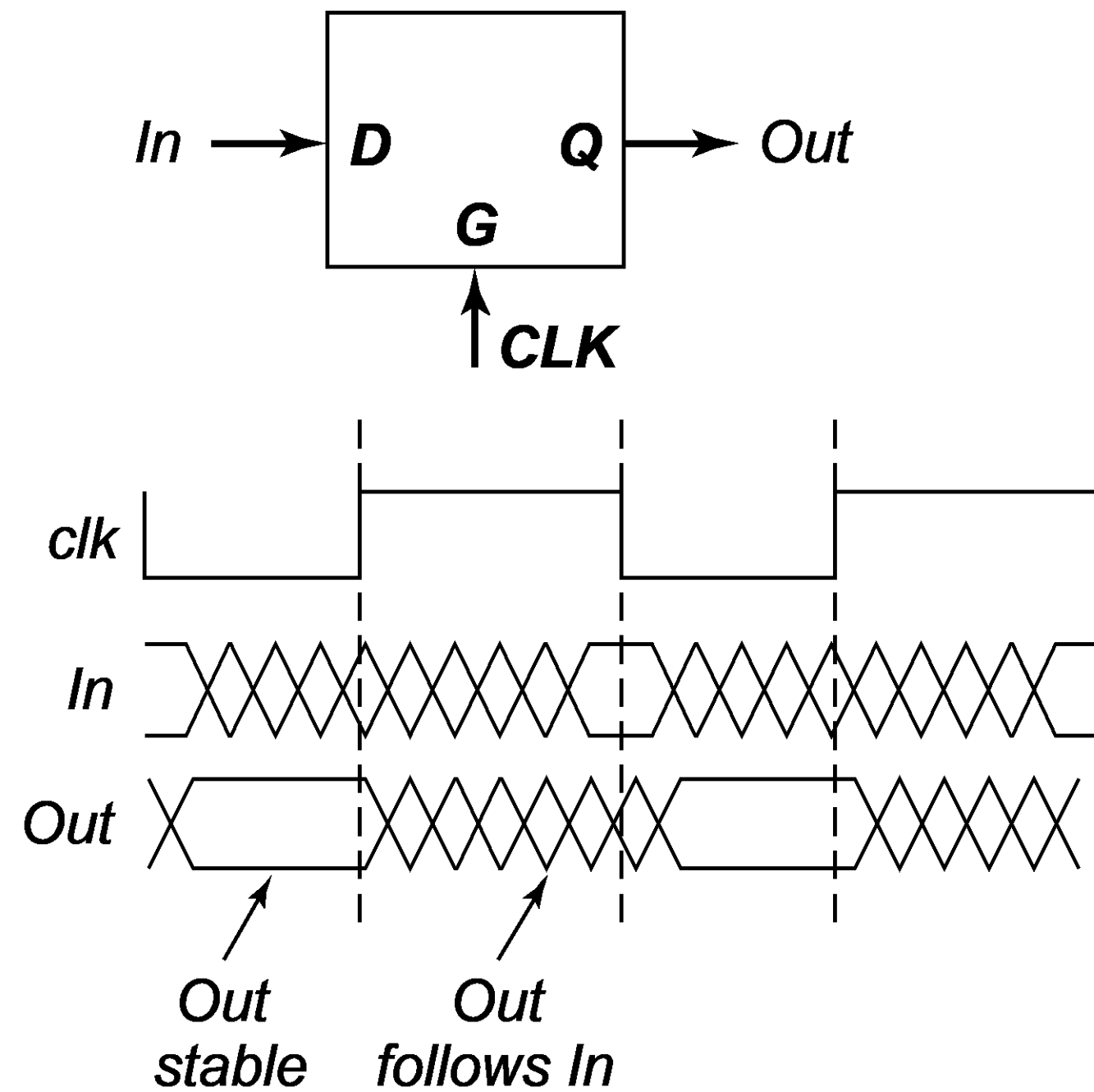

### Negative Latch

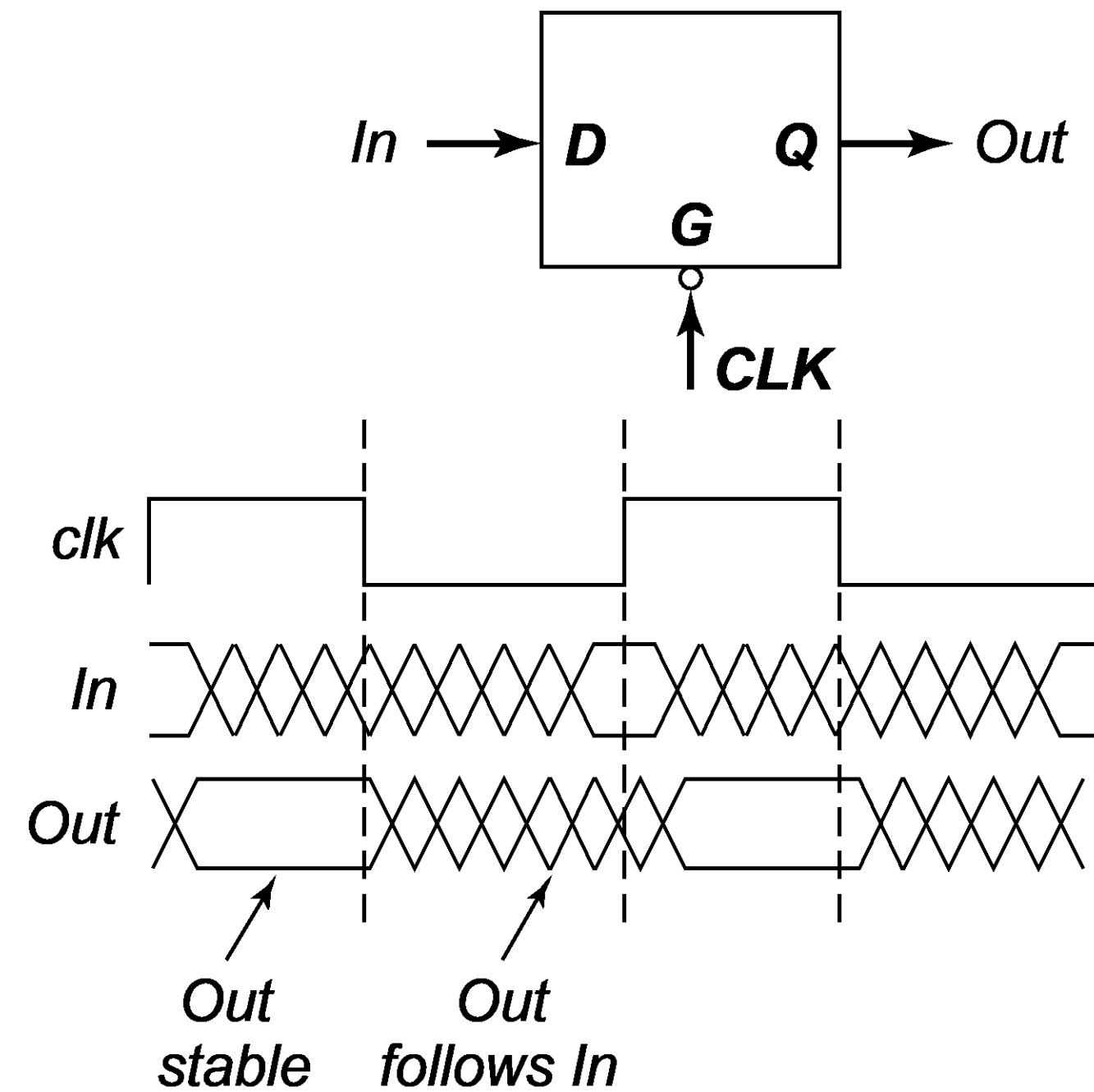




# LATCH-BASED DESIGN




- N latch is transparent when  $f = 0$

- P latch is transparent when  $f = 1$

 





# TIMING DEFINITIONS

 




# POSITIVE FEEDBACK: BI-STABILITY

  





# META-STABILITY

 


**Gain should be larger than 1 in the transition region**



 
# WRITING INTO A STATIC LATCH

Use the clock as a decoupling signal,  
that distinguishes between the transparent and opaque states




Converting into a MUX

 

Forcing the state  
(can implement as NMOS-only)



# MUX-BASED LATCH

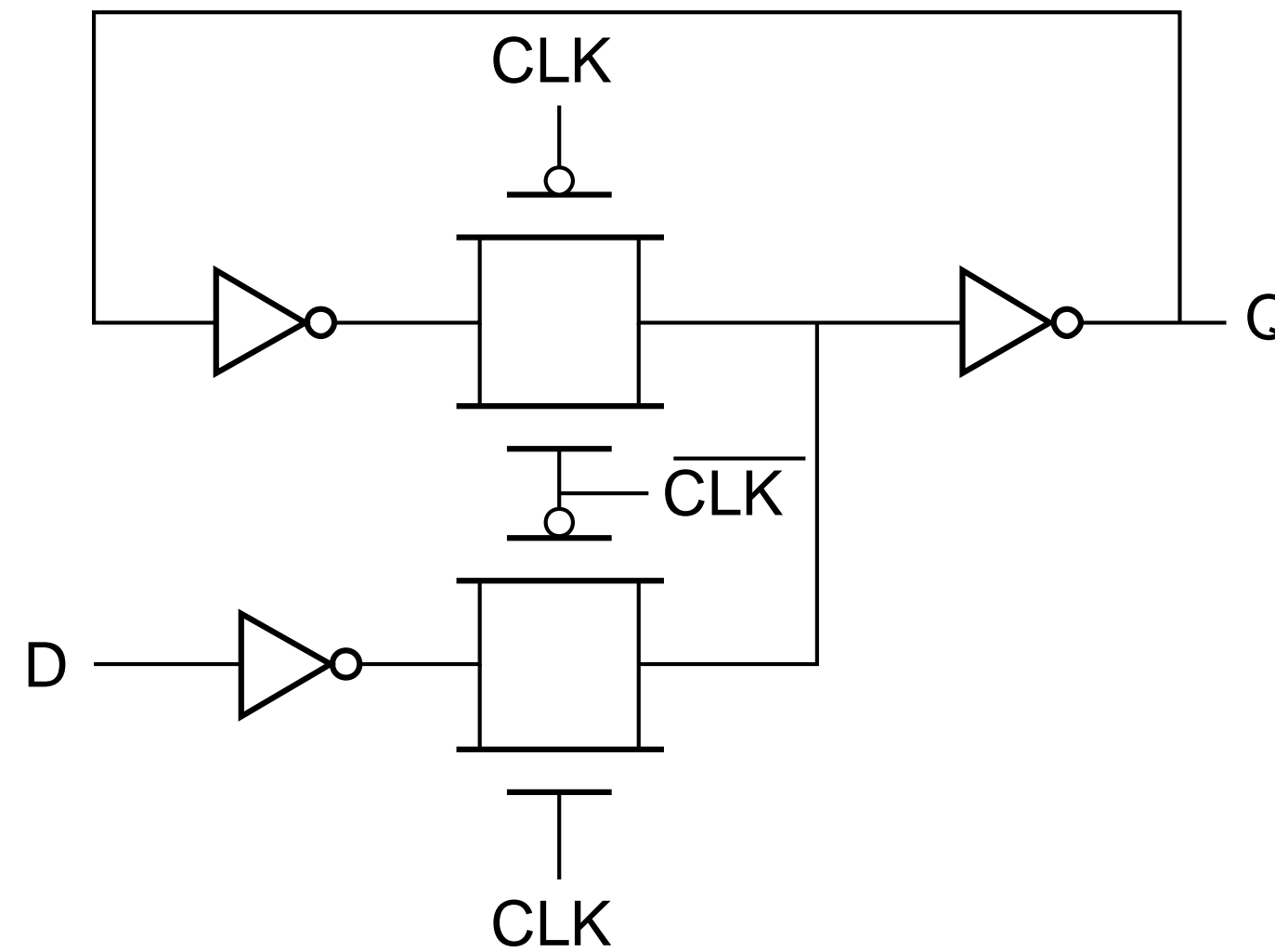



 
# MUX-BASED LATCHES




**Negative latch**  
(transparent when CLK= 0)



$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$


 
**Positive latch**  
(transparent when CLK= 1)



$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$



# MUX-BASED LATCH

 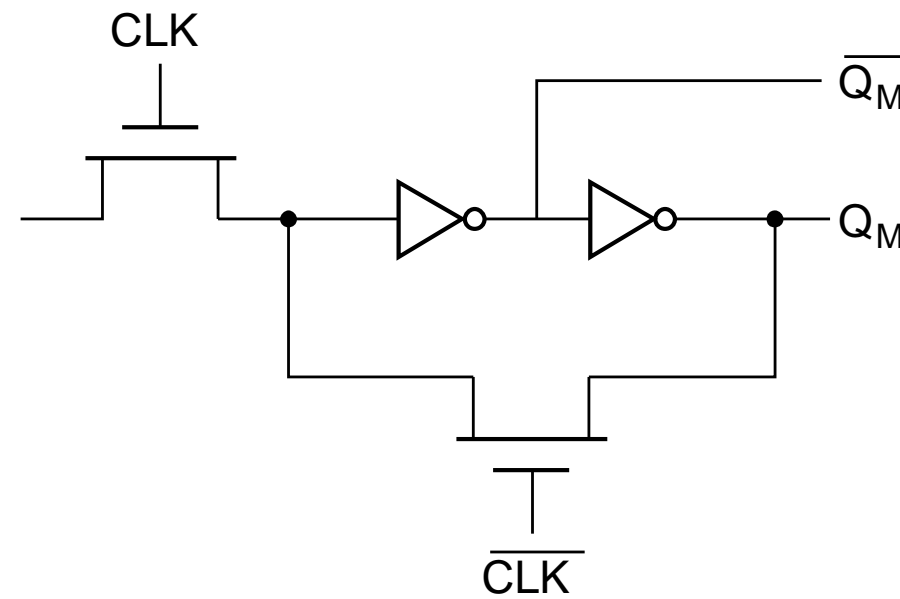


NMOS only

Non-overlapping clocks



# MASTER-SLAVE (EDGE-TRIGGERED) REGISTER

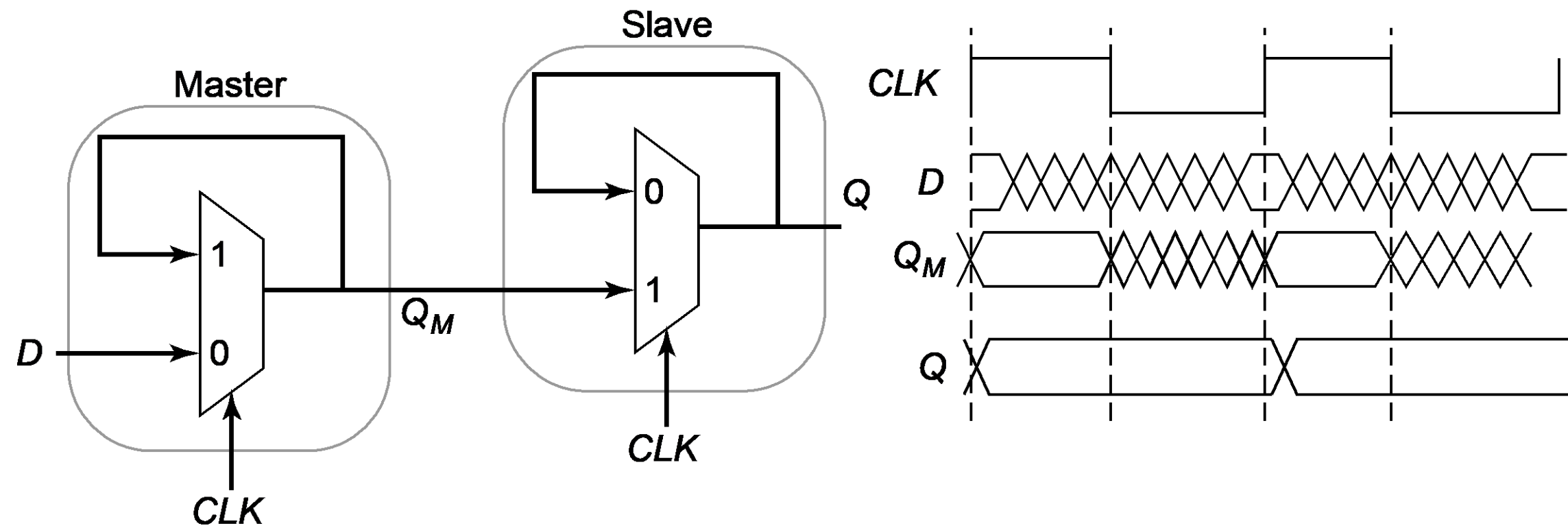


Two opposite latches trigger on edge  
Also called master-slave latch pair



# MASTER-SLAVE REGISTER




## Multiplexer-based latch pair

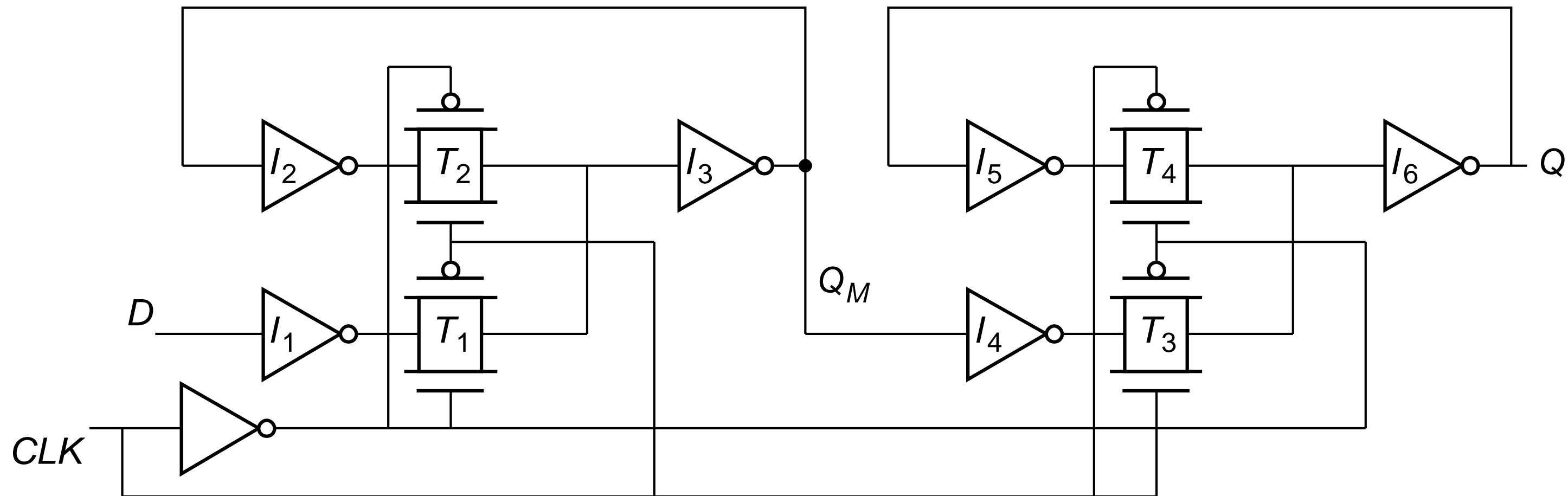




# CLK-Q DELAY

 






# SETUP TIME

 

 
(a)  $T_{\text{setup}} = 0.21 \text{ nsec}$



(b)  $T_{\text{setup}} = 0.20 \text{ nsec}$



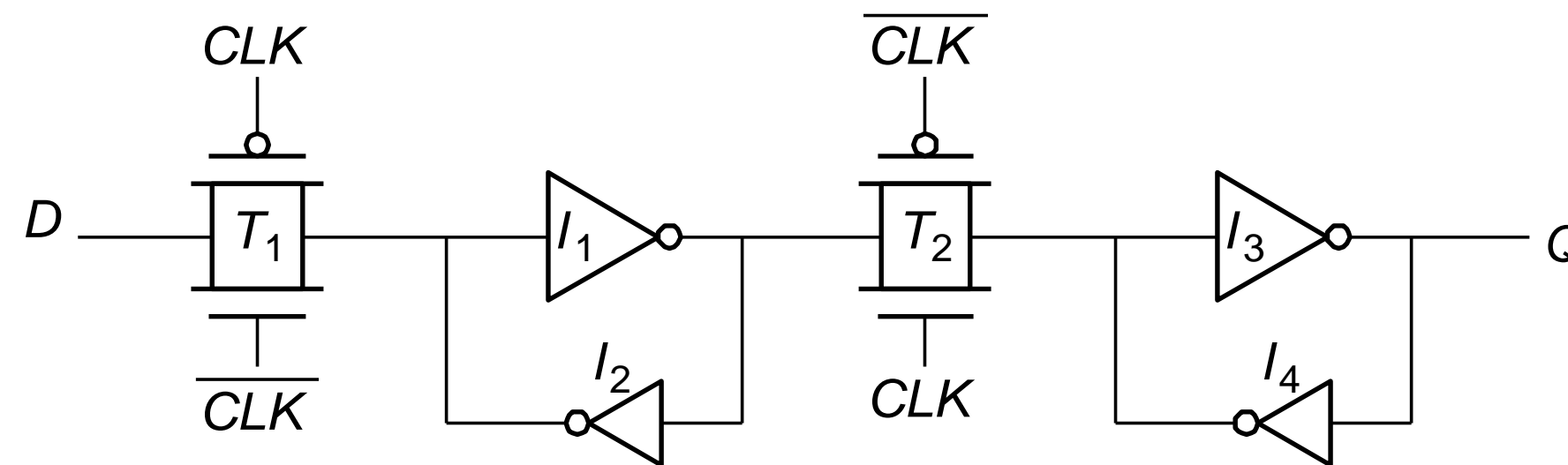
# REDUCED CLOCK LOAD MASTER-SLAVE REGISTER







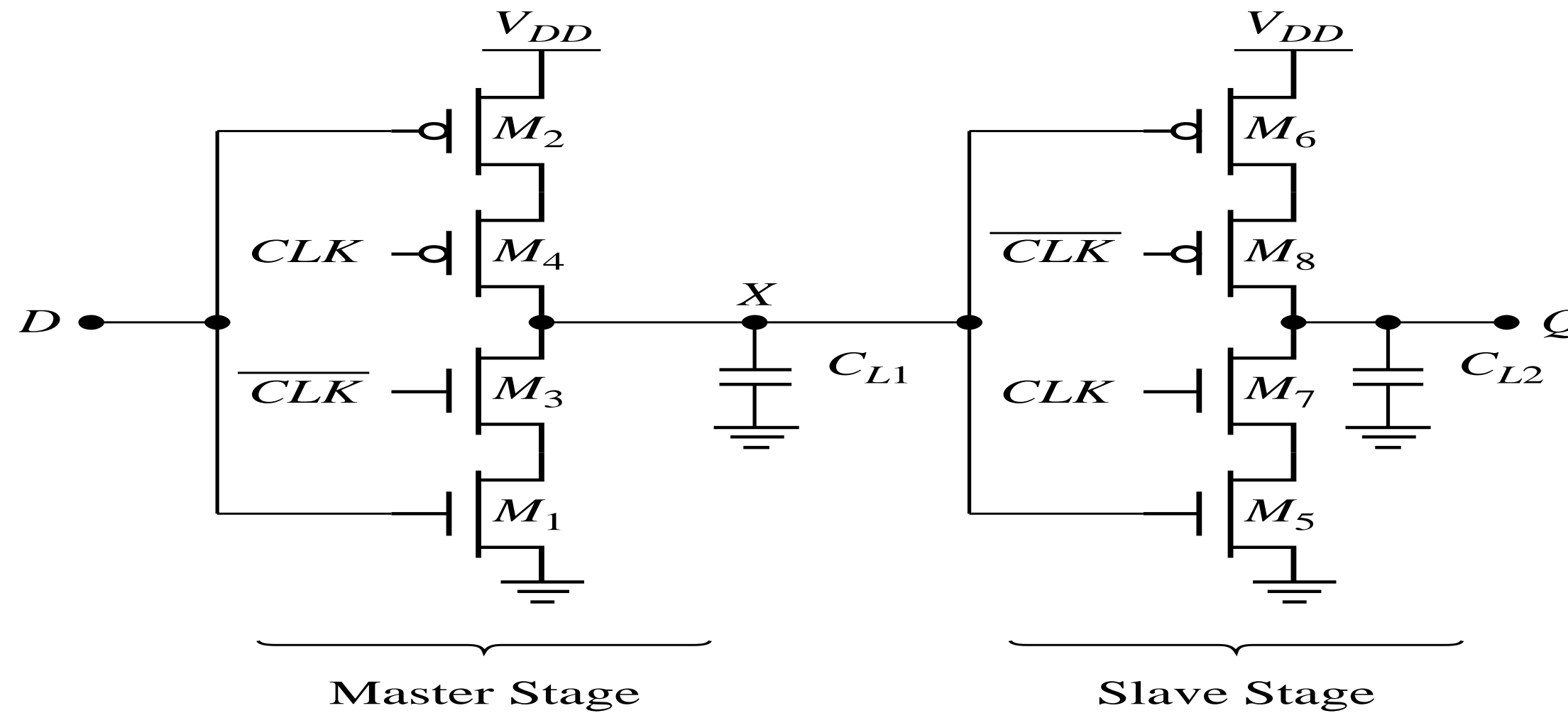
# OTHER LATCHES/REGISTERS: C<sup>2</sup>MOS



“Keepers” can be added to make circuit pseudo-static




# INSENSITIVE TO CLOCK-OVERLAP

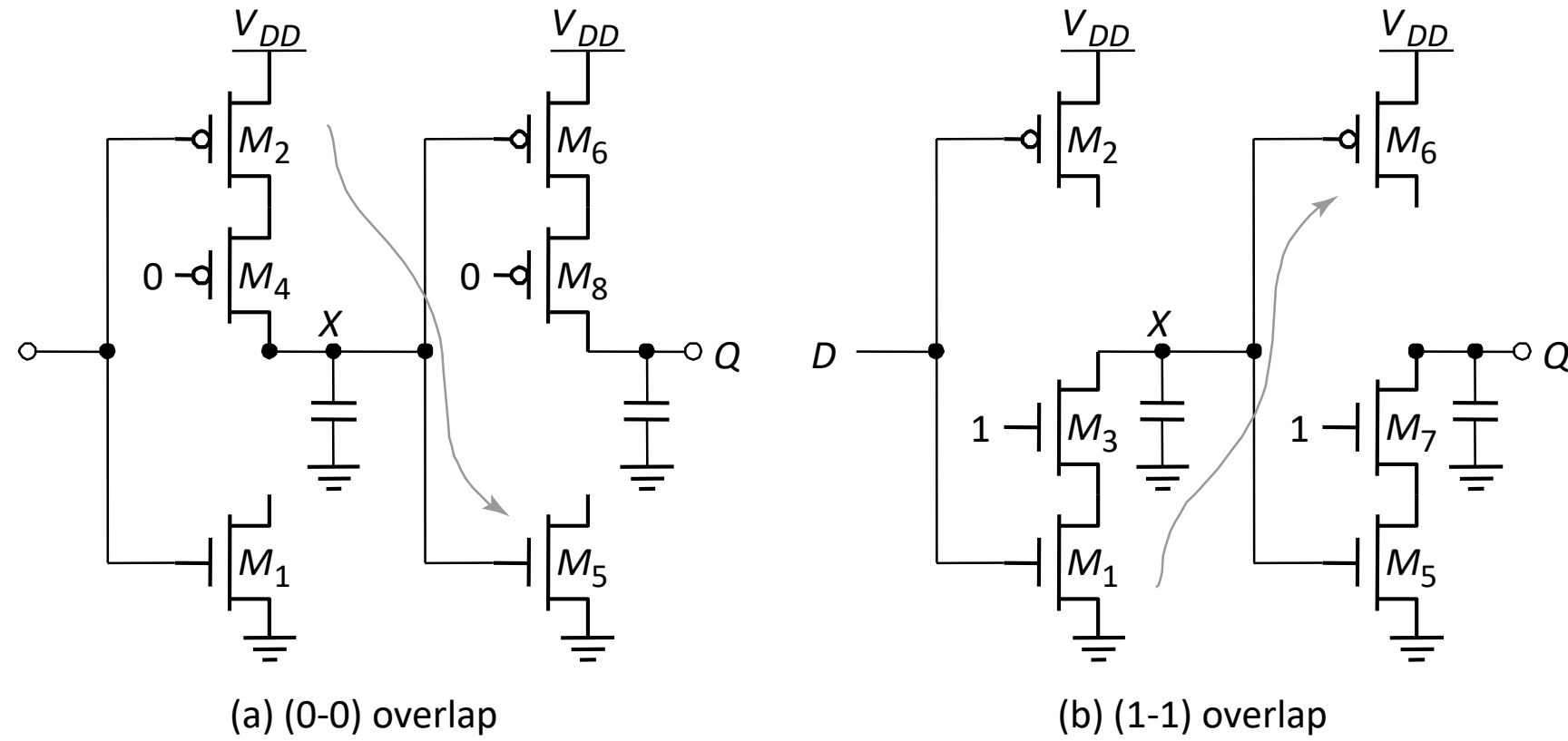




# OTHER LATCHES/REGISTERS: TSPC

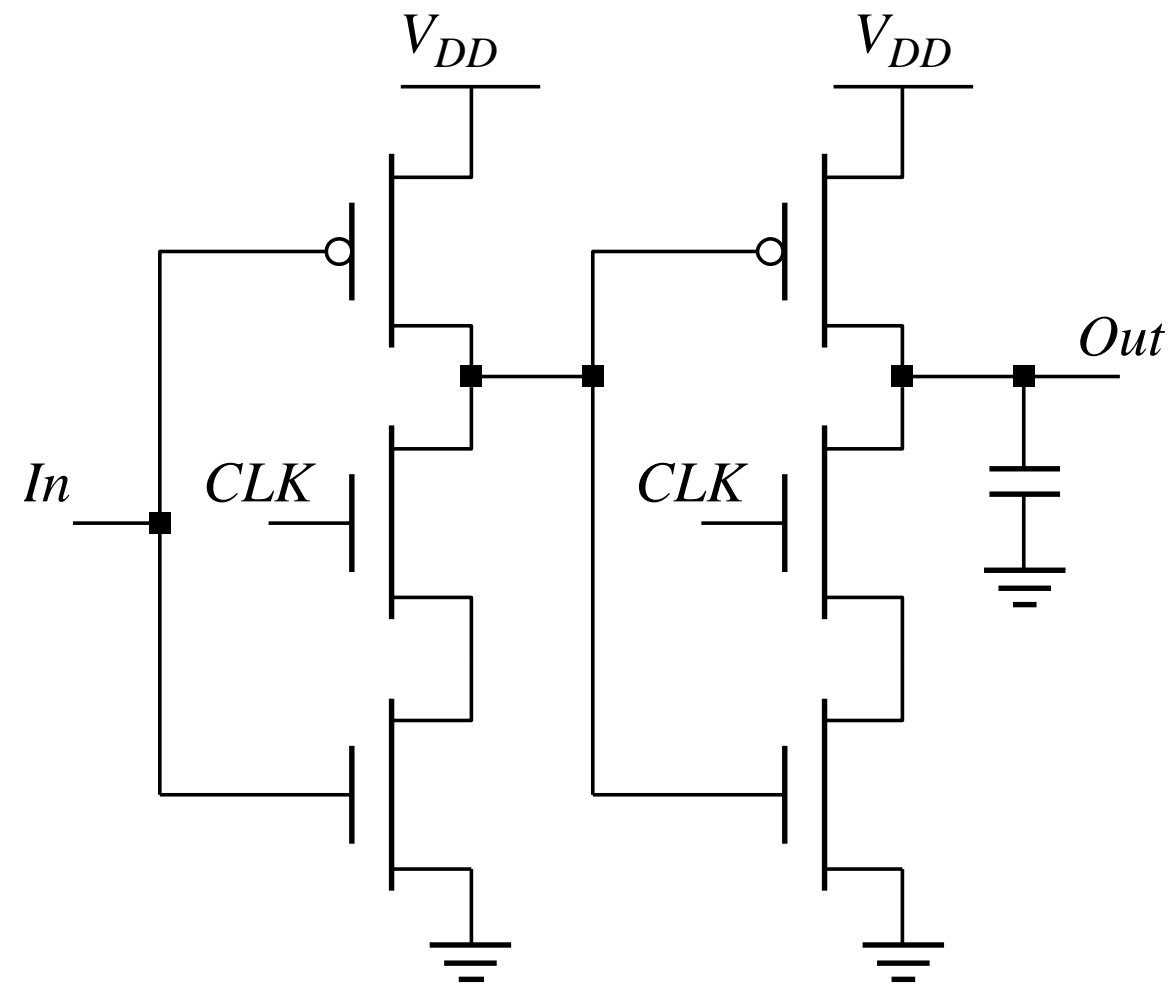

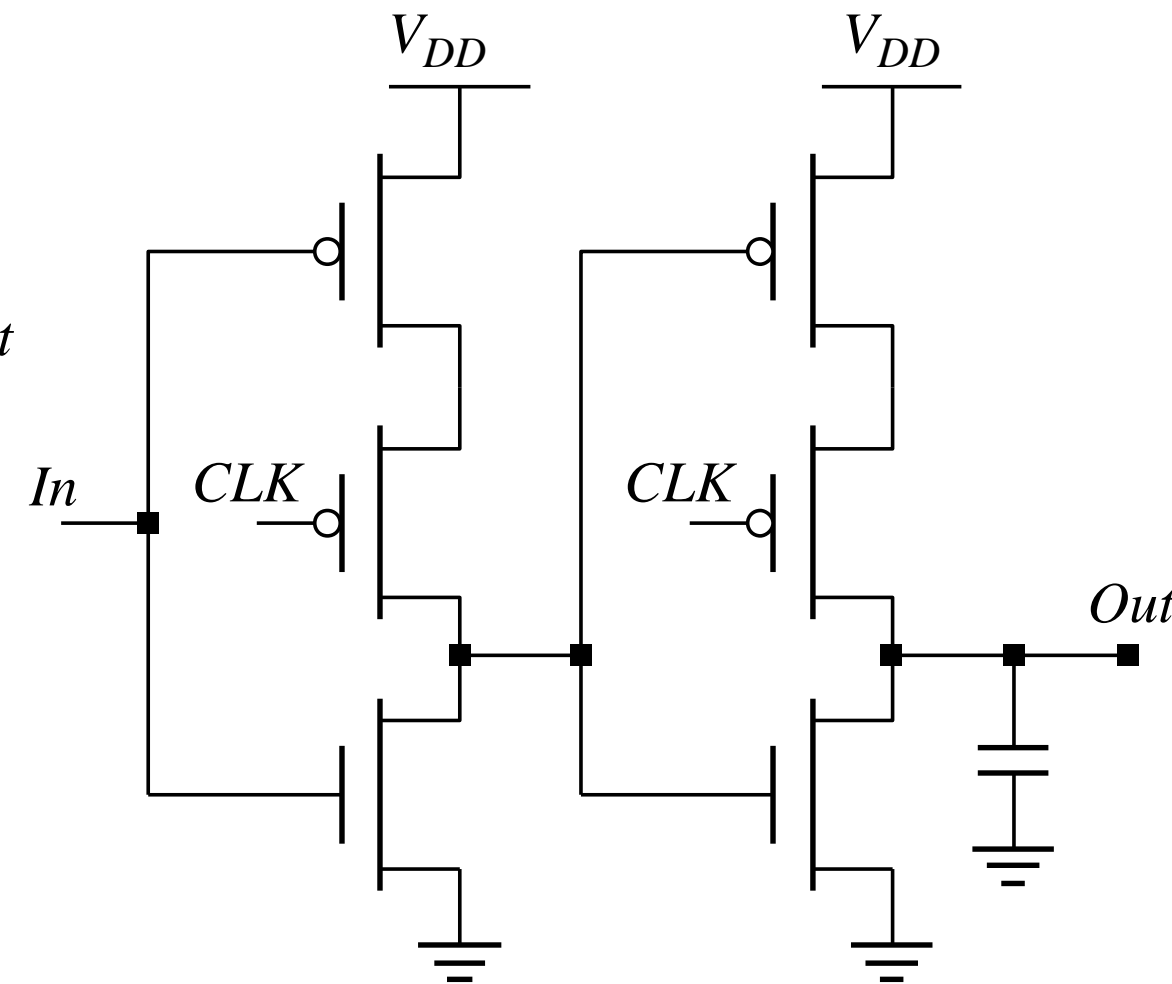Positive latch  
(transparent when CLK= 1)




Negative latch  
(transparent when CLK= 0)






# INCLUDING LOGIC IN TSPC

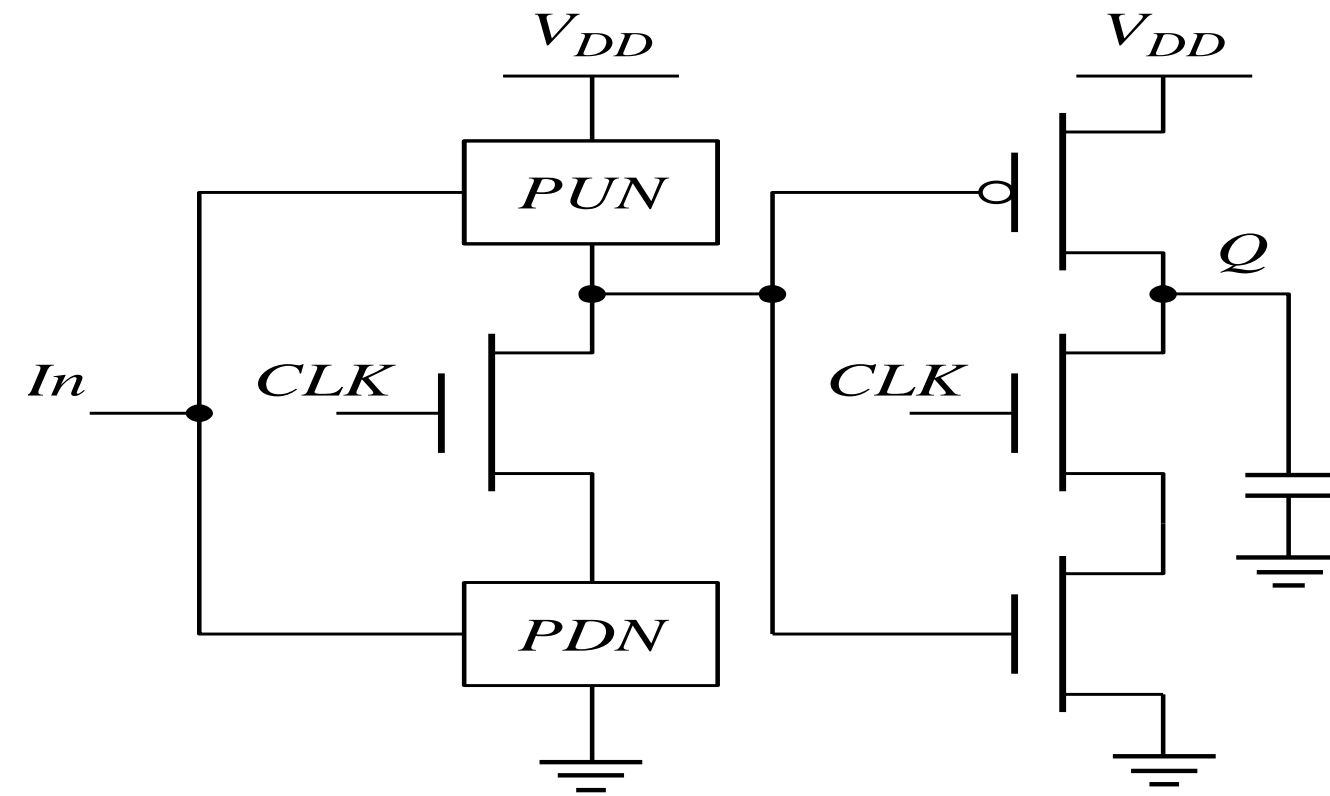

Example: logic inside the latch

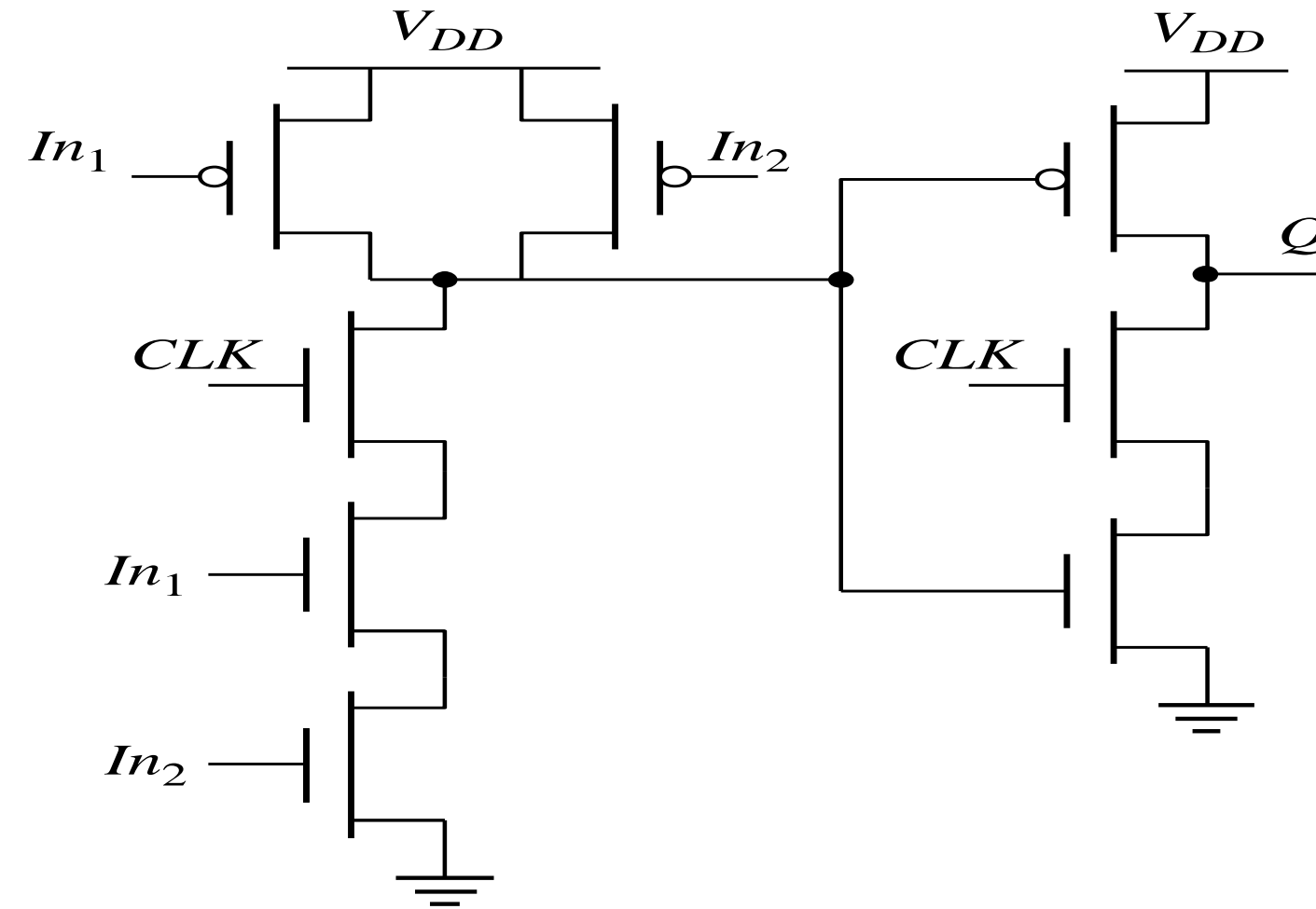


AND latch





# TSPC REGISTER

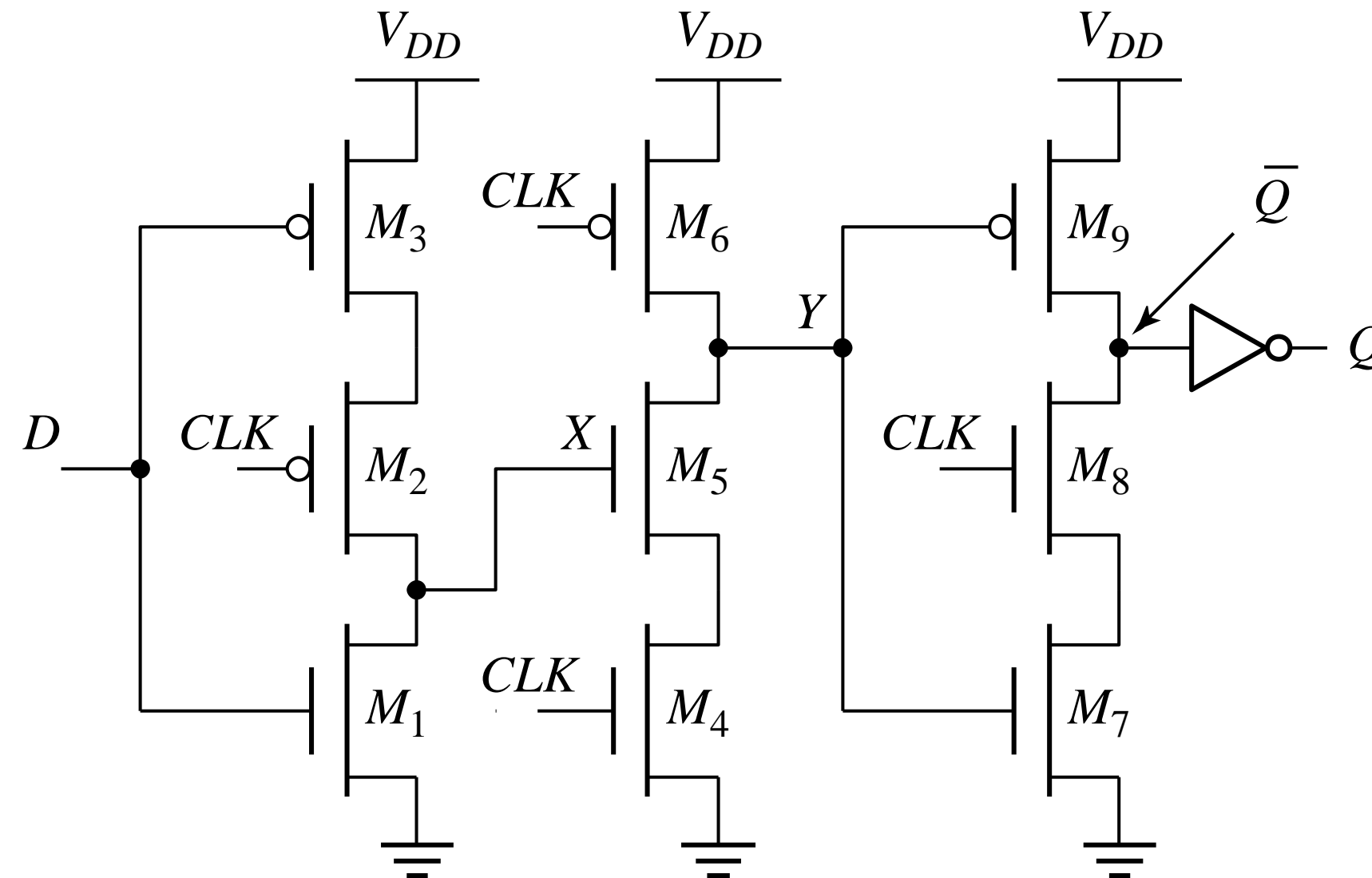






# PULSE-TRIGGERED LATCHES AN ALTERNATIVE APPROACH




Ways to design an edge-triggered sequential cell:

Master-Slave Latches

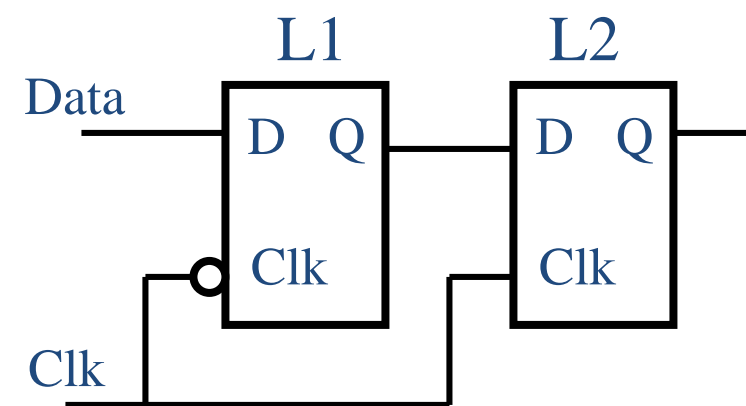

Pulse-Triggered Latch

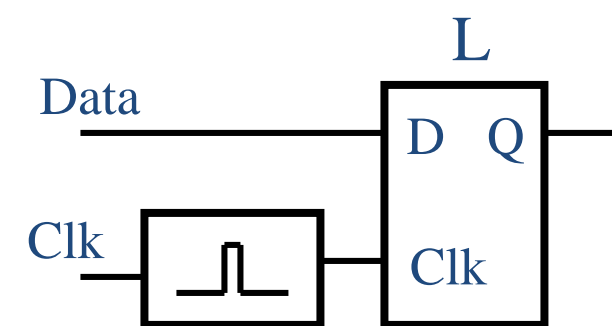



# ASSESSMENT



1. Compare Latch vs Register
2. Define Bi stability
3. Draw Master slave flip flop using latches





## SUMMARY & THANK YOU