



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

19ECB302–VLSI DESIGN

III YEAR/ V SEMESTER

UNIT 4 –VLSI TESTING

TOPIC 6 –BIST



OUTLINE




- INTRODUCTION
- BASIC CONCEPT OF TESTING
- PRINCIPLE OF TESTING
- DIFFICULTIES IN TESTING
- HOW TO DO TESTING
- CIRCUIT MODELING
- AUTOMATIC TEST PATTERN GENERATION (ATPG)
- DIFFICULTIES IN TEST GENERATION-2 TYPES
- TESTABLE DESIGN
- ACTIVITY
- BUILT-IN-SELF TEST (BIST)
- RANDOM NUMBER GENERATOR (RNG)
- SIGNATURE ANALYZER (SA)
- MEMORY BIST ARCHITECTURE
- CPU TEST CONTROL ARCHITECTURE
- TESTING METHODS
- ASSESSMENT
- SUMMARY & THANK YOU



BASIC CONCEPT OF TESTING



 Testing: To tell whether a circuit is good or bad



Related fields

Verification: To verify the correctness of a design


Diagnosis: To tell the faulty site

Reliability: To tell whether a good system will work correctly or not after some time.

Debug: To find the faulty site and try to eliminate the fault



PRINCIPLE OF TESTING

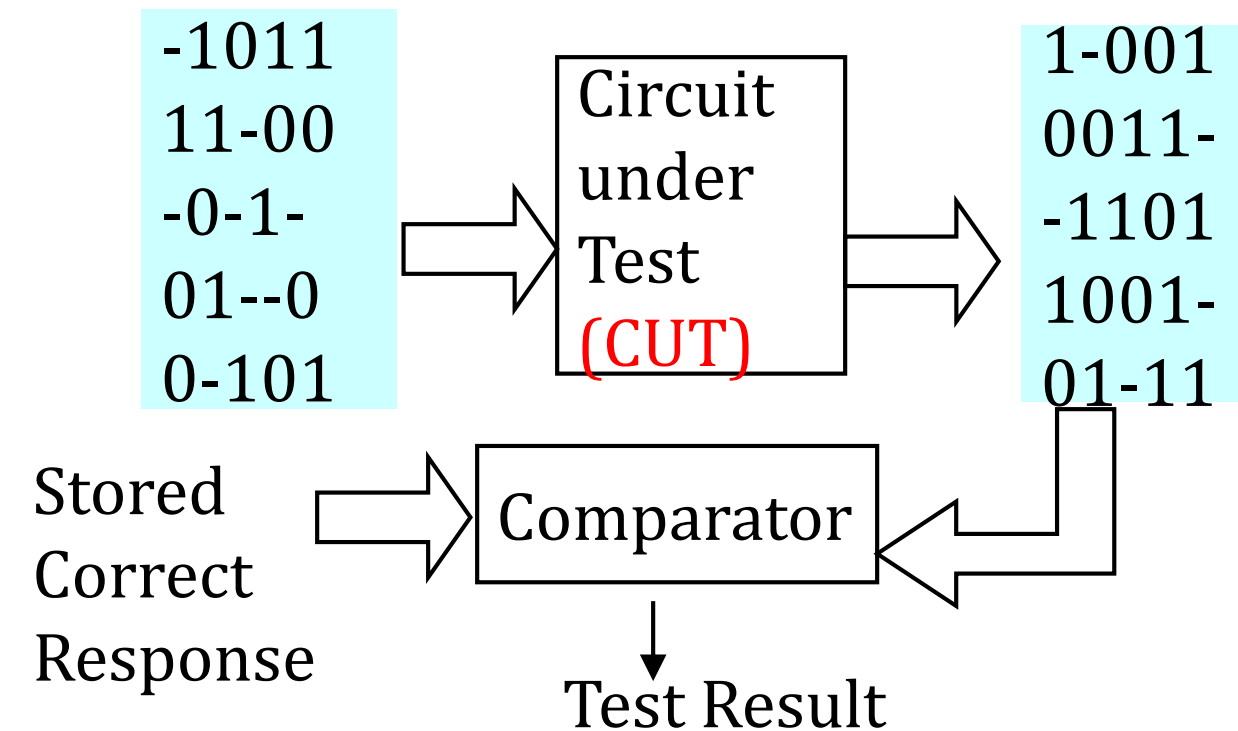


- Testing typically consists of
 - Applying set of test stimuli (input patterns, test vectors) to inputs of circuit under test (CUT), and
 - Analyzing output responses
- The quality of the tested circuits will depend upon the thoroughness of the test vectors



DIFFICULTIES IN TESTING



 - Fault may occur anytime
 - Design
 - Process
 - Package
 - Field
- Fault may occur at any place



- **VLSI circuit are large**
 - Most problems encountered in testing are NP-complete
- **I/O access is limited**



HOW TO DO TESTING



From designer's point of view:


- Circuit modeling
 - Fault modeling
- } Modeling
- Logic simulation
 - Fault simulation
 - Test generation
- } ATPG
- Design for test
 - Built-in self test
- } Testable design
- Synthesis for testability



CIRCUIT MODELING



 - **Functional model---** logic function
 - $f(x_1, x_2, \dots) = \dots$
 - Truth table
- **Behavioral model---** functional + timing
 - $f(x_1, x_2, \dots) = \dots$, Delay = 10
- **Structural model---** collection of interconnected components or elements






AUTOMATIC TEST PATTERN GENERATION



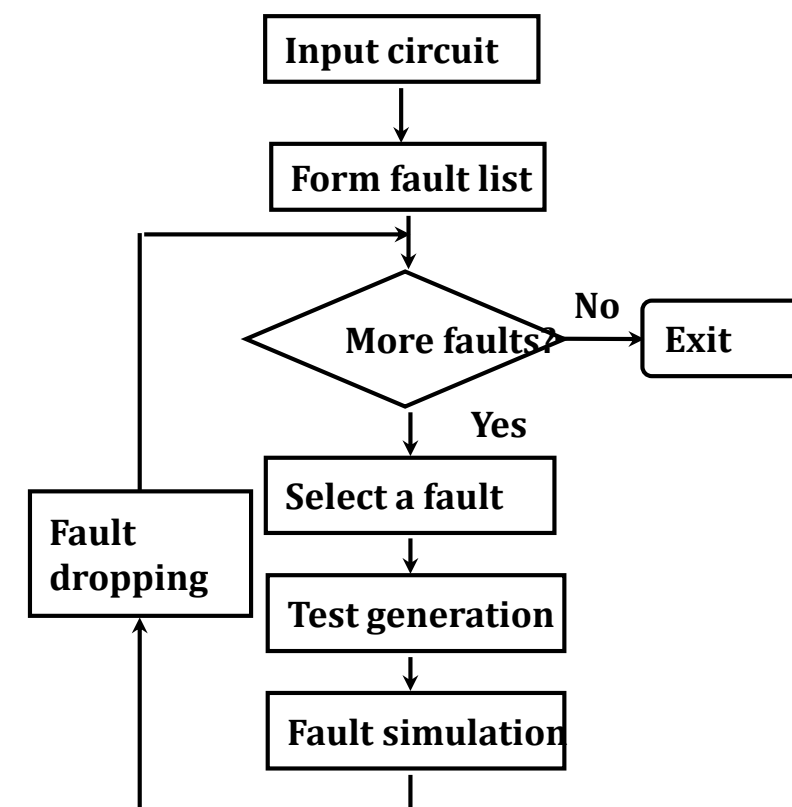- **ATPG:** Given a circuit, identify a set of test vectors to detect all faults under consideration.






TEST GENERATION

- **Given a fault, identify a test to detect this fault**

Example:

 

**To detect D s-a-0, D must be set to 1.
Thus A=B=1.**

**To propagate fault effect to the primary
output**

E must be 1. Thus C must be 0.


Test vector: A=1, B=1, C=0



DIFFICULTIES IN TEST GENERATION



1. Reconvergent fan-out

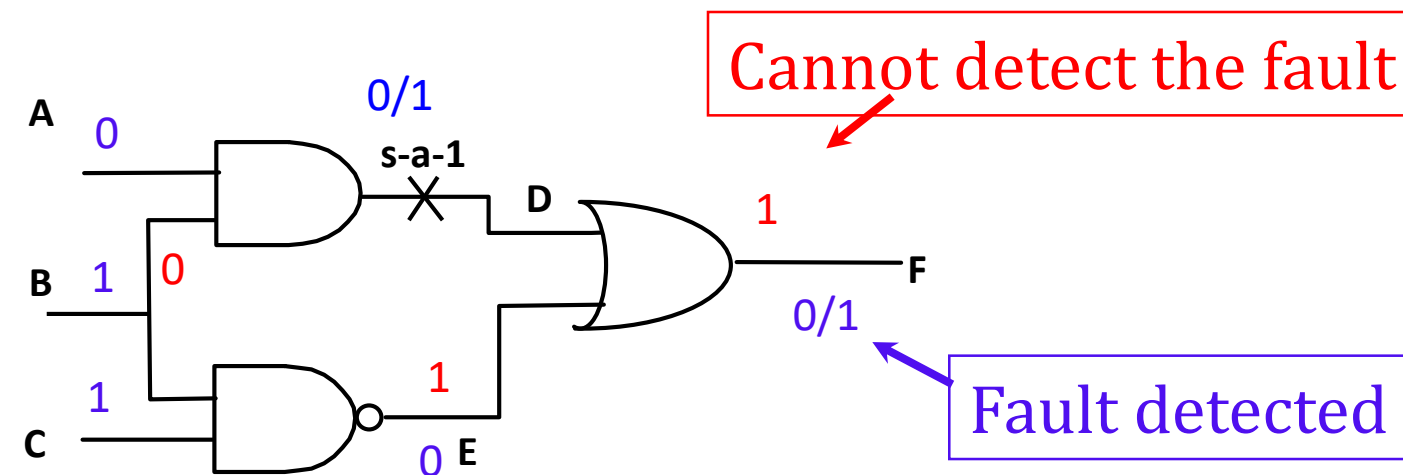




DIFFICULTIES IN TEST GENERATION (CONT.)



2. Sequential test generation

 



TESTABLE DESIGN



- Design for testability (DFT)
 - ad hoc techniques
 - Scan design
 - Boundary Scan
- **Built-In Self Test (BIST)**
 - **Random number generator (RNG)**
 - **Signature Analyzer (SA)**
- Synthesis for Testability



CLASS ROOM ACTIVITY



HOW CAN YOU DO YOUR INTERVIEW PREPARATION ????

Tell about yourself

Resume/CV –short & Neat

Aptitude,GD,Technical skill,HR interview

Tell about your final year project

Co & Extra curricular activities

Know about your company applying & Your job profile-Skill matching

Self confidence ,Body language


Knowledge ,Skill,Attitude,Team work, Adaptability etc...



BUILT-IN-SELF TEST (BIST)



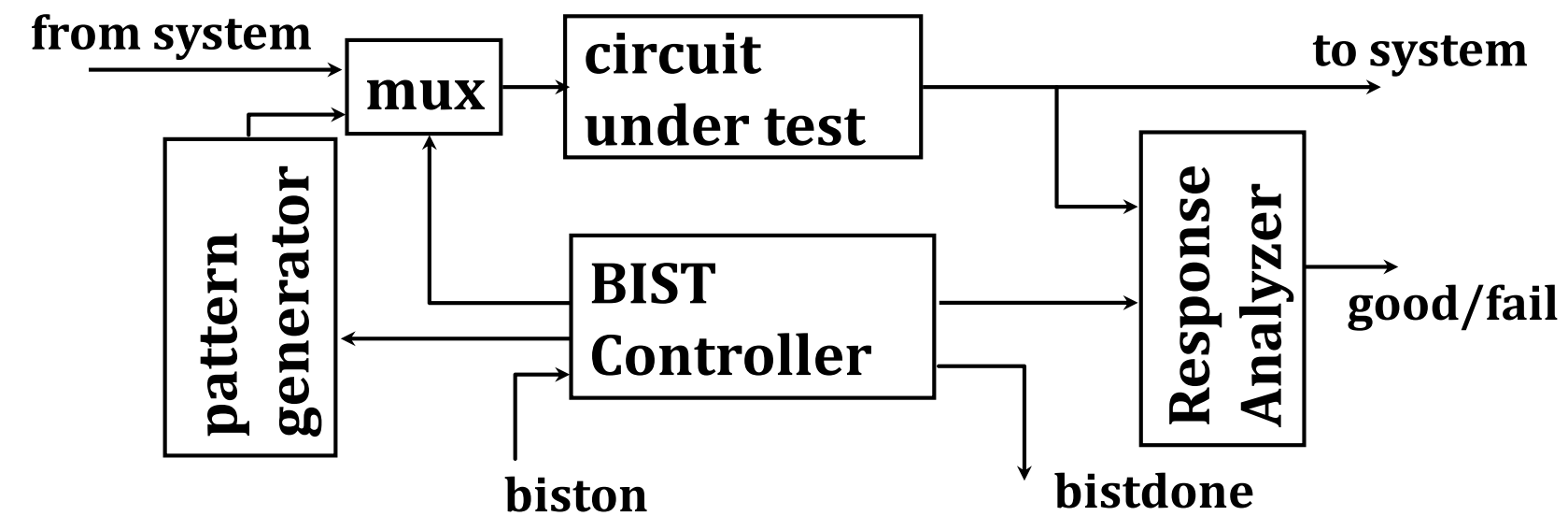- Places the job of device testing inside the device itself
- Generates its own stimulus and analyzes its own response





BASIC CONCEPTS



- We add extra hardware to the chip for test generation and response evaluation
 - Done on chip INSIDE
 - Additional hardware overload
- External control pins
- Input pin-Test control(TC)
- Output pin-Good/Bad






BUILT-IN-SELF TEST (BIST)



Built-in self-test lets blocks test themselves

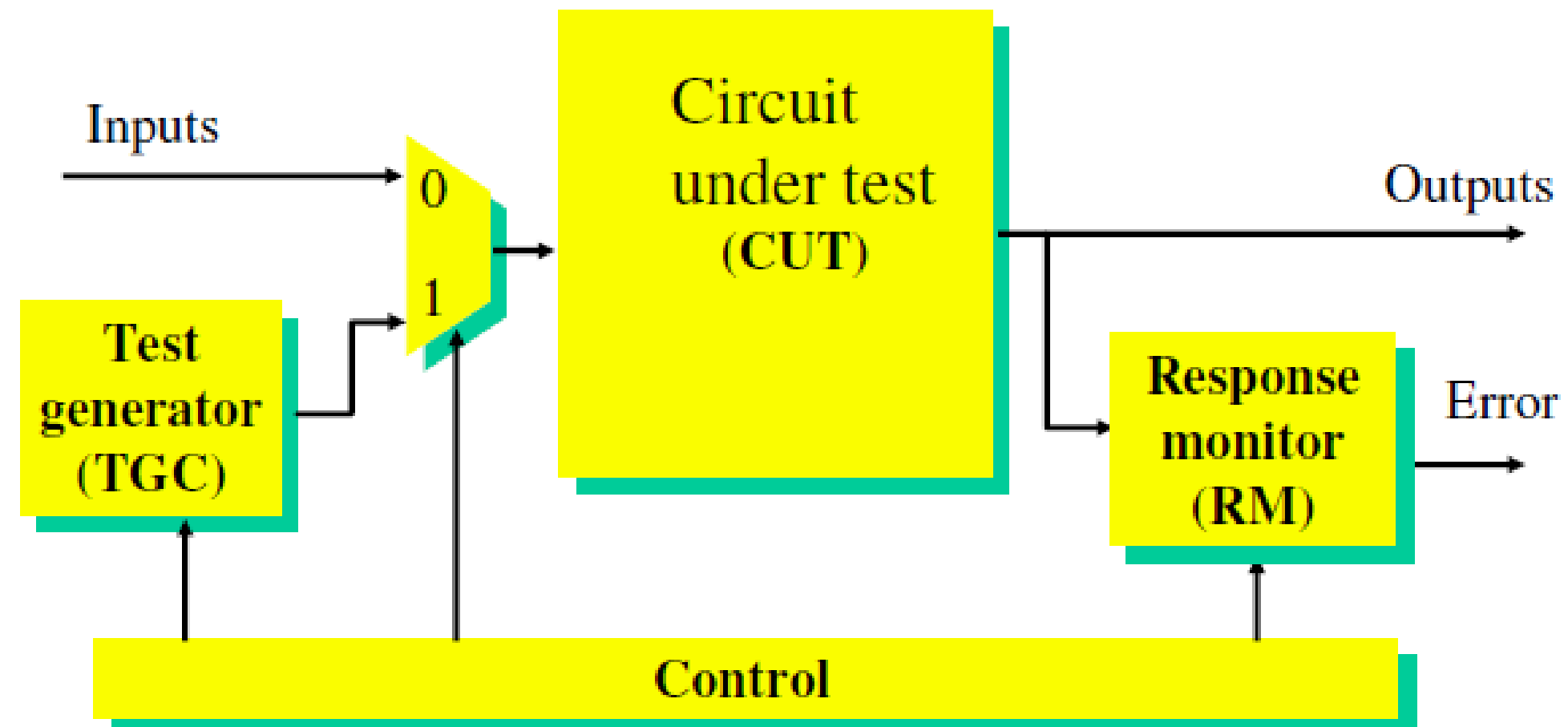- Generate pseudo-random inputs to comb. logic
- Combine outputs into a *syndrome*
- With high probability, block is fault-free if it produces






BUILT-IN-SELF TEST (BIST) ARCHITECTURE




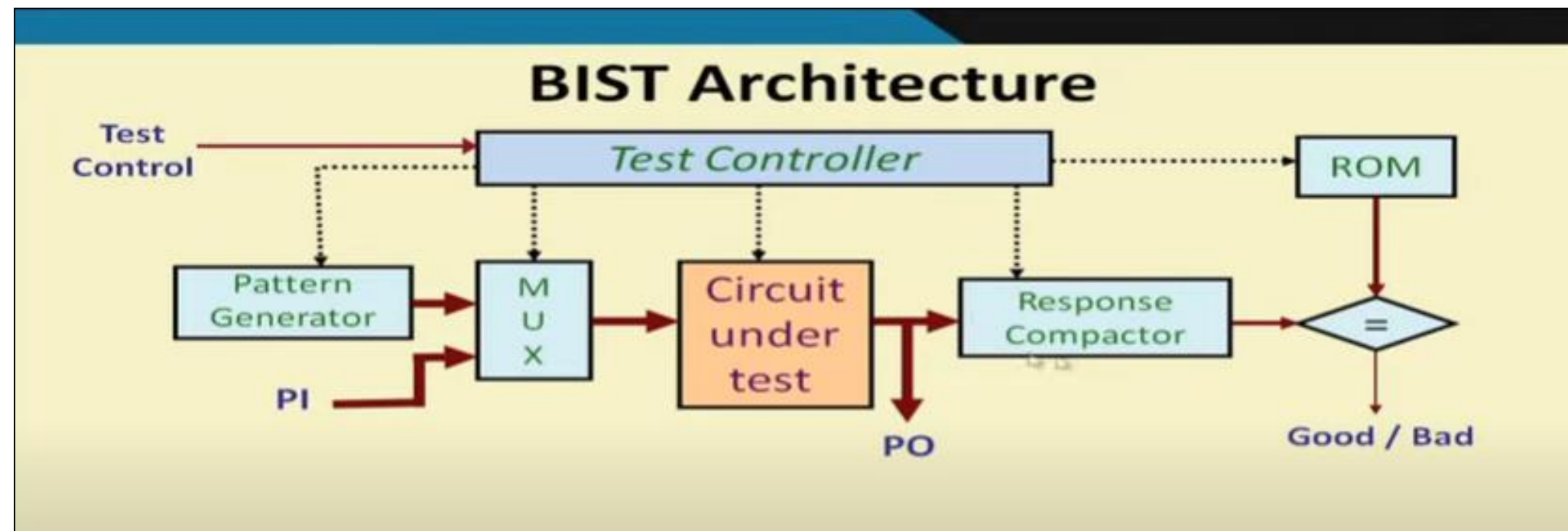- Two major tasks
 - Test pattern generation
 - Test result compaction
- Usually implemented by linear feedback shift register
- NETLIST -----Test Generation -----Test Vectors
- Error input----CUT-----Error output
- Automated Test Equipment ATE (Loaded Test Pattern) ---CUT----Output given to ATE





RANDOM NUMBER GENERATOR (RNG)

 


1. Generate “pseudo” random patterns
2. Period is $2^n - 1$
3. Pseudo Random pattern is an input test vectors
4. Fault coverage done by Fault simulation
 - Test length is large
 - much faster test generation
 - Continue until fault coverage 60-80% then switch to ATPG



SIGNATURE ANALYZER (SA)



Input sequence 10101111 (8 bits)

 

$$G(x) = 1 + x^2 + x^4 + x^5 + x^6 + x^7$$

$$P(x) = 1 + x^2 + x^4 + x^5$$

Time	Input stream	Register contents	Output stream
0	1 0 1 0 1 1 1 1	0 0 0 0 0	← Initial state
1	1 0 1 0 1 1 1	1 0 0 0 0	
.	.	.	
.	.	.	
5	1 0 1	0 1 1 1 1	
6	1 0	0 0 0 1 0	1
7	1	0 0 0 0 1	0 1
8		0 0 1 0 1	1 0 1
		⏟ Remainder	⏟ Quotient
		$R(x) = x^2 + x^4$	$1 + x^2$



SIGNATURE ANALYZER (SA) (CONT.)



- A LFSR performs polynomial division


$$\begin{array}{r} P(x): x^5 + x^4 + x^2 + 1 \\ \times Q(x): x^2 + 1 \\ \hline x^7 + x^6 + x^4 + x^2 + x^5 + x^4 + x^2 + 1 \\ = x^7 + x^6 + x^5 + 1 \end{array}$$

$$P(x)Q(x) + R(x) = x^7 + x^6 + x^5 + x^4 + x^2 + 1 = G(x)$$

- Probability of aliasing error = $1/2^n$ (n: # of FFs)




MEMORY BIST ARCHITECTURE

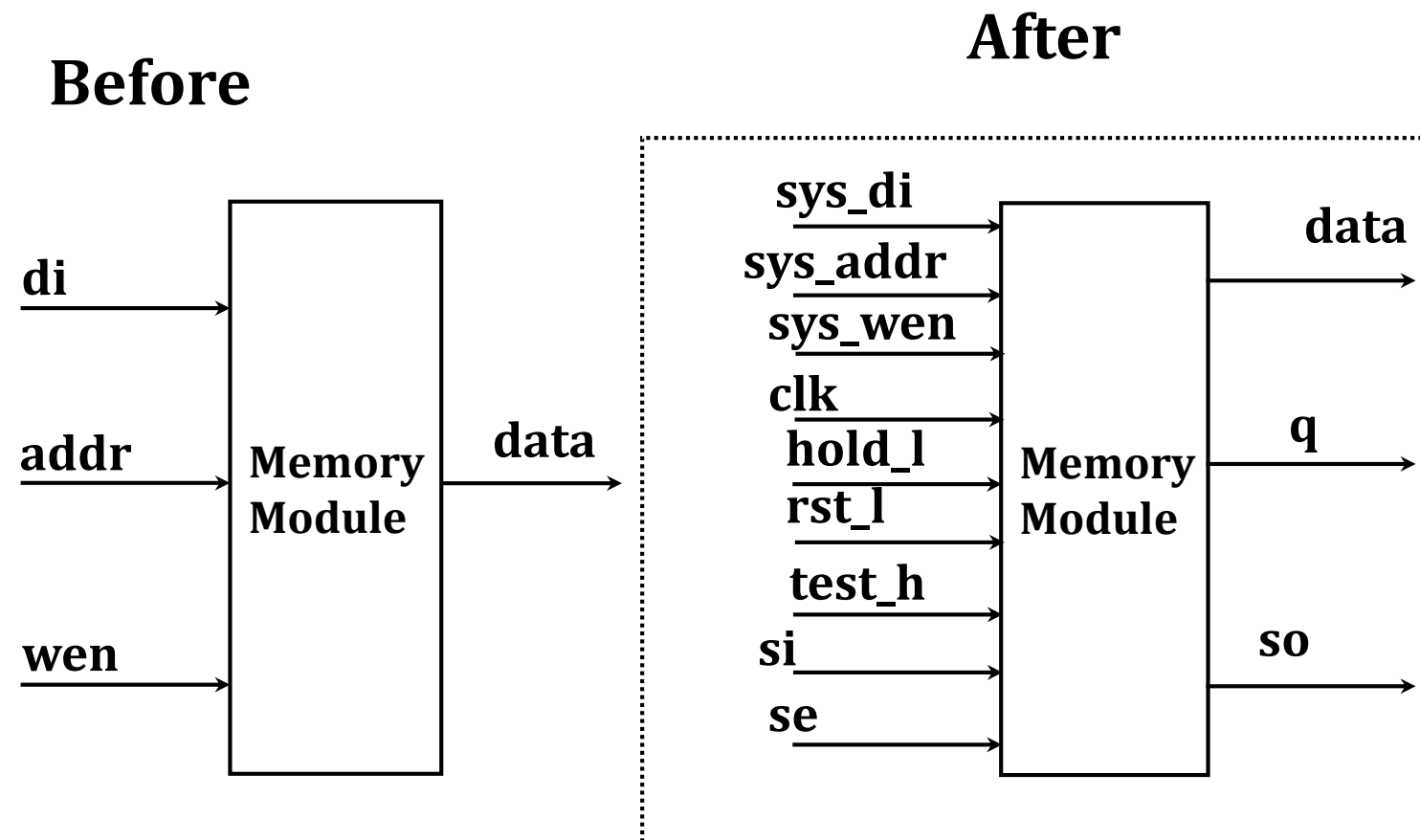




MEMORY BIST ARCHITECTURE (CONT.)

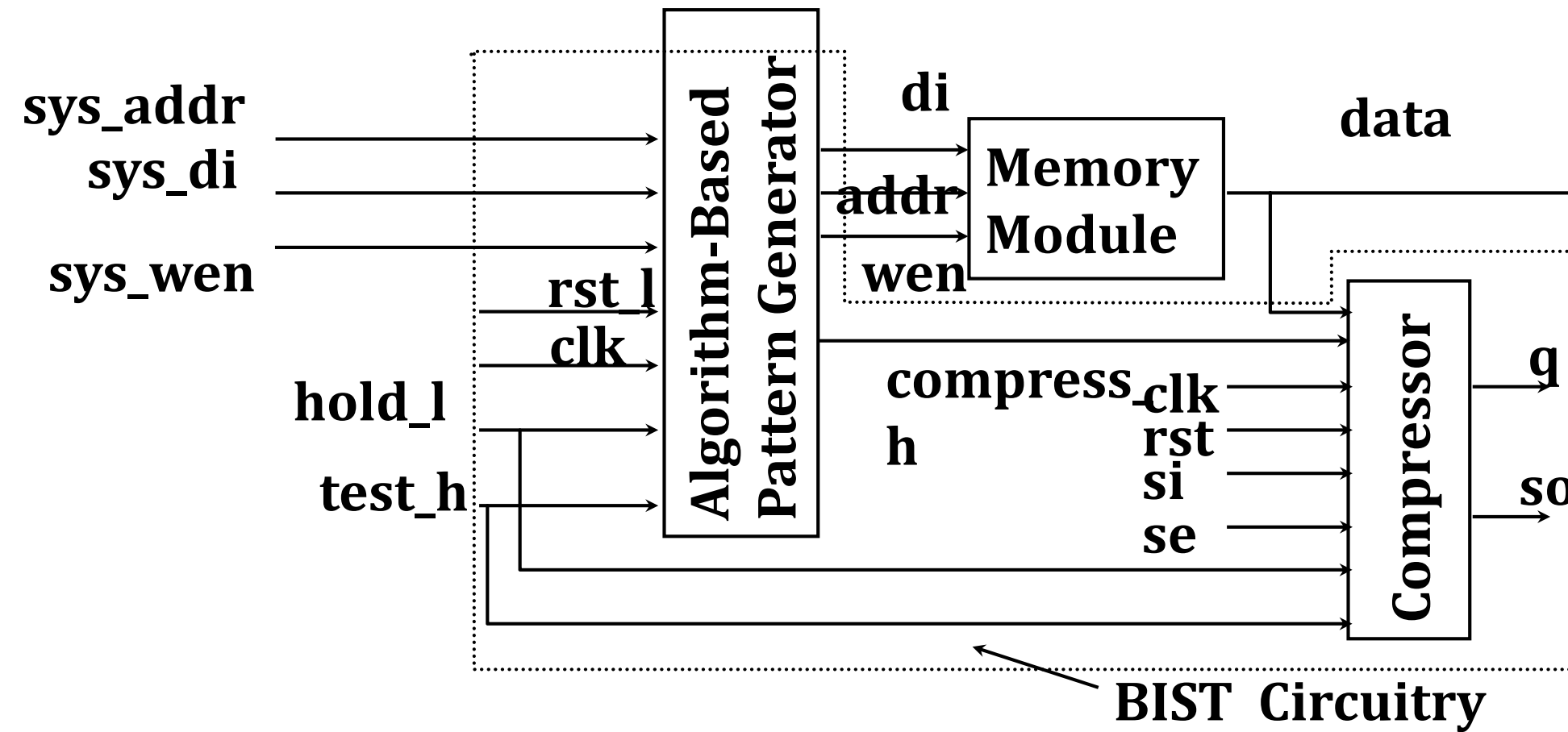



CPU TEST CONTROL ARCHITECTURE

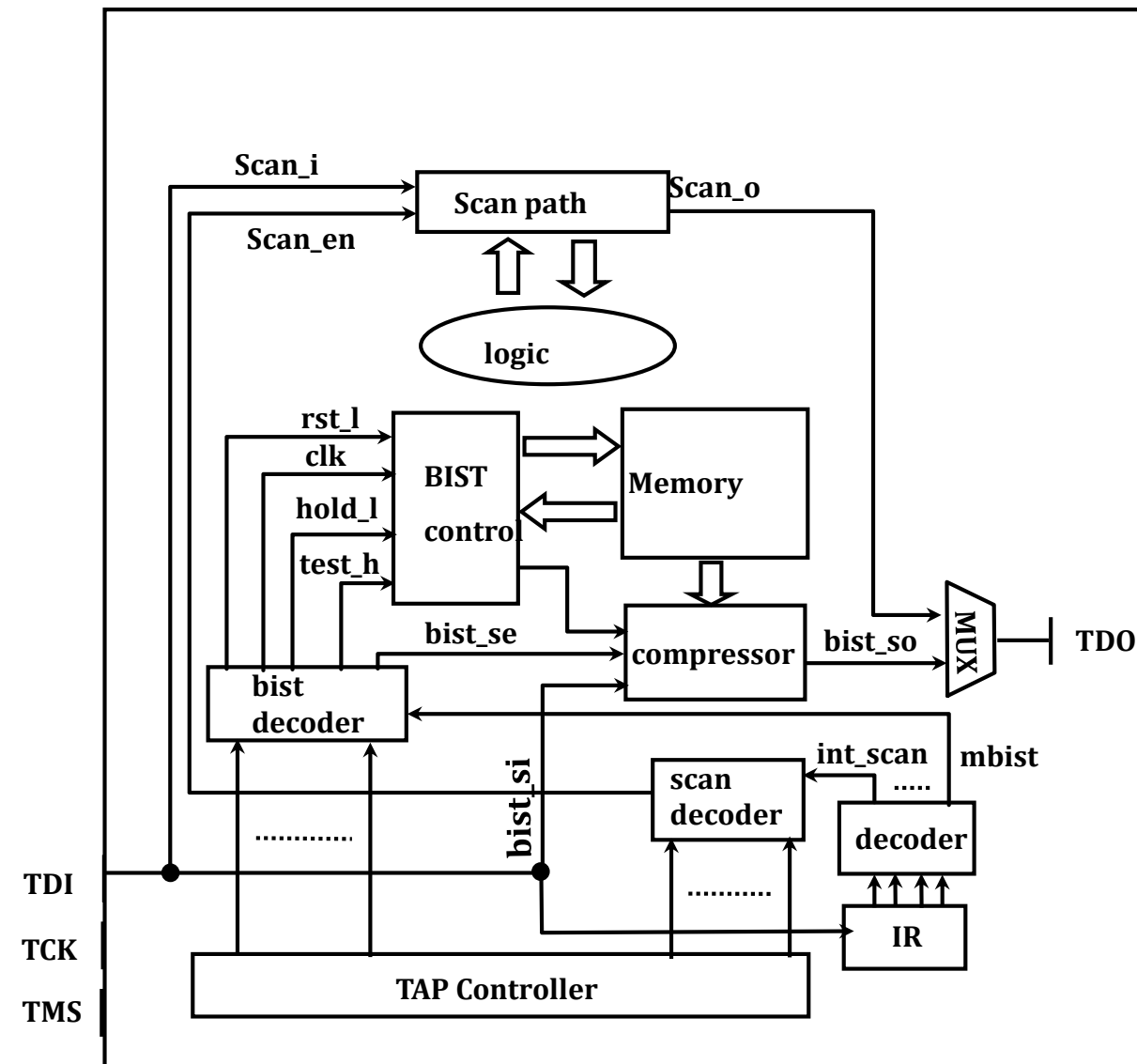



NEEDS OF BIST



- Field Test & Diagnosis (Software Test) - not needed expensive ATE
 - Low hardware fault coverage
 - Poor diagnostic resolution
 - Time consuming
- In Hardware – Lower system test effort & better diagnosis
 - Improve system maintenance & repair





TESTING METHODS



- A 32-bit adder --- ATPG
- A 32-bit counter --- Design for testability + ATPG
- A 32MB Cache memory --- BIST
- A 10^7 -transistor CPU --- All test techniques
- An SOC





ASSESSMENT



1. How can you make test generation?
2. How can you generate random number?
3. Why we use Signature Analyser in BIST?
4. List out the basic concepts of BIST
5. Draw the architecture of BIST.
6. Match all correctly

A 32-bit adder --- BIST

A 32-bit counter --- All test techniques

A 32MB Cache memory --- ATPG

A 10^7 -transistor CPU --- Design for testability +
ATPG





SUMMARY & THANK YOU