



Topic 2.8 : Multistage amplifiers-Cascade and Cascode amplifier

Multistage Amplifiers

Amplifier :-

- * Amplify a signal from a very weak source.
- * This is achieved by cascading number of amplifier stages known as multistage Amplifier.

Need for cascading:-


- * Amplification of a single stage amplifier is not sufficient so, we go for cascading amplifier.

Multistage Amplifier ✖ 2 Mark

- * Voltage gain & power gain from single stage small signal amplifier is not sufficient for practical applications.
- * Use more than one stage of amplifier to achieve necessary voltage & power gain. Such an amplifier is called multistage amplifier.
- * In multistage output of one stage is fed as input to the next stage.

Cascaded Amplifier ✖ 16 Mark

1. Two stage Cascaded Amplifier

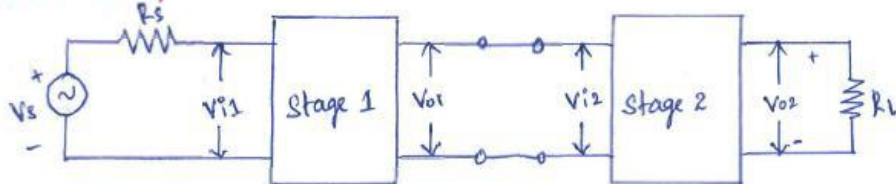



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech&B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU



* Output of the 1st stage is connected to the input of the 2nd stage.

* V_{i1} is the input of the 1st stage & V_{o2} is the output of the 2nd stage

* $\therefore \frac{V_{o2}}{V_{i1}}$ is the overall voltage gain of the 2nd stage amplifier & it can be given as


$$A_v = \frac{V_{o2}}{V_{i1}} = \frac{V_{o2}}{V_{i2}} \cdot \frac{V_{i2}}{V_{i1}} \quad \because V_{o1} = V_{i2}$$

$$= \frac{V_{o2}}{V_{i2}} \cdot \frac{V_{o1}}{V_{i1}}$$


$$A_v = A_{v2} \cdot A_{v1}$$

* So that we can say the voltage gain of multistage amplifier is the product of voltage gain of the individual stages.

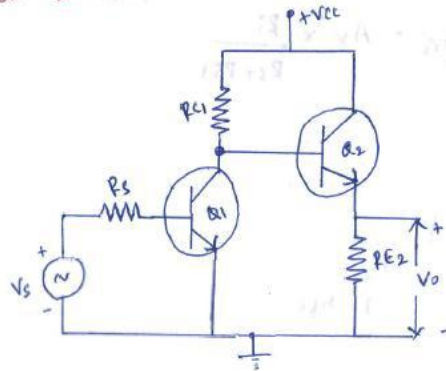Common Emitter - Common Collector Amplifier * 16 Mark.



Equivalent circuit:

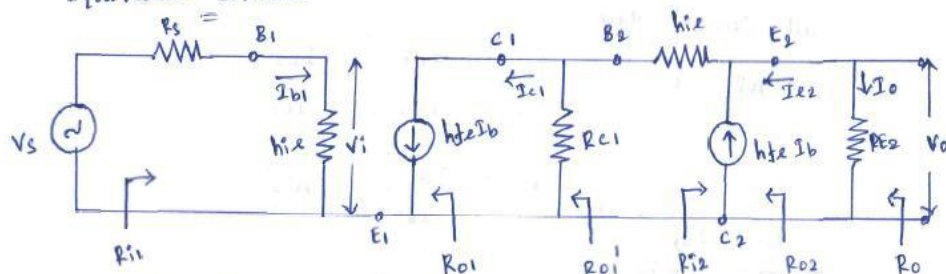

Analysis of 2nd stage (cc amplifier)

1. Current gain

$$A_{i2} = 1 + h_{fe}$$

2. Input Impedance

$$R_{i2} = h_{ie} + (1 + h_{fe}) R_{E2}$$

3. Voltage gain

$$A_{v2} = \frac{A_{i2} \times R_{L2}}{R_{i2}} = \frac{A_{i2} \times R_{E2}}{R_{i2}}$$

(b)



Analysis of 1st stage (CE amplifier)

1. Current gain

$$A_{i1} = -h_{fe}$$

3. Voltage gain

$$A_{v1} = \frac{A_{i1} \times R_{L1}}{R_{i1}}$$

2. Input Impedance

$$R_{i1} = h_{ie}$$


$$R_{L1} = R_{C1} \parallel R_{i2}$$

Overall Voltage gain

$$A_v = A_{v1} \times A_{v2}$$

Overall voltage gain (A_{Vs}) :-
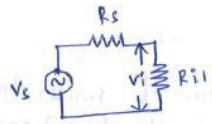
$$A_{Vs} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s}$$



$$V_i = V_s \times \frac{R_{i1}}{R_s + R_{i1}}$$

$$\therefore A_{Vs} = \frac{V_o}{V_i} \times \frac{V_s \times \frac{R_{i1}}{R_s + R_{i1}}}{V_s}$$

$$A_{Vs} = A_v \times \frac{R_{i1}}{R_s + R_{i1}}$$

Output Impedance

$$R_{o1} = \infty \rightarrow \text{for CE}$$

$$R_{o1}' = R_{o1} \parallel R_{C1}$$


$$R_{o2} = \frac{R_s + h_{ie}}{1 + h_{fe}} \Rightarrow \text{for CC} = \frac{R_{o1}' + h_{ie}}{1 + h_{fe}}$$

$$R_o = R_{o2} \parallel R_{E2}$$

Overall Current gain

$$A_i = \frac{I_o}{I_{b1}} = \frac{I_o}{I_{e2}} \times \frac{I_{e2}}{I_{b2}} \times \frac{I_{b2}}{I_{c1}} \times \frac{I_{c1}}{I_{b1}}$$
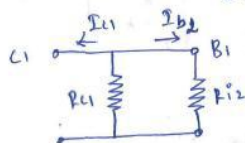
$$\frac{I_o}{I_{e2}} = -1 ; \frac{I_{e2}}{I_{b2}} = -A_{i2}$$



$$\frac{I_{b2}}{I_{c1}} = \frac{-R_{C1}}{R_{i2} + R_{C1}} ; \frac{I_{c1}}{I_{b1}} = A_{i1}$$

$$A_i = -1 \times (-A_{i2}) \times \left(\frac{-R_{C1}}{R_{i2} + R_{C1}} \right) \times A_{i1}$$

$$A_i = -A_{i1} A_{i2} \left(\frac{R_{C1}}{R_{i2} + R_{C1}} \right)$$


(62)



Two stage RC coupled CE-CB cascode Amplifier .X.16Mark.

* It consist of a CE amplifier stage in series with a CB amplifier.

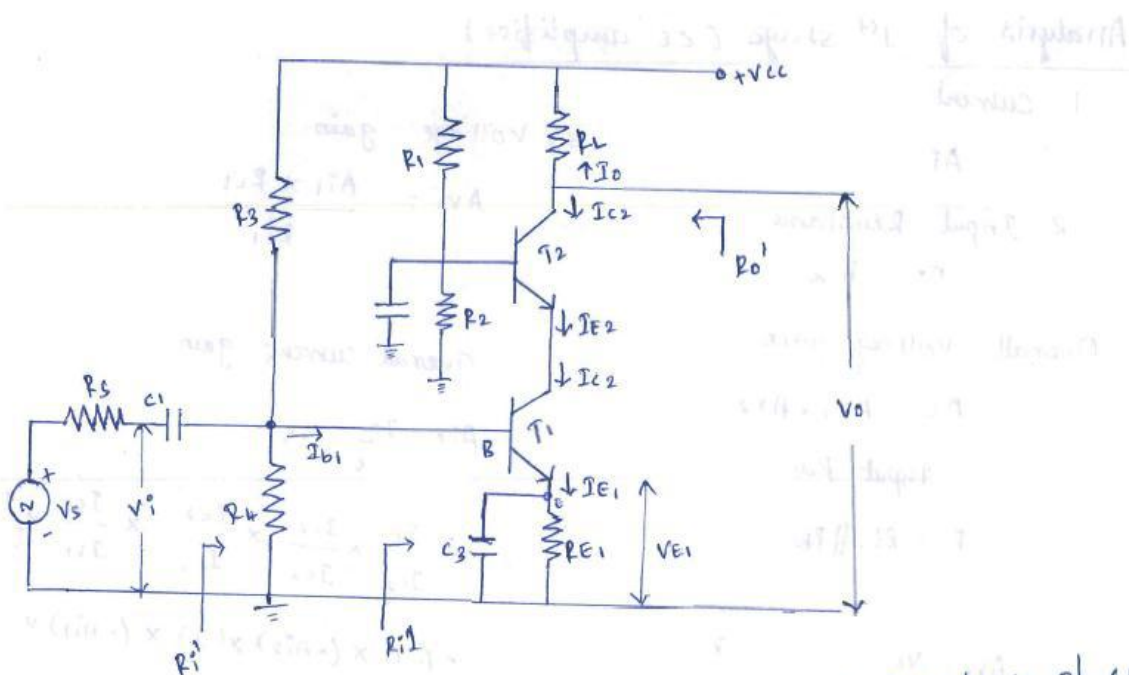* Transistor T_1 + its associated components operate as a CE amplifier stage, while the circuit of T_2 functions as a CB output stage.



* The cascode amplifier gives the high input impedance of CE amplifier, as well as the good voltage gain & high frequency performance of CB circuit.

* The I_{E1} for T_1 is set by V_{E1} & R_{E1} .

* I_{C1} approximately equals I_{E1} & I_{E2} is same as I_{C1} .

* $\therefore I_{C2}$ approximately equals I_{E1} .

* This current remains constant regardless of the level of V_{B2} , as long as V_{CE1} remains large enough for current operation of T_1 .