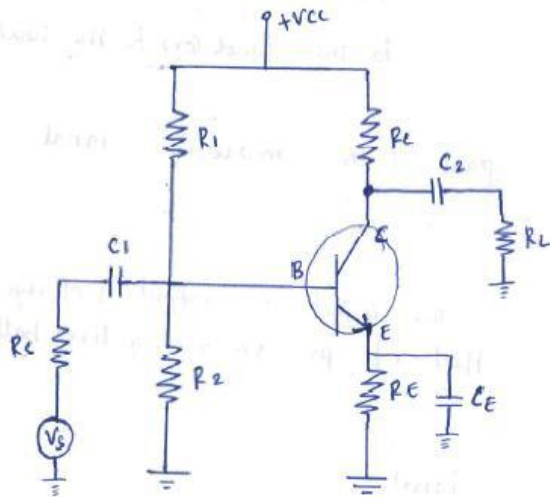




## Topic 2.4 : Single stage amplifiers-Common Emitter amplifier

### Common Emitter Amplifier



\* Amplifier is used to increase the signal level i.e. the amplifier is used to get a large signal output from a small signal input.

\* For Ex: We give sin wave as input. We get the same sin wave output. The frequency is not change but Amplitude increased.



\* To make the transistor as an amplifier, it's to be biased to operate in active region i.e. the Base-Emitter junction is forward bias and Base-collector junction is Reverse biased.

#### 1. Biasing circuit

\* Resistance  $R_1$ ,  $R_2$  &  $R_E$  forms the voltage divider bias circuit for the CE amplifier.

\* It sets the proper operating point for the CE amplifier.



# SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech&B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU



## 2. Input Capacitor $C_1$

- \* This capacitor couples the signal to the base of the transistor.
- \* It blocks any dc component present in the signal & passes only ac signals for amplification.
- \* Because of this biasing conditions are maintained constant.

## 3. Emitter Bypass Capacitor $C_E$

- \*  $C_E$  is connected in parallel with the  $R_E$  to provide a low resistance path to the amplified ac signal.
- \* If it's not inserted, the amplified ac signal passing through  $R_E$  will cause a voltage drop across it.
- \* This will reduce the output voltage, reducing the gain of the amplifier.

## 4. Output Coupling Capacitor $C_2$

- \*  $C_2$  couples the output of the amplifier to the load (or) to the next stage of the amplifier.
- \* It blocks dc & passes only ac part of the amplifier signal.

## 5. Phase Reversal


- \* The phase relationship between the input & output voltages can be determined by considering the effect of positive & negative half cycle separately.

Consider positive half cycle of input signal :

- \* In which terminal 'A' is positive w.r. to 'B'.
- \* Due to this 2 voltages, ac & dc will be adding each other, increased forward bias on the  $V_E$  Base-Emitter junction.
- \* This will increase the base current  $I_B$ .
- \* The  $I_C$  is  $\beta$  times the  $I_B$  i.e.  $I_C = \beta I_B$  hence the  $I_C$  will also increase.
- \* This will increase the voltage drop across  $R_C$ .
- \* Since  $V_E = V_{CC} - I_C R_C$ , the increase in  $I_C$  results in a drop in  $V_E$ , as  $V_{CC}$  is constant.



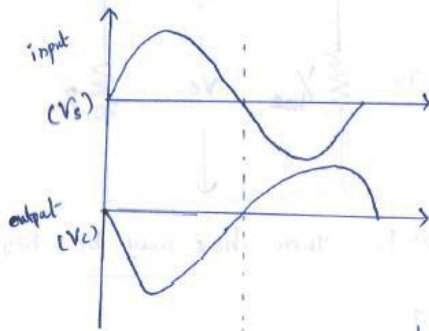\* Thus, as  $V_i$  increases in a positive direction,  $V_o$  goes in a negative direction & we get negative half cycle of output voltage for positive half cycle of the input.



Consider negative half cycle of input signal:

- \* In which terminal 'A' is negative w.r. to 'B'
- \* Due to this 2 voltages  $V_{be}$  &  $V_{dc}$  will be opposing to each other, decreased forward bias on the Base-Emitter junction.
- \* This will decrease the base current  $I_b$ .
- \* The  $I_c$  decreases & the voltage drop across  $R_c$  decreases, increase the output voltage.
- \* Thus as we get positive half cycle at the output for the negative half cycle of the input.
- \*  $\therefore$  We can say that there is a phase shift of  $180^\circ$  between input & output voltages for a CE amplifier.

