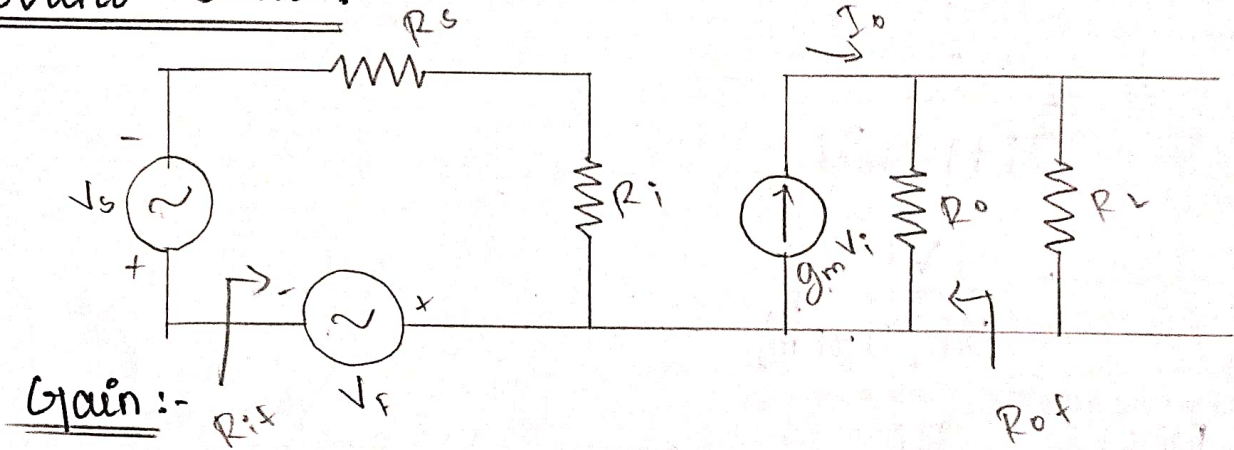


Current Series:



Gain :-

$$g_m = \frac{I_o}{V_s} = \frac{I_o}{V_i^o} \quad [ \because V_s = V_i ]$$

$$g_{mf} = \frac{I_o}{V_s} = \frac{I_o}{V_i^o + V_f} = \frac{G_m V_i^o}{V_i^o + \beta I_o} \quad ( I_o = G_m V_i^o )$$

$V_f = \beta I_o$

$$= \frac{G_m V_i^o}{V_i^o + \beta G_m V_i^o} = \frac{G_m V_i^o}{V_i^o [1 + \beta G_m]}$$

$$G_{mf} = \frac{G_m}{(1 + \beta G_m)}$$

Input Resistance :

$$R_i^o = \frac{V_s}{I_i^o}$$

$$R_i^o = \frac{V_i^o}{I_i^o} \quad [V_s = V_i^o]$$

$$R_{if}^o = \frac{V_s}{I_i^o} = \frac{V_i^o + V_F}{I_i^o} \quad [ \because V_s = V_i^o + V_F ]$$


$$= \frac{V_i^o + \beta I_o}{I_i^o} \quad [V_F = \beta I_o]$$

$$R_{if}^o = \frac{V_i^o + \beta G_m V_i^o}{I_i^o} \quad [I_o = G_m V_i^o]$$

$$R_{if}^o = \frac{V_i^o [1 + \beta G_m]}{I_i^o}$$

$$R_{if}^o = R_i^o (1 + \beta G_m)$$

Output resistance :

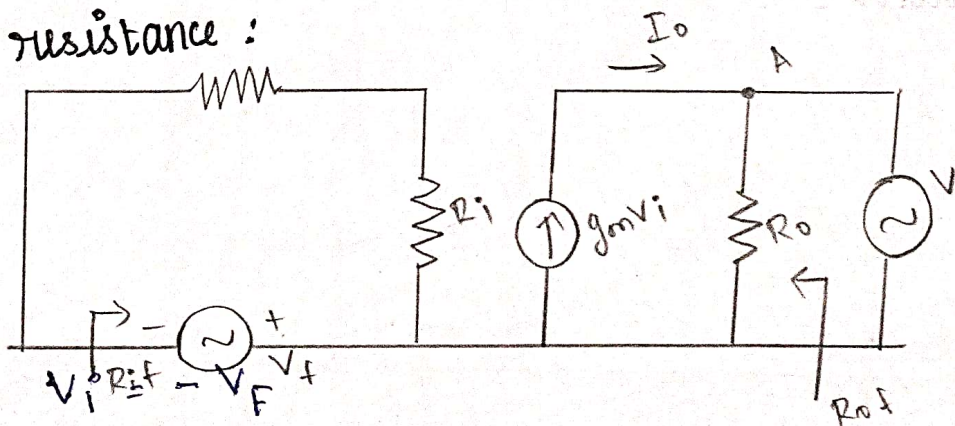

$$V_i^o = -\beta I_o \quad \& \quad V_F = \beta I_o$$

here,

$$I = I_o$$

$$\therefore V_i^o = \beta I$$

From o/p ckt, apply KCL,

$$\frac{V}{R_o} = I + G_m V_i$$

$$I = -G_m V_i + \frac{V}{R_o}$$

$$= -G_m \beta I + \frac{V}{R_o}$$

$$I + G_m \beta I = \frac{V}{R_o}$$

$$I [1 + G_m \beta] = \frac{V}{R_o}$$

$$R_o = \frac{V}{I} [1 + G_m \beta]$$

$$\boxed{R_{of} = R_o}$$