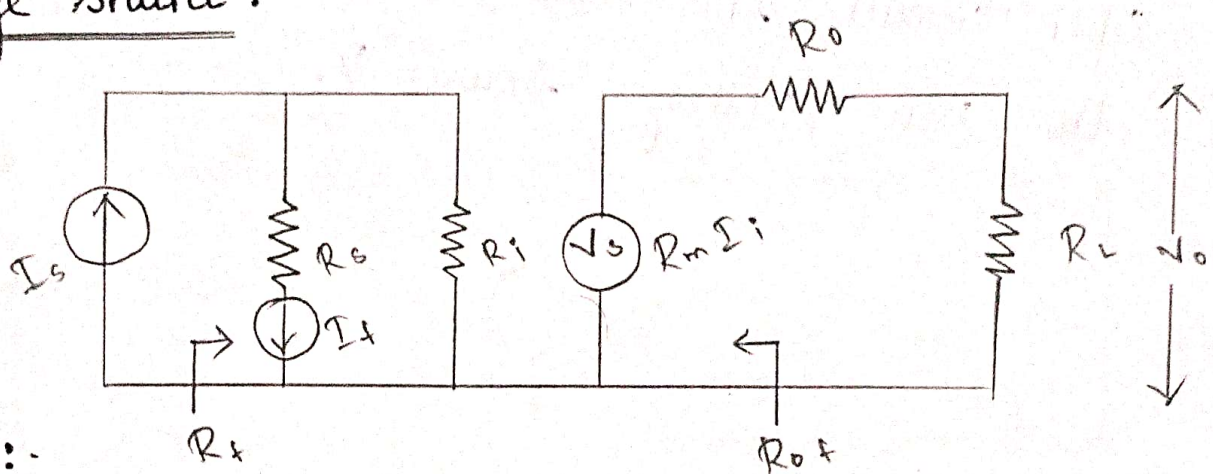


Voltage shunt :



Gain:-

$$R_m = \frac{V_o}{I_s} = \frac{V_o}{I_i}$$

$$R_{mf} = \frac{V_o}{I_i + I_f}$$

$$= \frac{V_o}{I_i + \beta I_o}$$

$$= \frac{R_m I_i}{I_i + \beta R_m I_i} \quad [I_f = \beta R_m I_i]$$

$$= \frac{R_m I_i}{I_i [1 + \beta R_m]}$$

$$\boxed{R_{mf} = \frac{R_m}{1 + \beta R_m}}$$

Input Resistance:

$$R_i = \frac{V_i}{I_i}$$

$$R_i = \frac{V_i}{I_i}$$

$$= \frac{V_i}{I_s}$$


$$R_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_i + I_f}$$

$$= \frac{V_i}{I_i + \beta R_m I_i}$$

$$= \frac{V_i}{I_i [1 + \beta R_m]}$$

$$R_{if} = \frac{R_i}{1 + \beta R_m}$$

Output Resistance:

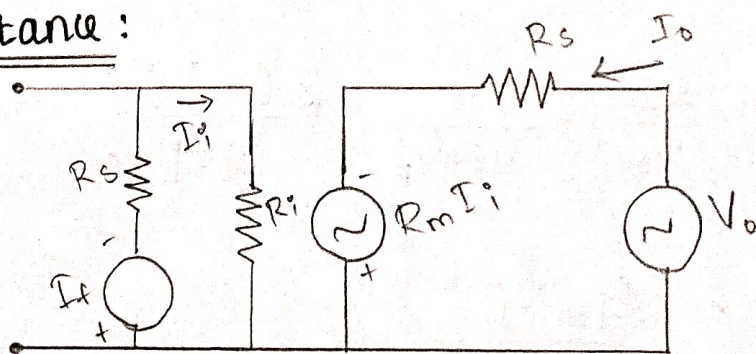

$$I_s = 0, I_i = -I_f \quad \{ I_s = I_i + I_f \}$$

apply KVL at output node:

$$\begin{aligned} \frac{V_o}{R_o} &= I_o R_o + R_m I_i \\ &= I_o R_o + R_m (-I_f) \end{aligned}$$

$$V_o = I_o R_o - R_m I_f \quad \{ I_f = \beta V_o \}$$

$$= I_o R_o - R_m \beta V_o$$

$$I_o R_o = V_o + R_m \beta V_o$$

$$= V_o + [1 + R_m \beta] V_o$$

$$R_o f = \frac{V_o [1 + R_m \beta]}{I_o}$$

$$\boxed{R_o f = R_o}$$