



**SNS COLLEGE OF TECHNOLOGY**

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



***23EET202 / DIGITAL ELECTRONICS AND  
INTEGRATED CIRCUITS  
II YEAR / III SEMESTER***

***UNIT-II: DESIGN OF COMBINATIONAL AND  
SEQUENTIAL CIRCUITS***

***FLIP FLOPS – SR, D***

Dr.R.Senthil Kumar



# *TOPIC OUTLINE*

Memory devices

RS Flip Flop

D Flip Flop

IC Devices

Recap






# RS FLIP FLOP

 
## RS Flip Flop

- The RS flip flop is the basic memory element with **clock input** as enable point (**Clocked RS Latch**)
- Two input signals, S - set and R - signal.
- E - clock signal acting as enable.





# RS Flip Flop – Circuit, Truth table

 

$S$	$R$	$Q$	$Q'$
0	0	1	0
0	1	0	1
1	0	1	0
1	1	?	?





# RS Flip-Flop - Characteristics table



$C$	$S$	$R$	$Q(t)$	$Q(t+1)$	
0	X	X	0	0	No change
0	X	X	1	1	
1	0	0	0	0	No change
1	0	0	1	1	
1	0	1	0	0	Reset
1	0	1	1	0	
1	1	0	0	1	Set
1	1	0	1	1	
1	1	1	0	?	Forbidden
1	1	1	1	?	



# RS Latch / RS Flip Flop

  

Latch

  


Flip-flop



# D FLIP FLOP

 
## D Flip flop

- The D stands for “Data” or “Delay” Flip flop
- It has one input signal, **D which is set when it is “1” and reset when it is “0”**
- The demerit of SR flip flop is forbidden value, ie the input - S & R is ‘1’. It is over comed here.





 
# D Flip-Flop: Circuit, block, truth table



Inputs		Outputs	
CK	D	Q	$\bar{Q}$
0	X	No change	
1	0	0	1
1	1	1	0

 





# D Flip-Flop: Ch. table

$C$	$D$	$Q(t)$	$Q(t+1)$
0	X	0	0
0	X	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

No change

Reset

Set (Data)



# LATCH / FLIP-FLOP DEVICES

Device	# of Elements	Description
74LS73A	2	Negative-edge triggered JK flip-flop with clear
7474	2	Positive-edge triggered D flip-flop with preset and clear
74LS75	4	D Latch with enable
7476	2	Pulse-edge triggered JK flip-flop with preset and clear
74111	2	Master-slave JK flip-flop with preset, clear, and data lock out
74116	2	4-bit hazard-free D latch with clear and dual enable
74175	4	Positive-edge triggered D flip-flop with clear
74273	8	Positive-edge triggered D flip-flop with clear
74276	4	Negative-edge triggered JK flip-flop with preset and clear
74279	4	SR latch with active-low inputs



# SUMMARIZE



**...A CASE STUDY &  
THANK YOU**