



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



23EET202 / DIGITAL ELECTRONICS AND INTEGRATED CIRCUITS II YEAR / III SEMESTER

UNIT-II: DESIGN OF COMBINATIONAL AND SEQUENTIAL CIRCUITS

FLIP FLOPS – JK,T



TOPIC OUTLINE

JK Flip Flop

T Flip Flop

Triggering pulses


Recap





JK FLIP FLOP

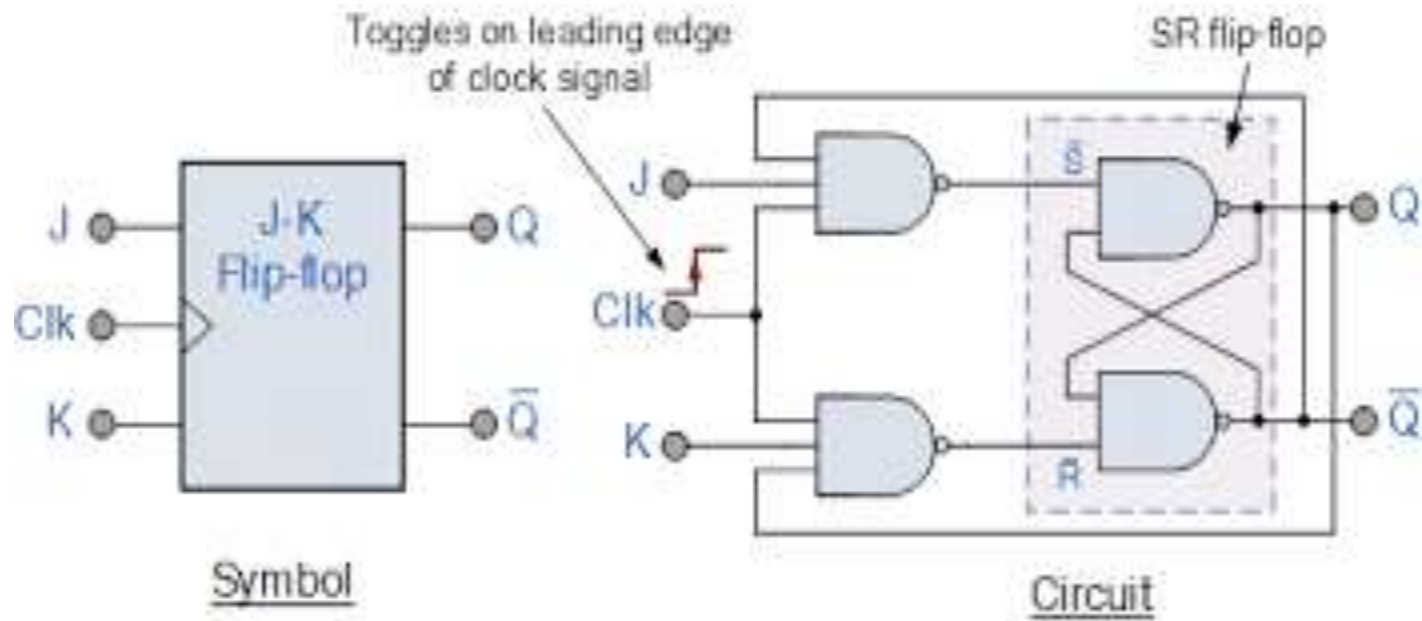
- The JK flip flop consist of two RS flip flop
- Two input signals, J - set and K - reset
- $SR = 1$, **forbidden** is over come with **next change**





JK Ch. Table and equation

J	K	$Q(n)$	$Q(n+1)$	
0	0	0	0	Hold
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	1	Toggle
1	1	1	0	

 

Ch. equation:
 $Q^+ = K'Q + JQ'$




T (TOGGLE) FLIP-FLOP

T	$Q(n)$	$Q(n+1)$
0	0	0
0	1	1
1	0	1
1	1	0

Hold

Toggle

 


$$\text{Ch. Eqn: } Q^+ = TQ' + T'Q$$



MASTER SLAVE FLIP-FLOPS


A *master slave flip-flop* consists of two latches and an inverter.

Master-slave RS flip-flop

 



Master-Slave JK Flip-Flops

 




TRIGGERING PULSES

Positive edge-triggered RS flip-flop timing diagram.

 
(The opposite is negative edge triggered)





TRIGGERING PULSES

 Positive edge-triggered JK flip-flop timing diagram





Edge / Level-Triggered Timing

Type	When inputs are sampled	When outputs are valid
Unclocked latch	Always	Propagation delay from input change
Level-sensitive latch	Clock high	Propagation delay from input change
Positive-edge latch	Clock low-to-high transition	Propagation delay from rising edge of clock
Negative-edge latch	Clock high-to-low transition	Propagation delay from falling edge of clock
Master/slave flip-flop	Clock high-to-low transition	Propagation delay from falling edge of clock



SUMMARIZE



...THANK YOU