



# SNS COLLEGE OF TECHNOLOGY

Coimbatore-35  
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

### 19ECB231 – DIGITAL ELECTRONICS

II YEAR/ III SEMESTER

UNIT 2 – COMBINATIONAL CIRCUITS


TOPIC - HALF ADDER & FULL ADDER


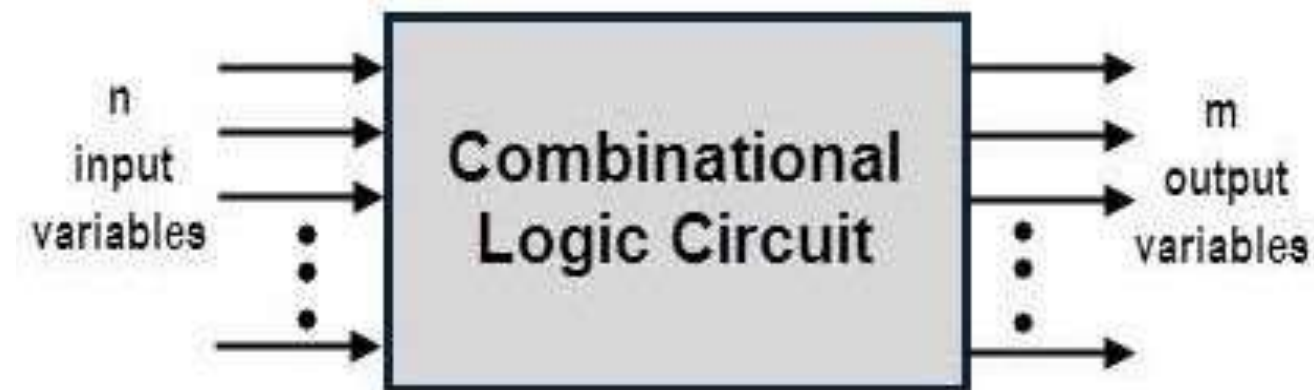
## WHAT IS COMBINATIONAL CIRCUIT?



- Output is function of input only  
i.e. no feedback



Combinational Logic Circuits are memoryless digital logic circuits whose output at any instant in time depends only on the combination of its inputs.



# HALF ADDER



## Half Adder


Adds 1-bit plus 1-bit

Produces Sum and Carry

$$\text{SUM } S = A.\bar{B} + \bar{A}.B$$

$$\text{CARRY } C = A.B$$

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

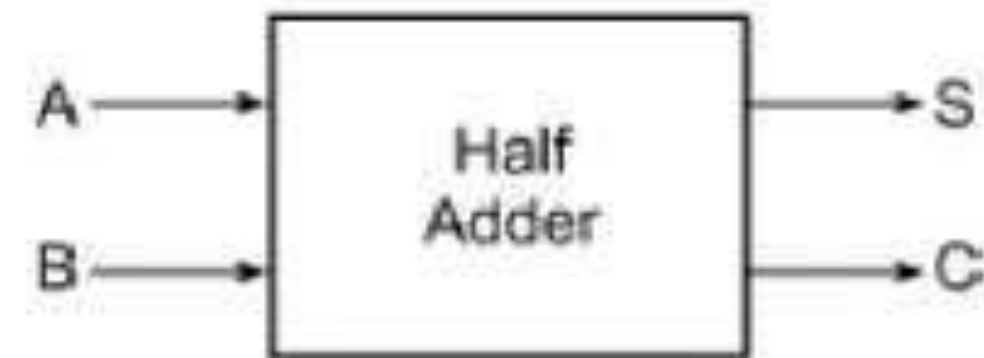



# HALF ADDER



For Carry

A \ B	0	1
0	0	0
1	0	1

$$\text{Carry} = AB$$


For Sum

A \ B	0	1
0	0	1
1	1	0

$$\begin{aligned}\text{Sum} &= A\bar{B} + \bar{A}B \\ &= A \oplus B\end{aligned}$$




# HALF ADDER

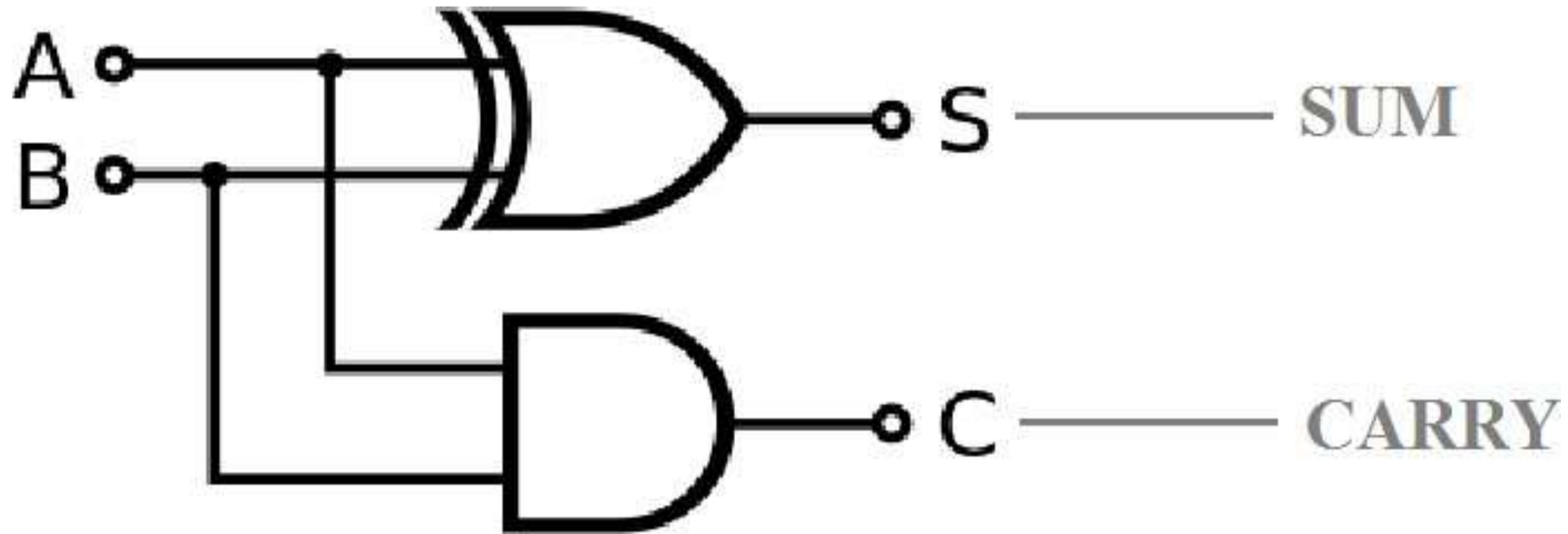



# FULL ADDER

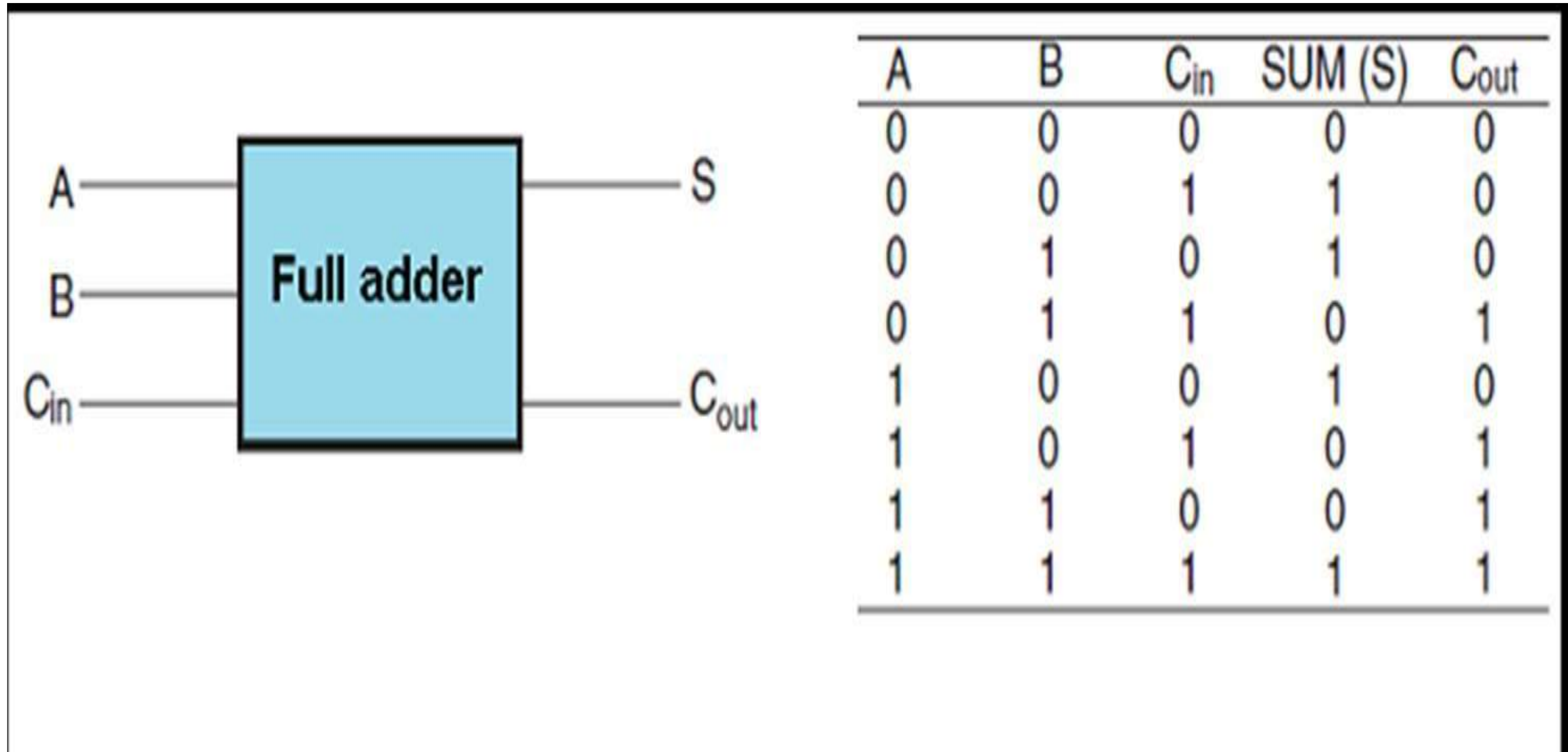



# FULL ADDER

**For Carry ( $C_{out}$ )**

$A \backslash BC_{in}$	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C_{out} = AB + AC_{in} + BC_{in}$$



**For Sum**

$A \backslash BC_{in}$	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$Sum = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$



# LOGICAL DIAGRAM

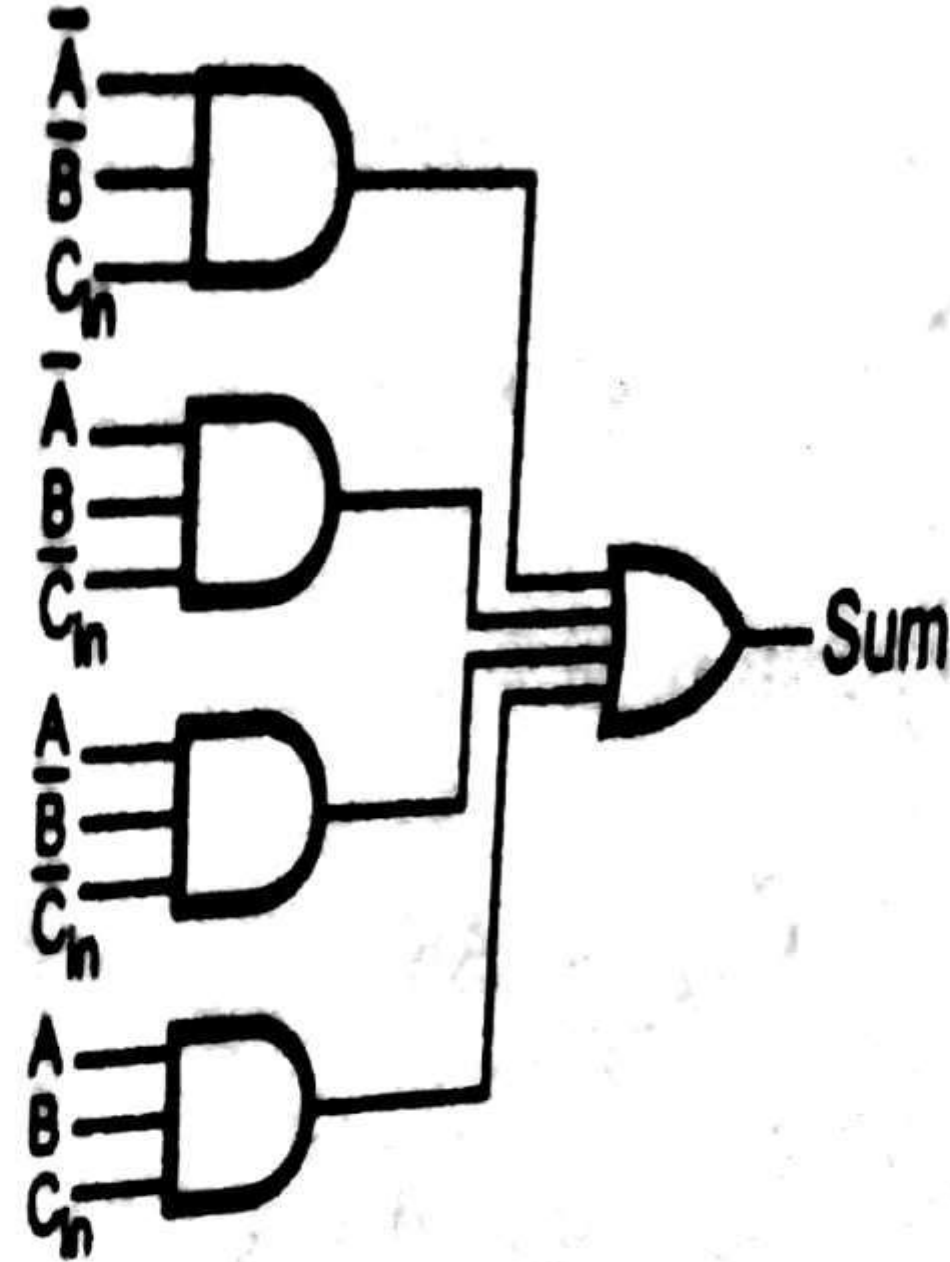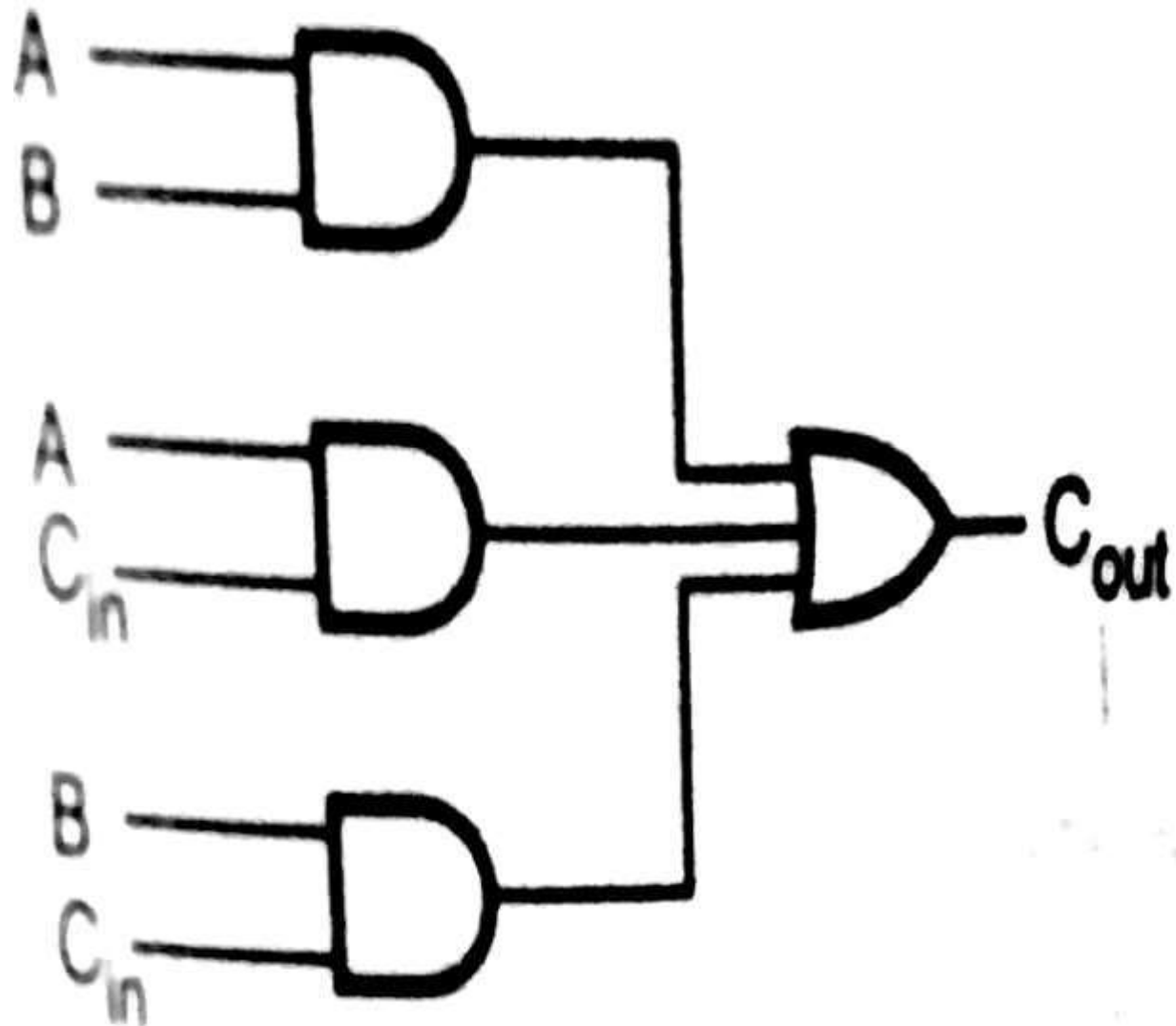






## FULL ADDER

$$\begin{aligned}\text{Sum} &= \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + ABC_{in} \\ &= C_{in} (\bar{A} \bar{B} + AB) + \bar{C}_{in} (\bar{A} B + A \bar{B}) \\ &= C_{in} (A \cdot B) + \bar{C}_{in} (A \oplus B) \\ &= C_{in} (\overline{A \oplus B}) + \bar{C}_{in} (A \oplus B) \\ &= C_{in} \oplus (A \oplus B)\end{aligned}$$




# LOGICAL DIAGRAM

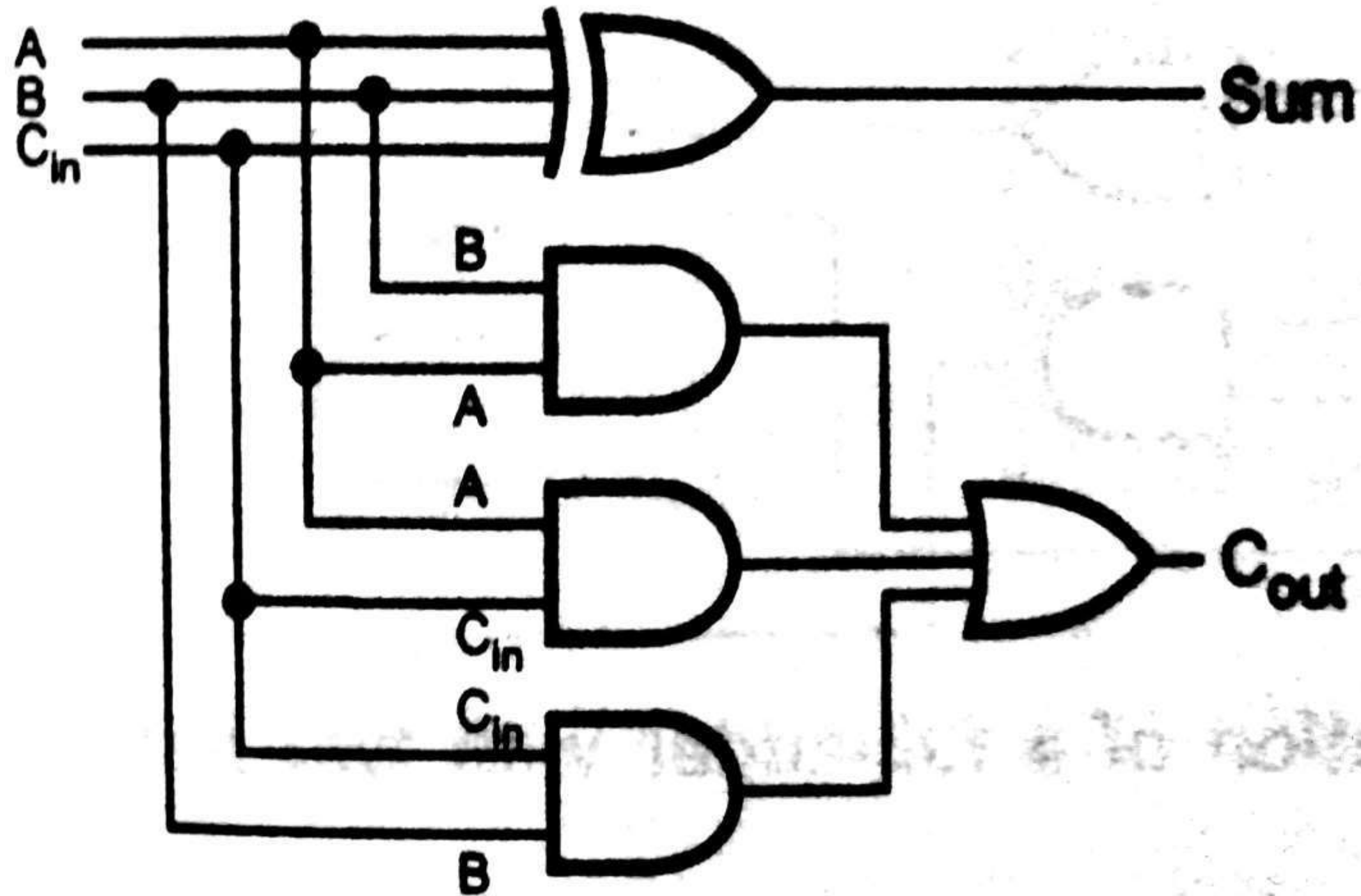



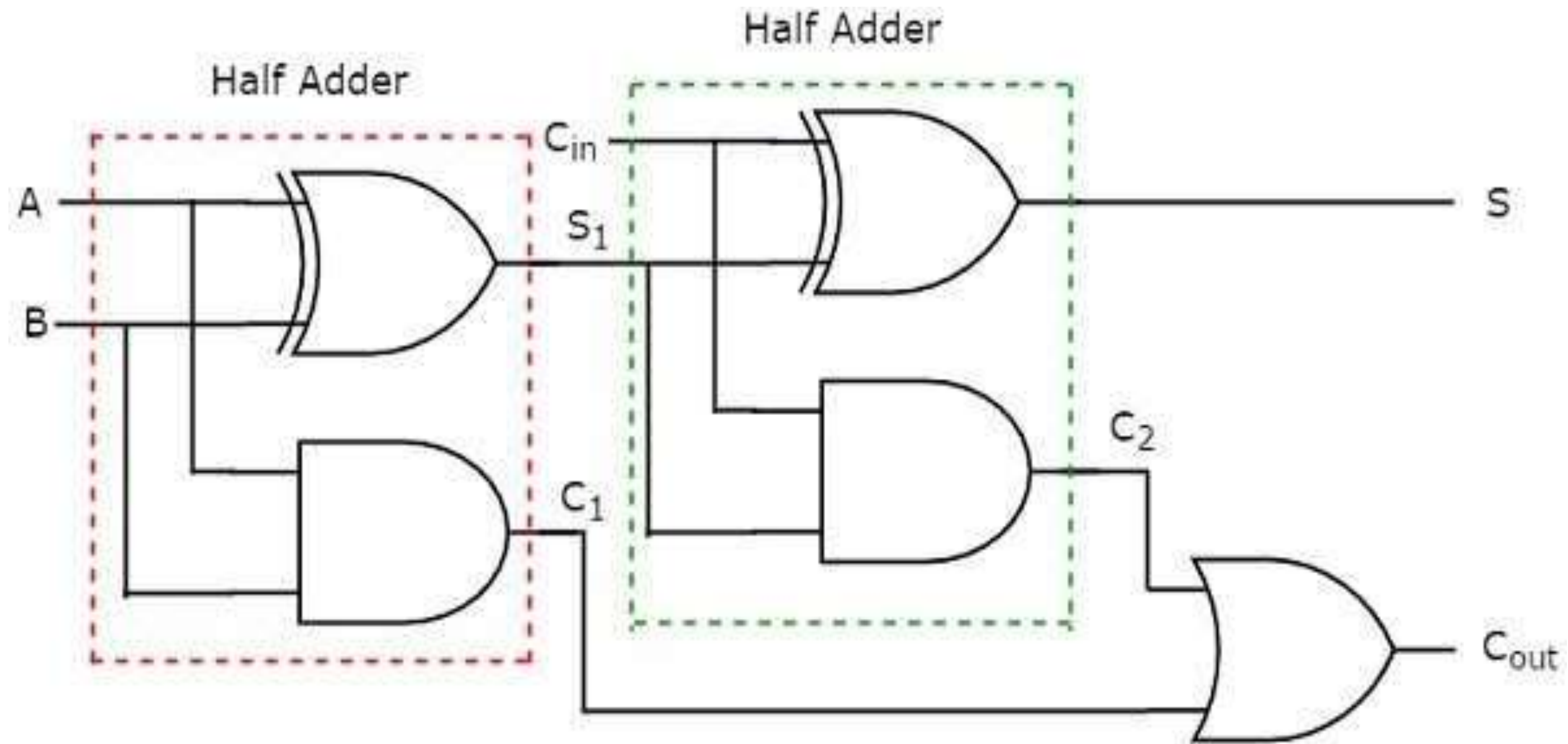
# IMPLEMENTATION OF FULL ADDER USING TWO HALF ADDERS





# APPLICATIONS OF COMBINATIONAL CIRCUITS

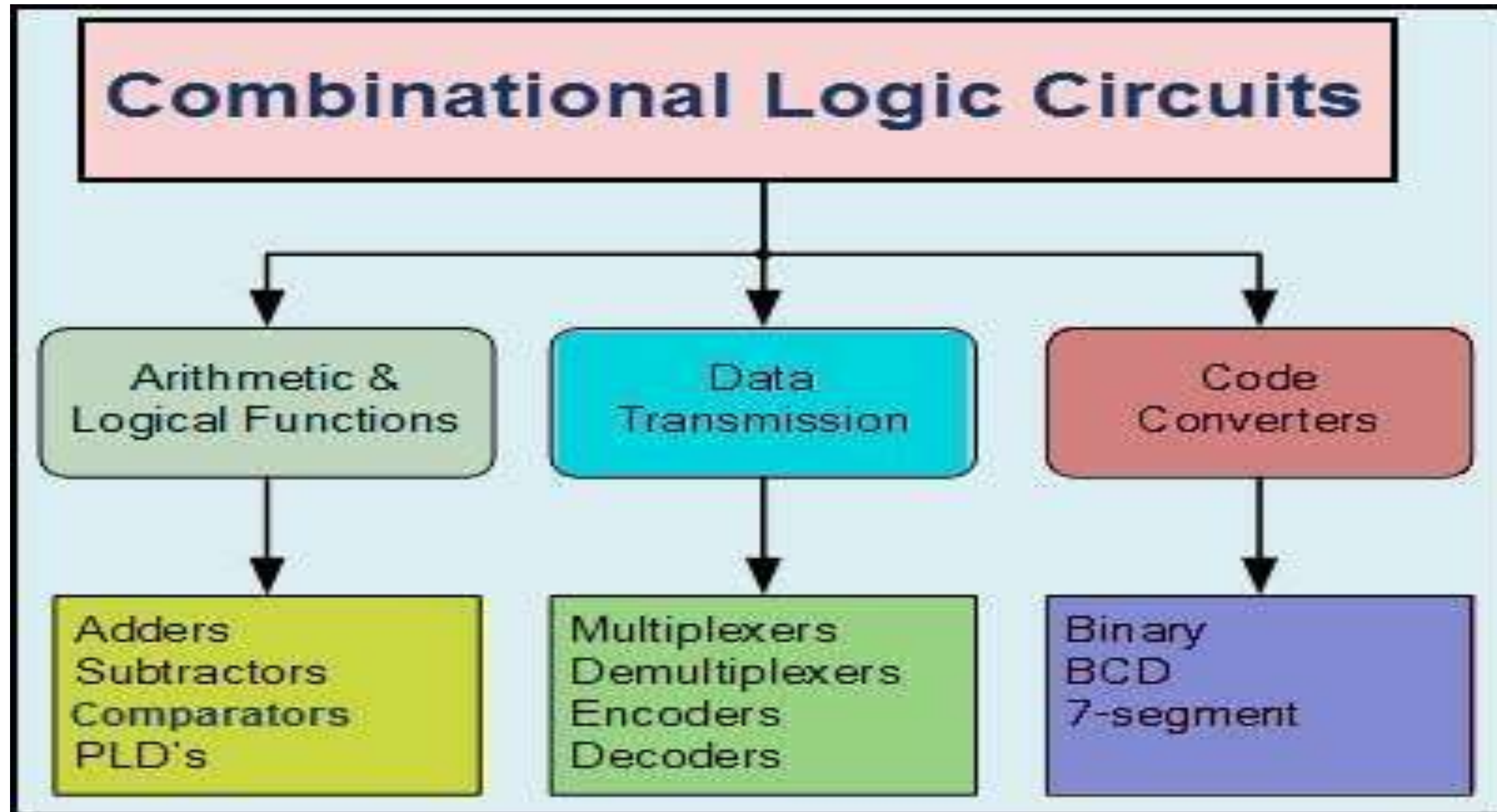



## ASSESSMENTS



1. Draw the block diagram of Half adder.
2. Draw the logical diagram of Full adder.



**THANK YOU**