



SNS COLLEGE OF TECHNOLOGY
Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

**23ECB201 – DIGITAL SYSTEM
DESIGN**

II YEAR/ III SEMESTER

UNIT 4 – DESIGN OF SEQUENTIAL CIRCUITS

TOPIC –DESIGN OF SEQUENTIAL CIRCUITS




Finite State Machines

- Two types of sequential circuits (or finite state machines)
 - Mealy machine
 - Output is function of present state and present input
 - Moore machine
 - Output is function of present state only



Moore State Machines:

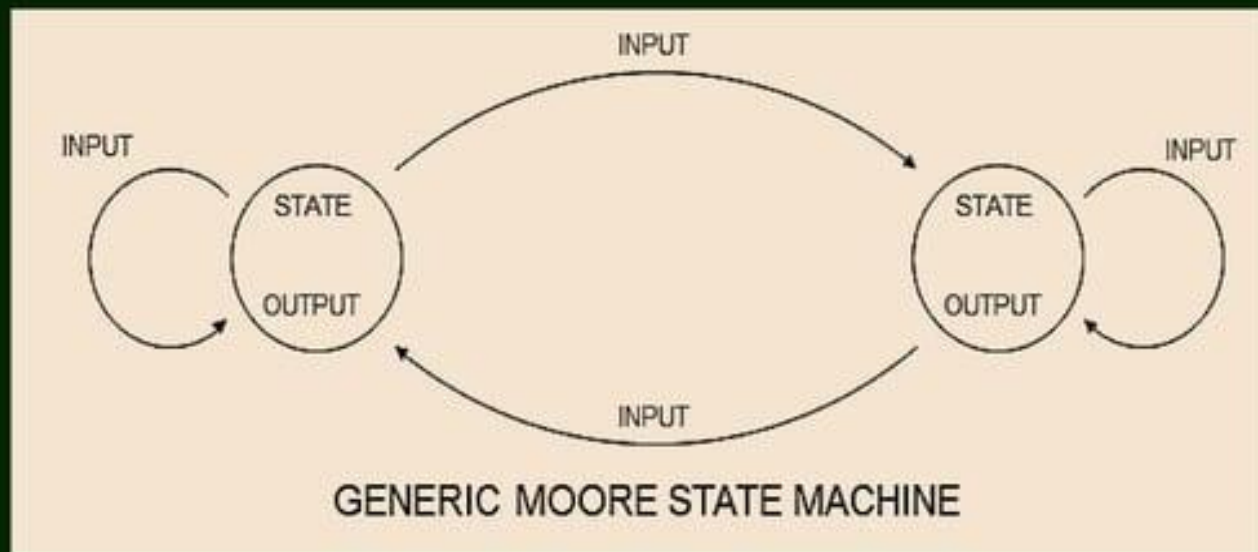- Outputs determined solely by the current state






State Table

Prev. State	X	O ₂	O ₁	O ₀	Next State ⁺
A	0	0	0	0	B
A	1	0	0	0	A
B	0	0	0	1	B
B	1	0	0	1	C
D	0	1	1	1	B
D	1	1	1	1	A
C	0	0	1	1	B
C	1	0	1	1	D



State Diagram

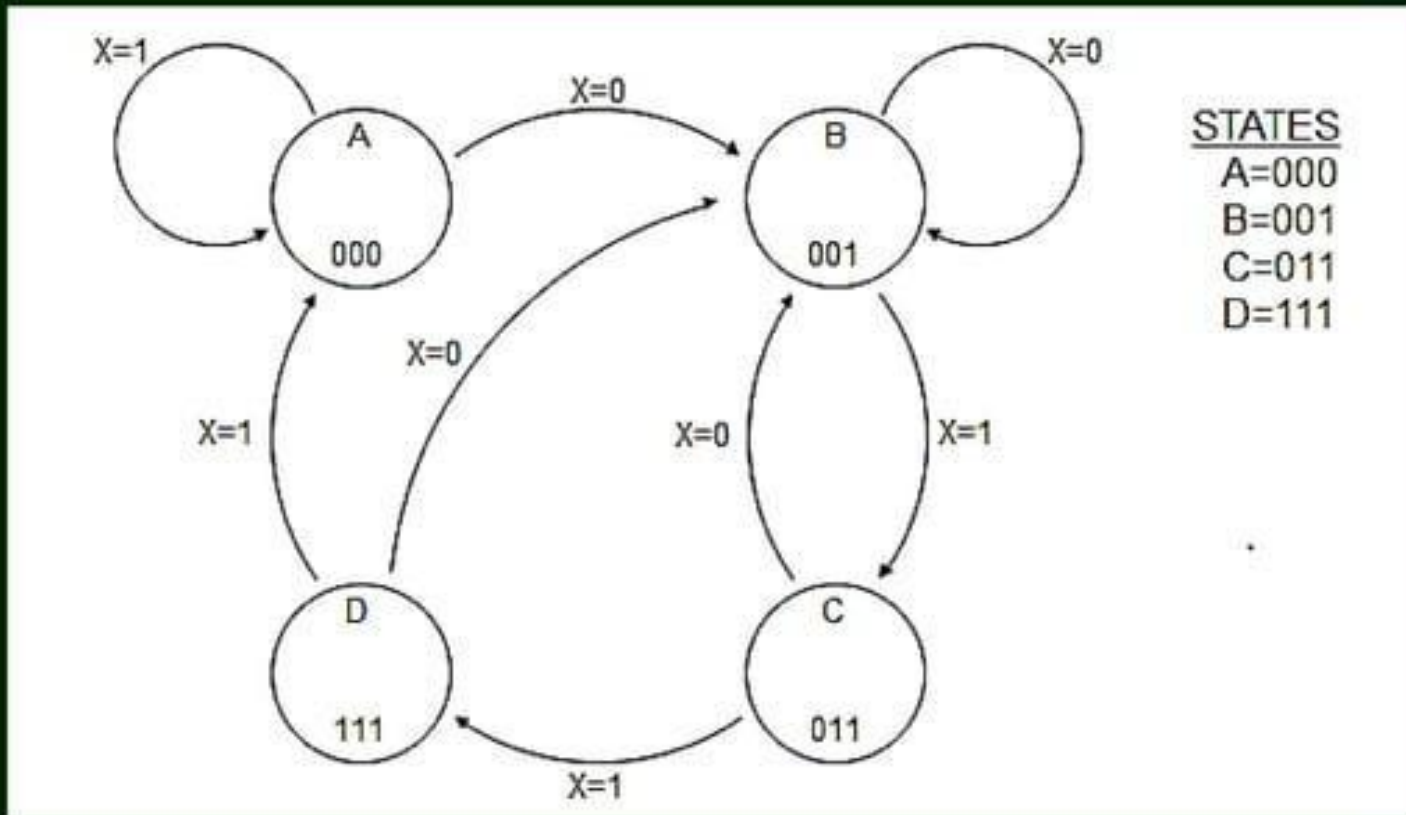



Moore State Machines:


- State Table

PS	NS		z (=B)
	X=0	X=1	
AB	AB	AB	
00	00	11	0
01	00	11	1
10	10	01	0
11	11	10	1




Moore State Machines:

- State Diagram

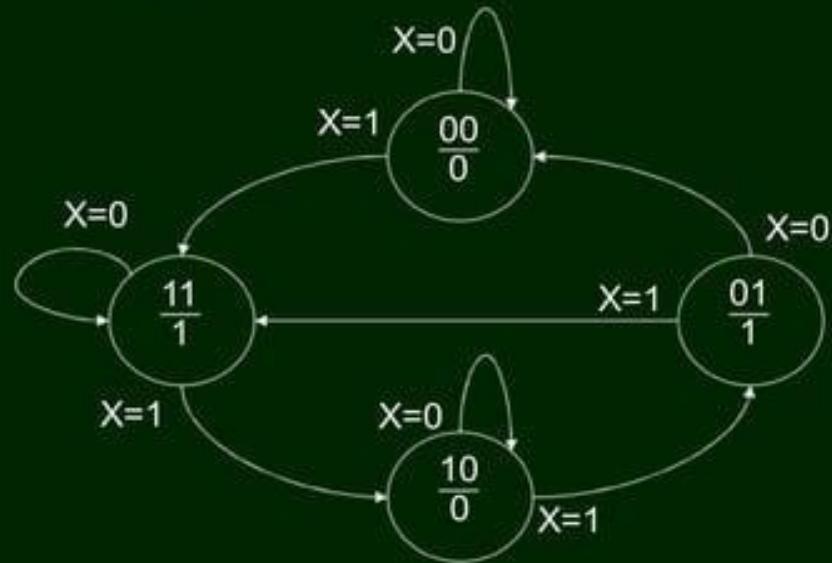



Moore Machine

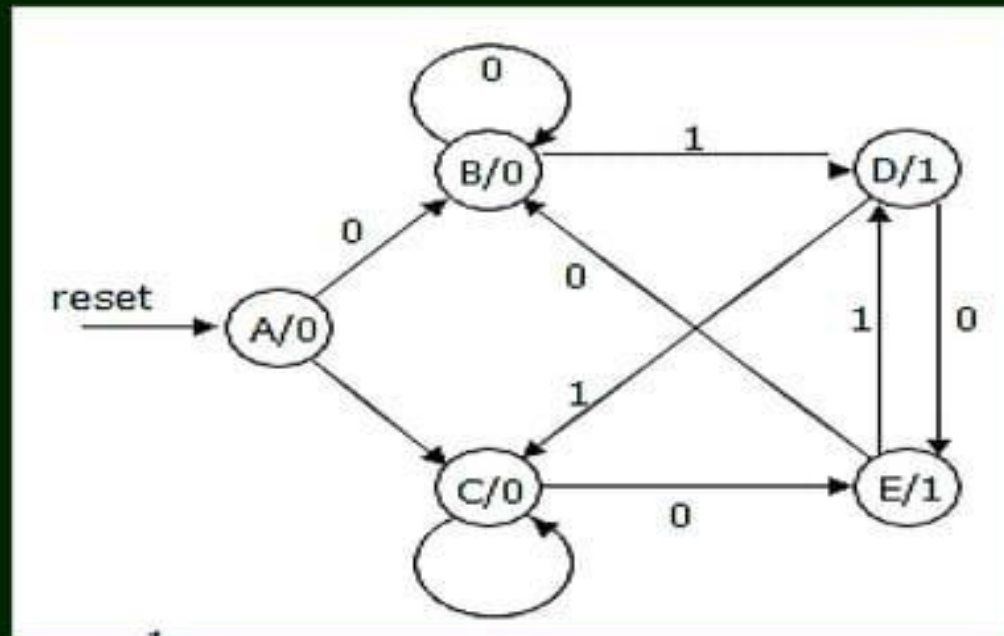




Moore Machine

reset	input	current state	next state	output
1	—	—	A	
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1



Moore FSM – Example : State diagram

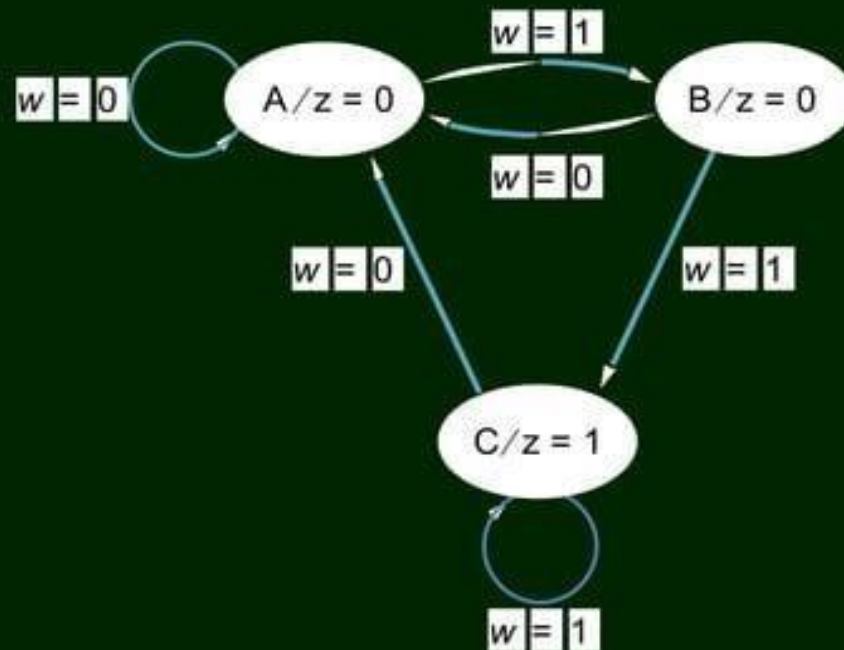




Moore FSM – Example : State table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1



State Diagram

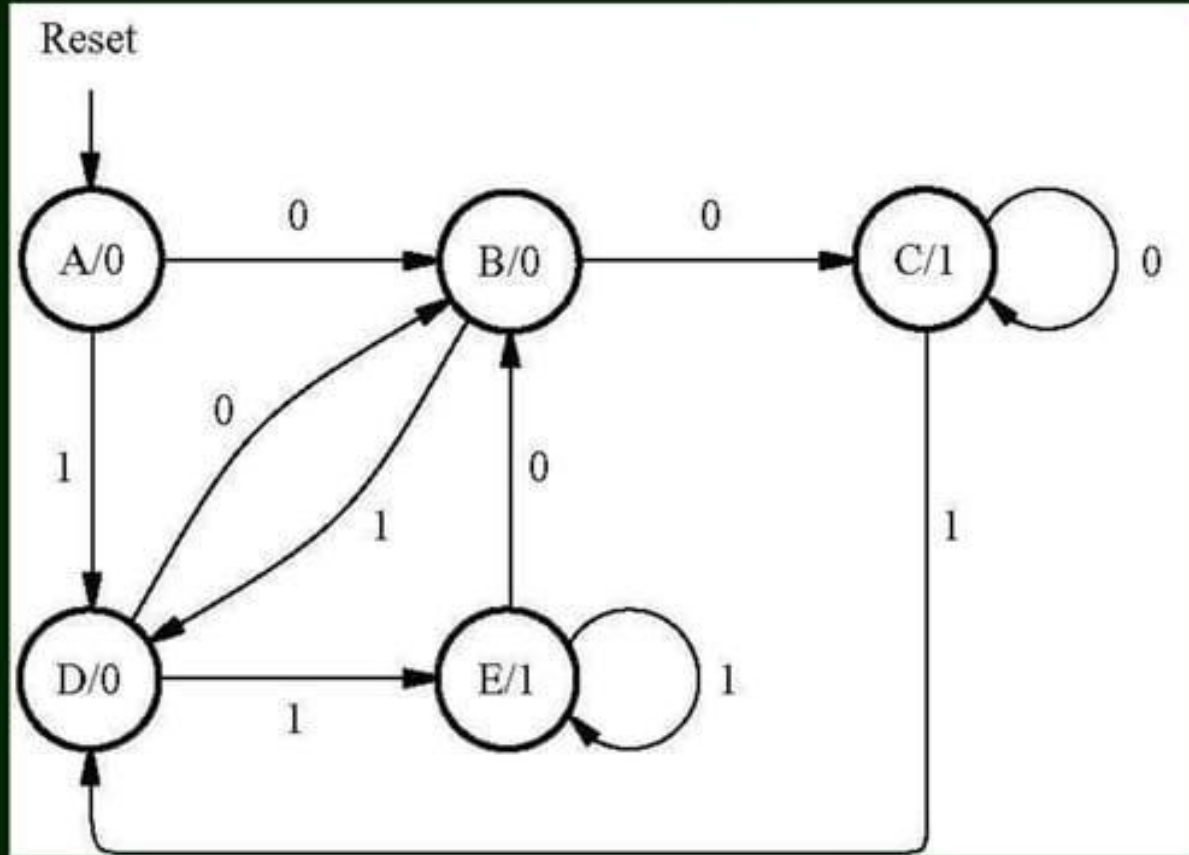




State Table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	B	D	0
B	C	D	0
C	C	D	1
D	B	E	0
E	B	E	1



Mealy State Machines:

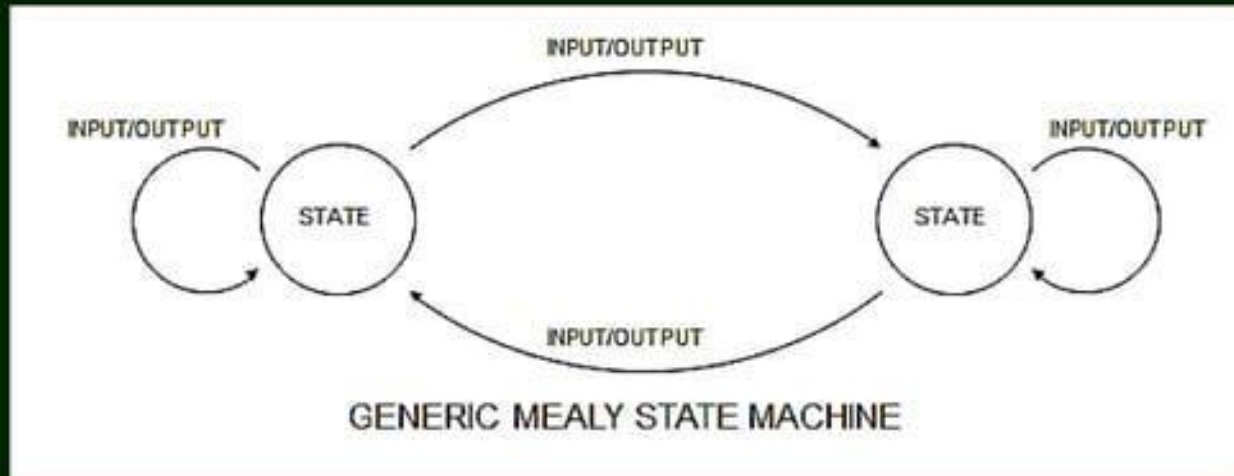- Outputs determined by the current state and the current inputs.






State	Q ₂	Q ₁	Q ₀	X	Z	State ⁺	q ₂ ⁺	q ₁ ⁺	q ₀ ⁺
Start	0	0	0	0	0	First	0	0	1
Start	0	0	0	1	0	Start	0	0	0
First	0	0	1	0	0	First	0	0	1
First	0	0	1	1	0	Second	0	1	1
Success	0	1	0	0	0	First	0	0	1
Success	0	1	0	1	0	Start	0	0	0
Second	0	1	1	0	0	Delay	1	1	1
Second	0	1	1	1	1	Success	0	1	0
unused	1	0	*	*	X	X	X	X	X
SuccessD	1	1	0	0	0	Delay	1	1	1
SuccessD	1	1	0	1	1	Success	0	1	0
Delay	1	1	1	0	0	Delay	1	1	1
Delay	1	1	1	1	1	SuccessD	1	1	0



State Diagram

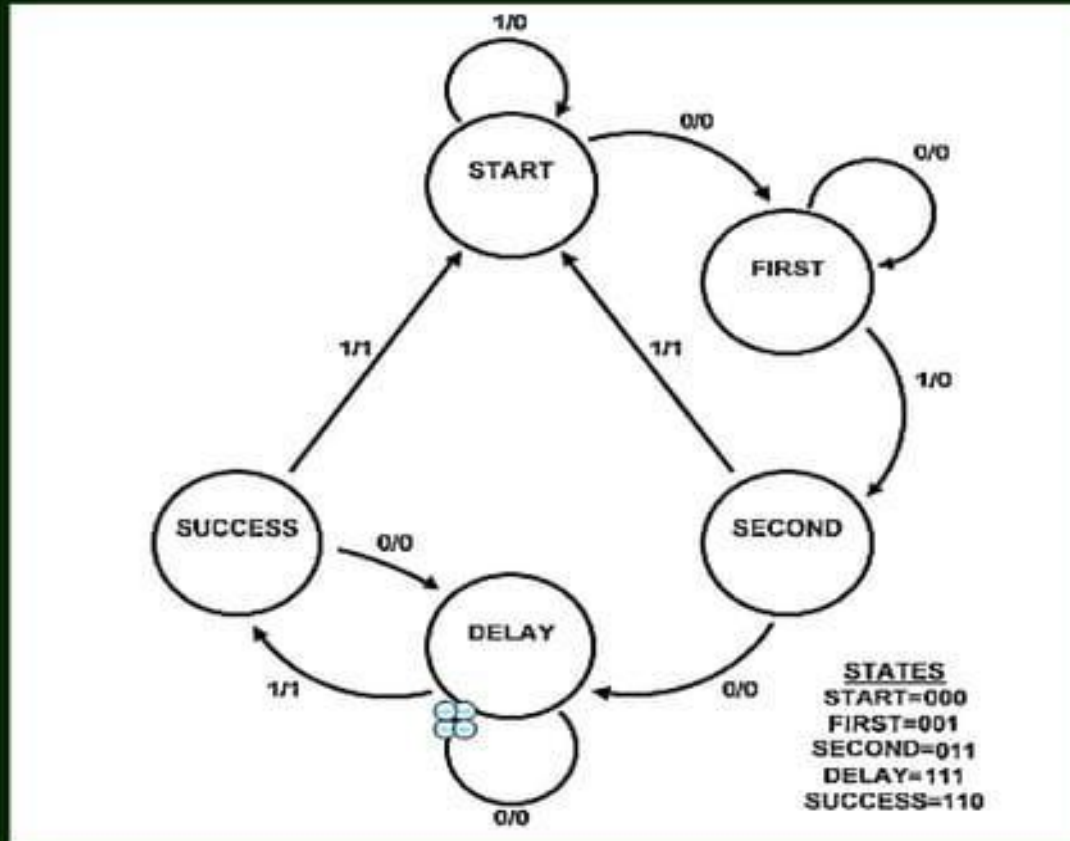



Mealy State Machines:


- State Table

PS	NS	
	x=0	x=1
AB	AB,z	AB,z
00	00,0	01,1
01	01,1	11,0
10	10,0	01,1
11	11,0	00,1




Mealy State Machines:

- State Diagram

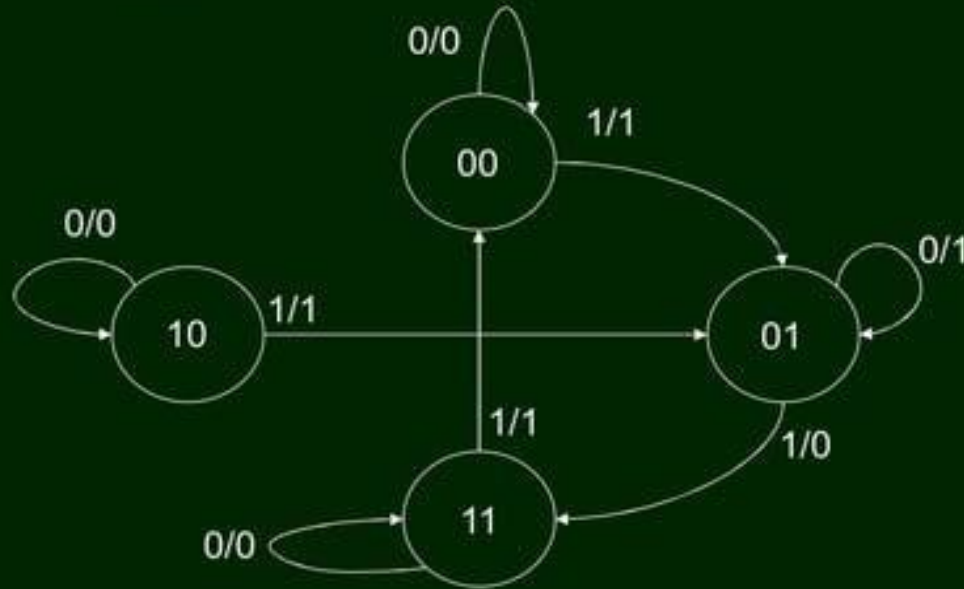




Mealy FSM – Example : State diagram

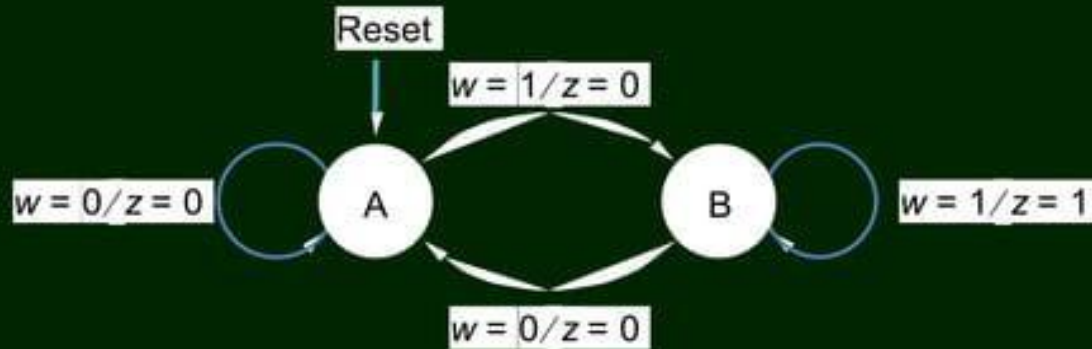



State Diagram

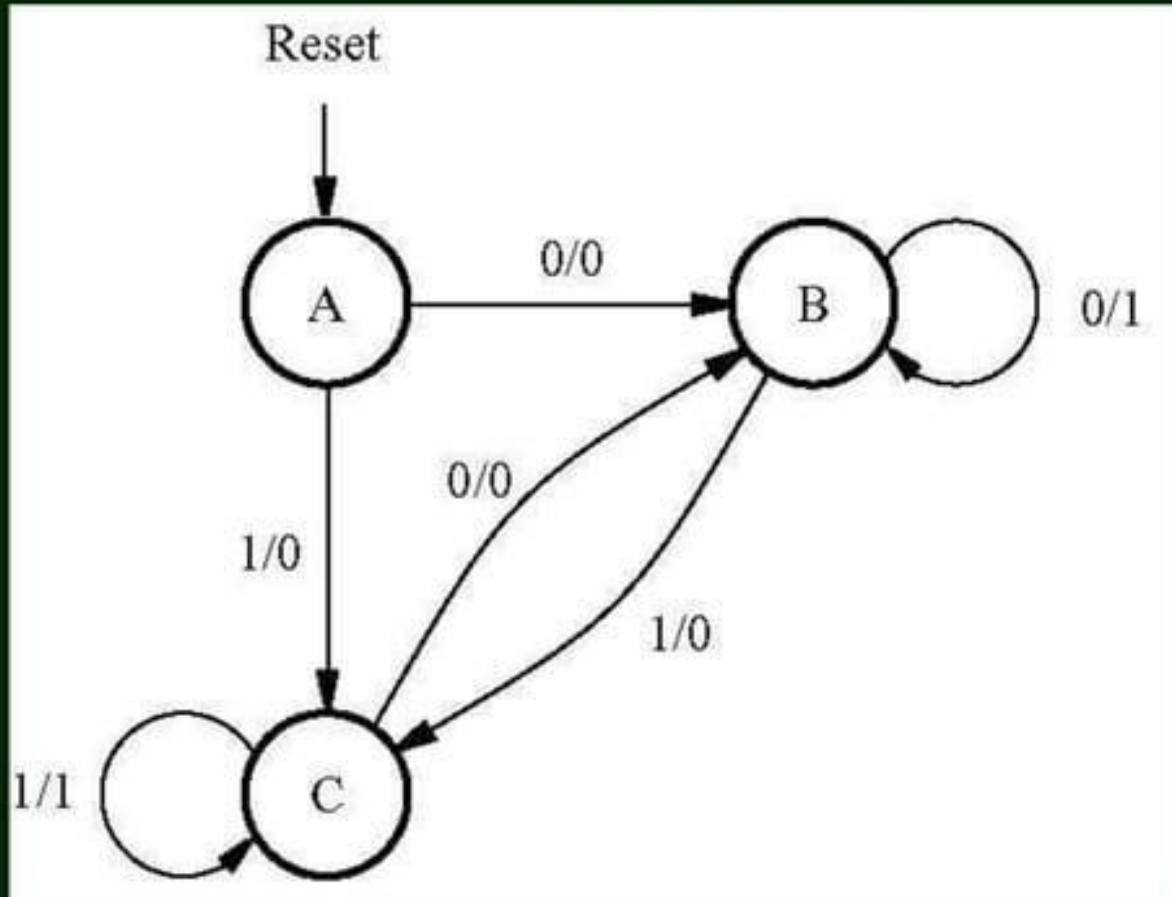



State Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	B	C	0	0
B	B	C	1	0
C	B	C	0	1



THANK YOU