



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ARTIFICIAL INTELLIGENCE AND MACHINE LEARNING

19ECB231 – DIGITAL ELECTRONICS

1

II YEAR/ III SEMESTER

UNIT 1 – MINIMIZATION TECHNIQUES AND LOGIC GATES

TOPIC – LOGIC GATES



LOGIC GATES




- AND
- OR
- NOT
- NAND
- NOR
- XOR
- XNOR




WHAT IS LOGIC GATE?

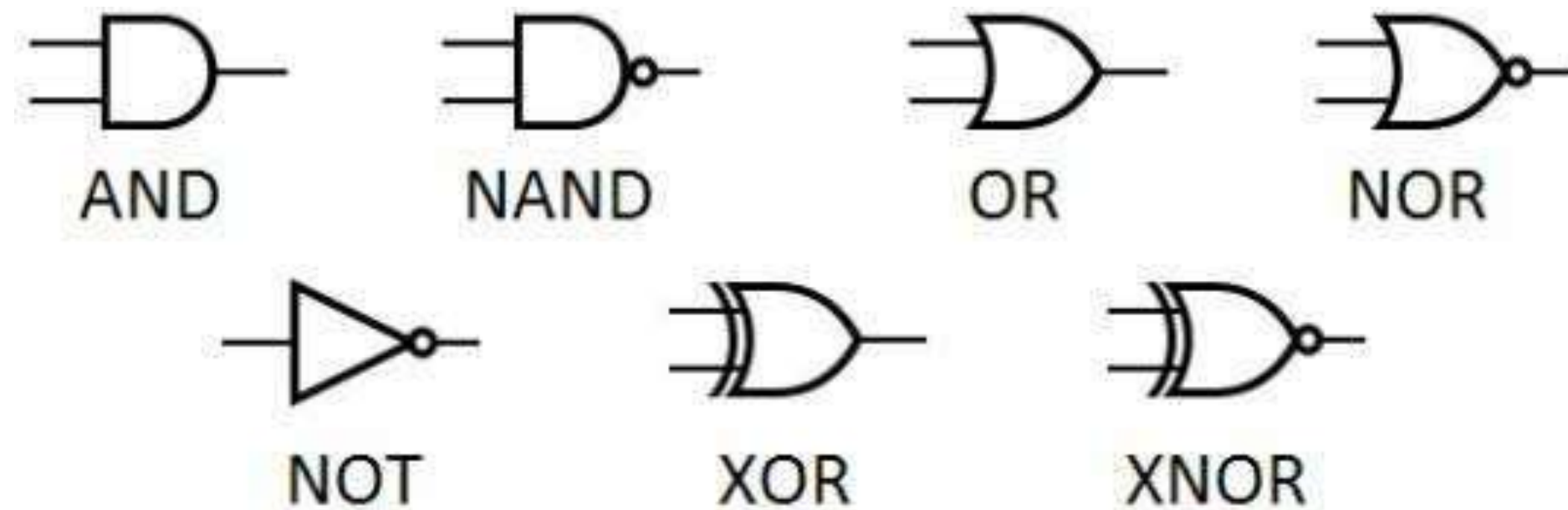- A Logic Gate is an idealized or physical electronic device which is used for implementing a boolean function, a logical operation performed on one or more binary inputs that produce a single binary output.






CLASSIFICATION OF LOGIC GATES

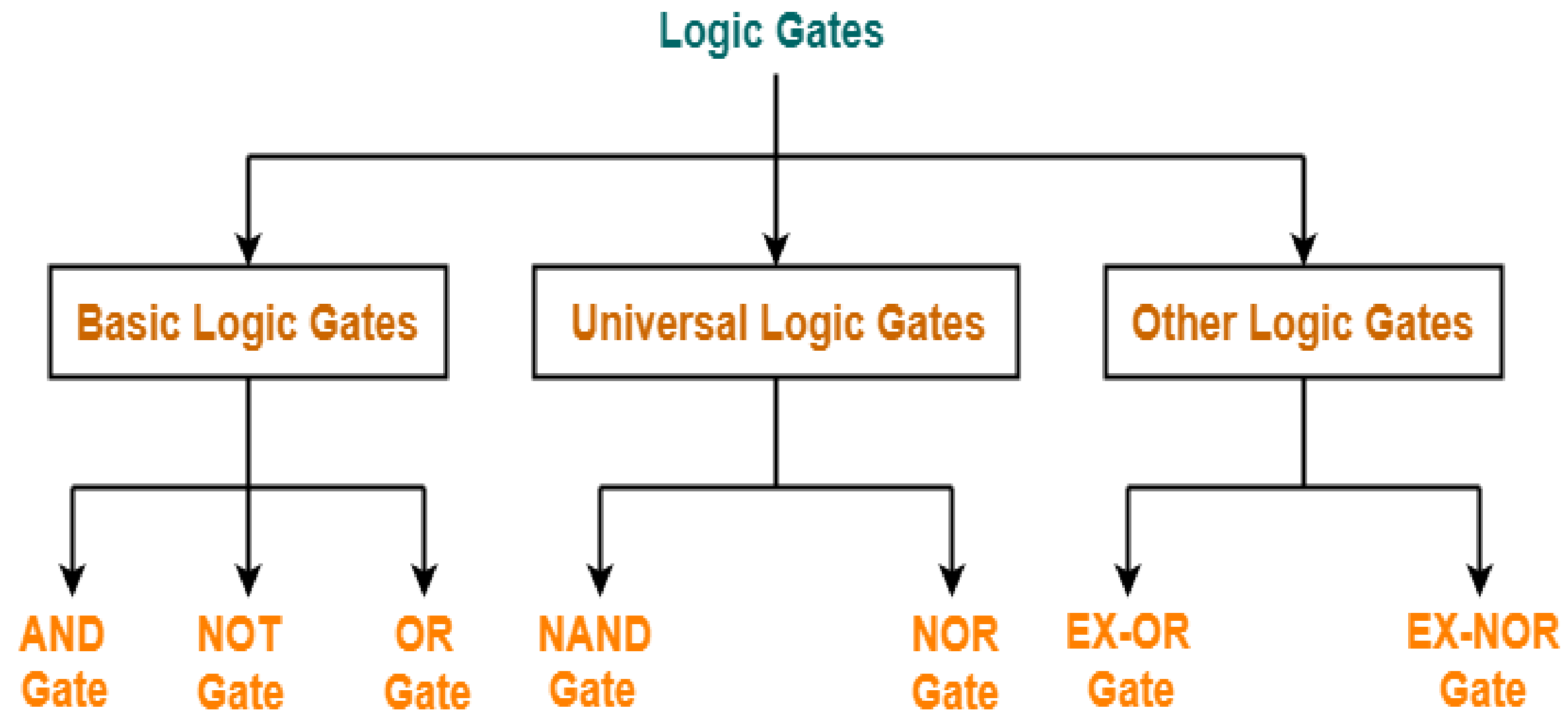




AND GATE

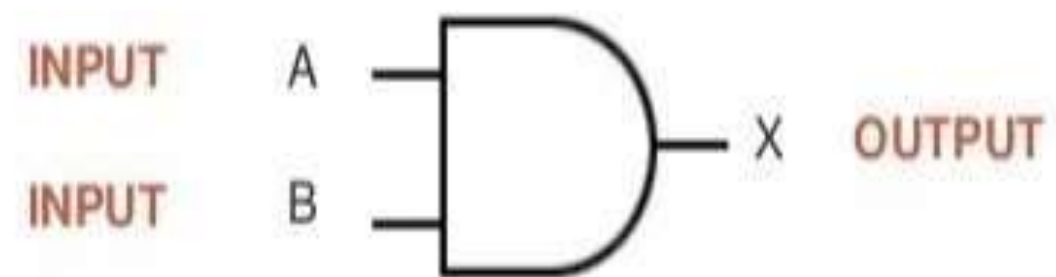

The output will be positive (true) when both inputs (the input one AND the input two) are positive (true).


$$X = A \text{ AND } B$$

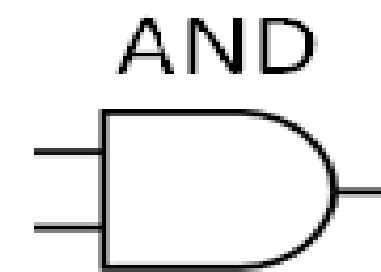

INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1



OR GATE

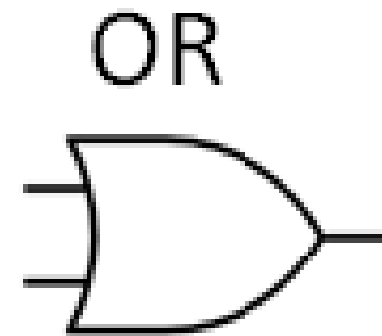

INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

In Boolean Algebra the OR function is the equivalent of addition so its output state represents the addition of its inputs.

In Boolean Algebra the OR function is represented by a “plus” sign (+) so for a two input OR gate the Boolean equation is given as:


$$Q = A+B,$$

that is Q equals either A OR B.



NOT GATE

NOT

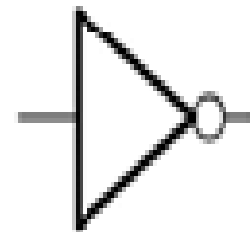


INPUT	OUTPUT
A	
0	1
1	0

The NOT function is not a decision making logic gate like that of AND or OR gates, but instead it is used to invert or complement a digital signal. In other words, its output state will always be the opposite of its input state.



NAND GATE

NAND

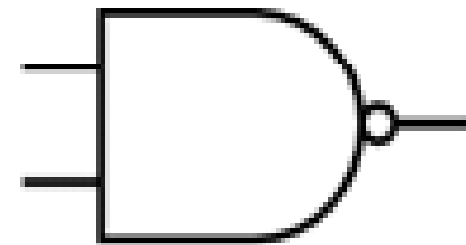


INPUT		OUTPUT
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

- The term NAND is a contraction of NOT-AND and implies an AND function with a complemented(inverted) output.
- The output will be HIGH,when any one of the inputs is LOW and the output will be LOW when both the inputs are HIGH.
- This operation is opposite to that of AND Gate.



NOR GATE

NOR

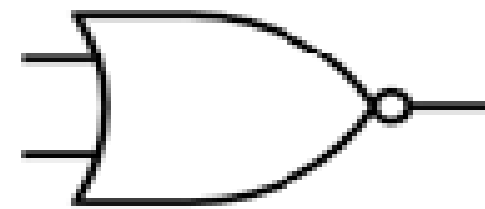

INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	0

- The term NOR is a contraction of NOT-OR and implies an OR function with a complemented(inverted) output.
- The output will be LOW, when any one of the inputs is HIGH and the output will be HIGH when both the inputs are LOW.
- This operation is opposite to that of OR Gate.



UNIVERSAL GATES




- The NAND and NOR gates are used to generate AND, OR and NOT functions.
- Any logic logic function can be implemented using NAND and NOR gates. So it is called as Universal gates.



EX-OR GATE





XOR

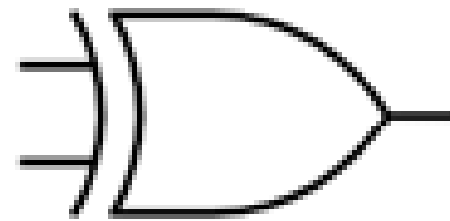


INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	0

Exclusive-OR Symbol

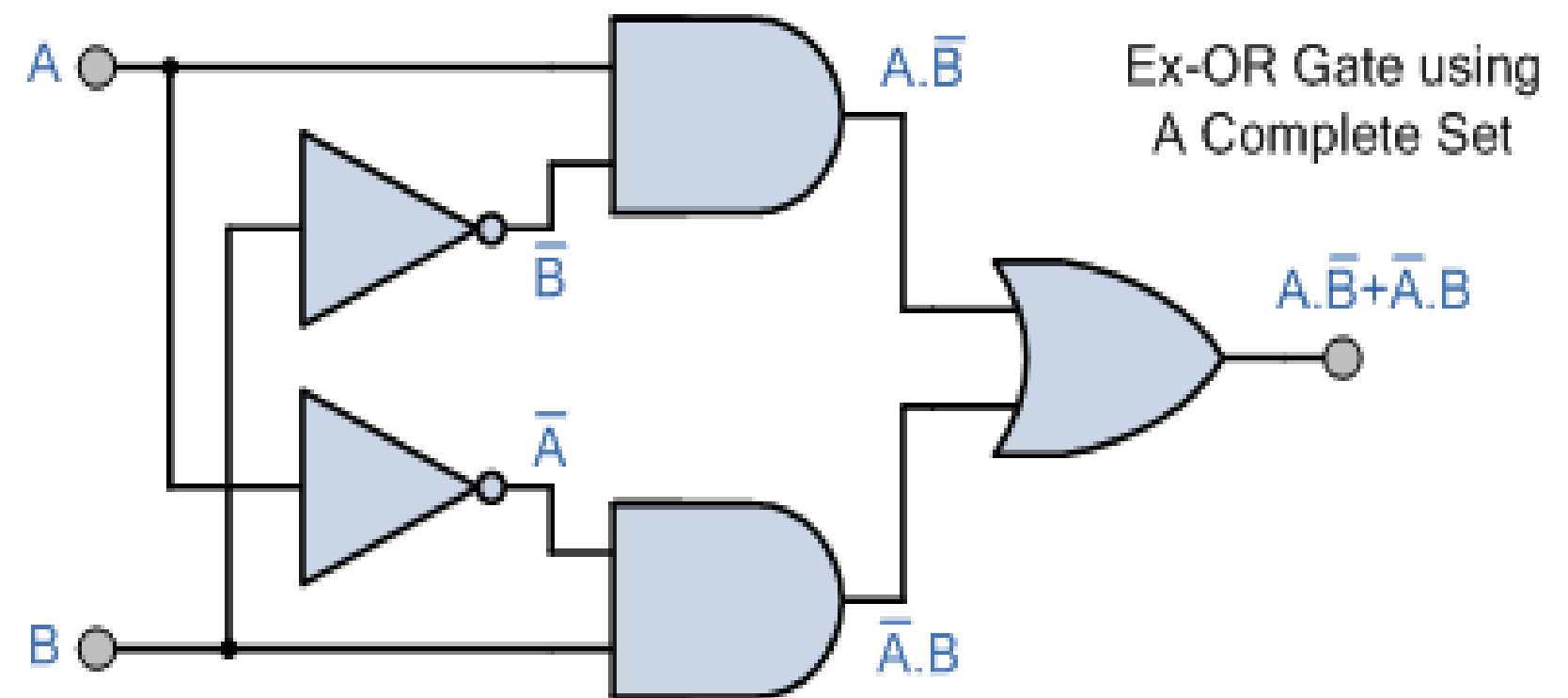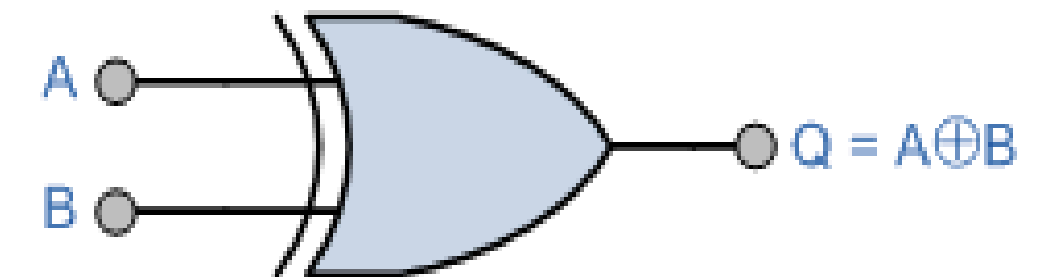





EX-NOR GATE

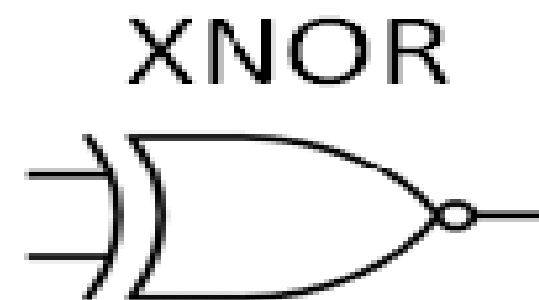


INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	1

Exclusive-NOR Symbol

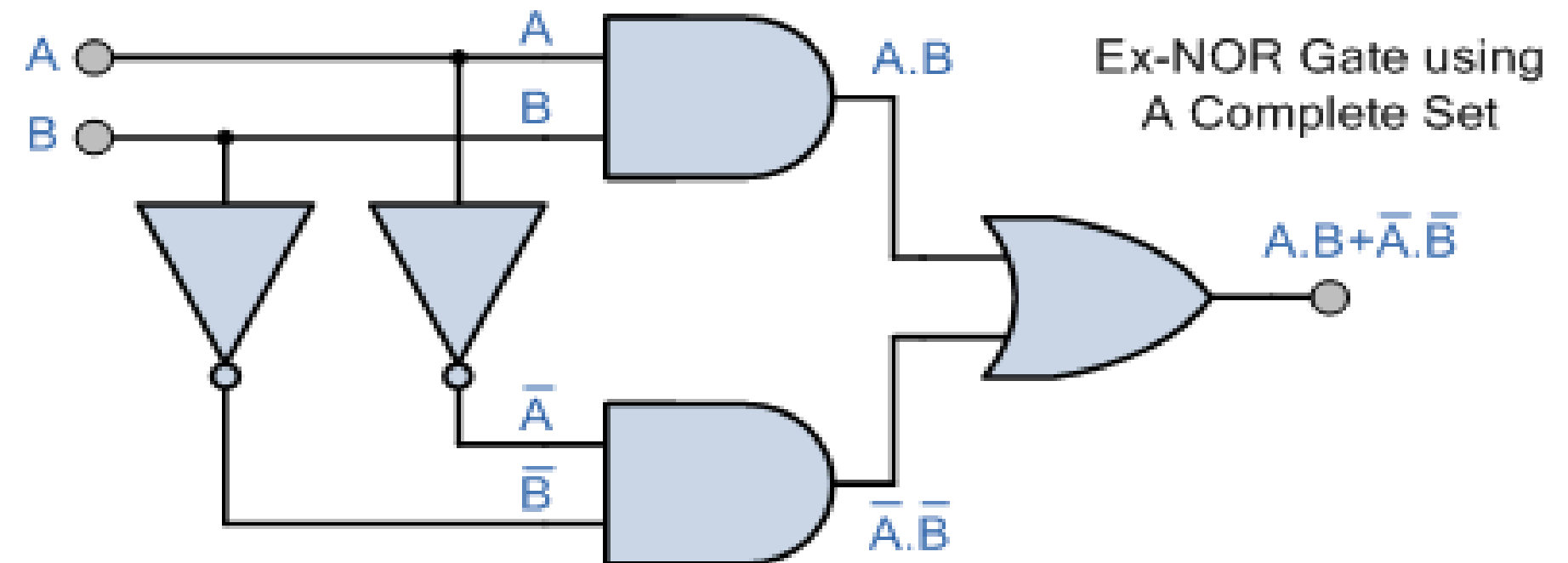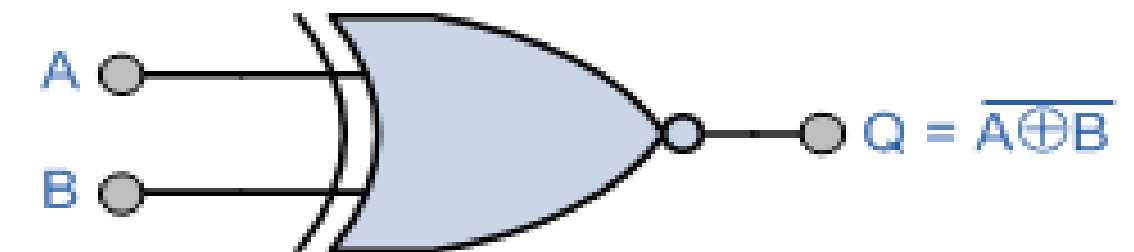



BOOLEAN EXPRESSION USING LOGIC GATES

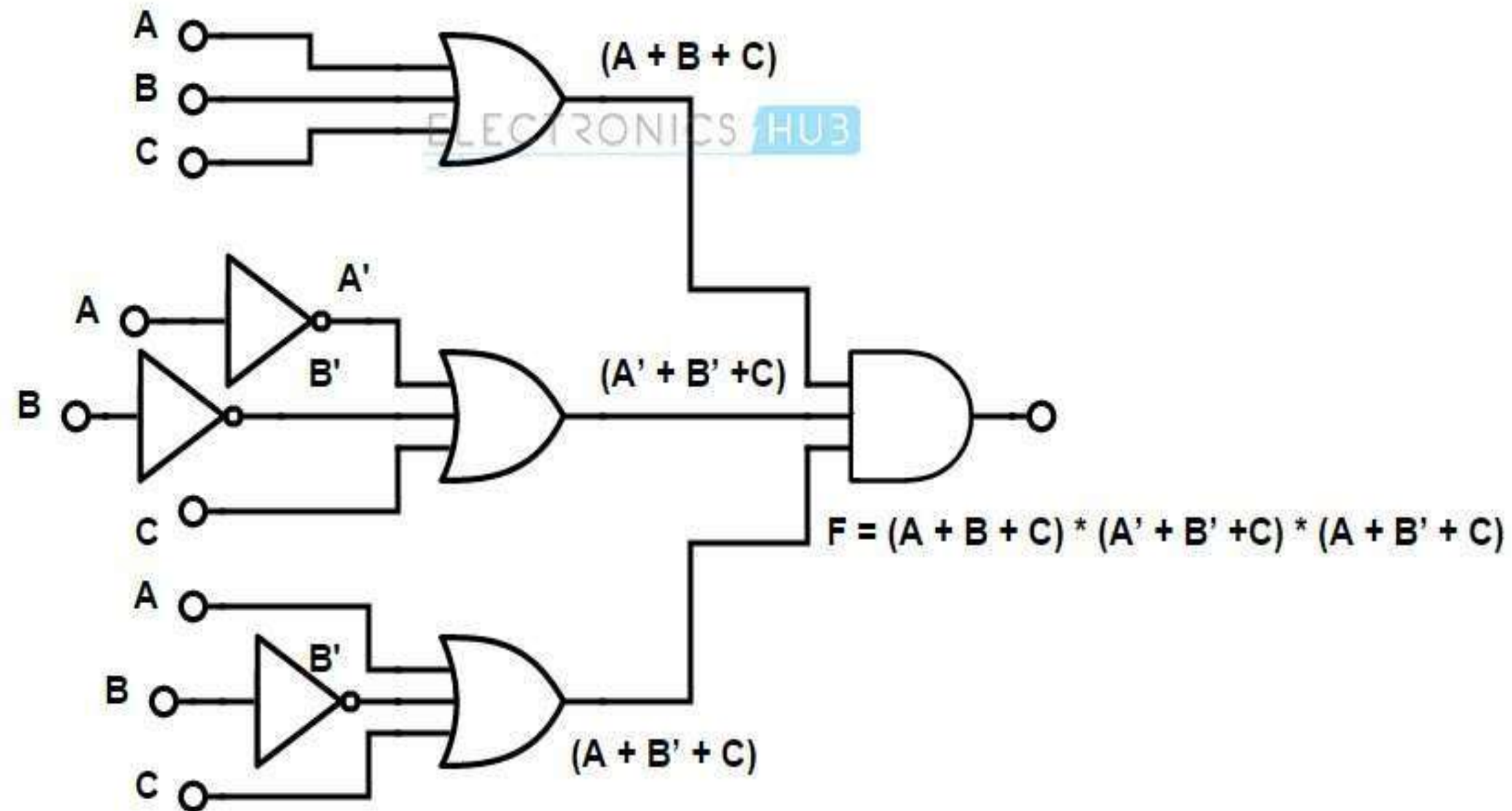



ASSESSMENTS



- 1.What are universal gates?Why it is called so?
- 2.Draw the symbols and truth tabl^r of NOT gate and AND gate?
- 3.Draw the symbols of EXOR gate and explain its truth table.



THANK YOU