



# SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech&B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU



Reg. No:

**B.E/B.Tech- Internal Assessment – II**  
**Academic Year 2024-2025 (ODD Semester)**  
**Third Semester**  
**Electronics and Communication Engineering**  
**23ECB201 – Digital System Design**

**B**

**Time: 1<sup>1/2</sup> Hours**

**Maximum Marks: 50**

**Answer All Questions**

**PART - A (5 x 2 = 10 Marks)**

		CO	Blooms
1.	What is a code converter? Classify different types of code converters.	CO2	UND
2.	Explain odd parity checker.	CO2	UND
3.	Distinguish Latch and Flip-Flop	CO3	ANA
4.	How state assignment is performed in sequential circuit design?	CO3	REM
5.	Compare static and dynamic hazard.	CO3	ANA

**PART – B (2\*13=26 Marks) & (1\*14=14 Marks)**

			CO	Blooms
6.	(a) What is the significance of using gray code? Develop a logic circuit to convert 4-bit binary code to gray code.	13	CO2	APP
	(OR)			
	(b) Construct a 2-bit magnitude comparator logic circuit with 3 outputs: A>B, A<B, A=B.	13	CO2	APP
7.	(a) If a logic circuit is prone to hazards, outline what design strategies would you employ to detect and resolve them?	13	CO3	UND
	(OR)			
	(b) Illustrate the functioning of a D flip-flop with appropriate tables and diagrams.	13	CO3	UND
8.	(a) Analyze the impact of input conditions on the state transitions of an SR flip-flop. How can understanding these transitions inform the design of more complex digital systems?	14	CO3	ANA

(OR)

- (b) Examine the operational principles of a JK flip-flop, including its truth table and characteristic equation. How do the inputs J and K interact to produce different output states? 14 CO3 ANA

**Bloom's Taxonomy:**

**REM** – Remember    **UND** – Understand    **APP**– Apply    **ANA**– Analyze    **EVA** – Evaluate

**CRT** - Create

**Faculty in-charge**

**Teaching Coordinator**

**HoD**

**Dean**