



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



23EET202 / DIGITAL ELECTRONICS AND LINEAR INTEGRATED CIRCUITS II YEAR / III SEMESTER UNIT-I: OPERATIONAL AMPLIFIER

OP-AMP INVERTING / NON INVERTING



TOPIC OUTLINE


Basics of Op-Amp
Inverting Op-Amp Circuits
Non Inverting Op-Amp Circuits





WHAT IS AN OP-AMP?


- An *Operational Amplifier* (known as an “Op-Amp”) is a device that is used to amplify a signal using an external power source
- Op-Amps are generally composed of:
 - Transistors, Resistors, Capacitors

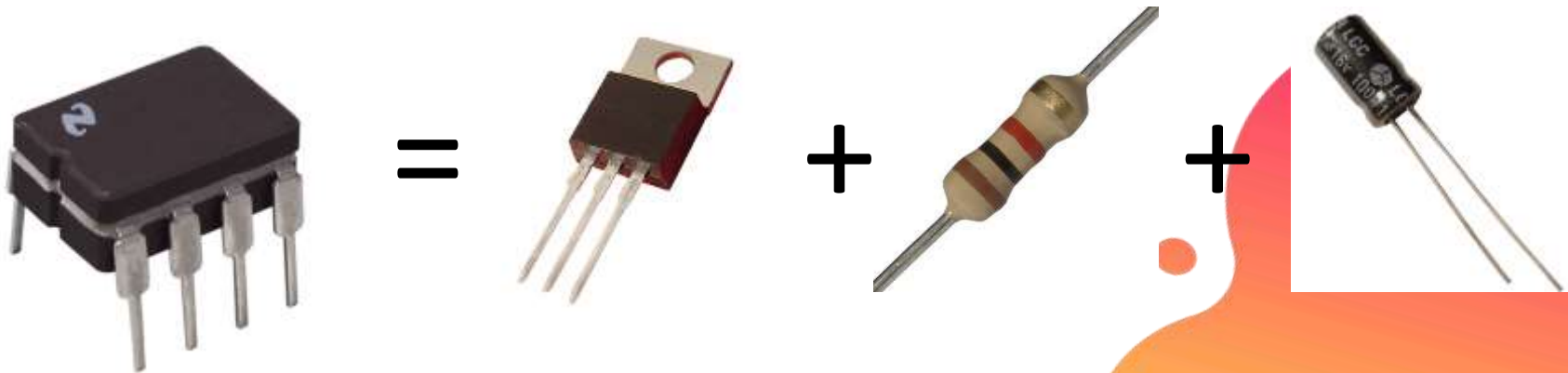




IC741 – PIN DETAILS

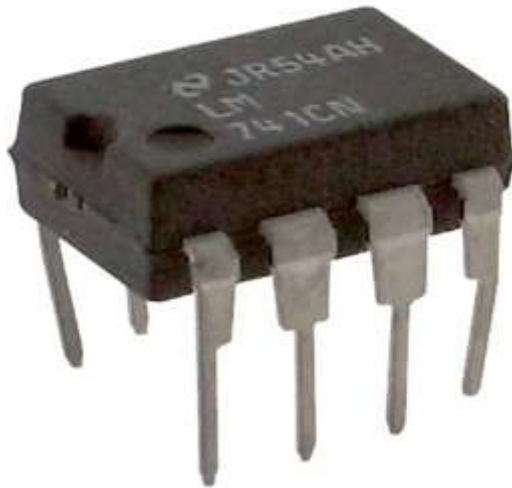- Leading to the advent of the modern IC which is still used even today (1967 – present)



Fairchild μ A741

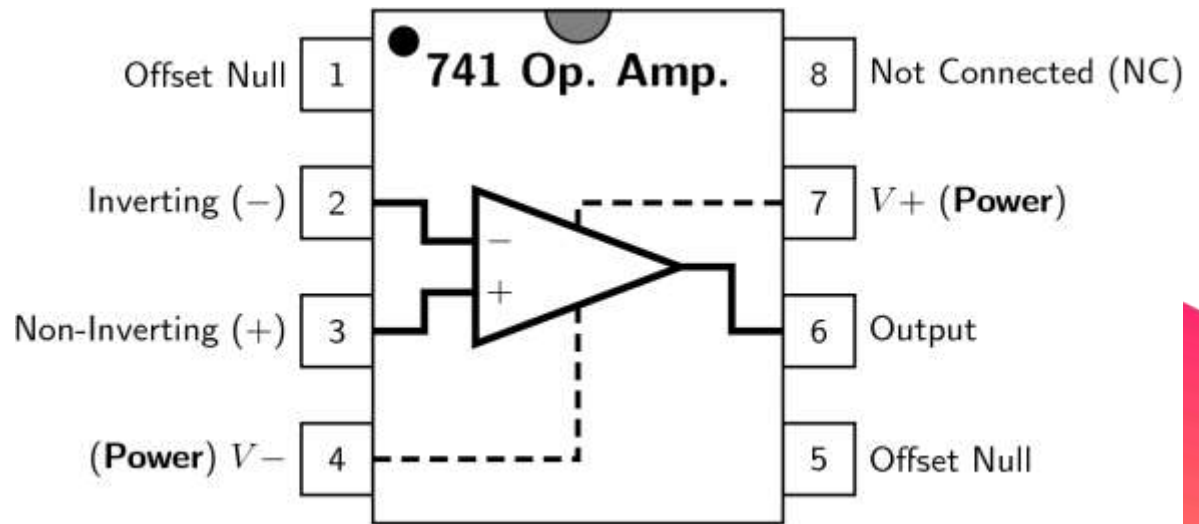


Electrical Schematic of μ A741



NON-INVERTING OP-AMP

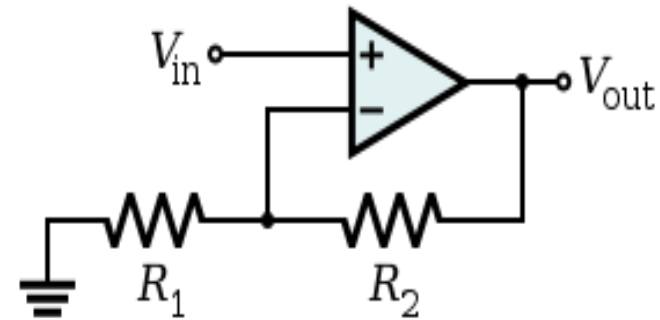- Amplifies the input voltage by a constant
- Closed loop op-amp
- Voltage input connected to non-inverting input
- Voltage output connected to inverting input through a feedback resistor
- Inverting input is also connected to ground
- Non-inverting input is only determined by voltage output





NON-INVERTING OP-AMP


$$V_o = K(V_+ - V_-) \text{ \& } R_2 = R_f$$

$R_1/(R_1+R_2) \leftarrow$ Voltage Divider

$$V_i = V_o (R_1/(R_1+R_2))$$

$$V_o/V_i = A_{cl} = [1 + (R_2/R_1)]$$


$$V_{out} = V_{in} (1 + (R_2/R_1))$$

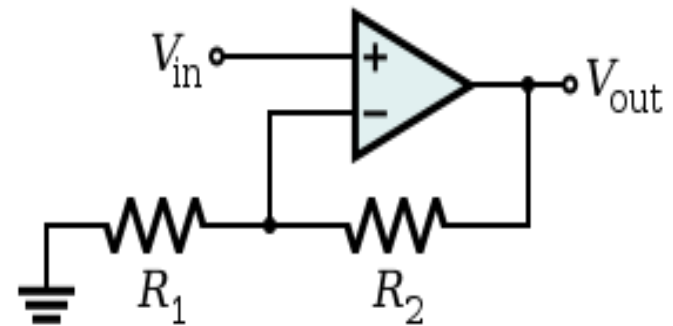



INVERTING OP-AMP

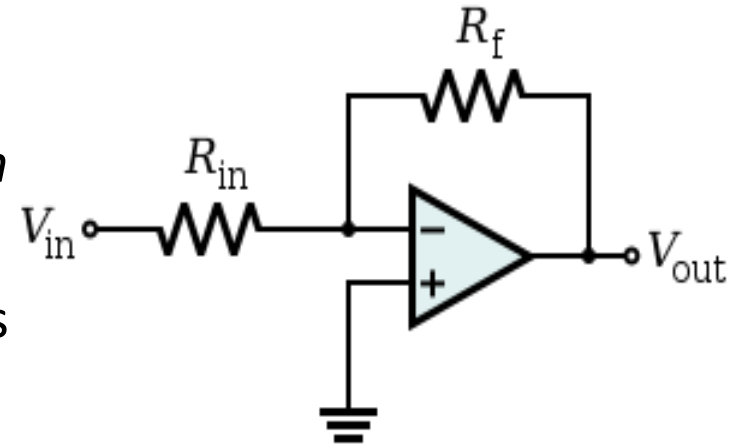- Amplifies and inverts the input voltage
- Closed loop op-amp
- Non-inverting input is determined by *both* voltage input and output
- The polarity of the output voltage is opposite to that of the input voltage
- Voltage input is connected to inverting input
- Voltage output is connected to inverting input through a feedback resistor
- Non-inverting input is grounded





INVERTING OP-AMP

$$V_{out} = K(V_+ - V_-)$$

Nodal equation at “a” (V_a) is


$$0 = ((V_a - V_i)/R_i) + ((V_a - V_o)/R_f)$$

Since V_a is virtual gnd = 0

$$0 = ((0 - V_i)/R_i) + ((0 - V_o)/R_f)$$

$$V_o / V_i = -R_f / R_i = A_{cl}$$

$$V_{out} = -V_{in} R_f / R_{in}$$

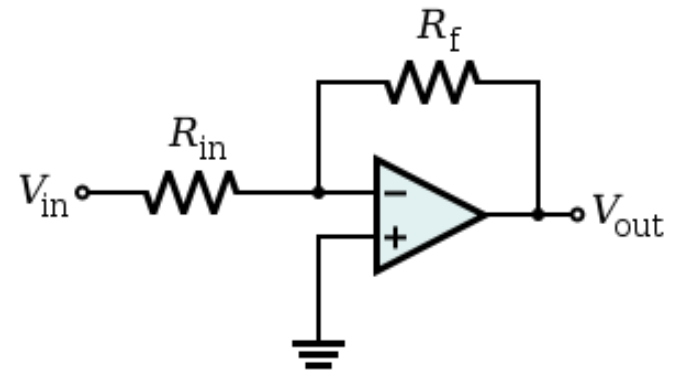



THANK YOU

