



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



23EET202 / DIGITAL ELECTRONICS AND LINEAR INTEGRATED CIRCUITS II YEAR / III SEMESTER UNIT-IV: OPERATIONAL AMPLIFIER

OP-AMP BASIC APPLICATIONS



TOPIC OUTLINE


Basics Applications-1
Integrator
Differentiator
Summer
Subtractor
Differential Amplifier





INTEGRATOR OP-AMP

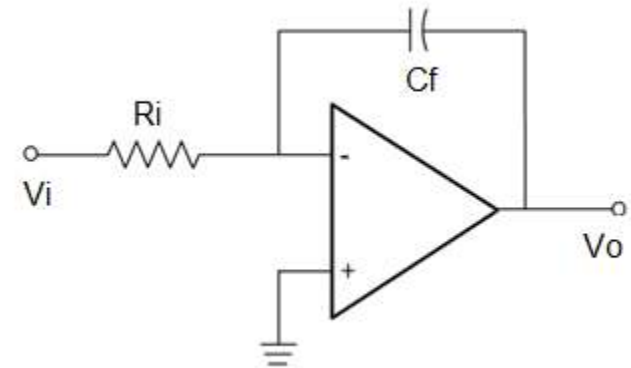- Integrates the inverted input signal over time
- Closed loop op-amp
- Voltage output is connected to inverting input through a *capacitor*
- The resistor and capacitor form an RC circuit
- Magnitude of the output is determined by length of time voltage is present at input
- The longer the input voltage is present, the greater the output






INTEGRATOR OP-AMP

- At node 'a': the nodal eqn is,
 $(V_i/R_i) + (C_f (dV_o/dt)) = 0$
- $(dV_o/dt) = -[V_i/(R_i C_f)]$
- Integrating both sides of the above equation, then
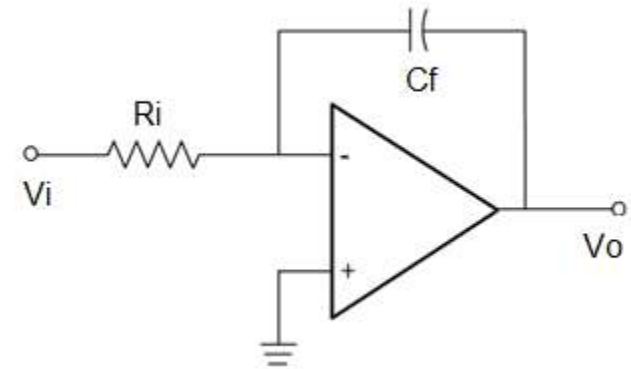
$$V_o = -\frac{1}{R_i C_f} \int_0^t V_i(\tau) d\tau$$






INTEGRATOR OP-AMP

- When the circuit is first connected the capacitor acts as a short. Gain is less than 1, V_{out} is 0
- As time progresses, and the capacitor charges, it's effective resistance increases. Now V_{out} is increasing as well
- When the capacitor is fully charged it acts as an open circuit with infinite resistance. Now V_{out} goes into saturation (~80% power supply voltage)
- The rate of voltage output increase depends on the RC time constant

$$V_{out} = -V_{in} R_C / R_{in}$$

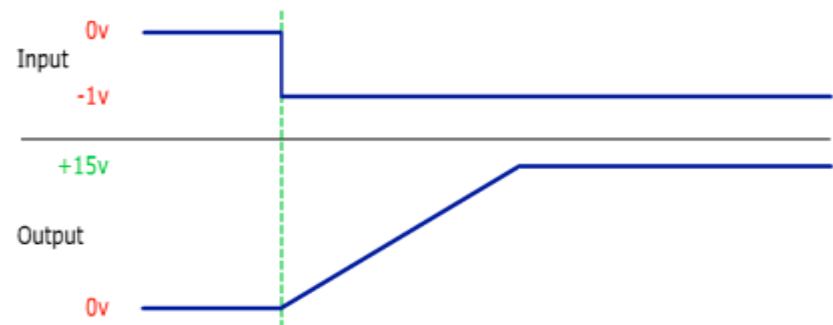
$$V_o = -\frac{1}{R_i C_f} \int_0^t V_i(\tau) d\tau$$





INTEGRATOR OP-AMP

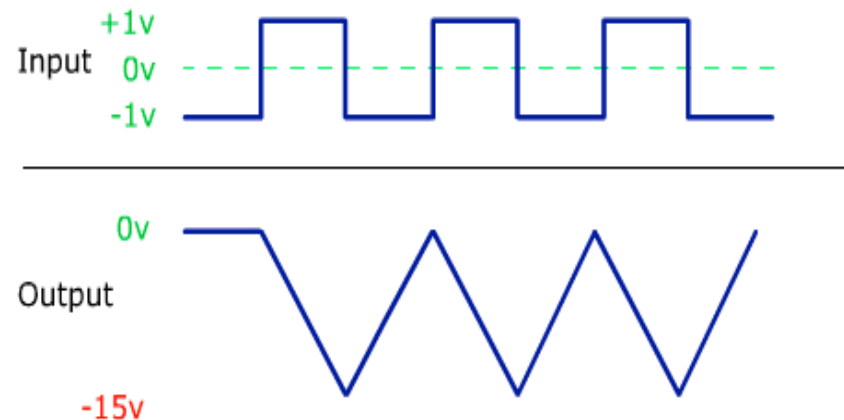
- An integrating op-amp circuit can create a sawtooth signal if a square wave is applied at V_i





DIFFERENTIATOR OP-AMP

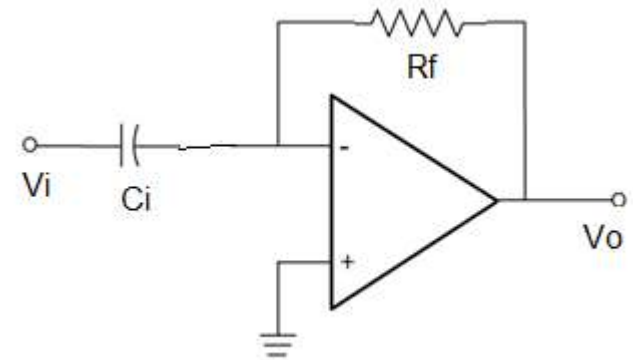- Differentiates the inverted input signal over time
- Closed loop op-amp
- Voltage output is connected to inverting input through a *resistor*
- The resistor and capacitor form an RC circuit
- Magnitude of the output is determined by length of time voltage is present at input
- The longer the input voltage is present, the greater the output.
- If INPUT is SQUARE – OUTPUT is SPIKE wave.






DIFFERENTIATOR OP-AMP

- At node 'a': the nodal eqn is,
 $[C_i(d/dt)(V_i - V_a)] - [(V_a - V_o)/R_f] = i_c$
- Since V_a is virtual gnd, $i_e = 0$
- $C_i(dV_i/dt) + (V_o/R_f) = 0$

assuming $i_c = 0$

$$V_o = -R_f C_i (dV_i/dt)$$

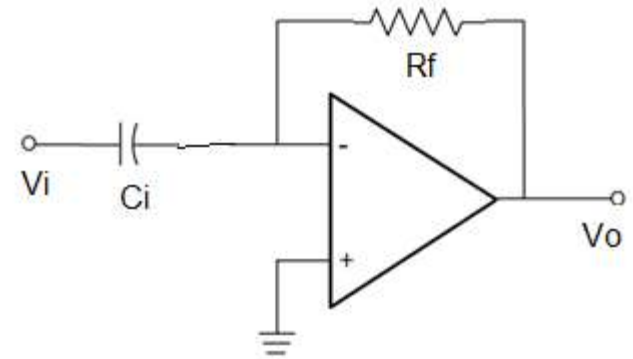- A differentiator op-amp circuit can create a cosine wave signal with 180 degree phase shift if a sine wave is applied at V_i






SUMMING OP-AMP

Output voltage

$$V_{OUT} = - \left(V_{IN1} \frac{R_F}{R_{G1}} + V_{IN2} \frac{R_F}{R_{G2}} + V_{IN3} \frac{R_F}{R_{G3}} + \dots \right)$$


If $R_{G1}=R_{G2}=R_{G3}=R_F$, then
 $V_{OUT} = -(V_{in1} + V_{in2} + V_{in3})$

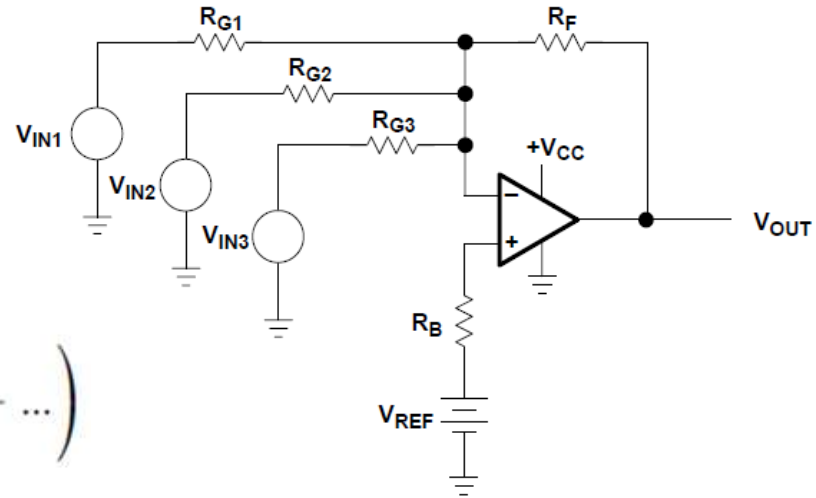The summing amplifier does exactly as the name suggests by adding up the voltages given to it and producing an output voltage which is the sum of the input voltages scaled by the feedback resistance and input resistance





SUMMING OP-AMP

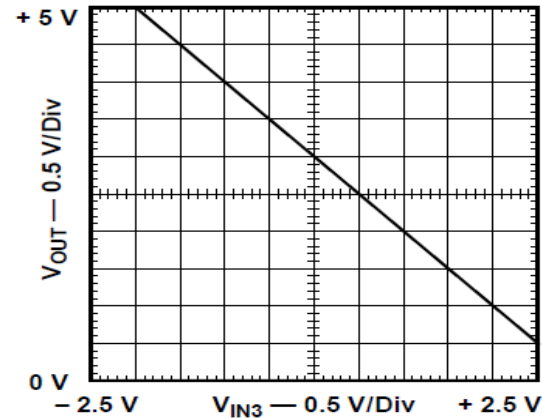


$V_{IN1} = 1 \text{ V}$ $V_{CC} = 5 \text{ V}$
 $V_{IN2} = -1.5 \text{ V}$ $V_{REF} = 0.625 \text{ V}$
 $V_{IN3} = 5 \text{ Vp-p}$ Op Amp = TLV247x
 $R_{G1} = R_{G2} = R_{G3} = R_F = 10 \text{ k}$

$$V_{OUT} = - \left(V_{IN1} \frac{R_F}{R_{G1}} + V_{IN2} \frac{R_F}{R_{G2}} + V_{IN3} \frac{R_F}{R_{G3}} + \dots \right) + V_{REF} \left(1 + \frac{R_F}{R_{G1} \parallel R_{G2} \parallel R_{G3} \dots} \right)$$

The graph shown above is a plot of output voltage V_{out} vs input voltage V_{in3}



SUBTRACTOR OP-AMP

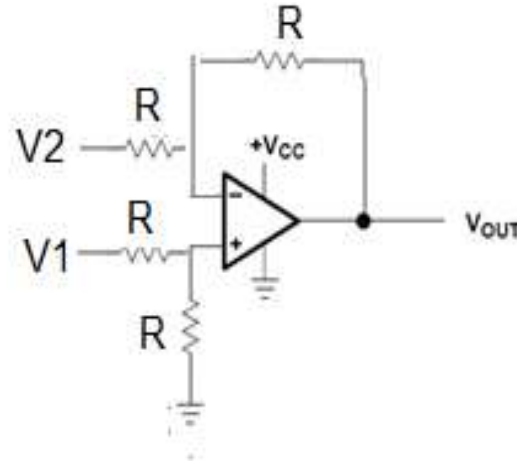

Using Superposition principle:

If V_{o1} is output due to $V1$ alone (making $V2$ grounded), then, input is $V1/2$

for non inv i/p: $V_o = [1+R_f/R_i]V_i$

$$V_{o1} = V1/2 [1+R/R] = V1.$$

Similarly, If V_{o2} is the output for $V2$ alone, then


$$V_{o2} = -(R/R)V2 = -V2.$$

for inv i/p: $V_o = V_i(R_f/R_i)$

Now, $V_o = V_{o1} + V_{o2} = V1 - V2$. Therefore the output is the difference between the inputs.



DIFFERENTIAL OP-AMPLIFIER

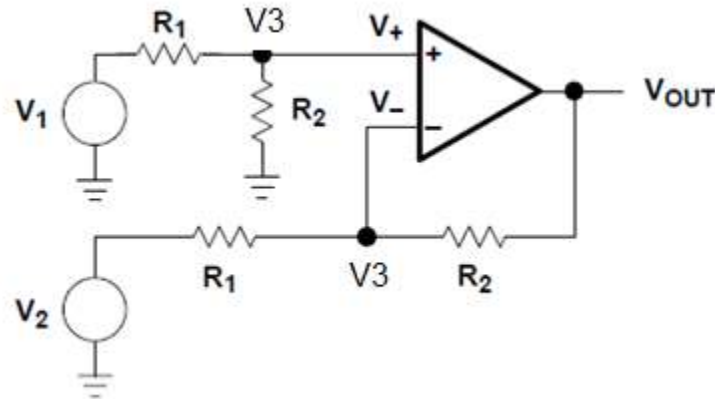

Voltage relations

$$\text{at node 'a': } \frac{V3-V2}{R1} + \frac{V3-Vo}{R2} = 0$$

$$\text{at node 'b': } \frac{V3-V1}{R1} + \frac{V3}{R2} = 0$$

- The purpose of the differential amplifier is to produce an output proportional to the difference of the input voltages
- V_+ is given by the voltage divider equation



DIFFERENTIAL AMPLIFIER

Output voltage

$$V_{OUT2} = V_2 \left(-\frac{R_4}{R_3} \right)$$

$$V_{OUT} = V_1 \frac{R_2}{R_1 + R_2} \left(\frac{R_3 + R_4}{R_3} \right) - V_2 \frac{R_4}{R_3}$$

$$V_O = (V_1 - V_2) \frac{R_2}{R_1}$$

V_{out} as we see is the difference of voltage V_1 & V_2 multiplied by the resistance R_2 & R_1 which scales the difference



RECOLLECT

IC 741.....
Application?

Thank You

