



# **SNS COLLEGE OF TECHNOLOGY**

(An Autonomous Institution)

**COIMBATORE-35**

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



## **LINEAR AND DIGITAL CIRCUITS** **II YEAR / III SEMESTER** **UNIT-I: OPERATIONAL AMPLIFIER**

### **OP-AMP BASICS AND CHARACTERISTICS**



# TOPIC OUTLINE

## What is an Op-Amp?

History

Pin Details IC741

Characteristics of **Ideal** Op-Amps

Characteristics of **Real** Op-Amps


**Basics** of Op-Amp




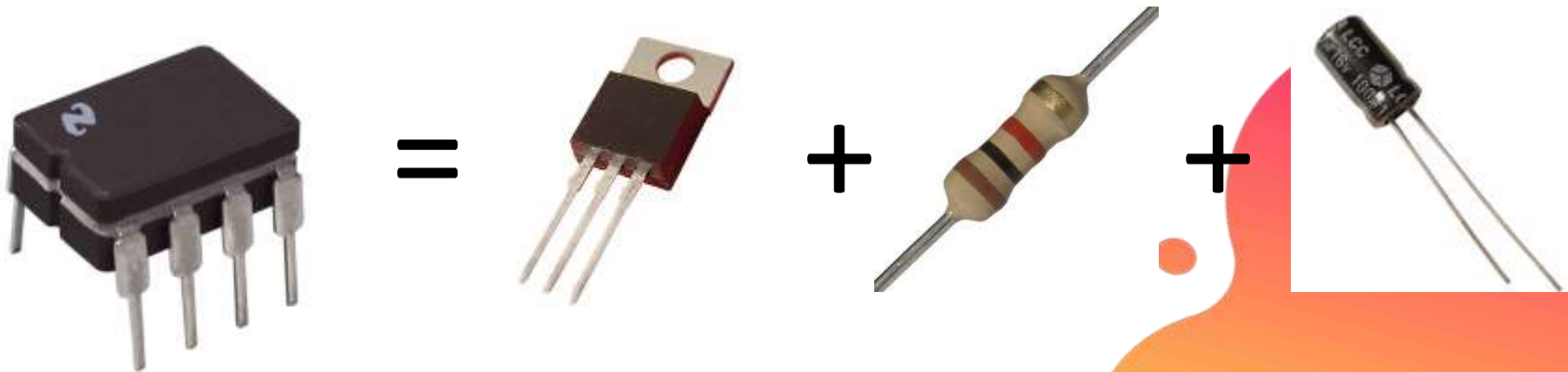
# WHAT IS AN OP-AMP?


- An *Operational Amplifier* (known as an “Op-Amp”) is a device that is used to amplify a signal using an external power source
- Op-Amps are generally composed of:
  - Transistors, Resistors, Capacitors





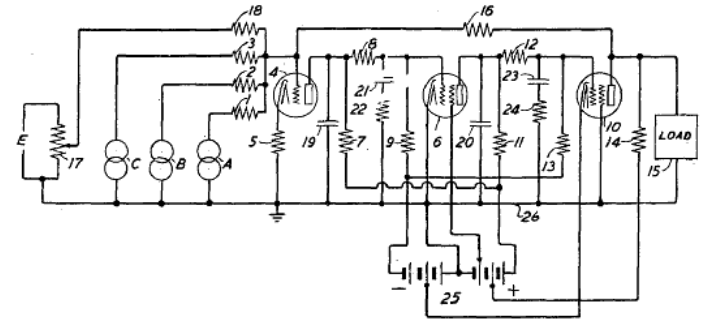
# BRIEF HISTORY


- First patent for Vacuum Tube Op-Amp (1946)



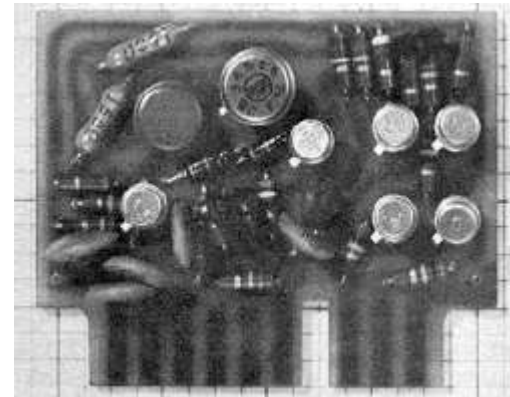- First Commercial Op-Amp available (1953)



- First discrete IC Op-Amps (1961)

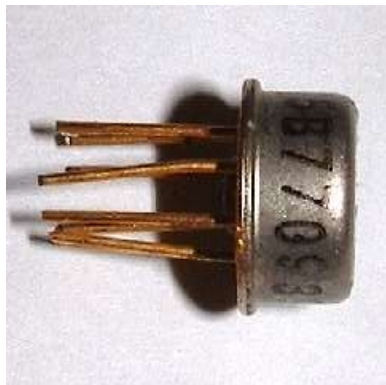


- First commercially successful Monolithic Op-Amps (1965)



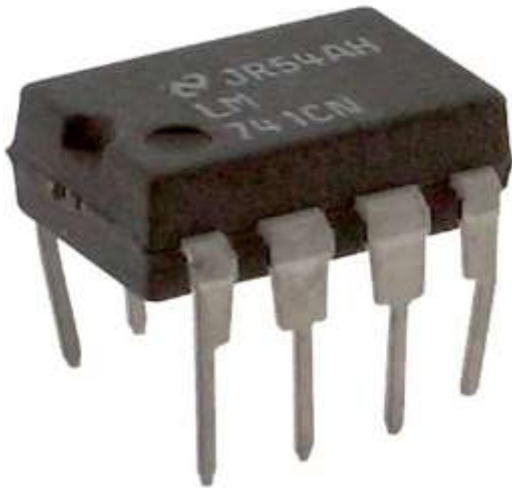
# IC741 – PIN DETAILS

- Leading to the advent of the modern IC which is still used even today (1967 – present)



Fairchild  $\mu$ A741

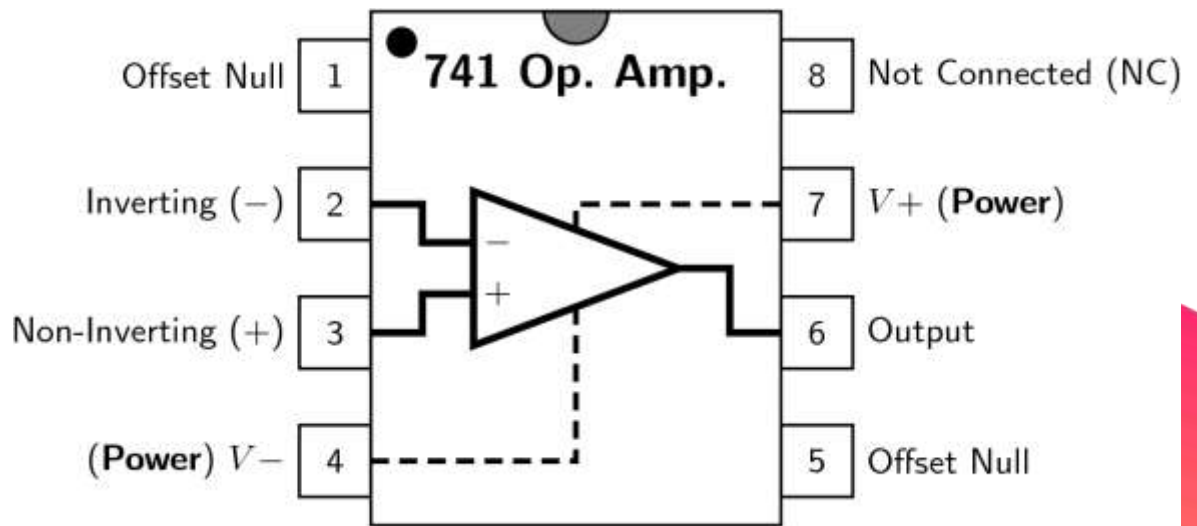

Electrical Schematic of  $\mu$ A741




# AN IDEAL OP-AMP

- Infinite voltage gain
- Infinite input impedance
- Zero output impedance
- Infinite bandwidth
- Zero input offset voltage (i.e., exactly zero out if zero in).




# IDEAL VERSUS REAL OP-AMPS

Parameter	Ideal Op-Amp	Real Op-Amp
Voltage Gain	$\infty$	$10^5 - 10^9$
Gain Bandwidth (Hz)	$\infty$	1-20 MHz
Input Resistance ( $R_i$ )	$\infty$	$10^6 - 10^{12} \Omega$
Output Resistance ( $R_o$ )	0	100 - 1000 $\Omega$

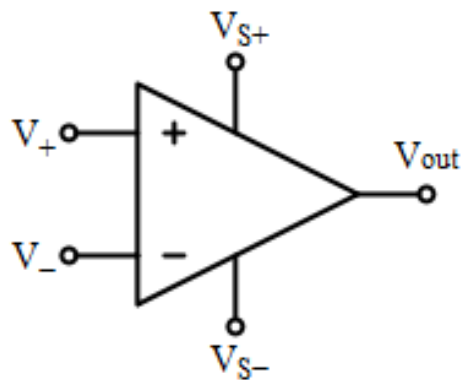

← Ideal

Real →

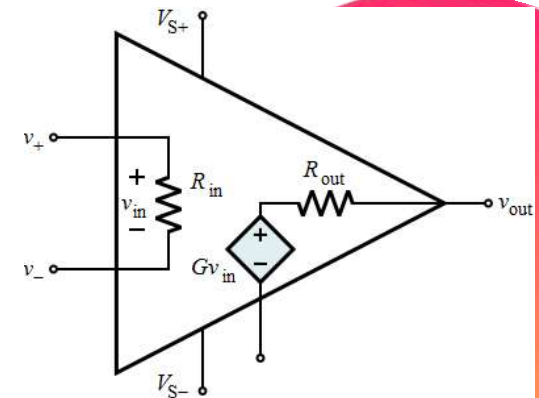



# BASICS OF AN OP-AMP

- An op-amp amplifies the difference of the inputs  $V_+$  and  $V_-$  (known as the differential input voltage)
- This is the equation for an *open loop* gain amplifier:

$$V_{out} = K(V_+ - V_-)$$


- K is typically very large – at around 10,000 or more for IC Op-Amps
- This equation is the basis for all the types of amps we will be discussing





# BASICS OF AN OP-AMP

A traditional Op-Amp:

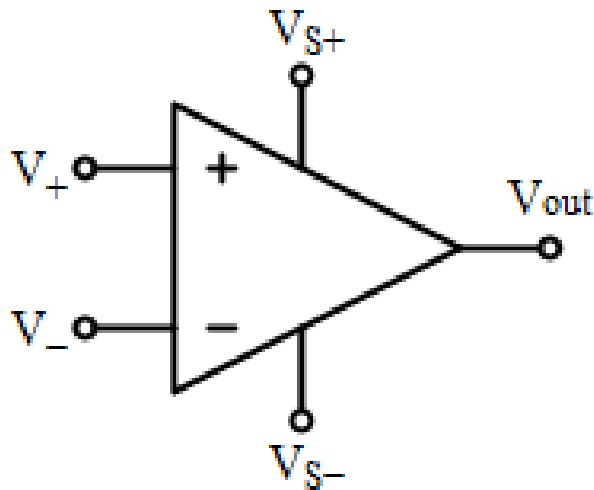

$V_+$  : non-inverting input

$V_-$  : inverting input

$V_{out}$  : output

$V_{S+}$  : positive power supply

$V_{S-}$  : negative power supply


$$V_{out} = K (V_+ - V_-)$$

- The difference between the two inputs voltages ( $V_+$  and  $V_-$ ) multiplied by the gain ( $K$ , “amplification factor”) of the Op-Amp gives you the output voltage
- The output voltage can only be as high as the difference between the power supply ( $V_{S+} / V_{S-}$ ) and ground (0 Volts)



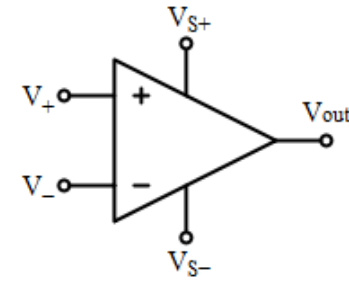
# Saturation

Saturation is caused by increasing/decreasing the input voltage to cause the output voltage to equal the power supply's voltage\*



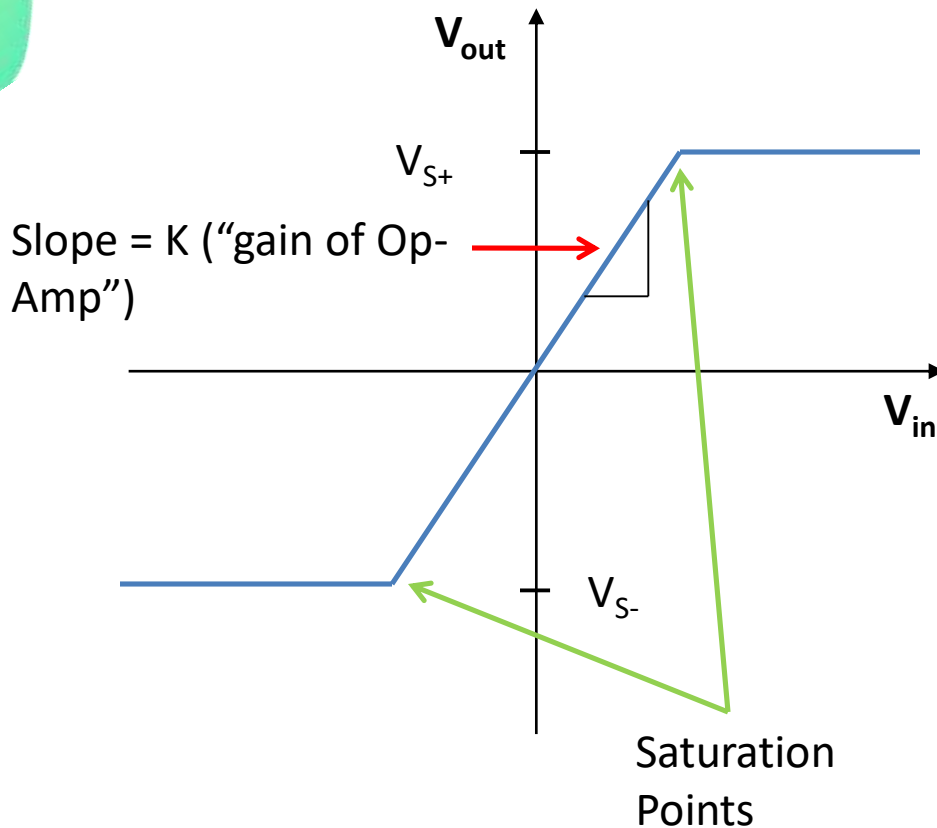The slope is normally much steeper than it is shown here. Potentially just a few millivolts (mV) of change in the difference between  $V_+$  and  $V_-$  could cause the op-amp to reach the saturation level




\* Note that saturation level of traditional Op-Amp is 80% of supply voltage with exception of CMOS op-amp which has a saturation at the power supply's voltage



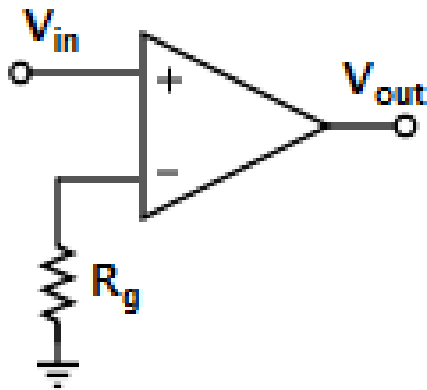
# Open Loop vs Closed Loop

- A closed loop op-amp has feedback from the output to the input, an open loop op-amp does not



Open Loop

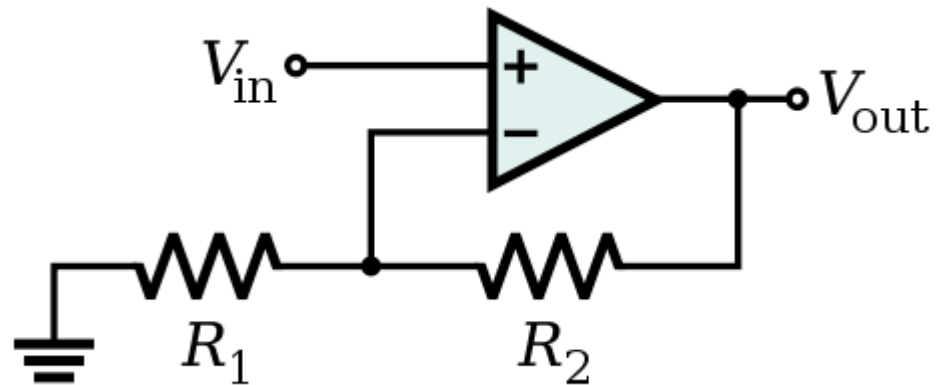

Closed Loop



# THANK YOU

