



SNS COLLEGE OF TECHNOLOGY
(An Autonomous Institution)
COIMBATORE-35



Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

**23EET202 / DIGITAL ELECTRONICS AND LINEAR
INTEGRATED CIRCUITS
II YEAR / III SEMESTER**

**UNIT-III: DESIGN OF SEQUENTIAL CIRCUITS, PLD,
VHDL**

Verilog HDL – PROGRAMMING - 1



TOPIC OUTLINE

VHDL – Types

Basic Gates – programming

Adders – programming

Subtractors – programming

Mux/Demux - programming





HDL

HDL - Hardware Descriptive Language: Describes the behaviour of Digital Circuits

Classified:

1. VHDL: Descriptive and deterministic language used to design digital electronic ICs for Specific applications and automation

Eg: PLD, CPLD, FPGA

2. Verilog HDL: Hardware Modelling language used to model digital electronic IC – For learners, simple as C programming

Eg: Combinational and simple sequential circuits



VHDL - VERILOG®HDL




Types:

1. Structural Module – Gates, HA, FA, HS, FS
2. Data Flow Module – Encoder, decoder, mux, demux
3. Behavioral Module – Counter, Register, FF



AND Gate

 

```
// Module Name:  Andgate  
module Andgate(i1, i2, out);  
    input i1;  
    input i2;  
    output out;  
        and (out,i1,i2);  
endmodule
```

Structural module....




Output

#	AND Gate		
#	-----		
#	Input1	Input2	Output
#	-----		
#	0	0	0
#	0	1	0
#	1	0	0
#	1	1	1
#	-----		




Waveform

 



OR Gate
 
```
// Module Name:  Orgate  
module Orgate(i1, i2, out);  
    input i1;  
    input i2;  
    output out;  
    or(out,i1,i2);  
endmodule
```






Output

#	OR Gate		
#	-----		
#	Input1	Input2	Output
#	-----		
#	0	0	0
#	0	1	1
#	1	0	1
#	1	1	1
#	-----		




Waveform

 



NAND Gate

 

```
// Module Name:  Nandgate  
module Nandgate(i1, i2, out);  
    input i1;  
    input i2;  
    output out;  
    nand(out,i1,i2);  
endmodule
```




Output

#	NAND Gate		
#	-----		
#	Input1	Input2	Output
#	-----		
#	0	0	1
#	0	1	1
#	1	0	1
#	1	1	0
#	-----		




Waveform

 



NOR Gate

 

```
// Module Name:  Norgate  
module Norgate(i1, i2, out);  
    input i1;  
    input i2;  
    output out;  
        nor(out,i1,i2);  
endmodule
```




Output

#	NOR Gate		
#	-----		
#	Input1	Input2	Output
#	-----		
#	0	0	1
#	0	1	0
#	1	0	0
#	1	1	0
#	-----		




Waveform

 



XOR Gate

 

```
// Module Name:  Xorgate  
module Xorgate(i1, i2, out);  
    input i1;  
    input i2;  
    output out;  
    xor(out,i1,i2);  
endmodule
```




Output

#	XOR Gate		
#	-----		
#	Input1	Input2	Output
#	-----		
#	0	0	0
#	0	1	1
#	1	0	1
#	1	1	0
#	-----		




Waveform

 



XNOR Gate

 

```
// Module Name: Xnorgate  
module Xnorgate(i1, i2, out);  
    input i1;  
    input i2;  
    output out;  
    xnor(out,i1,i2);  
endmodule
```




Output

#	XNOR Gate		
#	-----		
#	Input1	Input2	Output
#	-----		
#	0	0	1
#	0	1	0
#	1	0	0
#	1	1	1
#	-----		




Waveform

 



NOT Gate

 

```
// Module Name: Notgate  
module Notgate(in, out);  
    input in;  
    output out;  
    not(out,in);  
endmodule
```




Output

#	NOT Gate	
#	-----	
#	Input	Output
#	-----	
#	0	1
#	1	0
#	-----	




Waveform

 



Buffer

 

```
// Module Name: Buffer
module Buffer(in, out);
    input in;
    output out;
    buf(out,in);
endmodule
```




Output

#	BUFFER	
#	-----	
#	Input	Output
#	-----	
#	0	0
#	1	1
#	-----	



Waveform

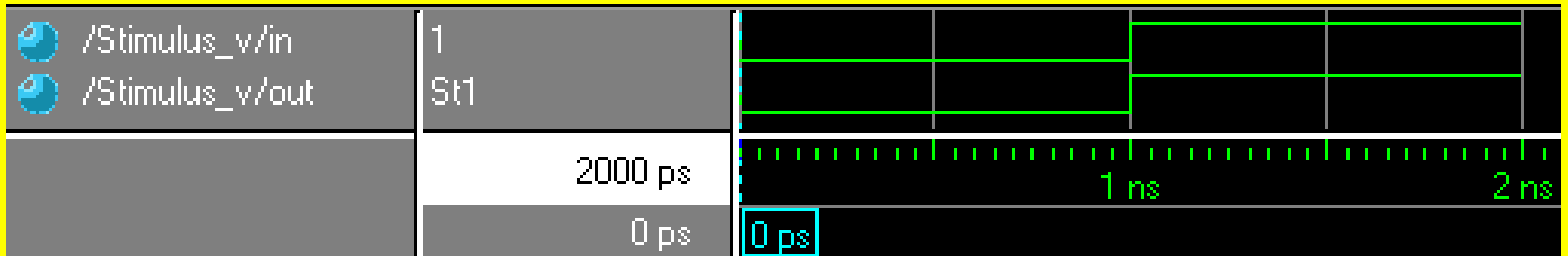



RECAP..



Thank You