



SNS COLLEGE OF TECHNOLOGY

(AN AUTONOMOUS INSTITUTION)

Approved by AICTE & Affiliated to Anna University
Accredited by NBA & Accredited by NAAC with 'A+' Grade,
Recognized by UGC saravanampatti (post), Coimbatore-641035.



Department of Biomedical Engineering

Course Name: 23BMT201 & Circuit Analysis

II Year : III Semester

Unit III -THREE PHASE SYSTEM

Topic : Phasor relationship for R, L, and C,



Resistive Load







- Phasor Diagram: shows the instantaneous phase of either voltage or current.
- For a resistor, the current follows the voltage, so the voltage and current are in phase ($\phi = 0$).

• If

$$v_R = V_R \sin \omega_d t$$

• Then
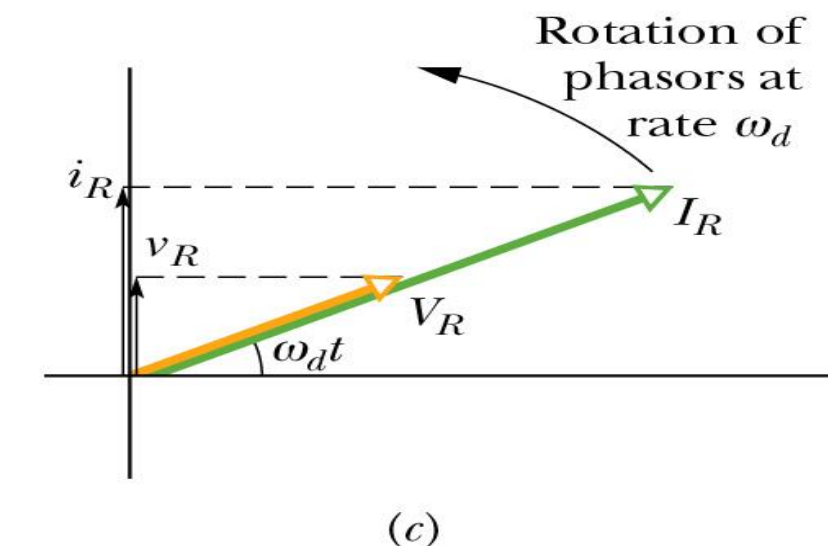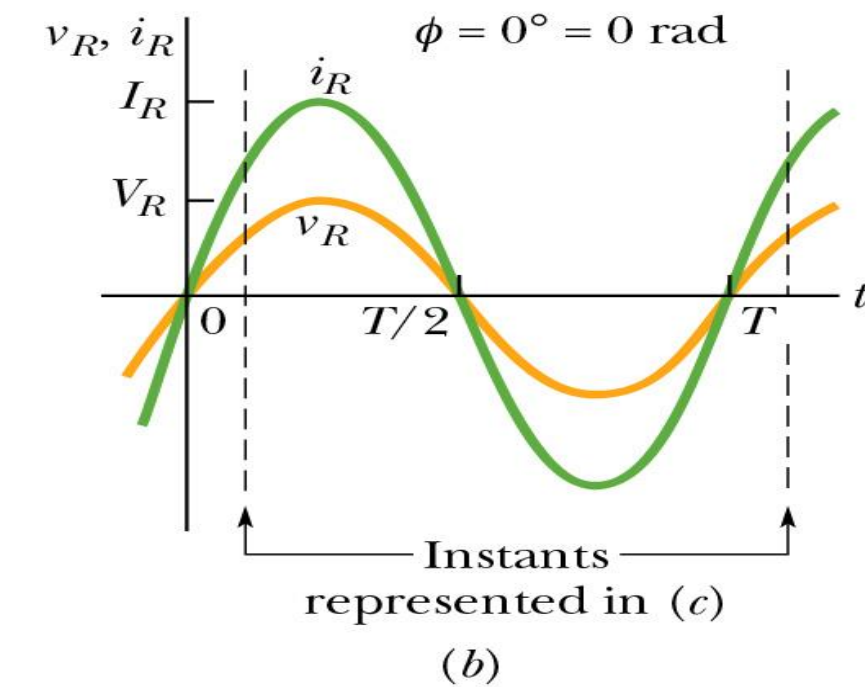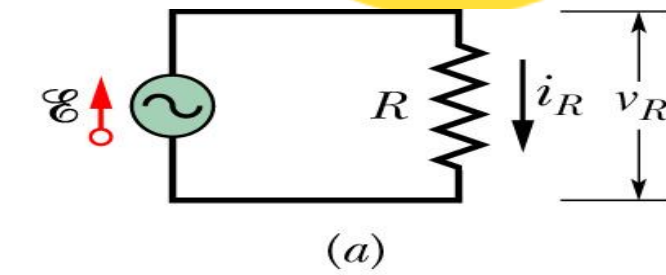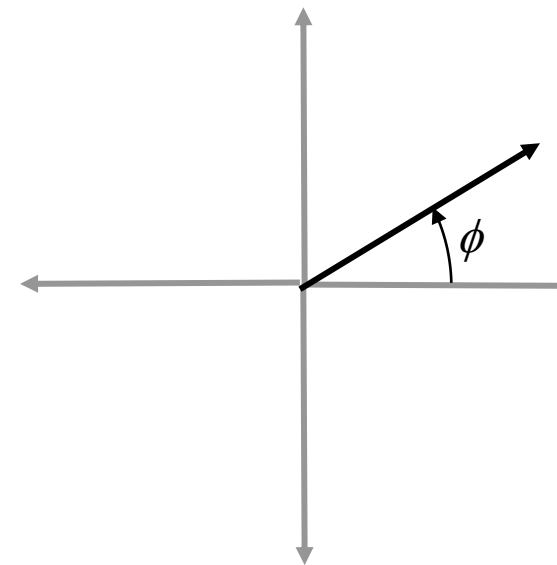
$$i_R = I_R \sin \omega_d t = \frac{V_R}{R} \sin \omega_d t$$





Capacitive Load

- For a capacitive load, the voltage across the capacitor is proportional to the charge

$$v_C = \frac{q}{C} = \frac{Q}{C} \sin \omega_d t$$

- But the current is the time derivative of the charge




$$i_C = \frac{dq}{dt} = \omega_d C V_C \cos \omega_d t$$

- In analogy to the resistance, which is the proportionality constant between current and voltage, we define the “capacitive reactance” as

$$X_C = \frac{1}{\omega_d C}$$

- So,
$$i_C = \frac{V_C}{X_C} \cos \omega_d t$$

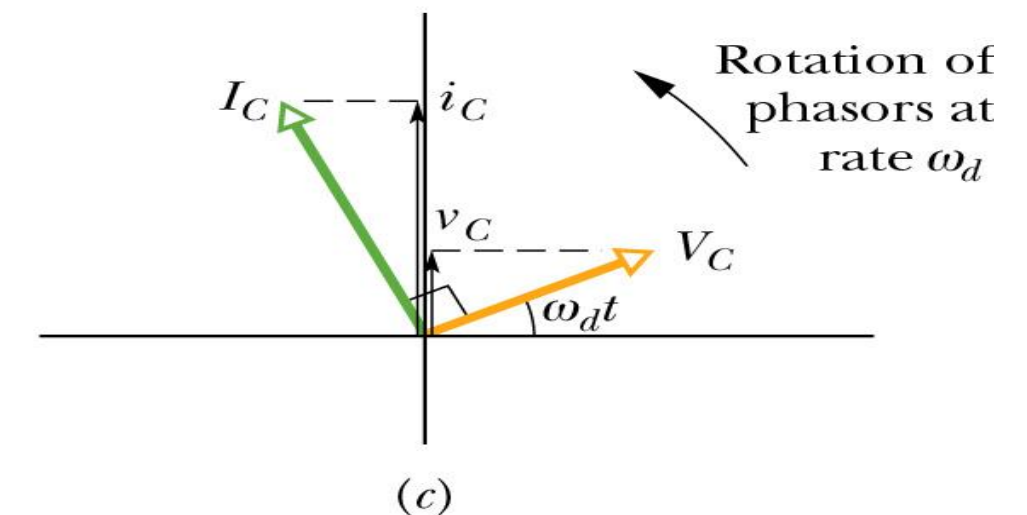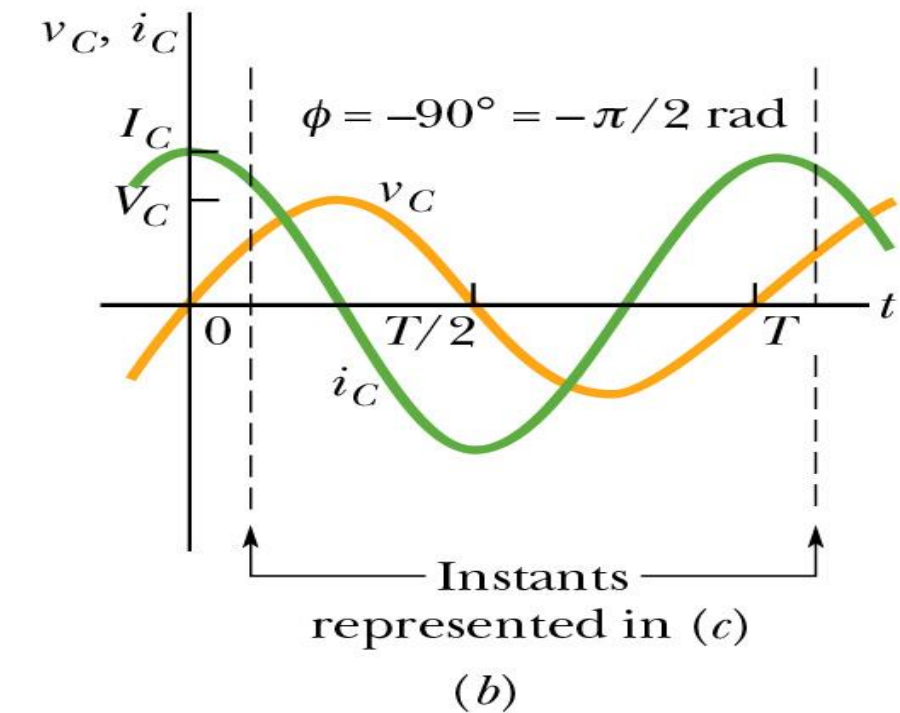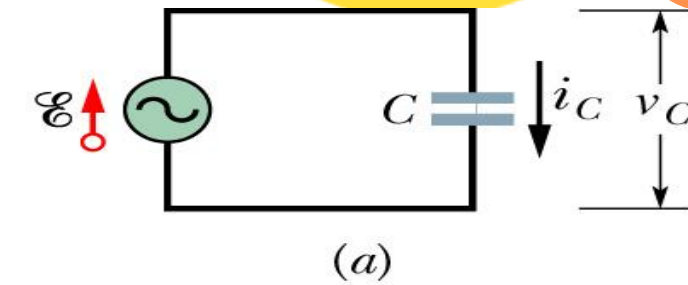- The phase relationship is that $\phi = -90^\circ$, and current leads voltage.





Inductive Load

- For an inductive load, the voltage across the inductor is proportional to the time derivative of the current

$$v_L = L \frac{di_L}{dt}$$

- But the current is the time derivative of the charge




$$i_L = \frac{V_L}{L} \int \sin \omega_d t dt = -\left(\frac{V_L}{\omega_d L}\right) \cos \omega_d t$$

- Again in analogy to the resistance, which is the proportionality constant between current and voltage, we define the “inductive reactance” as

$$X_L = \omega_d L$$

- So, $i_L = -\frac{V_L}{X_L} \cos \omega_d t$

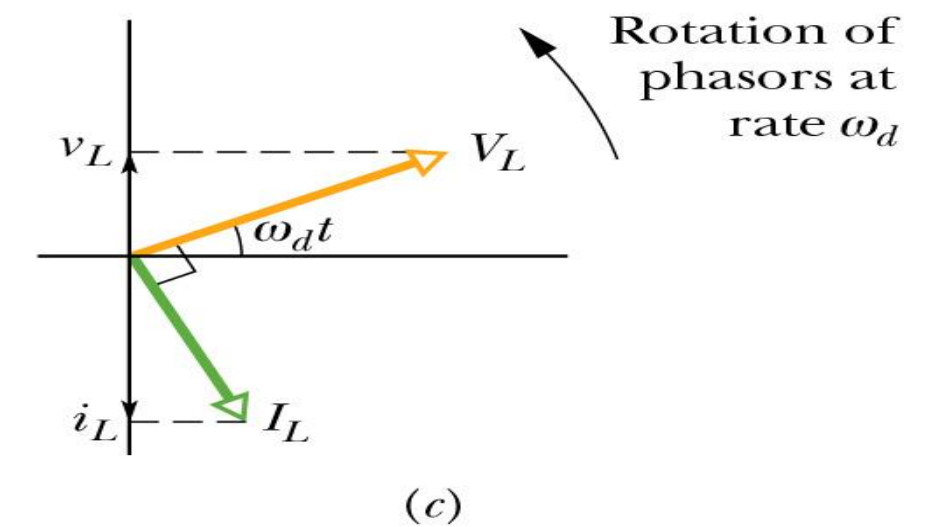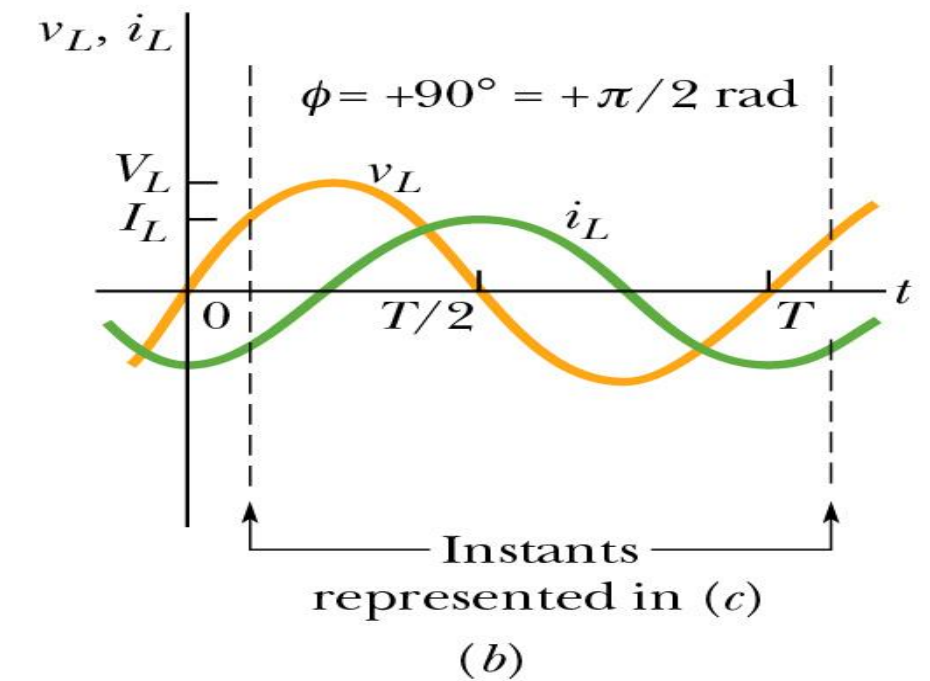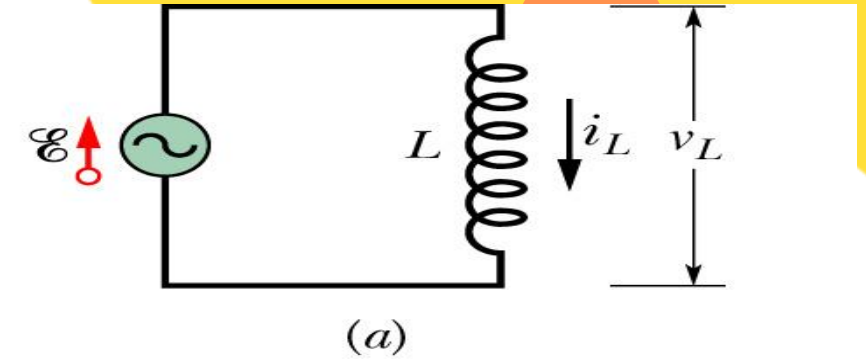- The phase relationship is that $\phi = +90^\circ$, and current lags voltage.





Inductive Load

| Circuit Element | Symbol | Resistance or Reactance | Phase of Current | Phase Constant | Amplitude Relation |
|-----------------|--------|-------------------------|---------------------------|--------------------|--------------------|
| Resistor | R | R | In phase with v_R | 0° (0 rad) | $V_R = I_R R$ |
| Capacitor | C | $X_C = 1/w_d C$ | Leads v_R by 90° | -90° (-p/2) | $V_C = I_C X_C$ |
| Inductor | L | $X_L = w_d L$ | Lags v_R by 90° | $+90^\circ$ (p/2) | $V_L = I_L X_L$ |