



SNS COLLEGE OF TECHNOLOGY

(AN AUTONOMOUS INSTITUTION)

Approved by AICTE & Affiliated to Anna University
Accredited by NBA & Accredited by NAAC with 'A+' Grade,
Recognized by UGC saravanampatti (post), Coimbatore-641035.



Department of Biomedical Engineering

Course Name: 23BMT201 & Circuit Analysis

II Year : III Semester

Unit III -THREE PHASE SYSTEM

Topic : Power Flow Analysis



Balanced Three-phase System



Possible Three-Phase Load Configurations:

- Depending on the end application, a three-phase load can be either
 - Wye-connected (or)
 - Delta-connected.
- A **balanced load** is one in which the **phase impedances are equal in magnitude and in phase**.
- However, a wye- or delta-connected load is said to be unbalanced if the phase impedances are not equal in magnitude or phase.

Vision Title 3




Balanced Three-phase System

Possible Three-Phase Load Configurations:

For a balanced wye-connected load,

$$Z_1 = Z_2 = Z_3 = Z_Y$$

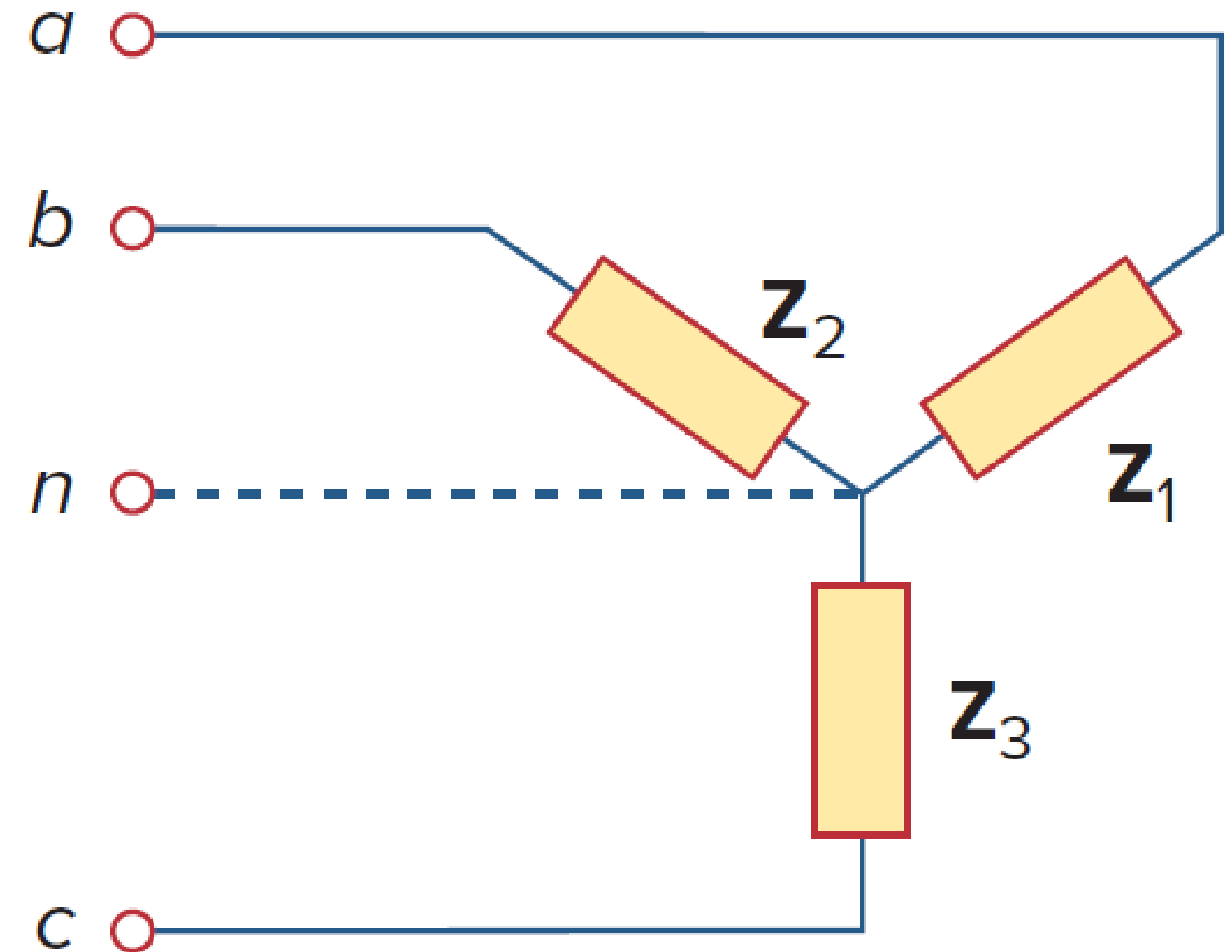where Z_Y is the load impedance per phase.





Balanced Three-phase System



Possible Three-Phase Load Configurations:


For a balanced delta-connected load,

$$Z_a = Z_b = Z_c = Z_{\Delta}$$

where Z_{Δ} is the load impedance per phase.

Impedance relation between Y and Δ connected load:
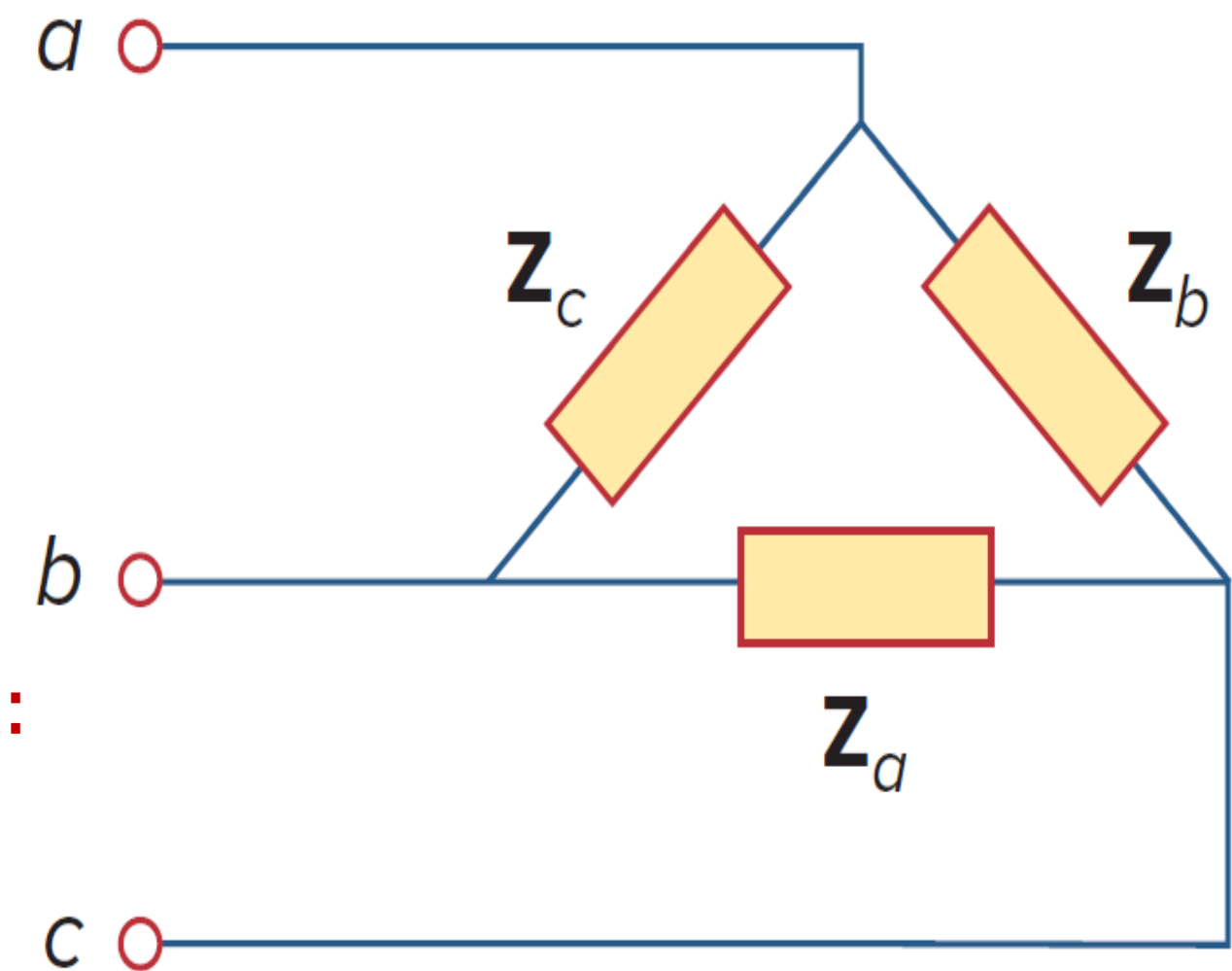
$$Z_{\Delta} = 3 \times Z_Y \text{ or } Z_Y = \frac{1}{3} \times Z_{\Delta}$$



Δ -connected load



Balanced Three-phase System



Possible Three-Phase Load Configurations:


For a balanced delta-connected load,

$$Z_a = Z_b = Z_c = Z_{\Delta}$$

where Z_{Δ} is the load impedance per phase.

Impedance relation between Y and Δ connected load:
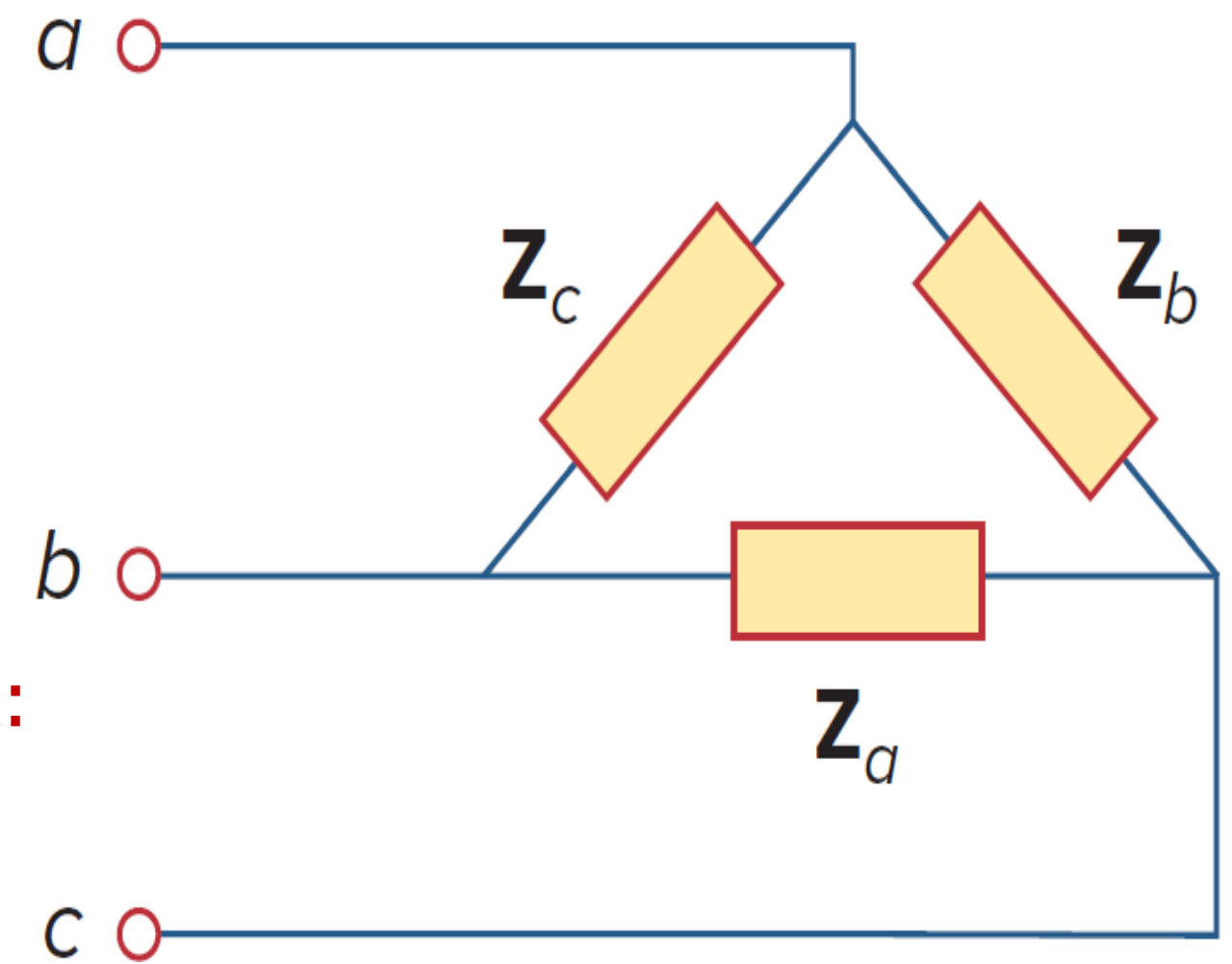
$$Z_{\Delta} = 3 \times Z_Y \text{ or } Z_Y = \frac{1}{3} \times Z_{\Delta}$$



Δ -connected load




Balanced Three-phase System



Balanced Wye-Wye Connection:

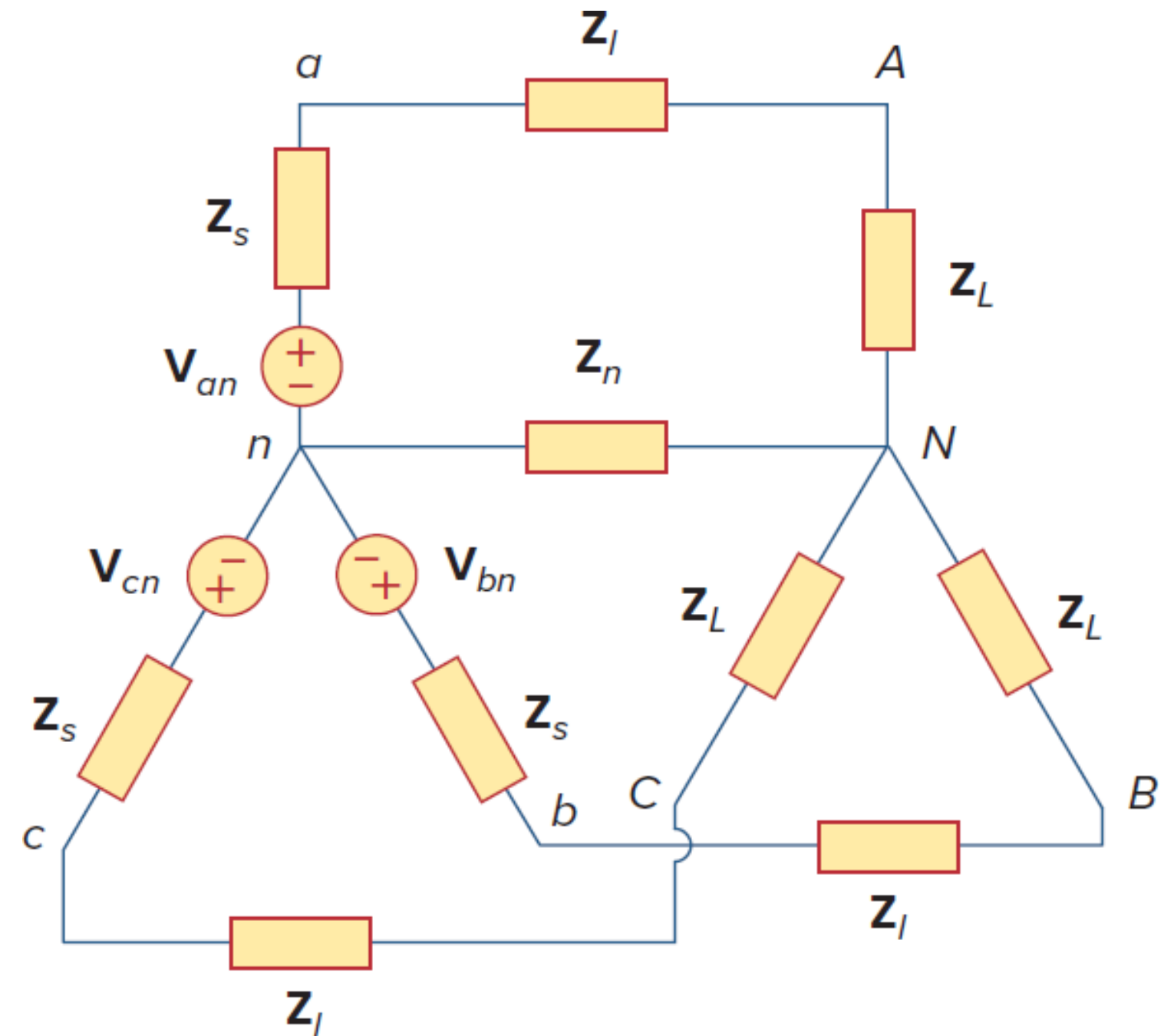A balanced Y-Y system is a three-phase system with a balanced Y-connected source and a balanced Y-connected load.



A balanced Y-Y system, showing the source, line, and load impedances




Balanced Three-phase System



Balanced Wye-Wye Connection:

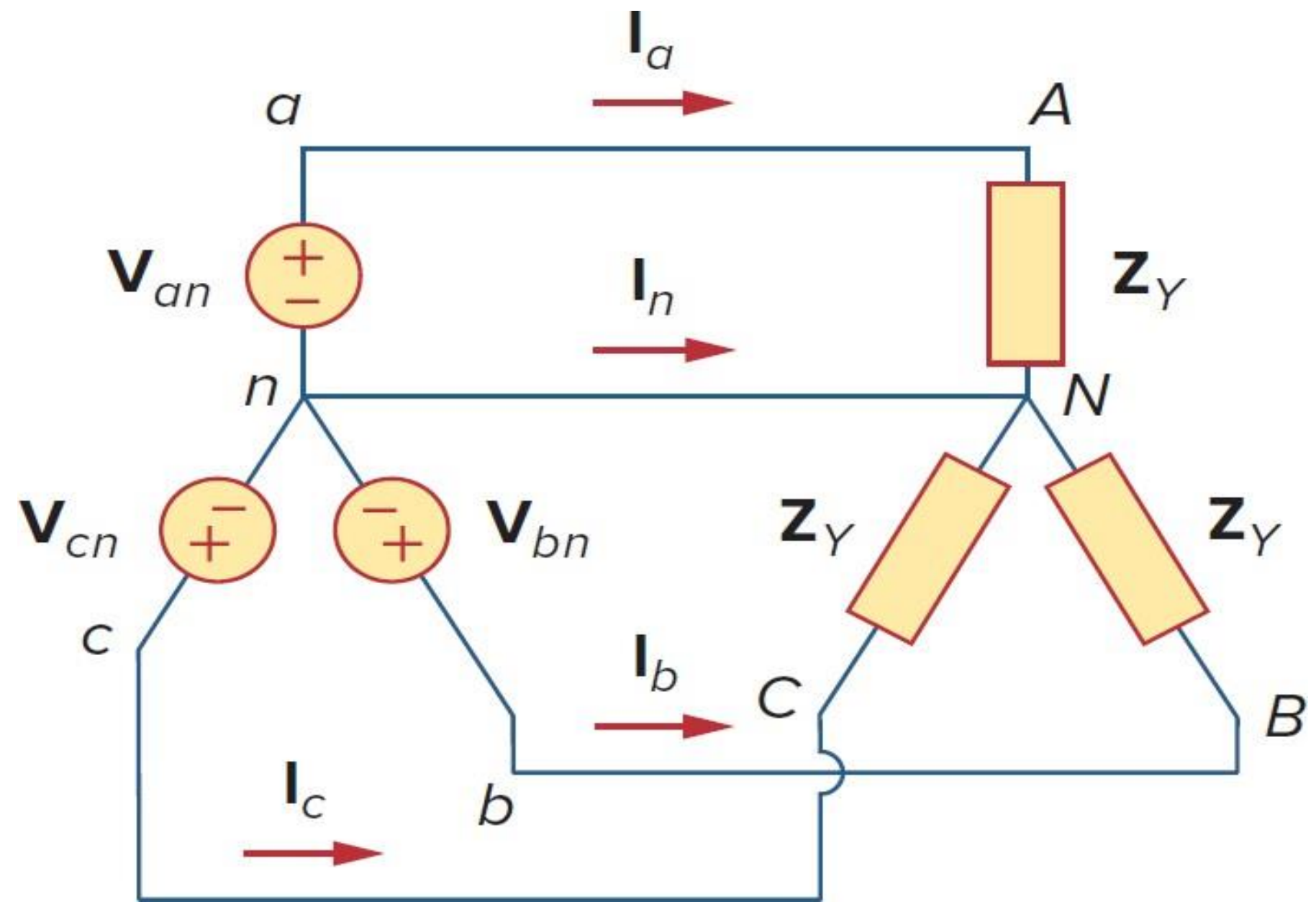- By lumping the impedances together,
$$Z_Y = Z_S + Z_l + Z_L$$
- Z_S and Z_l are often very small compared with Z_L , so one can assume that $Z_Y = Z_L$ if no source or line impedance is given.



Balanced Y-Y connection with $Z_Y = Z_S + Z_l + Z_L$



Balanced Three-phase System


Balanced Wye-Wye Connection:

Assuming the positive sequence, the phase voltages (or line-to neutral voltages) are,

$$V_{an} = V_p \angle 0^\circ, \quad V_{bn} = V_p \angle -120^\circ, \quad V_{cn} = V_p \angle +120^\circ$$

The line-to-line voltages or simply line voltages V_{ab} , V_{bc} , and V_{ca} are related to the phase voltages as,
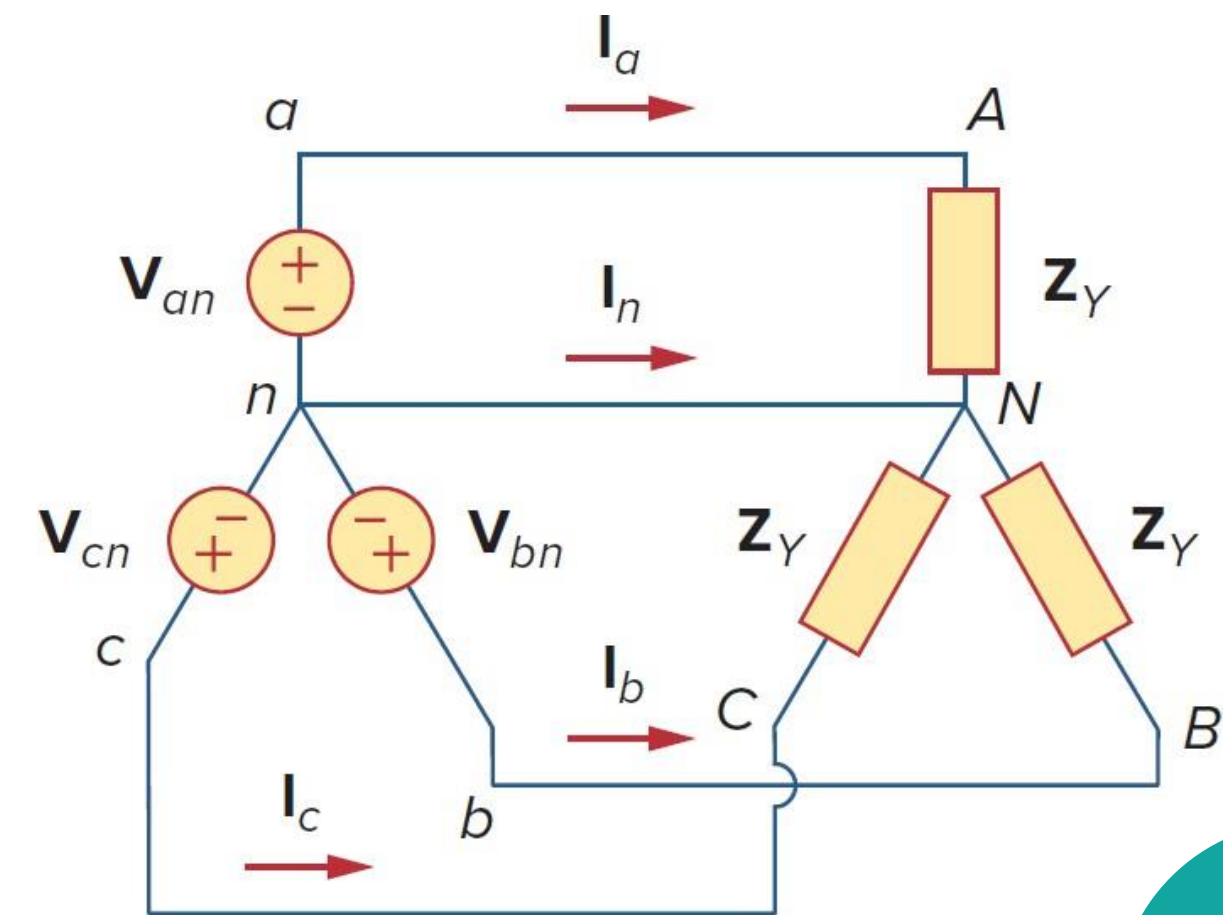
$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} = V_{an} - V_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ \\ &= V_p \left(1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \angle 30^\circ \end{aligned}$$





Balanced Three-phase System

Balanced Wye-Wye Connection:

Similarly, one can obtain:

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3}V_p \angle -90^\circ$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3}V_p \angle -210^\circ$$


Thus, the magnitude of the line voltages is,

$$V_L = \sqrt{3}V_p$$

where

$$V_p = |V_{an}| = |V_{bn}| = |V_{cn}| \text{ and}$$

$$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}|$$

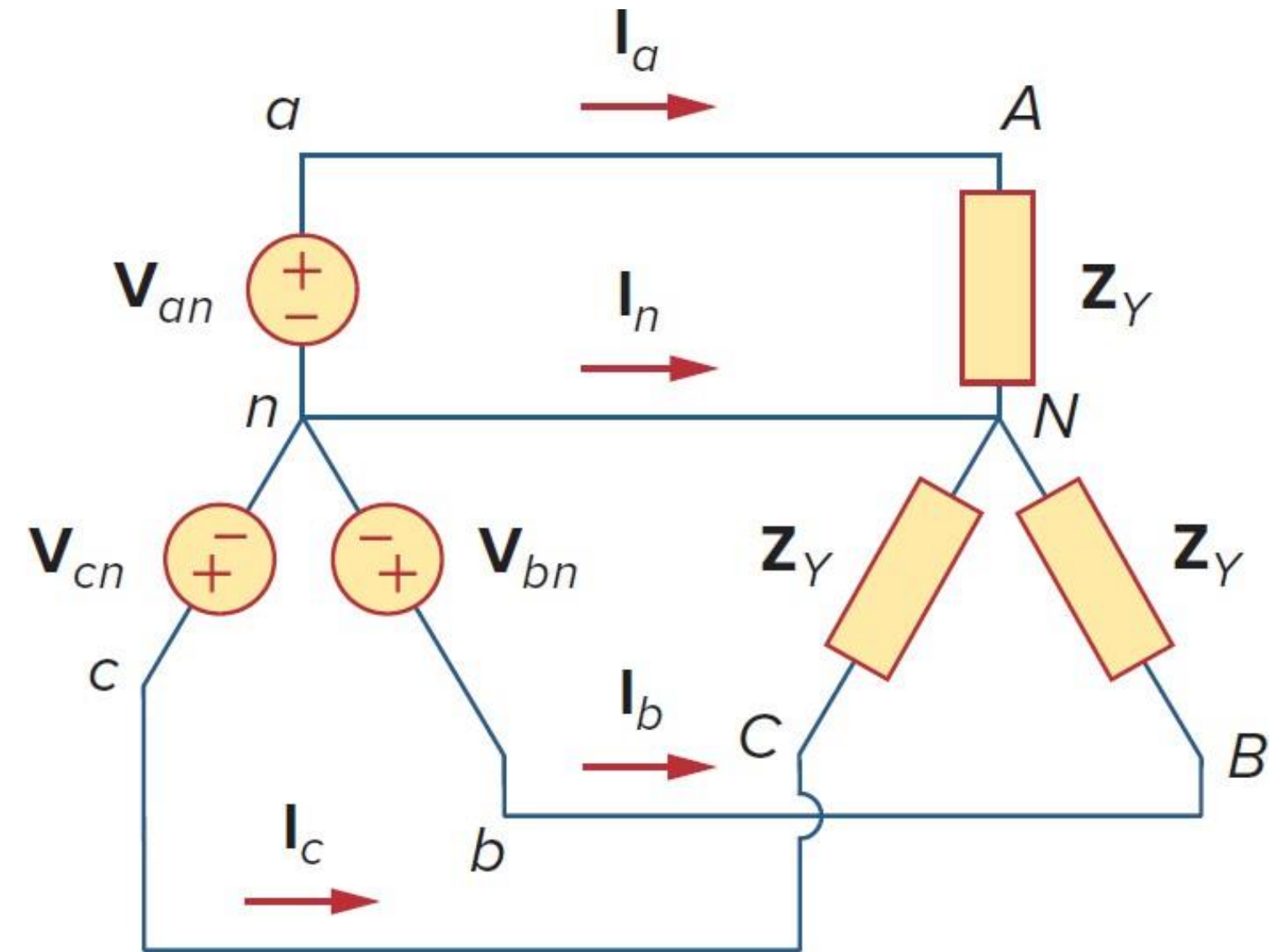




Balanced Three-phase System



Balanced Wye-Wye Connection:

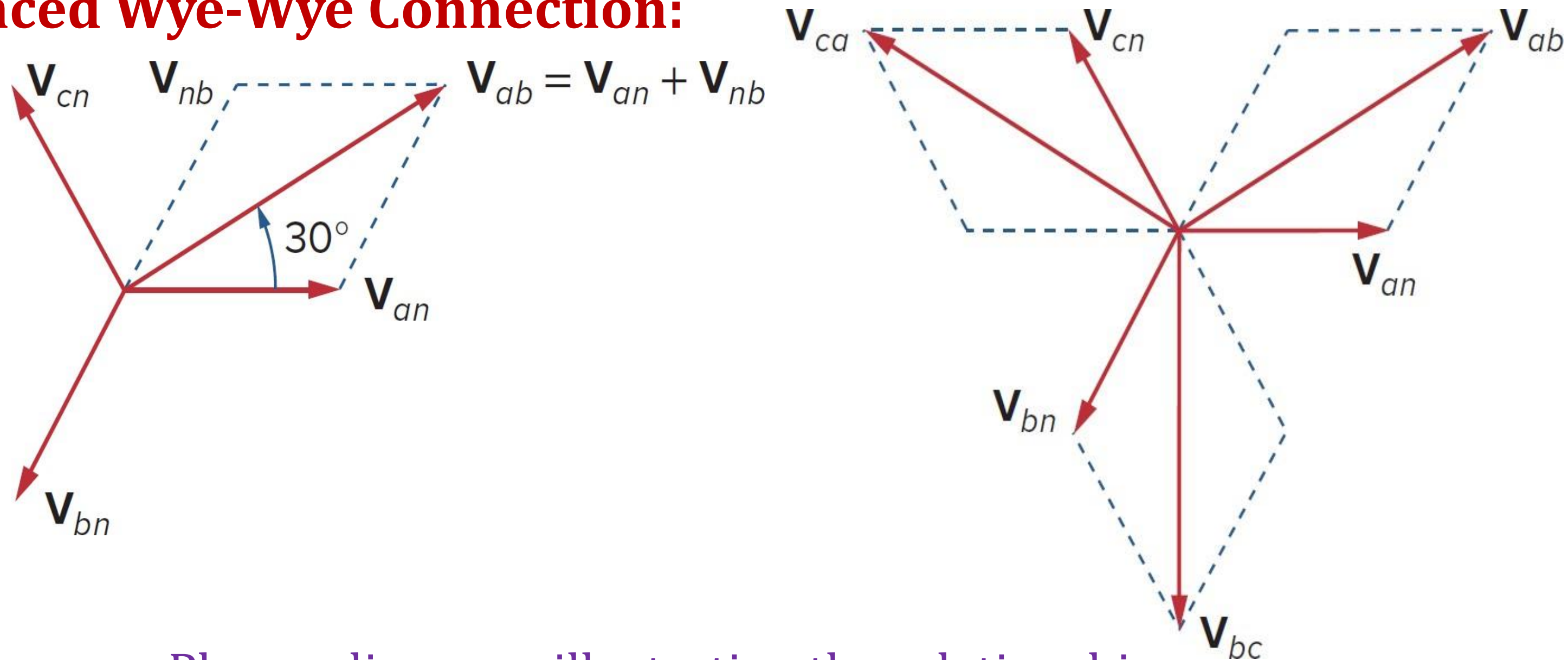

Phasor diagrams illustrating the relationship between line voltages and phase voltages



Balanced Three-phase System




Balanced Wye-Wye Connection:

By applying KVL to each phase, line currents are obtained:

$$I_a = \frac{V_{an}}{Z_Y}$$

$$I_b = \frac{V_{bn}}{Z_Y} = \frac{V_{an} \angle -120^\circ}{Z_Y} = I_a \angle -120^\circ$$
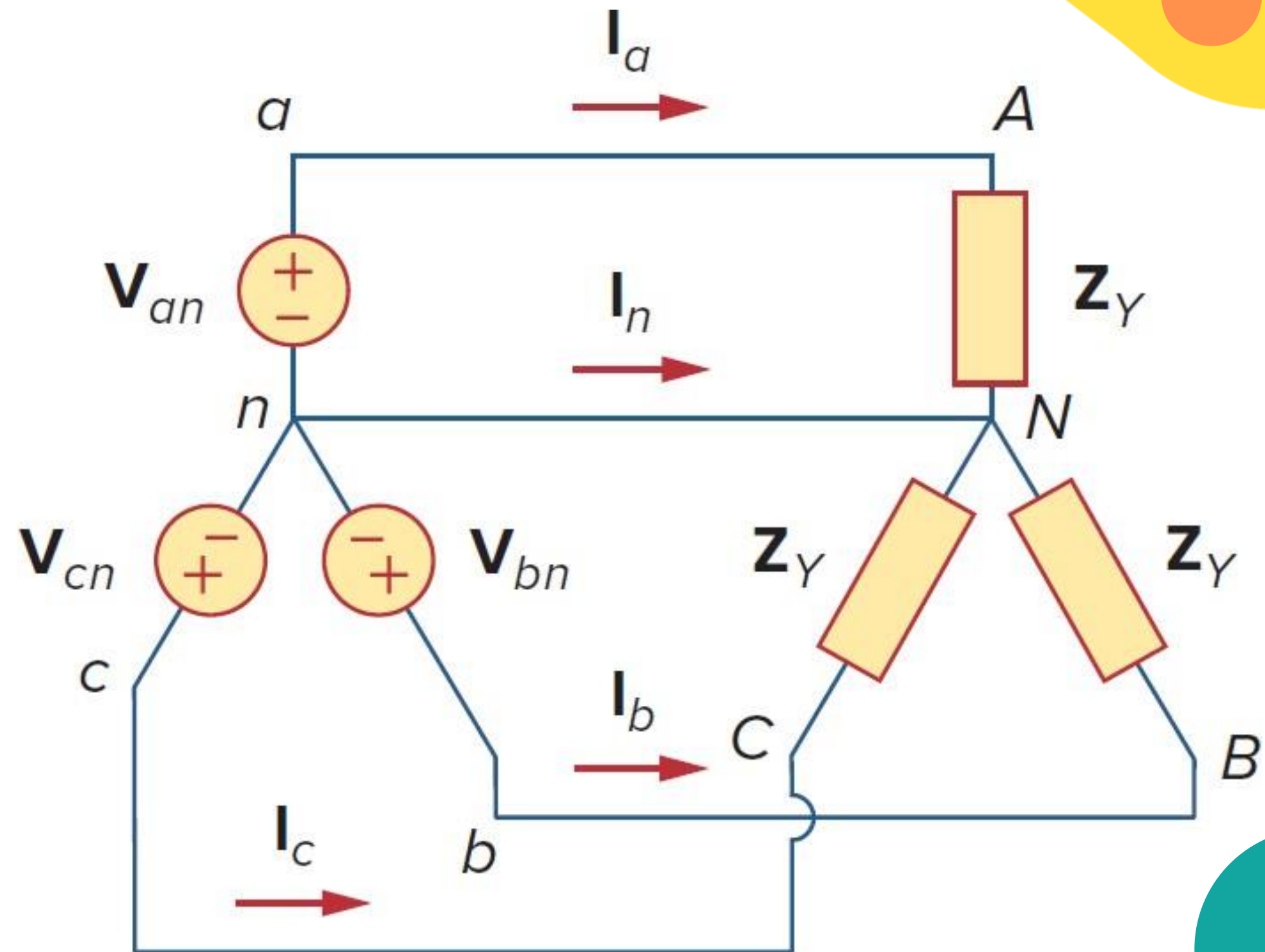
$$I_c = \frac{V_{cn}}{Z_Y} = \frac{V_{an} \angle -240^\circ}{Z_Y} = I_a \angle -240^\circ$$



Balanced Y-Y connection



Balanced Three-phase System



Balanced Wye-Wye Connection:


Now, one can readily infer that the line currents add up to zero,

$$I_a + I_b + I_c = 0$$

Therefore,

$$I_n = -(I_a + I_b + I_c) = 0 \quad (\text{or})$$

$$V_{nN} = Z_n I_n = 0$$

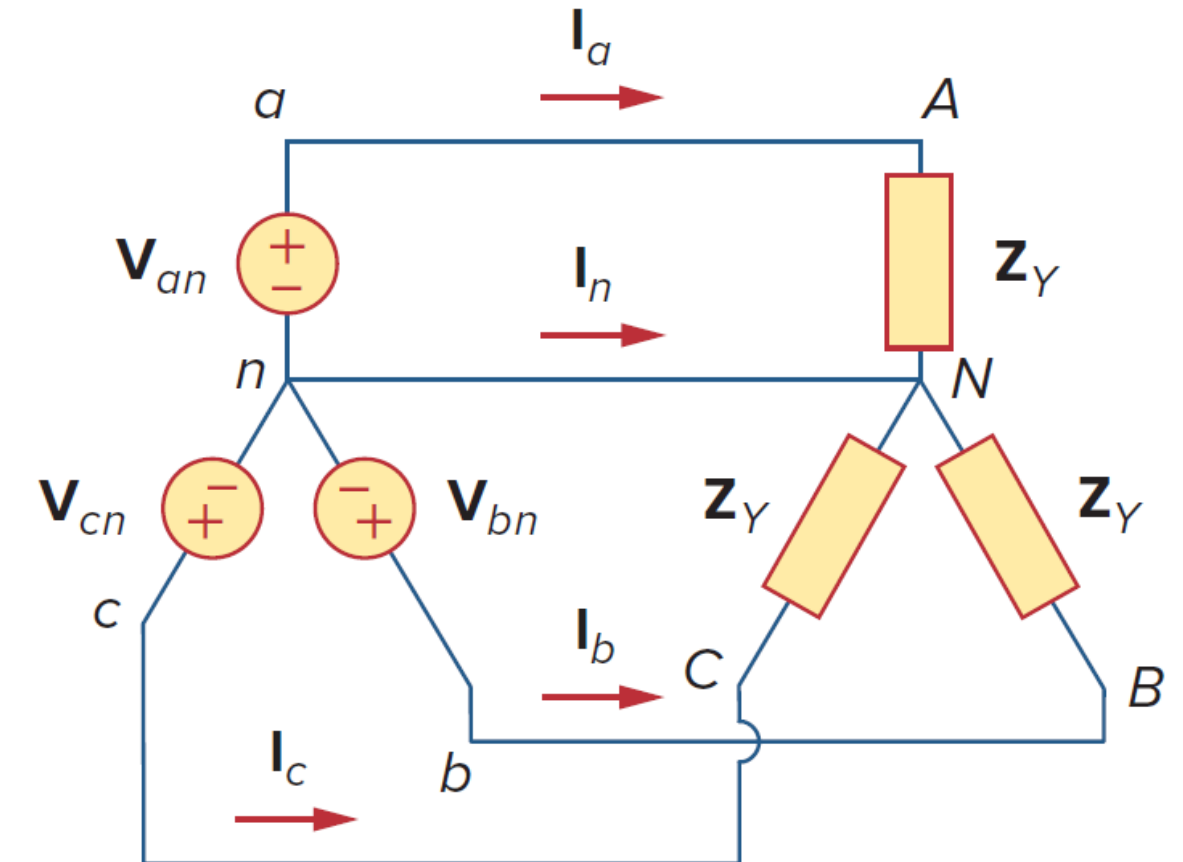

- The **line current** is the current in each line, the **phase current** is the current in each phase of the source or load.
- In the Y-Y system, the **line current is the same as the phase current.**