



SNS COLLEGE OF TECHNOLOGY

(AN AUTONOMOUS INSTITUTION)

Approved by AICTE & Affiliated to Anna University
Accredited by NBA & Accredited by NAAC with 'A+' Grade,
Recognized by UGC saravanampatti (post), Coimbatore-641035.



Department of Biomedical Engineering

Course Name: 23BMT201 & Circuit Analysis

I Year : II Semester

Unit IV –TRANSIENT RESPONSE FOR DC AND AC CIRCUITS


Topic : Step Response of RL Circuits



Real Life Applications – Photo Flash



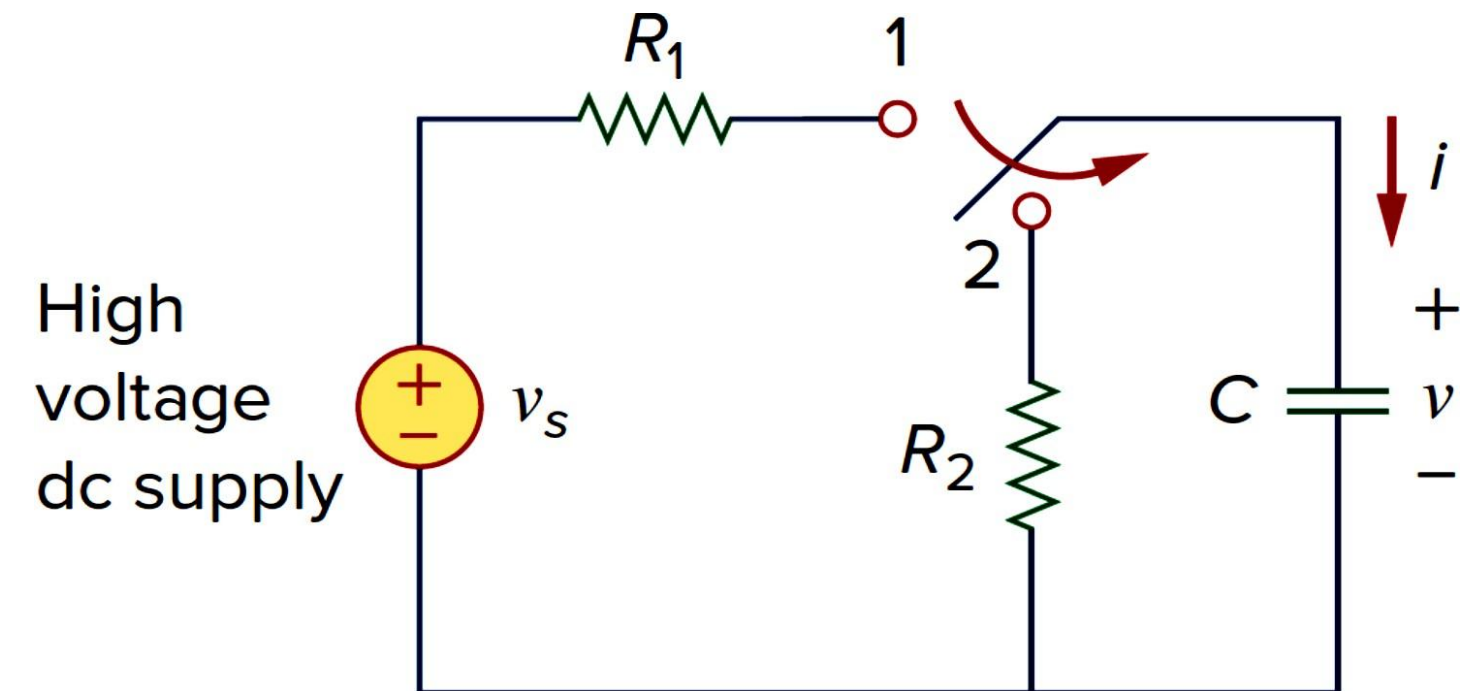Digital Camera Flash Light utilizes a RC circuit to create a short duration high current pulse to energize the flash light.



Circuit for a flash unit providing slow charge in position 1 and fast discharge in position 2 ($R_1 \gg R_2$).





Real Life Applications – Relay Circuits



Vision Title 3

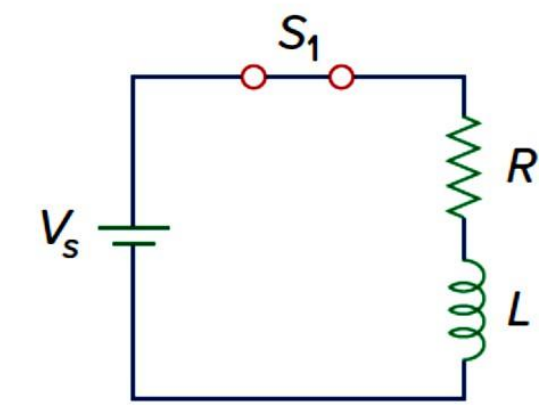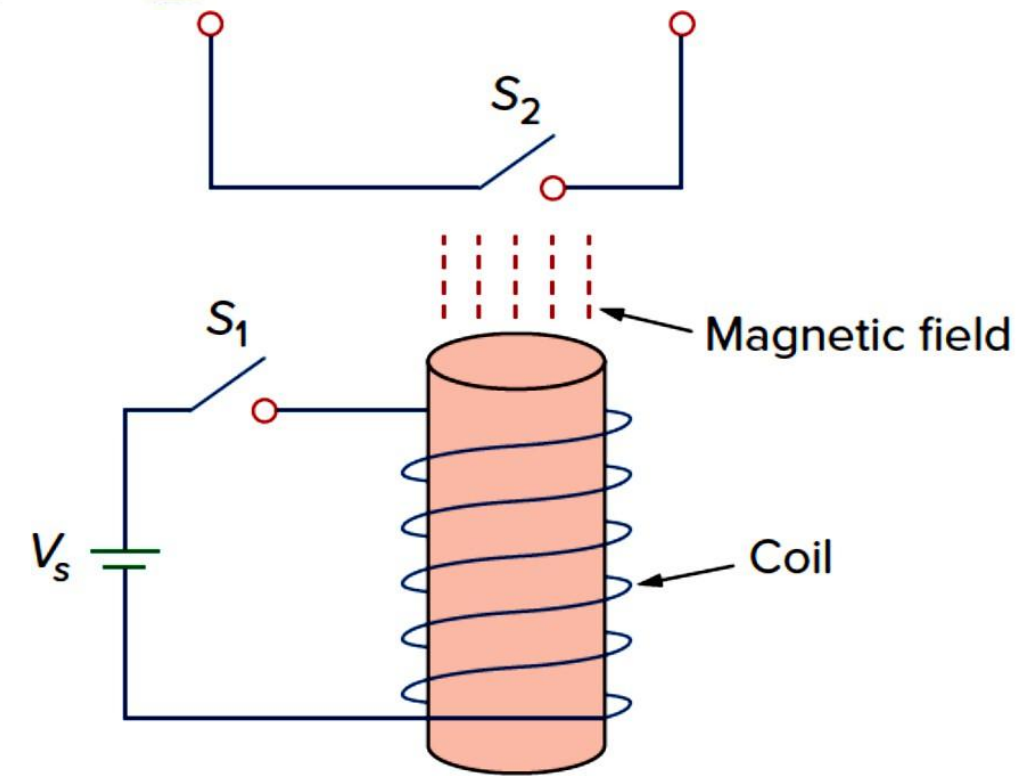
Relay coil is nothing but an RL circuit used to control the switching of another circuit






Step Response of an RL Circuit

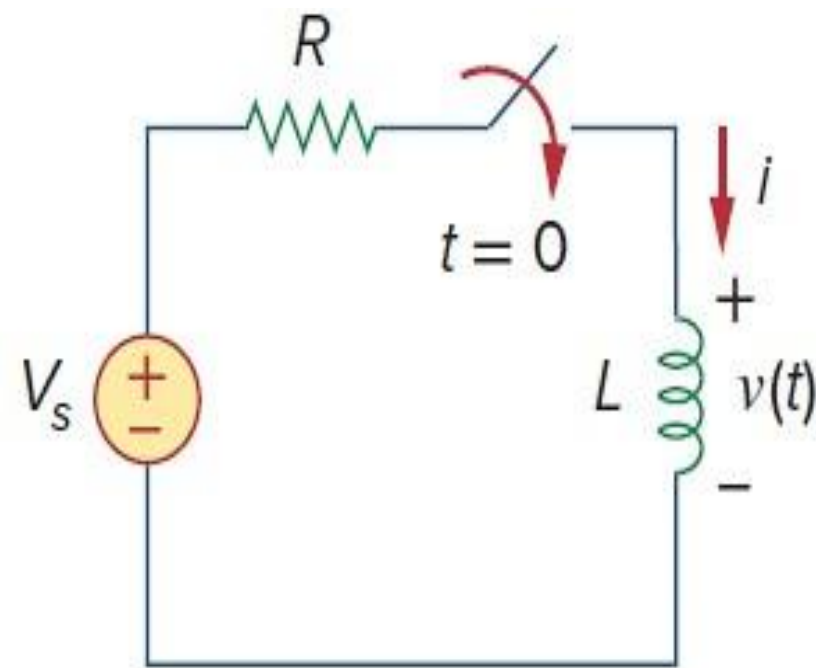When a DC source is suddenly turned on, the source voltage or current can be modelled as a step function



(a)

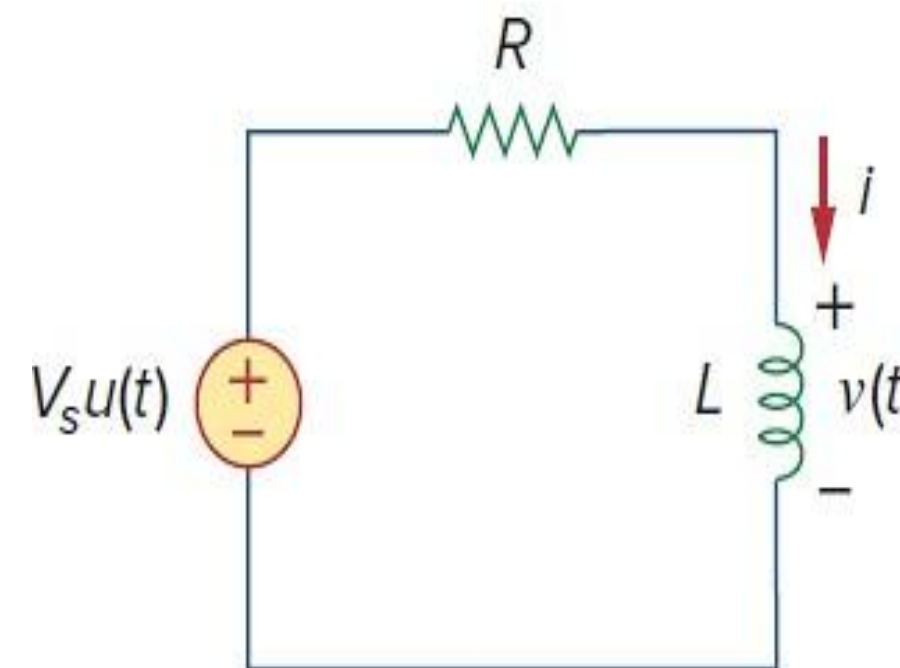

(b)

Vision Title 3


Analysis: The response is the sum of the transient response and the steady-state response, $i = i_t + i_{ss}$



Step Response of an RL Circuit

- Transient response is always a decaying exponential,
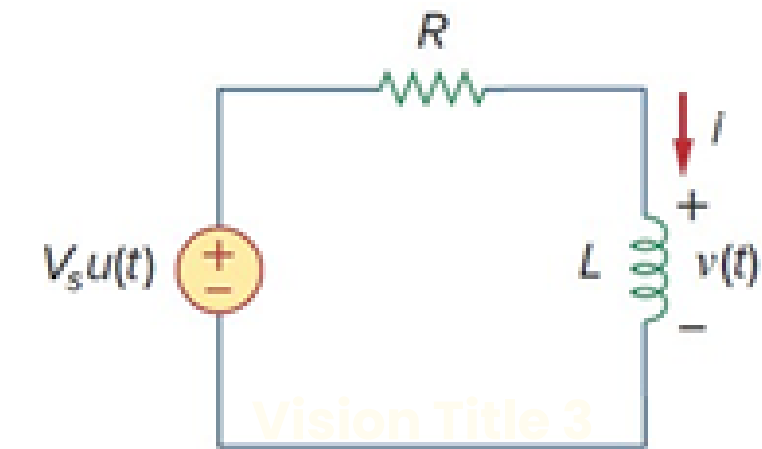
$$i_t = Ae^{-\frac{t}{\tau}}; \tau = \frac{L}{R}$$



- The steady-state response is the value of the current a long time after the switch is closed (practically after ~ 5 time constants).
- The transient response essentially dies out after $\sim 5\tau$ and the inductor effectively becomes a short circuit (voltage across it is zero).
- The entire source voltage V_s appears across R . Thus, the steady-state response is

$$i_{ss} = \frac{V_s}{R}; i = Ae^{-\frac{t}{\tau}} + \frac{V_s}{R}$$



Step Response of an RL Circuit

- Determine the constant A from the initial value of i .
- Let I_0 be the initial current through the inductor.

$$i(0^+) = i(0^-) = I_0$$

$$\text{At } t = 0, I_0 = A + \frac{V_s}{R}$$

$$A = I_0 - \frac{V_s}{R}$$


On substitution,

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R}\right)e^{-\frac{t}{\tau}}$$


This is the complete response of the RL circuit

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

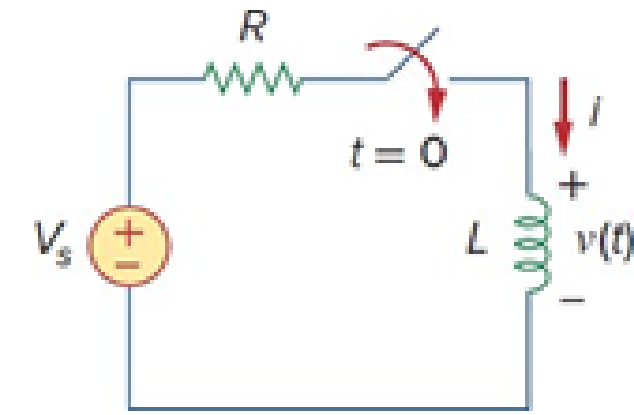where, $i(0)$ and $i(\infty)$ are the initial and final values of i , respectively.



(a)

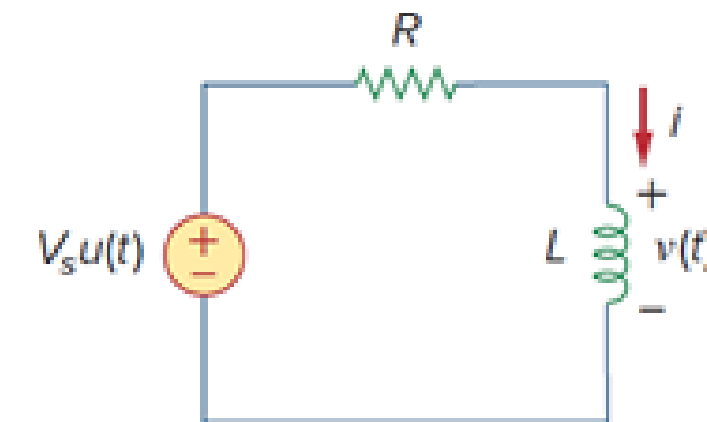

(b)




Step Response of an RL Circuit

If the switching takes place at time $t = t_0$ instead of $t = 0$,
$$i(t) = i(\infty) + [i(t_0) - i(\infty)]e^{-(t-t_0)/\tau}$$

If $I_0=0$,

$$i(t) = \begin{cases} 0 & t < 0 \\ \frac{V_s}{R}(1 - e^{-t/\tau}) & t > 0 \end{cases}$$
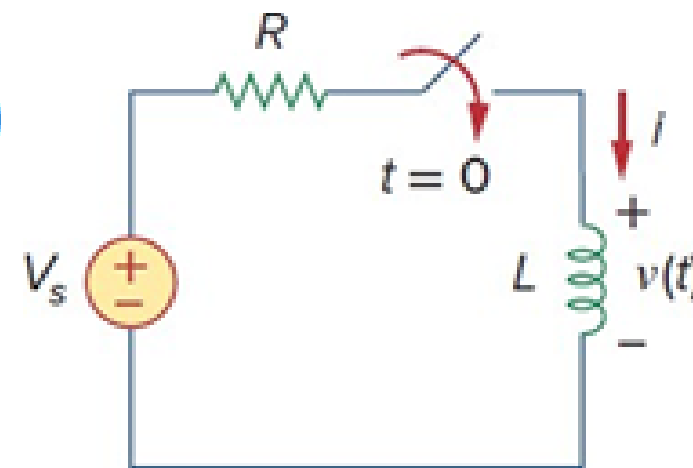
$$i(t) = \frac{V_s}{R}(1 - e^{-t/\tau})u(t)$$



The voltage across the inductor is,




$$v(t) = L \frac{di}{dt} = \frac{V_s L}{\tau R} e^{-t/\tau}; \quad \tau = \frac{L}{R} \quad t > 0$$

$$v(t) = V_s e^{-t/\tau} u(t)$$

This is the step response of the RL circuit with no initial inductor current.



Step Response of an RL Circuit

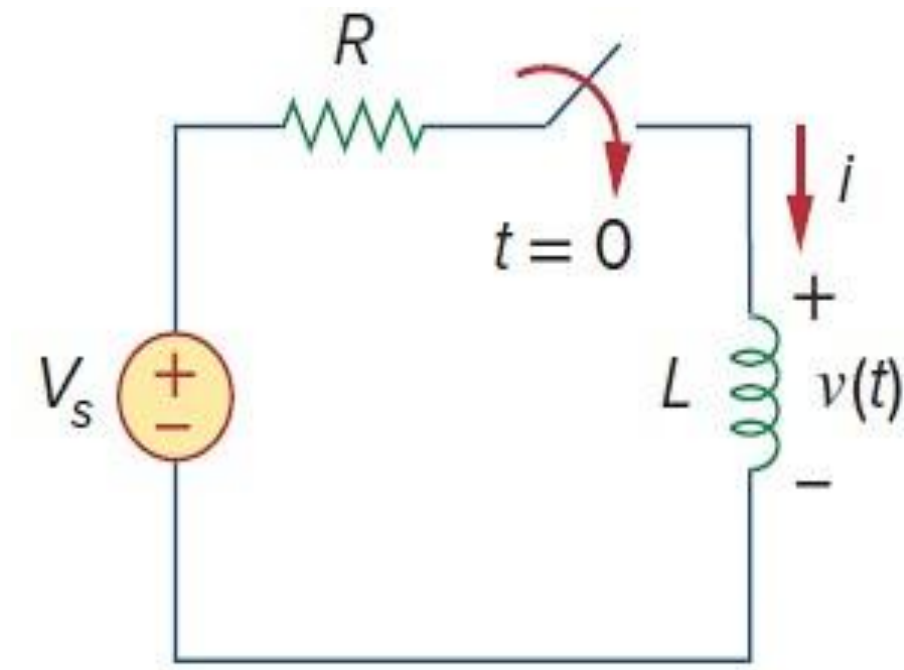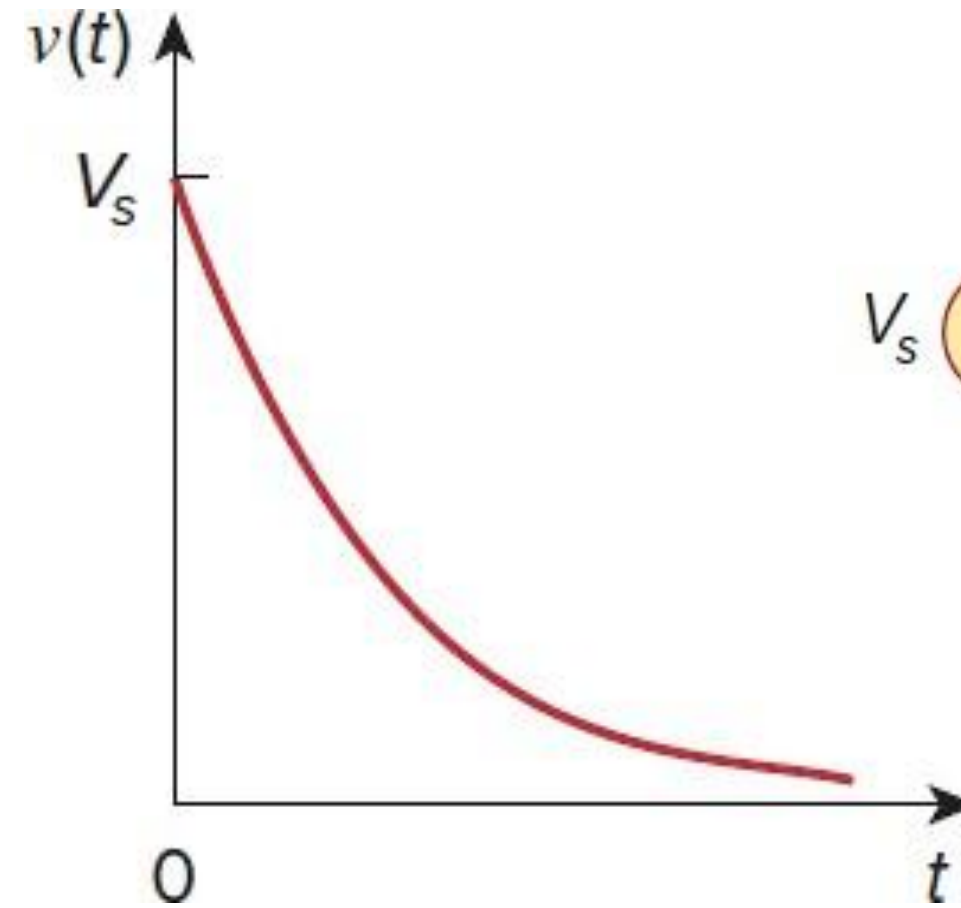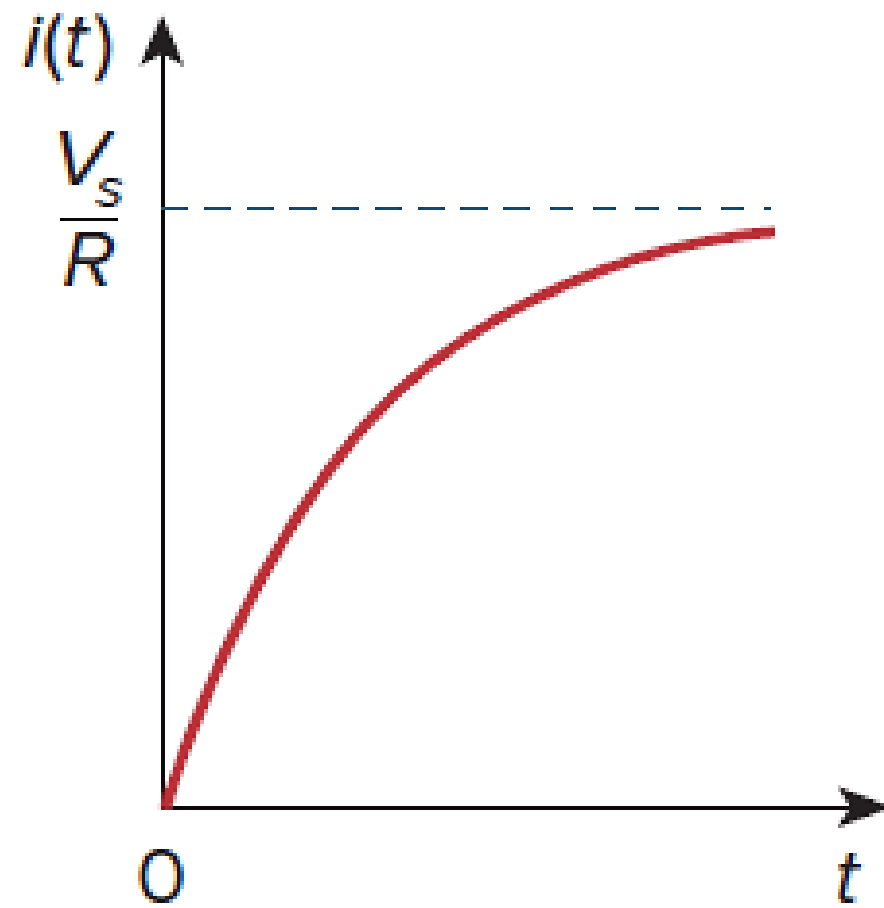

Step responses of an RL circuit with no initial inductor current