



# **SNS COLLEGE OF TECHNOLOGY**

## **(AN AUTONOMOUS INSTITUTION)**

Approved by AICTE & Affiliated to Anna University  
Accredited by NBA & Accredited by NAAC with 'A+' Grade,  
Recognized by UGC saravanampatti (post), Coimbatore-641035.



## **Department of Biomedical Engineering**

**Course Name: 23BMT201 & Circuit Analysis**

**I Year : II Semester**

**Unit IV –TRANSIENT RESPONSE FOR DC AND AC CIRCUITS**


**Topic : Basic RL and RC Circuits**


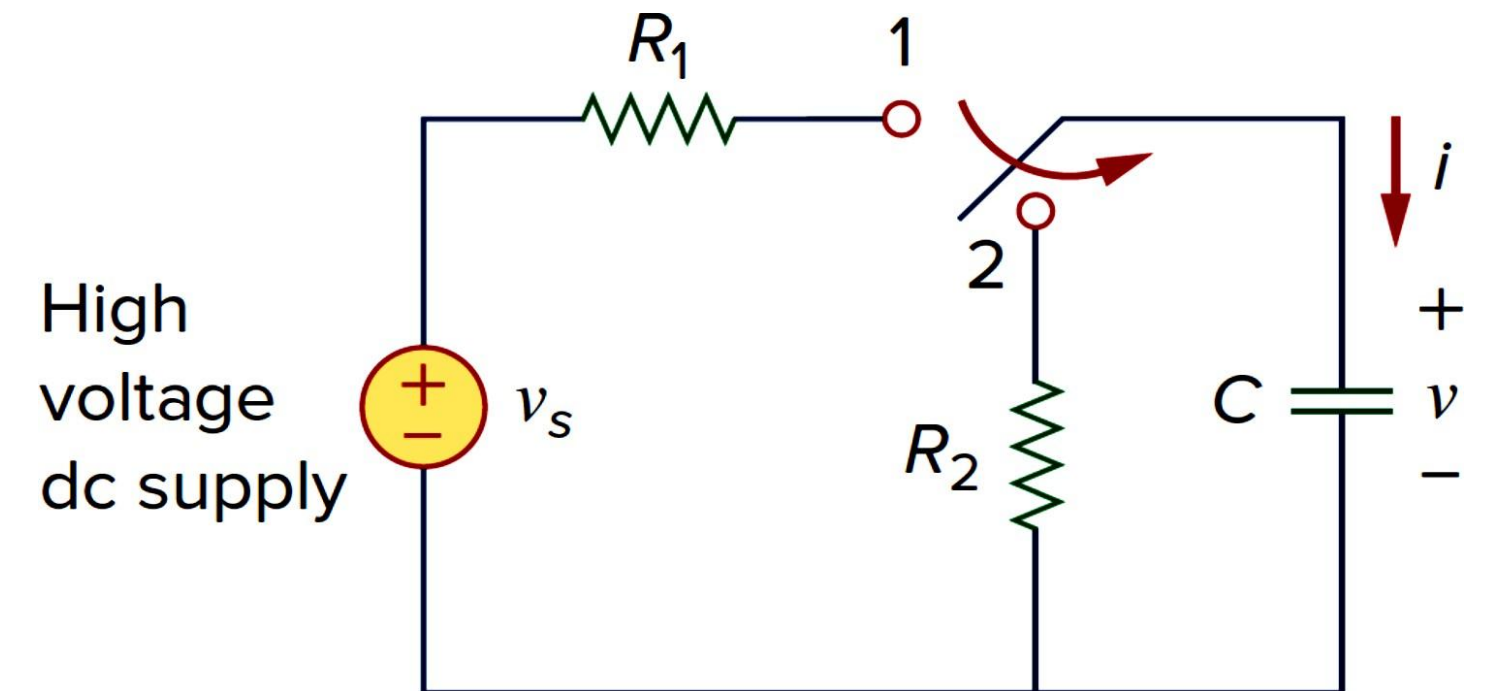
## Real Life Applications – Photo Flash



Digital Camera Flash Light utilizes a RC circuit to create a short duration high current pulse to energize the flash light.



Circuit for a flash unit providing slow charge in position 1 and fast discharge in position 2 ( $R_1 \gg R_2$ ).




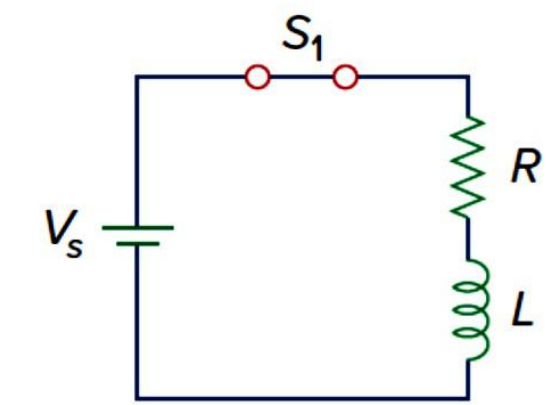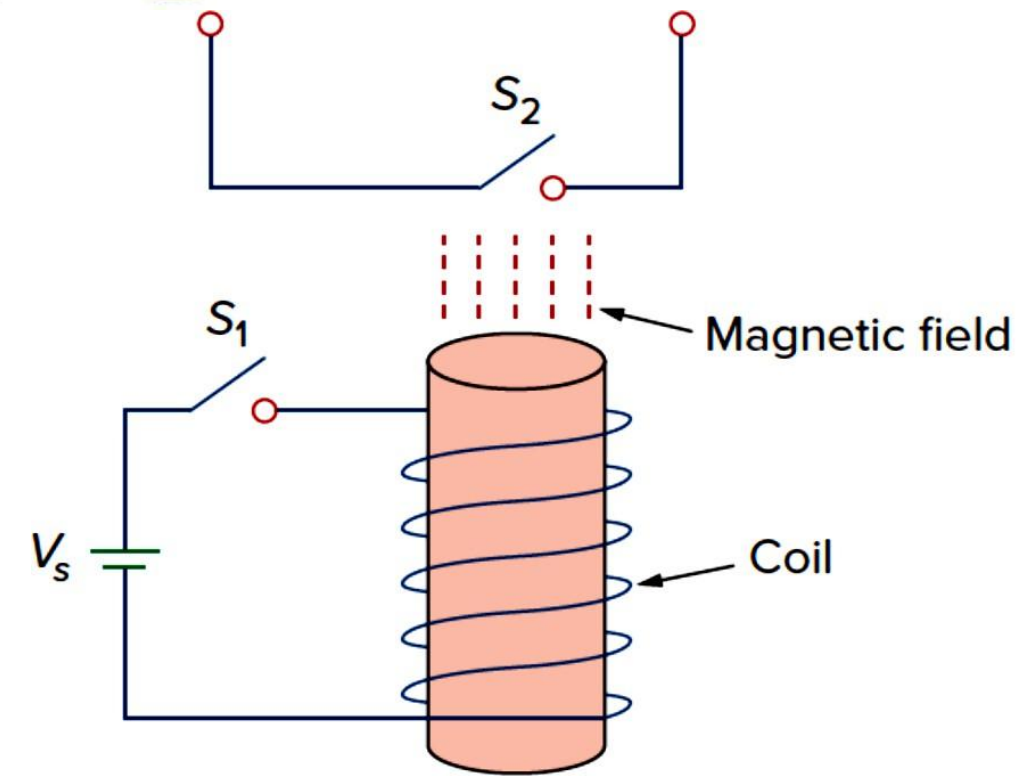
# Real Life Applications – Relay Circuits



Vision Title 3

Relay coil is nothing but an RL circuit used to control the switching of another circuit






# Step Response of an RC Circuit

When a DC source is suddenly turned on, the source voltage or current can be modelled as a step function

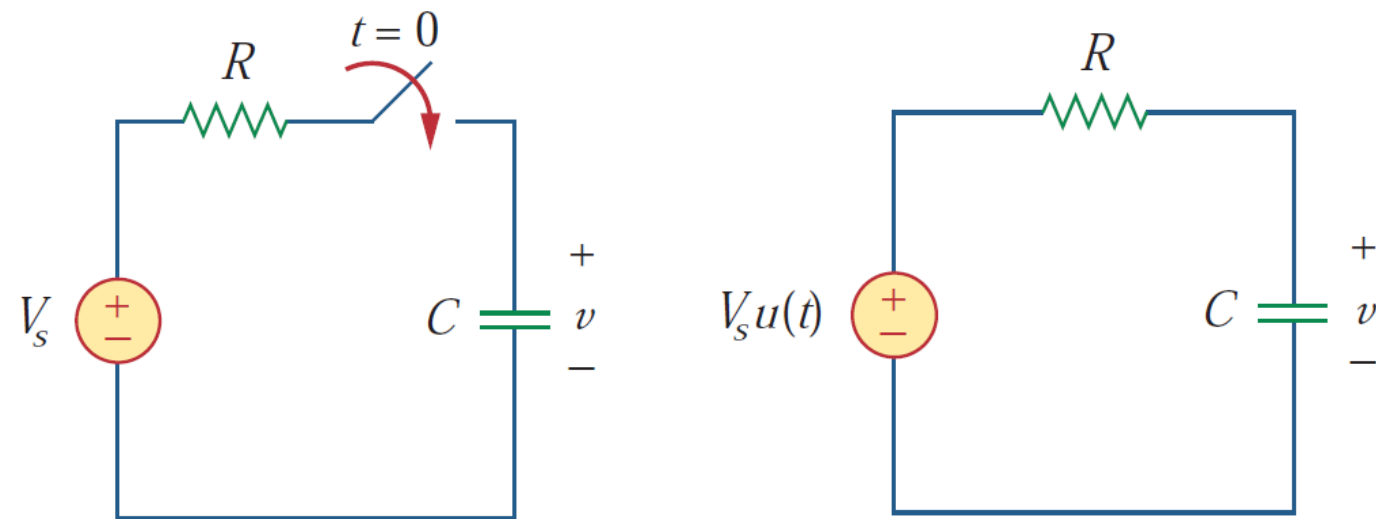**The step response of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source**



$u(t)$ : Unit-step function  
 $= 0$  for  $t < 0$   
 $= 1$  for  $t > 0$




# Step Response of an RC Circuit
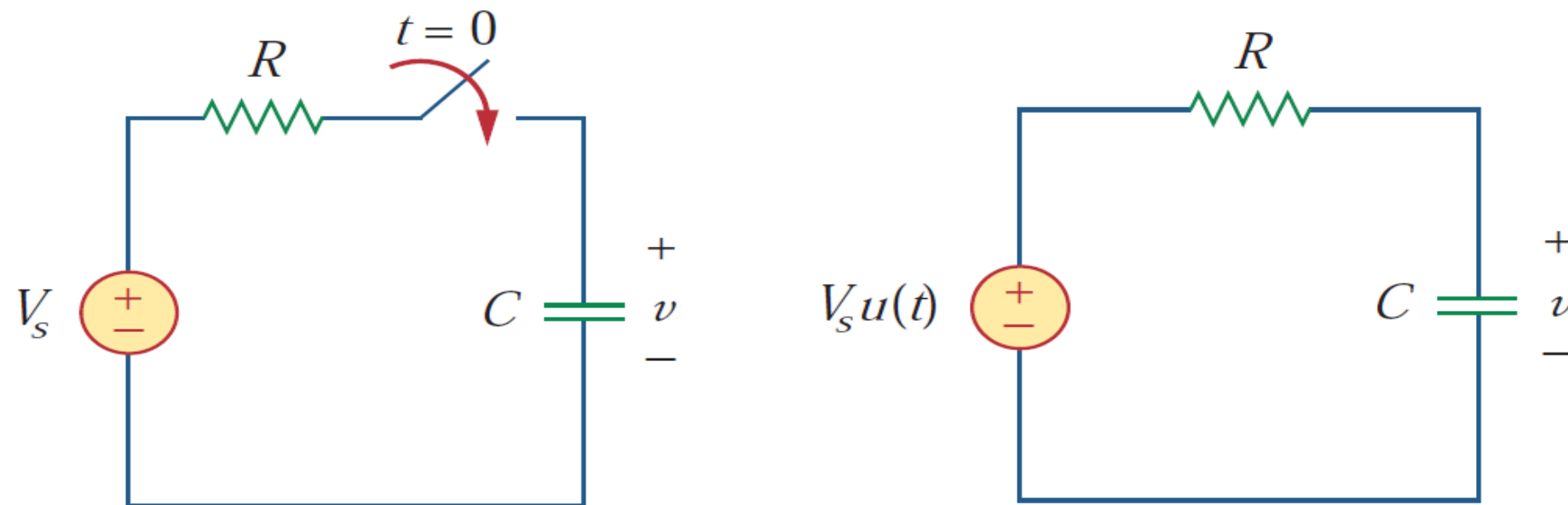
## Analysis:

- Consider the RC circuit in Fig. (a) which can be replaced by the circuit in Fig. (b) for  $t > 0$ , where  $V_s$  is a constant dc voltage source.
- Select the capacitor voltage  $v$  as the circuit response to be determined.
- Assume an initial voltage  $V_0$  on the capacitor.

Since, capacitor voltage cannot change instantaneously,  $v(0^-) = v(0^+) = V$



Vision Title 3



## Step Response of an RC Circuit

On applying KCL,

$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0$$



$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s u(t)}{RC}$$

where,  $v$  is the voltage across the capacitor. For  $t > 0$ ,

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC}$$

$$\frac{dv}{dt} = - \frac{v - V_s}{RC}$$


$$\frac{dv}{v - V_s} = - \frac{dt}{RC}$$

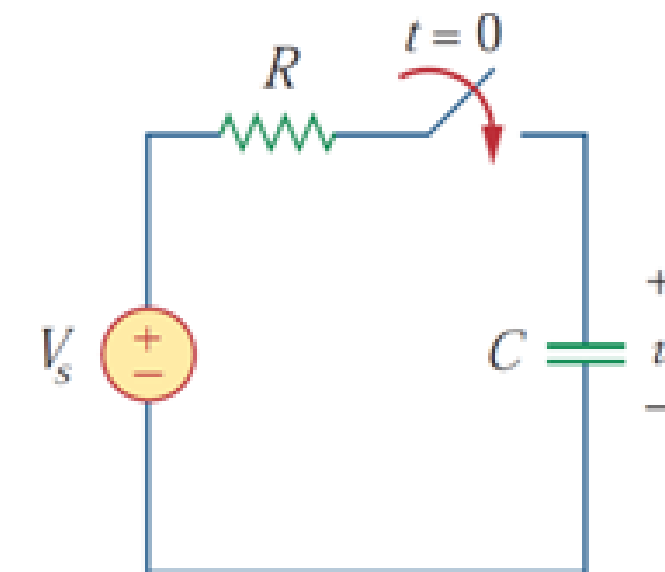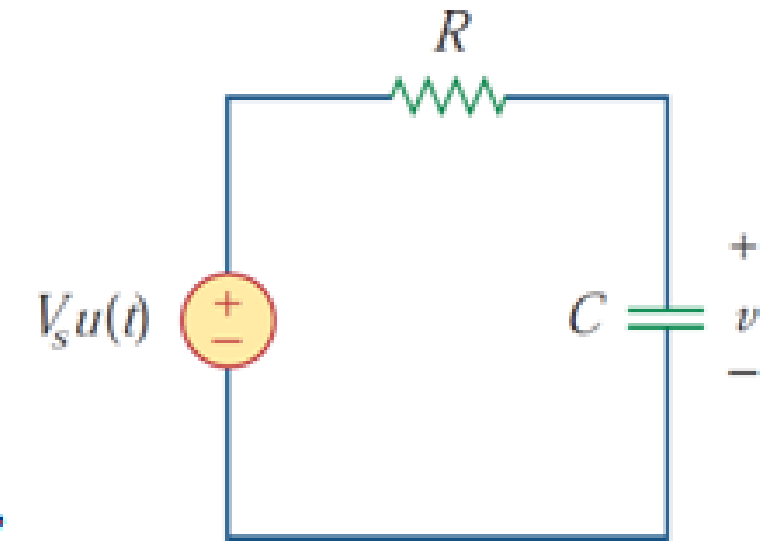



## Step Response of an RC Circuit

On integration,  $\ln(v - V_s) \Big|_{V_0}^{v(t)} = - \frac{t}{RC} \Big|_0^t$

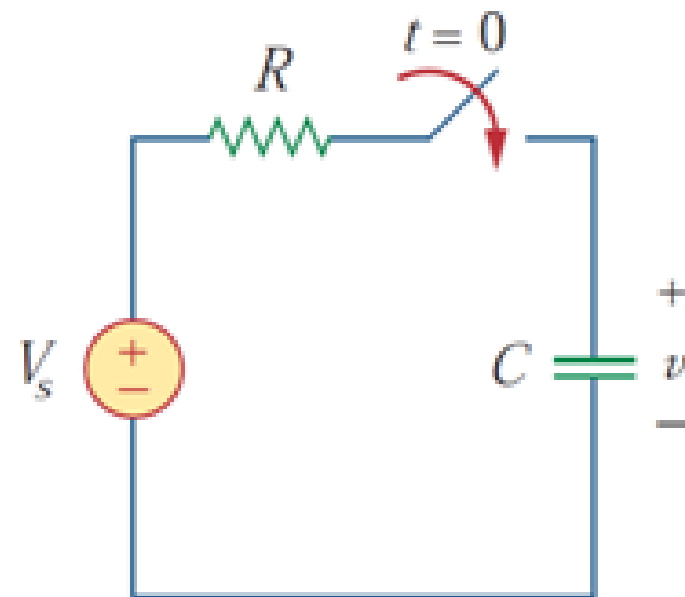

$$\ln(v(t) - V_s) - \ln(V_0 - V_s) = - \frac{t}{RC} + 0; \quad \ln \frac{v - V_s}{V_0 - V_s} = - \frac{t}{RC}$$

Taking exponential on both sides



$$\frac{v - V_s}{V_0 - V_s} = e^{-\frac{t}{\tau}}, \tau = RC; \quad v(t) = V_s + (V_0 - V_s)e^{-\frac{t}{\tau}}, t > 0$$

$$v(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s)e^{-\frac{t}{\tau}} & t > 0 \end{cases}$$


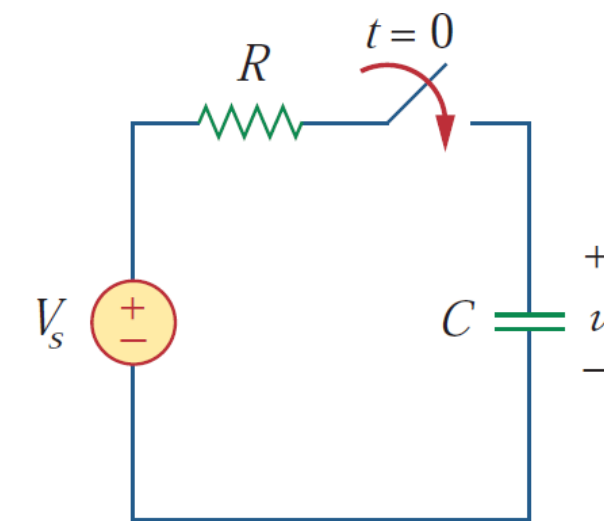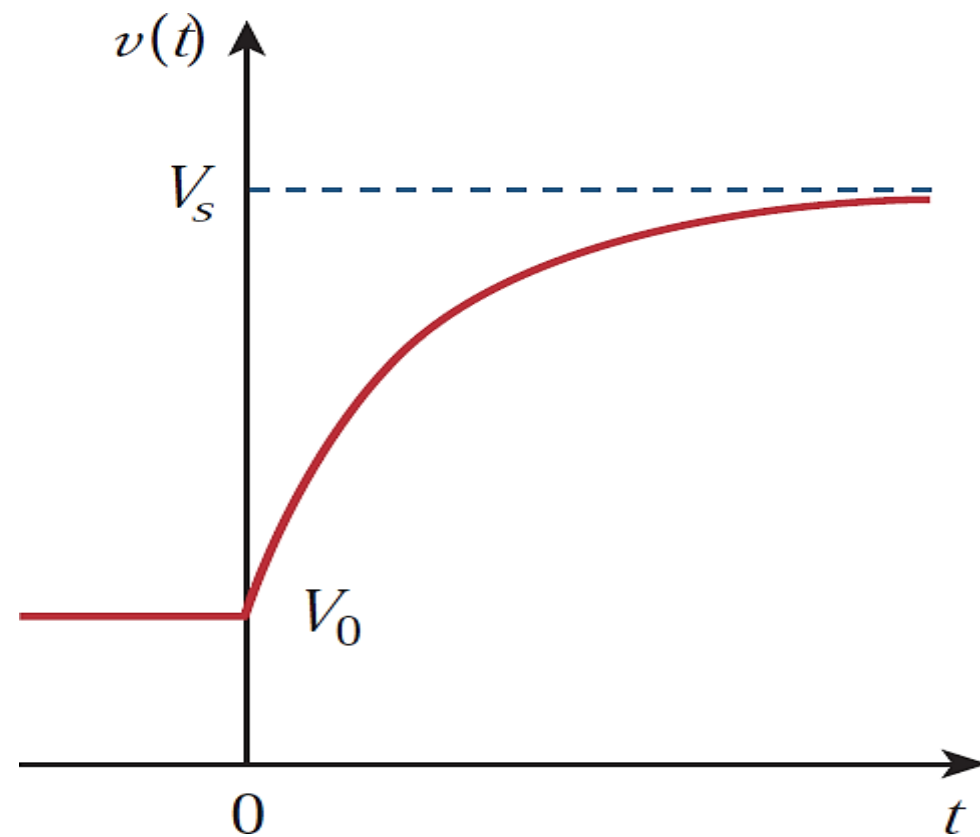
## Step Response of an RC Circuit

The complete response (or total response) of the RC circuit to a sudden application of a dc voltage source, assuming the capacitor is initially charged to  $V_0$  is shown below.



Vision Title 3






## Step Response of an RC Circuit

If the capacitor is uncharged initially i.e.  $V_0 = 0$

$$v(t) = \begin{cases} 0 & t < 0 \\ V_s(1 - e^{-\frac{t}{\tau}}) & t > 0 \end{cases}$$
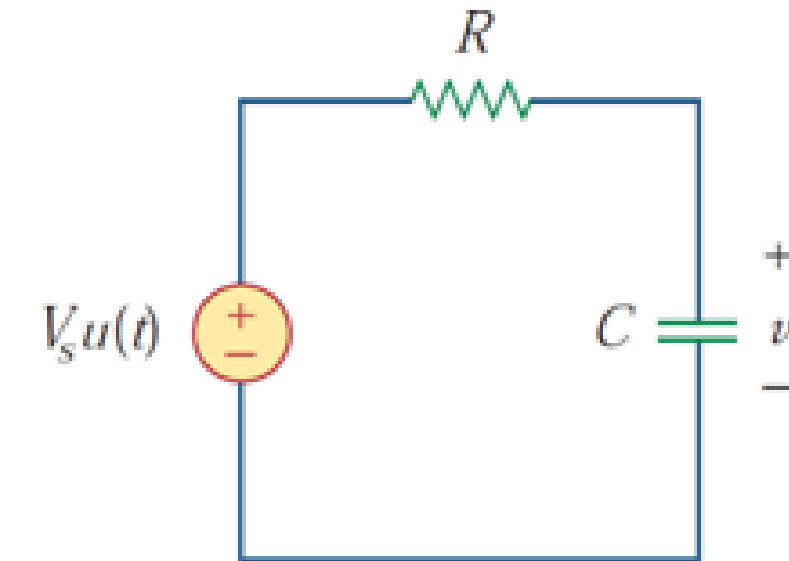
$$v(t) = V_s(1 - e^{-\frac{t}{\tau}})u(t)$$




This is the complete step response of the RC circuit when the capacitor is initially uncharged. The current through the capacitor is obtained as,

$$i(t) = C \frac{dv}{dt} = \frac{C}{\tau} V_s e^{-\frac{t}{\tau}}; \tau = RC; t > 0$$


$$i(t) = \frac{V_s}{R} e^{-\frac{t}{\tau}} u(t)$$




# Step Response of an RC Circuit

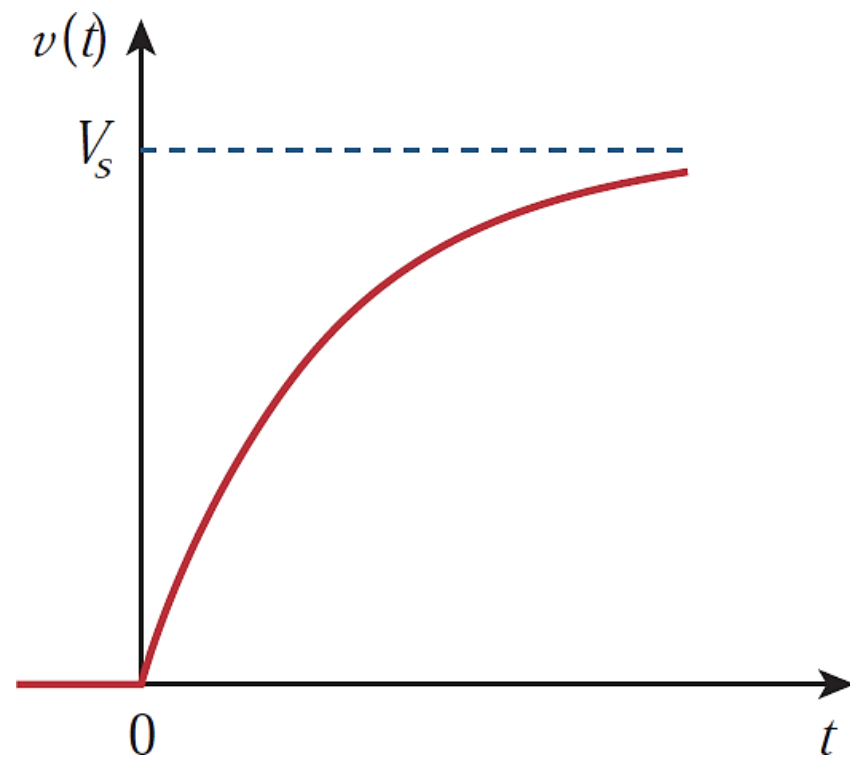

(a)

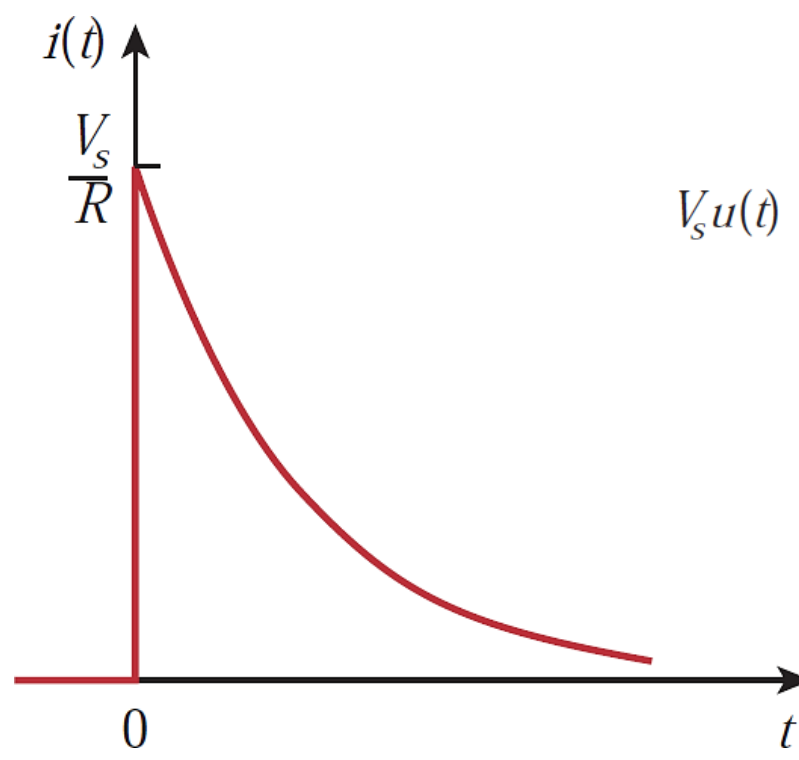

(b)

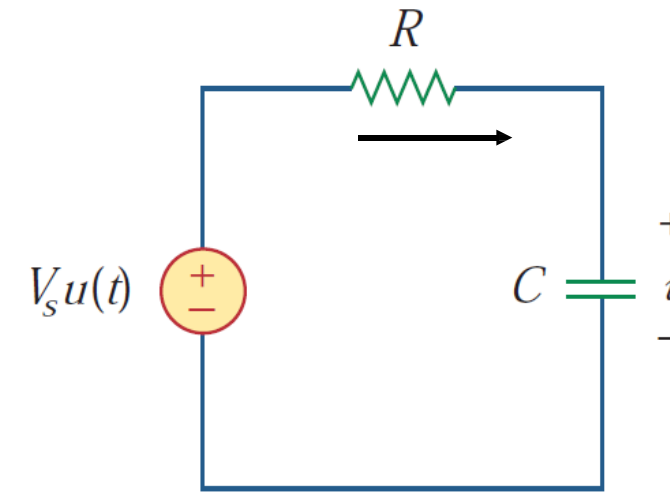

Vision Title 3

Step response of an RC circuit with initially uncharged capacitor