



# **SNS COLLEGE OF TECHNOLOGY**

## **(AN AUTONOMOUS INSTITUTION)**

Approved by AICTE & Affiliated to Anna University  
Accredited by NBA & Accredited by NAAC with 'A+' Grade,  
Recognized by UGC saravanampatti (post), Coimbatore-641035.



## **Department of Biomedical Engineering**

**Course Name: 23BMT201 & Circuit Analysis**

**I Year : II Semester**

**Unit V – RESONANCE CIRCUITS & COUPLED CIRCUITS**

**Topic : Frequency Response**



## When Resonance Occurs

- Resonance occurs in any circuit that has energy storage elements, **at least one inductor and one capacitor.**
- Under resonance, **the total impedance is equal to the resistance only** and **maximum power is drawn** from the supply by the circuit.
- Under resonance, the total **supply voltage and supply current are in phase.** So, the **power factor (PF) becomes unity.**
- At resonance,  $L$  and  $C$  elements exchange energy freely as a function of time, which results in sinusoidal oscillations either across  $L$  or  $C$ .
- **TYPES OF RESONANCE**
  - Series resonance.
  - Parallel resonance

Vision Title 3



# Applications of Resonance



- Resonant circuits (series or parallel) are used in many applications such as **selecting the desired stations in radio and TV receivers.**
- Most common applications of resonance are based on the **frequency dependent response. (“tuning” into a particular frequency/channel)**
- A series resonant circuit is used as **voltage amplifier.**
- A parallel resonant circuit is used as **current amplifier.**
- A resonant circuit is also used as a **filter.**

Vision Title 3



## Resonance in Series RLC Circuit

**Resonance** is a condition in an *RLC* circuit in which the **capacitive and inductive reactances are equal** in magnitude, thereby resulting in a purely resistive impedance.


The input impedance is as follows,

$$Z = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

At resonance, the net reactance becomes zero. Therefore,

$$\omega_r L = \frac{1}{\omega_r C} \Rightarrow \omega_r = \frac{1}{\sqrt{LC}} \text{ rad/s}; f_r = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

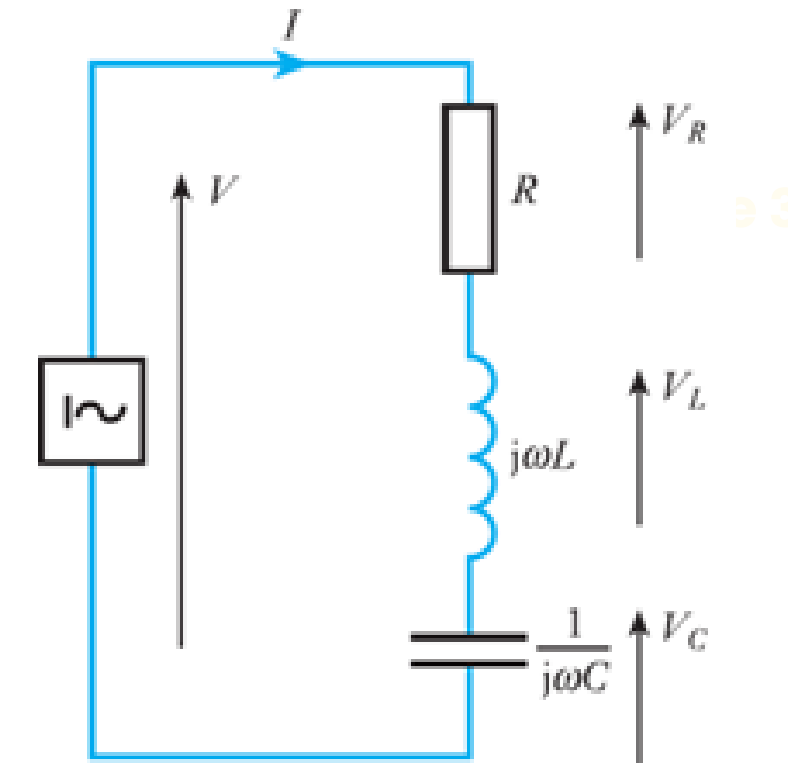where  $\omega_r$  and  $f_r$  represent resonant frequency in rad/s and in Hz, respectively



Series resonant *RLC* circuit




# REACTANCE ( $X_L, X_C$ ) VS FREQUENCY PLOTS

The value of the reactance  $X$  of the circuit is,

$$X = \omega L - \frac{1}{\omega C}$$

Depends on frequency

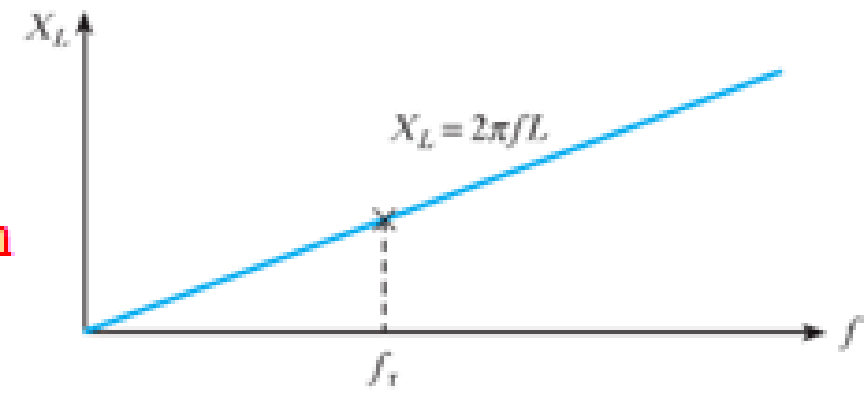Variation of inductive reactance with frequency




The inductive reactance:

$$|X_L| = \omega L = 2\pi fL$$

Increases linearly with frequency

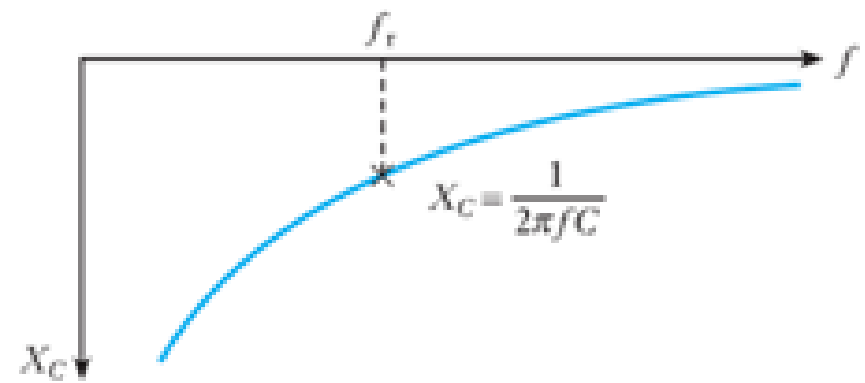
Variation of Capacitive reactance with frequency



The capacitive reactance:

$$|X_C| = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$


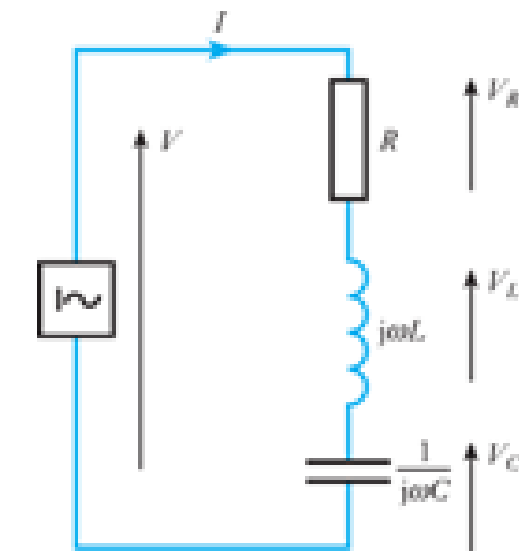
Decreases with frequency and it is largest at low frequencies





# Variation of Reactance and Impedance with Frequency

- At resonant frequency  $f_r$ ,  $|Z| = R$ , the power factor is unity (**purely resistive**).
- Below  $f_r$ ,  $|X_L| < |X_C|$ , so the circuit is more **capacitive** and the power factor is leading.
- Above  $f_r$ ,  $|X_L| > |X_C|$ , so the circuit is more **inductive** and the power factor is lagging.

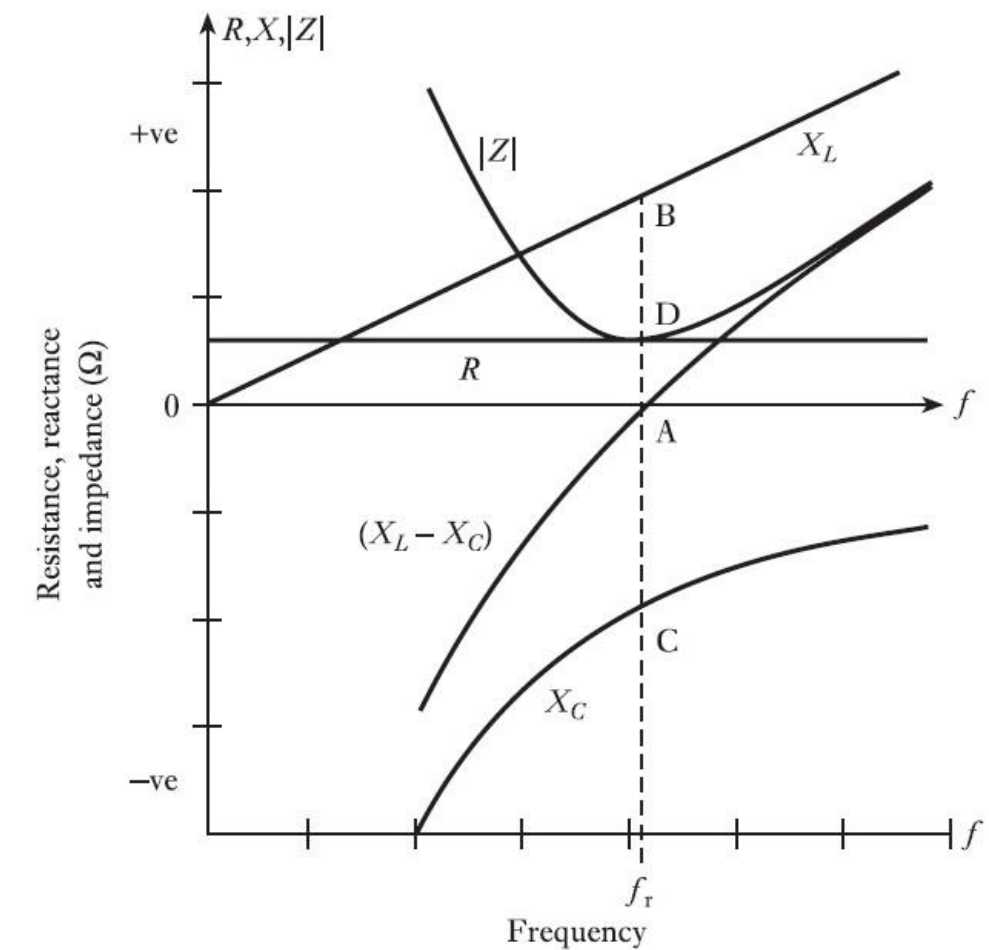
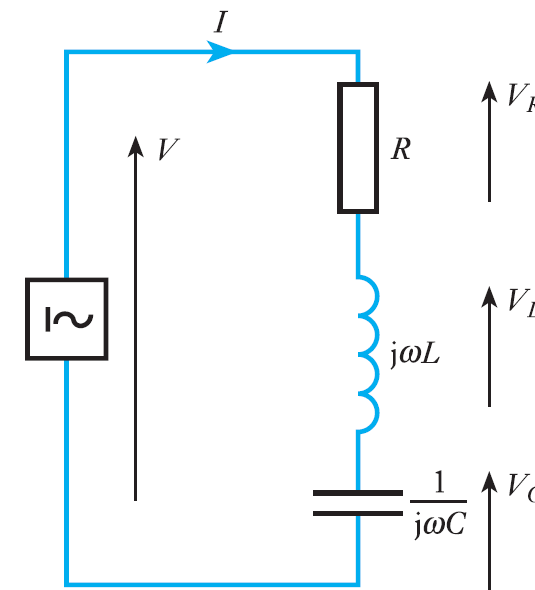




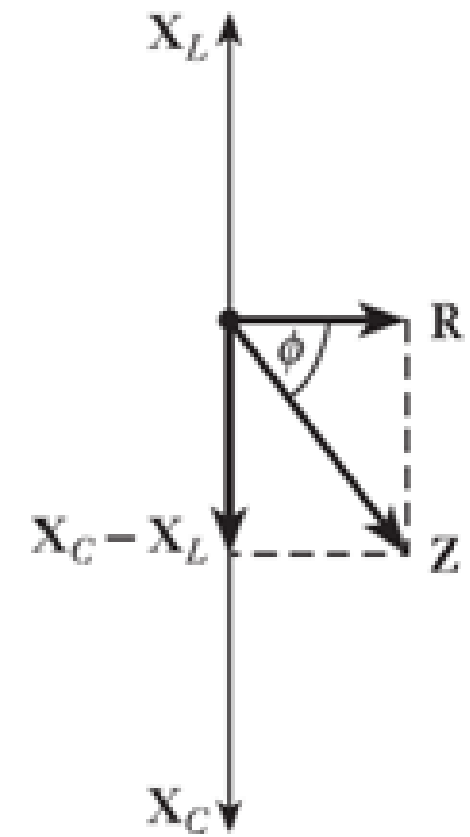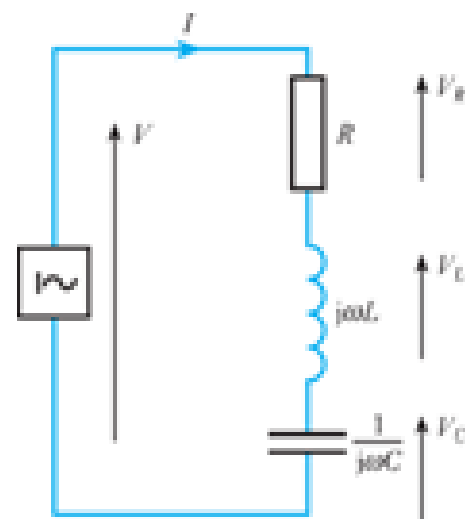
# Impedance Phasor Diagrams

The phase of the circuit impedance is given by


$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$



Below  $f_r$ ,  $X_C > X_L$

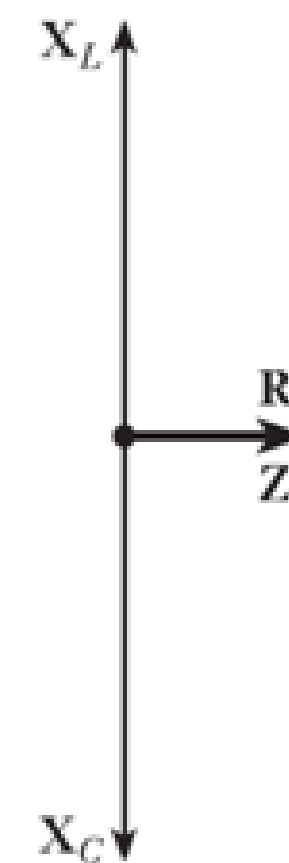

At  $f_r$ ,  $X_C = X_L$ ,  $Z = R$

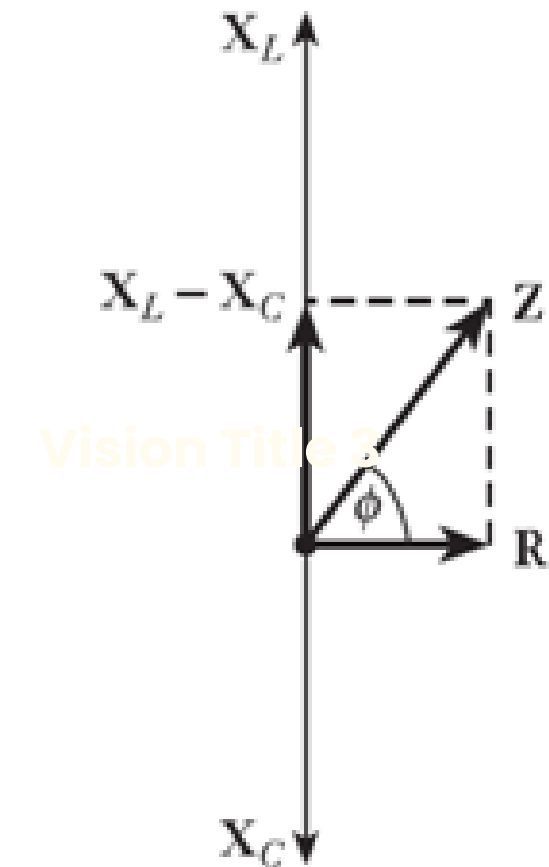

Above  $f_r$ ,  $X_L > X_C$

- Below  $f_r$ ,  $X_L < X_C$ ,  $\phi$  is negative, the circuit is capacitive.
- At resonance ( $f_r$ ),  $X_L = X_C$ ,  $\phi$  is zero, the circuit is purely resistive.
- Above  $f_r$ ,  $X_L > X_C$ ,  $\phi$  is positive, the circuit is inductive.



# The Current in a Series RLC Circuit


The circuit current is given by

$$I = \frac{V}{Z \angle \phi} = \frac{V \angle -\phi}{Z}$$

$$I = \frac{V}{\sqrt{\left\{ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right\}}} \angle -\tan^{-1} \left( \frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

The current is maximum when  $\omega L = 1/(\omega C)$ , when the circuit is resistive ( $\phi = 0$ ). Therefore,

$$I_m = \frac{V}{R}$$

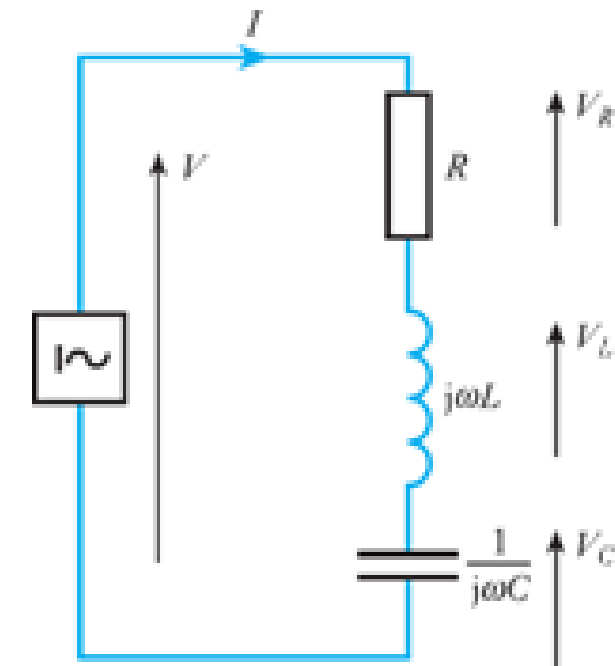





# Variation of Magnitude and Phase of Current with Frequency

- The current is maximum at resonant frequency ( $f_r$ ).

Variation of magnitude  $|I|$  and phase of current with frequency in a series RLC circuit

