



# **SNS COLLEGE OF TECHNOLOGY**

## **(AN AUTONOMOUS INSTITUTION)**

Approved by AICTE & Affiliated to Anna University  
Accredited by NBA & Accredited by NAAC with 'A+' Grade,  
Recognized by UGC saravanampatti (post), Coimbatore-641035.



## **Department of Biomedical Engineering**

**Course Name: 23BMT201 & Circuit Analysis**

**I Year : II Semester**

**Unit V – RESONANCE CIRCUITS & COUPLED CIRCUITS**

**Topic : Q Factor & Bandwidth**



## Quality Factor (Q)

- The “sharpness” of the resonance in a resonant circuit is measured quantitatively by the quality factor  $Q$ .
- The quality factor relates the maximum or peak energy stored to the energy dissipated in the circuit per cycle of oscillation:

Vision Title 3

$$Q = 2\pi \left( \frac{\text{Peak energy stored in the circuit}}{\text{Energy dissipated by the circuit in one period at resonance}} \right)$$

- It is also regarded as a measure of the energy storage property of a circuit in relation to its energy dissipation property.




# Quality Factor (Q)

- In the series *RLC* circuit, the quality factor (*Q*) is,

$$Q = 2\pi \left[ \frac{\frac{1}{2} LI^2}{\frac{1}{2} I^2 R \left( \frac{1}{f_r} \right)} \right] = \frac{2\pi f_r L}{R}$$
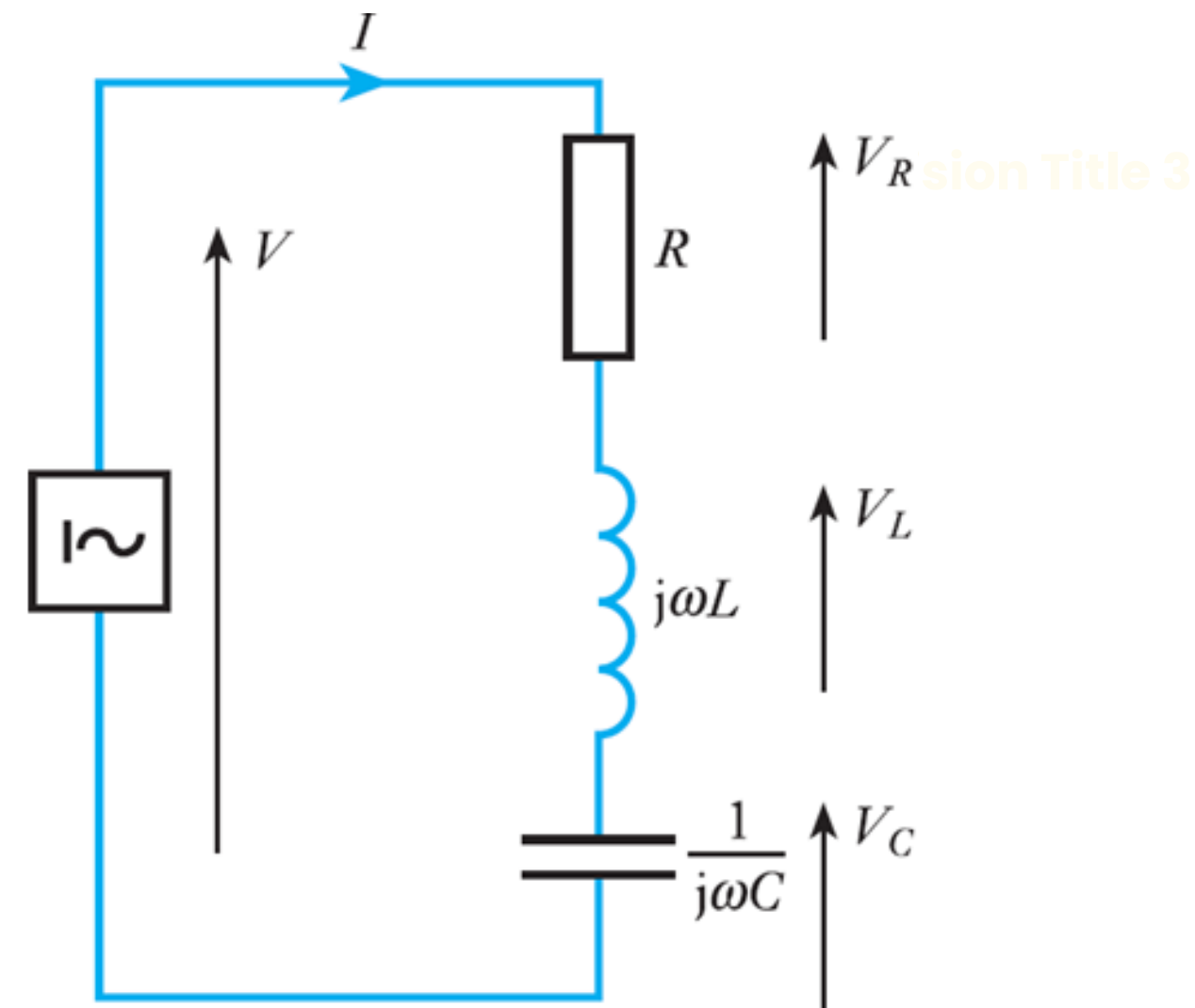
$$Q = \frac{\omega L}{R} = \frac{1}{\omega_r CR} = \frac{1}{R} \sqrt{\frac{L}{C}}$$





## Quality Factor (Q)

- The  $Q$  factor is also defined as the ratio of the reactive power, of either the capacitor or the inductor to the average power of the resistor at resonance:


$$Q = \left( \frac{\text{Reactive power}}{\text{Average power}} \right)$$

- For inductive reactance  $X_L$  at resonance:

$$Q = \left( \frac{\text{Reactive power}}{\text{Average power}} \right) = \frac{I^2 X_L}{I^2 R} = \frac{\omega L}{R}$$


- For capacitive reactance  $X_C$  at resonance:
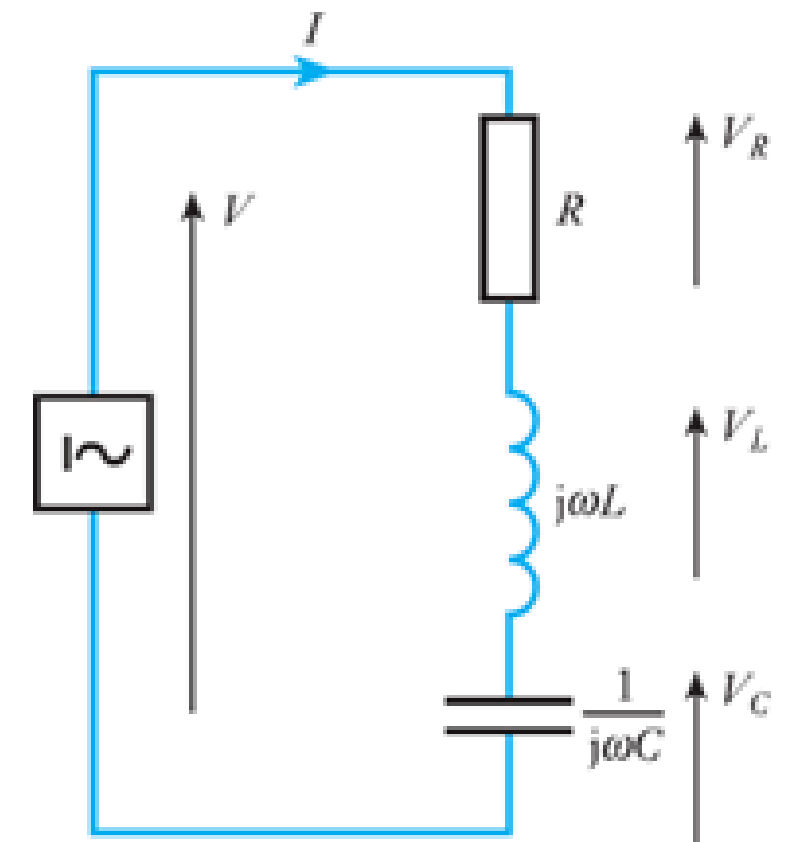
$$Q = \left( \frac{\text{Reactive power}}{\text{Average power}} \right) = \frac{I^2 X_C}{I^2 R} = \frac{1}{\omega_r C R}$$







# Voltages in A Series RLC Circuit

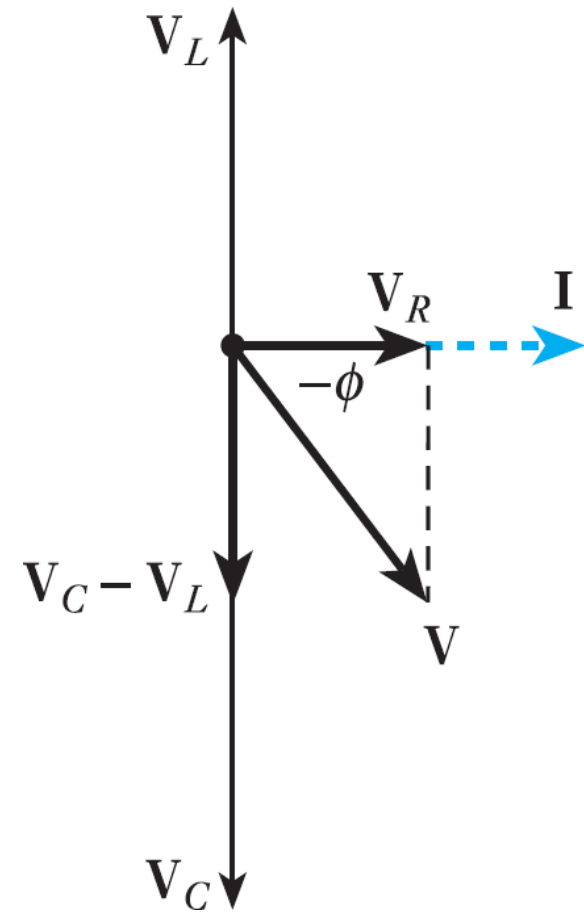

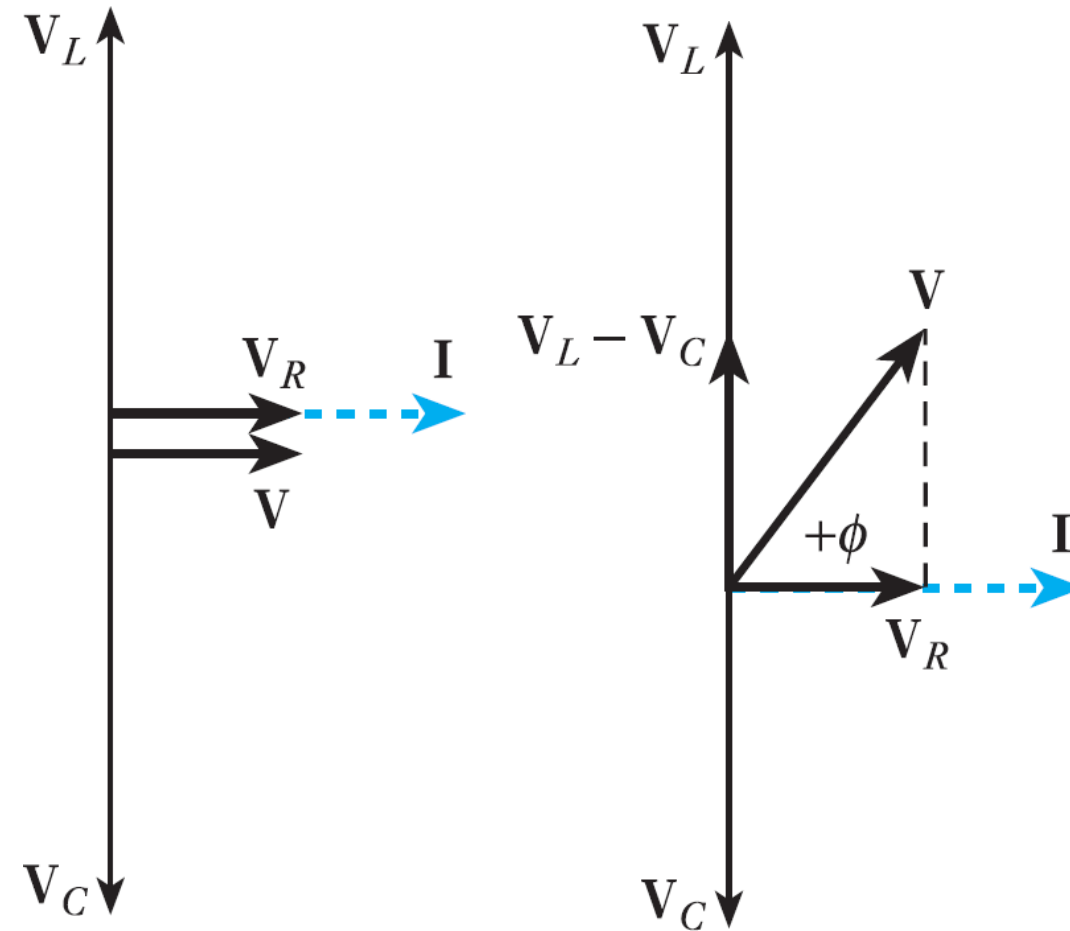
(a)  $f < f_r$   
Capacitive,  
 $I$  leads  $V$



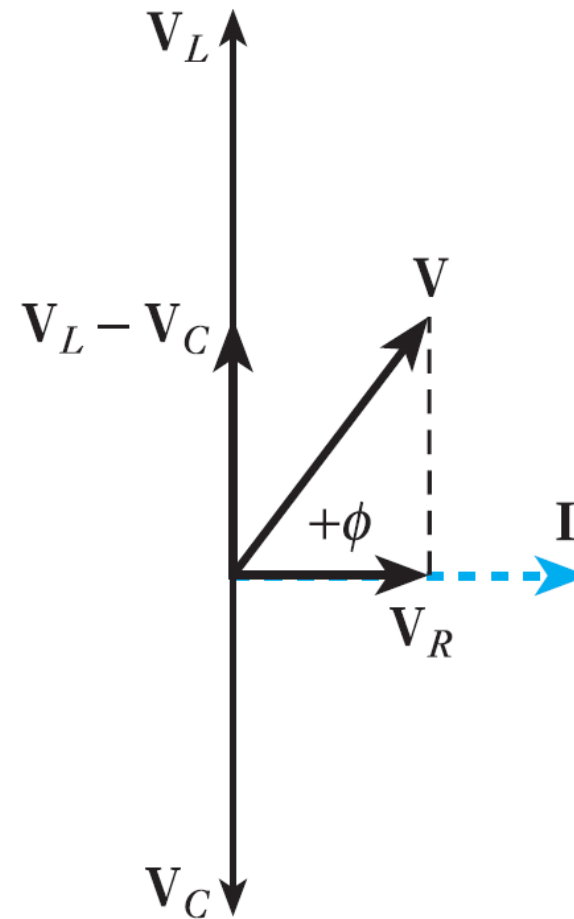(b)  $f = f_r$   
Resistive,  
 $V$  and  $I$  in  
phase



(c)  $f > f_r$   
Inductive,  
 $I$  lags  $V$

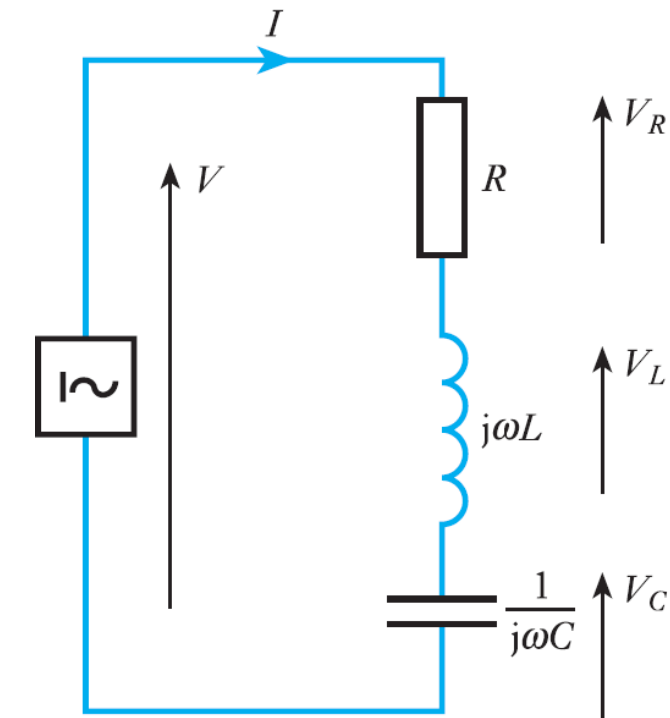

Title 3



## Voltages Across RLC Elements at Resonance

The voltage across resistor at  $f_r$  is,


$$V_R = I_R \times R = I_m \times R = \frac{V}{R} \times R \Rightarrow V_R = V$$

The voltage across inductor at  $f_r$  is,

$$|V_L| = X_L \times I_L = \omega L_r \times I_m = \omega L_r \times \frac{V}{R} = \frac{\omega L}{R} V = QV$$
$$\Rightarrow |V_L| = QV$$

The voltage across capacitor at  $f_r$  is,

$$|V_C| = X_C \times I_C = \frac{1}{\omega C} \times I_m = \frac{1}{\omega C} \times \frac{V}{R} = \frac{1}{\omega C R} V = QV \Rightarrow |V_C| = QV$$

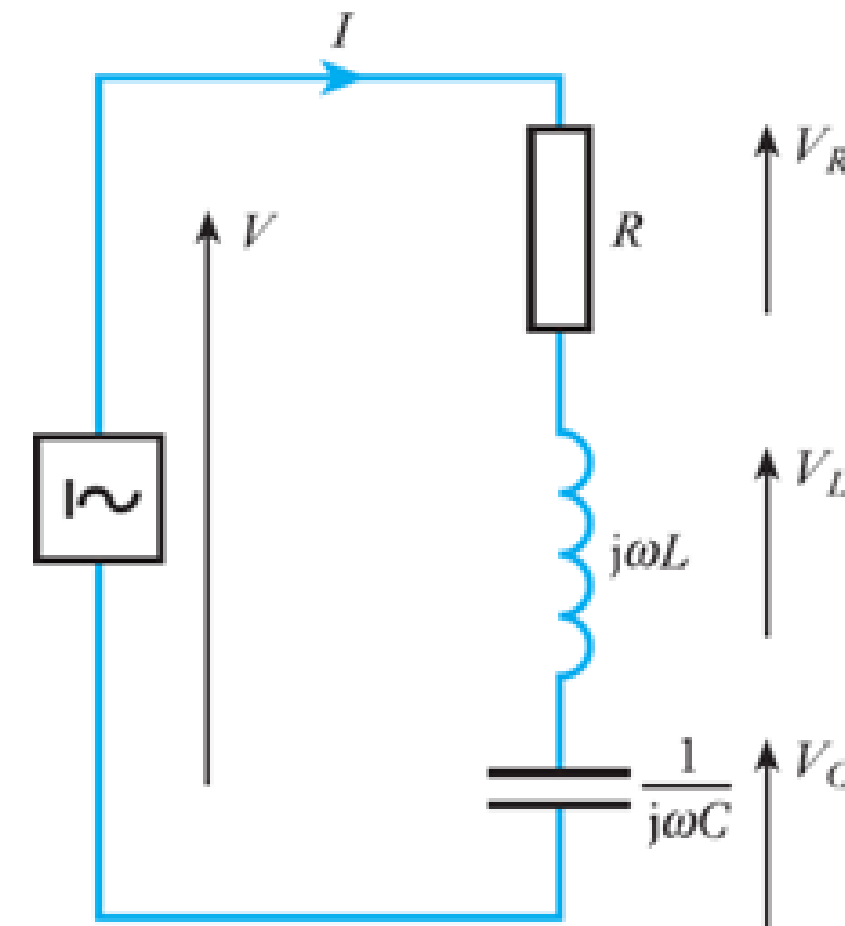



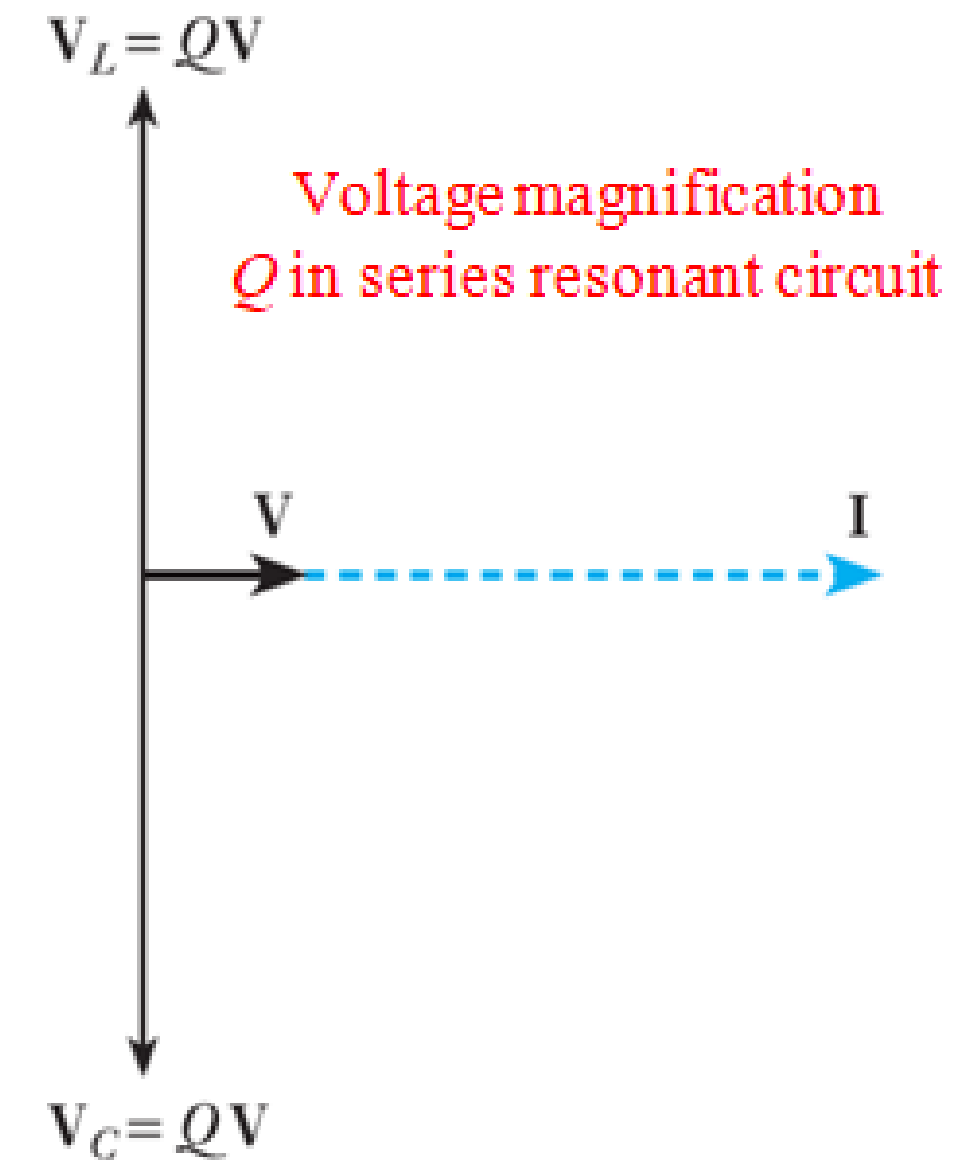
## Voltages Across RLC Elements at Resonance



- $Q$  is termed as  $Q$  factor or voltage magnification, because  $V_C$  or  $V_L$  equals  $Q$  multiplied by the source voltage  $V$ .
- In a series  $RLC$  circuit, values of  $V_L$  and  $V_C$  can actually be very large at resonance and can lead to component damage if not recognized and subject to careful design.

$$Q = \frac{\omega L}{R} = \frac{1}{\omega CR} = \frac{1}{R} \sqrt{\left(\frac{L}{C}\right)}$$




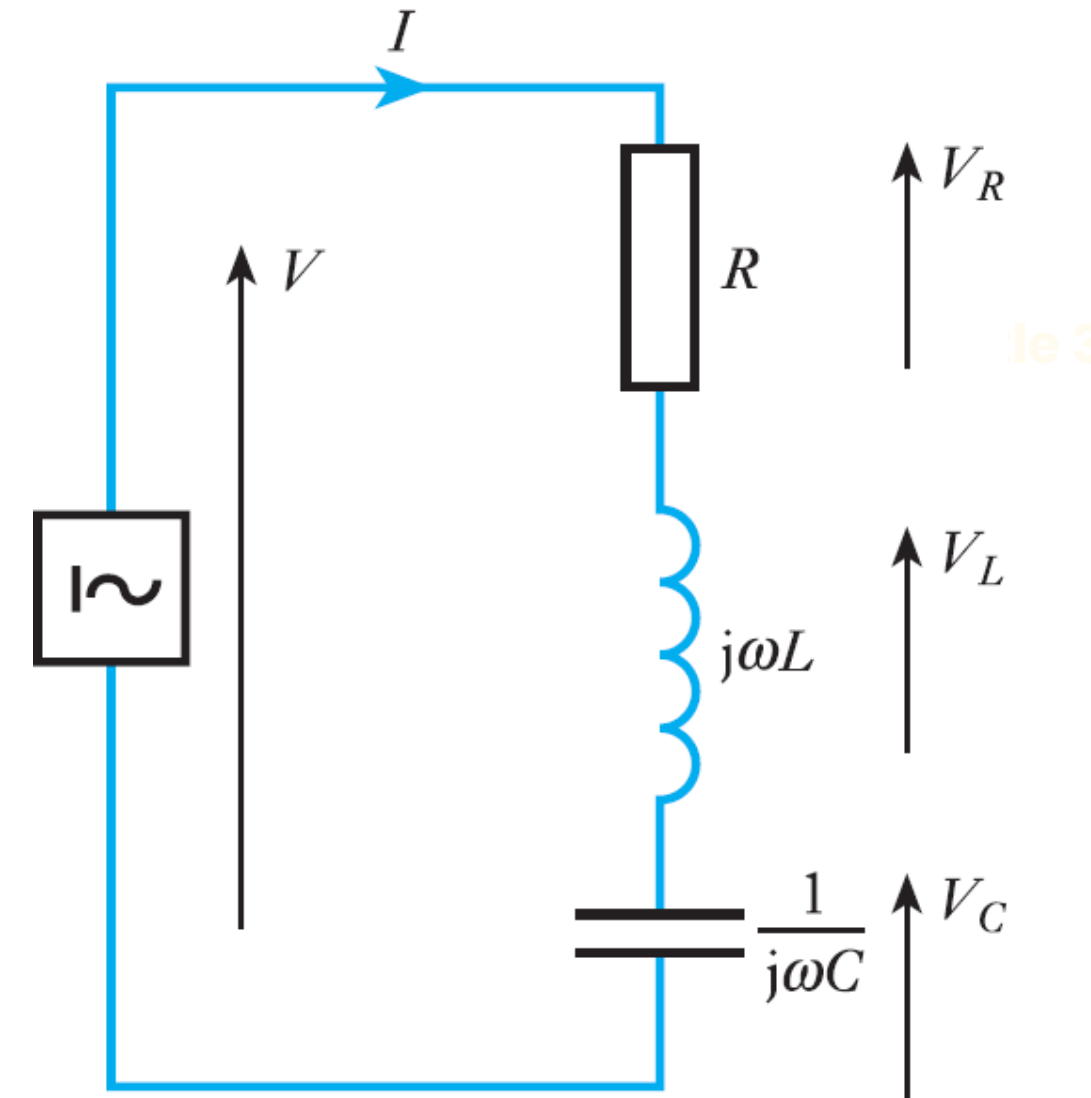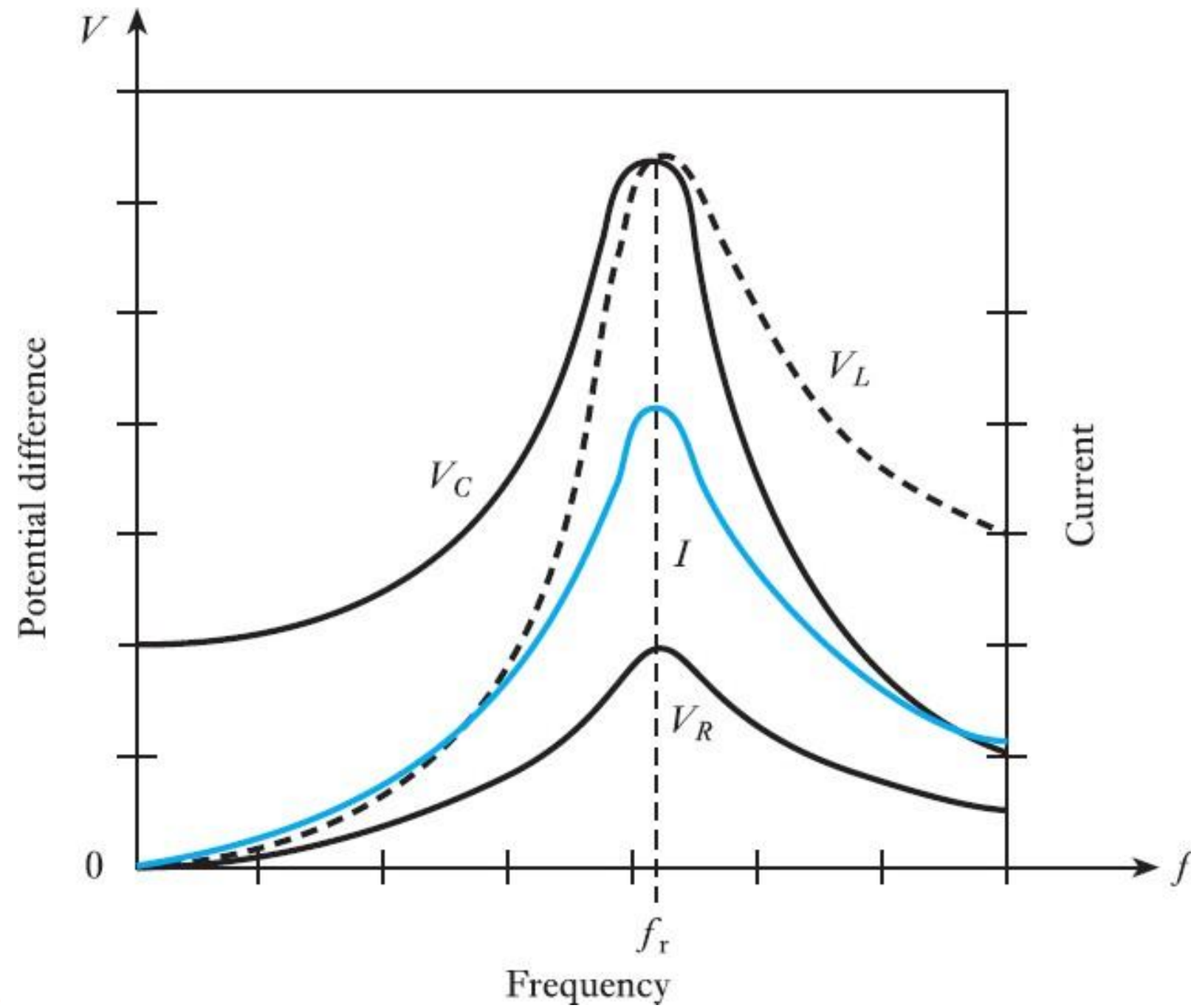
# Voltages Across RLC Elements at Resonance







## Bandwidth and Half Power Frequencies


- In a series  $RLC$  circuit, at resonance, maximum power is drawn. i.e.,

$$P_r = I_{\max}^2 \times R; \text{ where } I_{\max} = \frac{V}{R} \text{ at resonance}$$

- Bandwidth represents the range of frequencies for which the power level in the signal is at least half of the maximum power.

$$\frac{P_r}{2} = \frac{I_{\max}^2 \times R}{2} = \left( \frac{I_{\max}}{\sqrt{2}} \right)^2 \times R$$

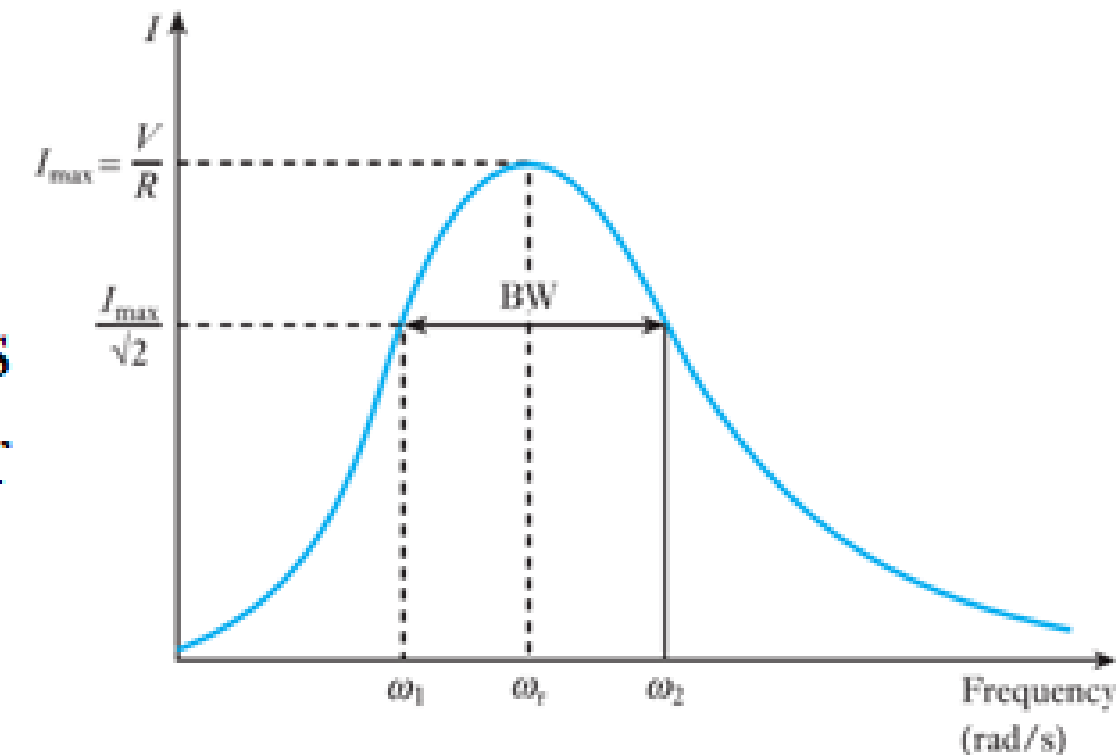- The bandwidth of a circuit is also defined as the frequency range between the half-power points when  $I = I_{\max}/\sqrt{2}$ .






# Bandwidth and Half Power Frequencies

- Thus, the condition for half-power is given when

$$|I| = \frac{I_{\max}}{\sqrt{2}} = \frac{V}{R\sqrt{2}}$$

- The vertical lines either side of  $|I|$  indicate that only the magnitude of the current is under consideration – but the phase angle will not be neglected.
- The impedance corresponding to half power-points including phase angle is
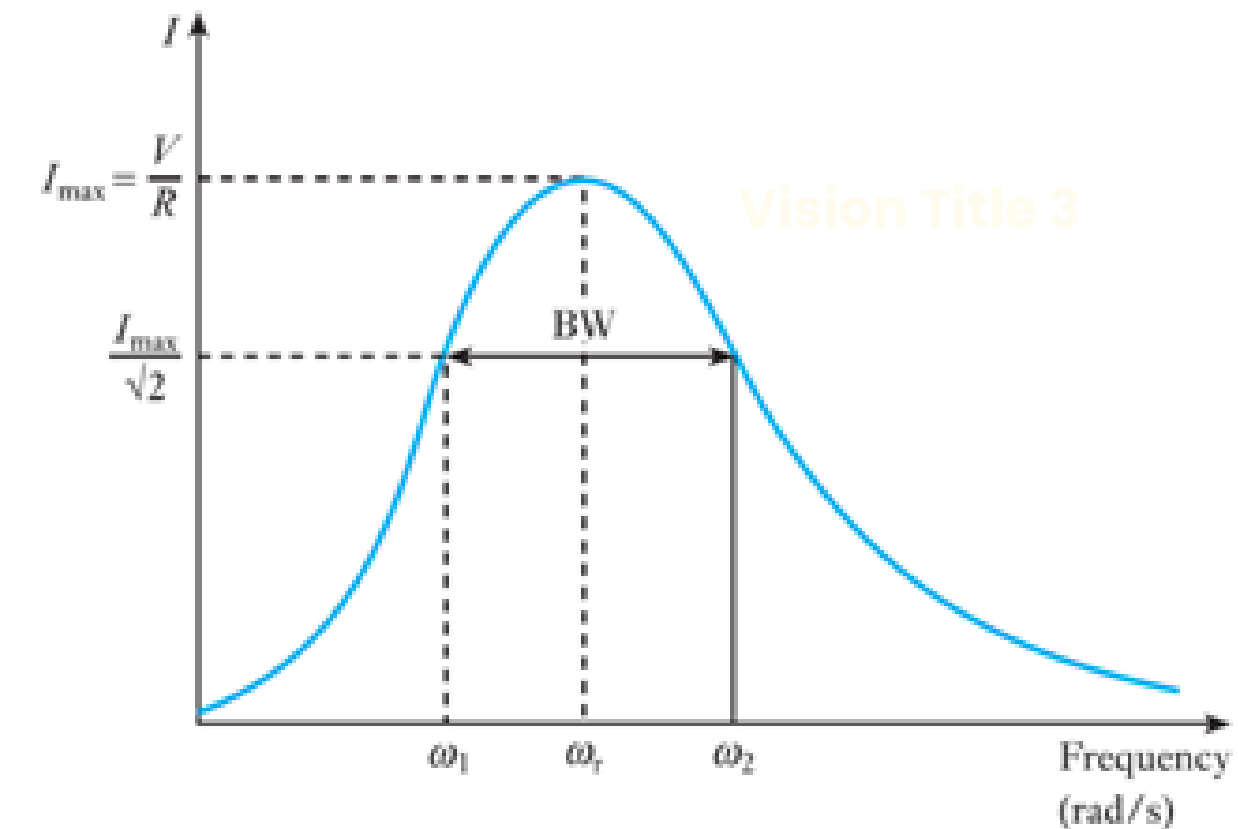
$$Z(\omega_{1/2}) = R \sqrt{2} \angle \pm 45^\circ$$



The resonance peak, bandwidth and half-power frequencies



## Bandwidth and Half Power Frequencies


- The impedance in the complex form

$$Z(\omega) = R(1 \pm j1)$$

- Thus for half power,

$$I = \frac{V}{R(1 \pm j1)} \quad \text{and} \quad Z = R(1 \pm j1)$$

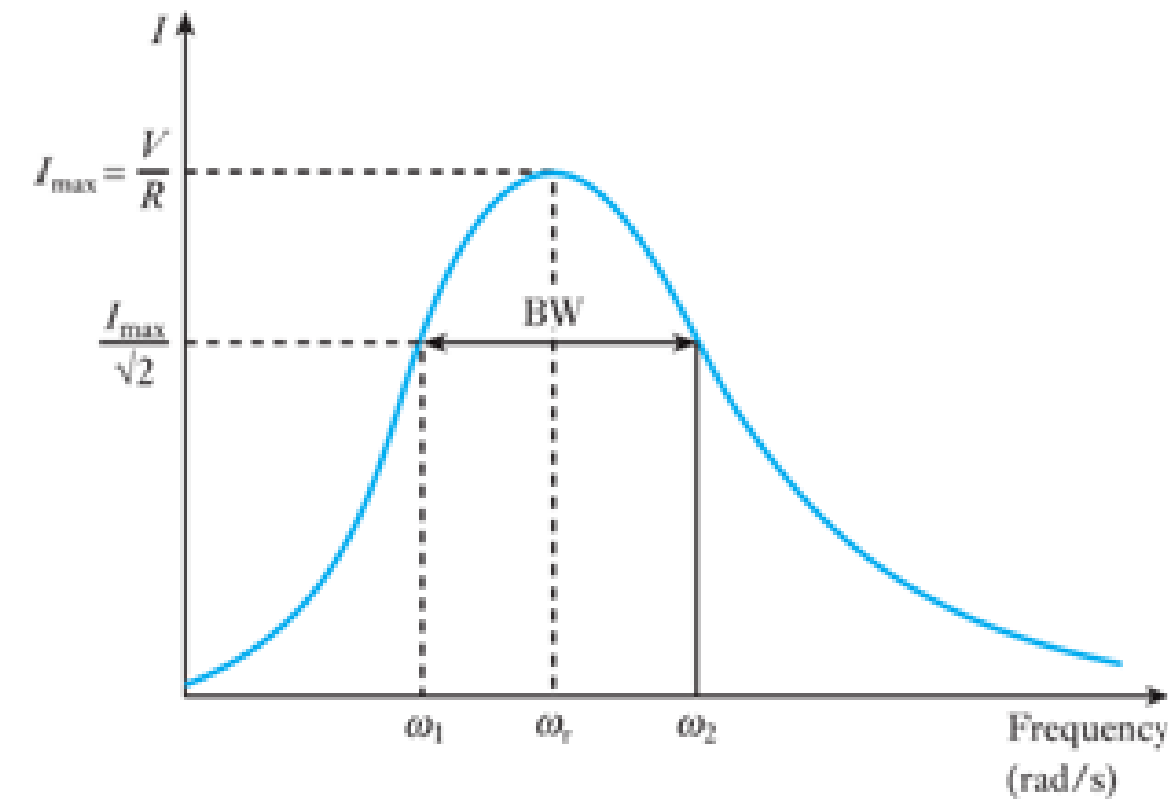- At the half-power points, the phase angle of the current is  $45^\circ$ . Below the resonant frequency, at  $\omega_1$ , the circuit is capacitive and  $Z(\omega_1) = R(1 - j1)$ .
- Above the resonant frequency, at  $\omega_2$ , the circuit is inductive and  $Z(\omega_2) = R(1 + j1)$ .





## Bandwidth and Half Power Frequencies

- Now, the circuit impedance is given by,


$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right) = R\left(1 + j\left(\frac{\omega L}{R} - \frac{1}{\omega CR}\right)\right)$$

- At half power points,  $Z = R(1 \pm j1)$
- By comparison of above two equations, resulting in

$$\frac{\omega L}{R} - \frac{1}{\omega CR} = \pm 1$$

- As we know,
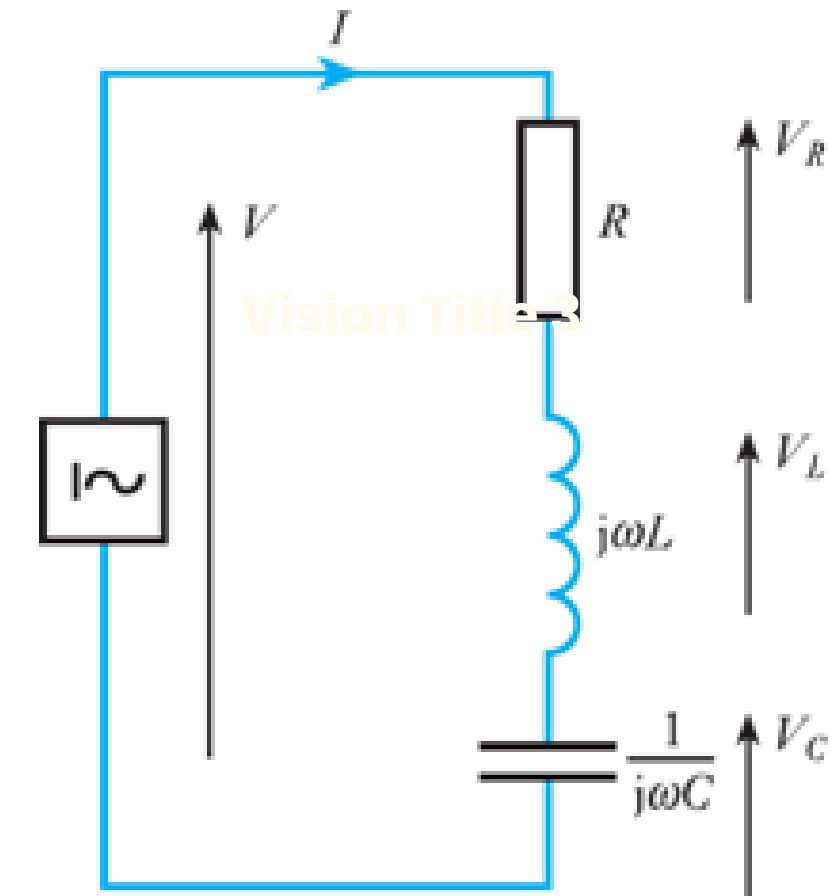
$$Q = \frac{\omega_r L}{R} = \frac{1}{\omega_r CR}$$





## Bandwidth and Half Power Frequencies

- Now, by multiplying and dividing with  $\omega_r$ :


$$\frac{\omega L \omega_r - 1}{R \omega} = \pm 1 \Rightarrow \frac{\omega}{\omega_r} Q - \frac{\omega_r}{\omega} Q = \pm 1 \Rightarrow Q \left( \frac{\omega}{\omega_r} - \frac{\omega_r}{\omega} \right) = \pm 1$$

- For  $\omega_2$ :

$$Q \left( \frac{\omega_2}{\omega_r} - \frac{\omega_r}{\omega_2} \right) = 1$$

- For  $\omega_1$ :
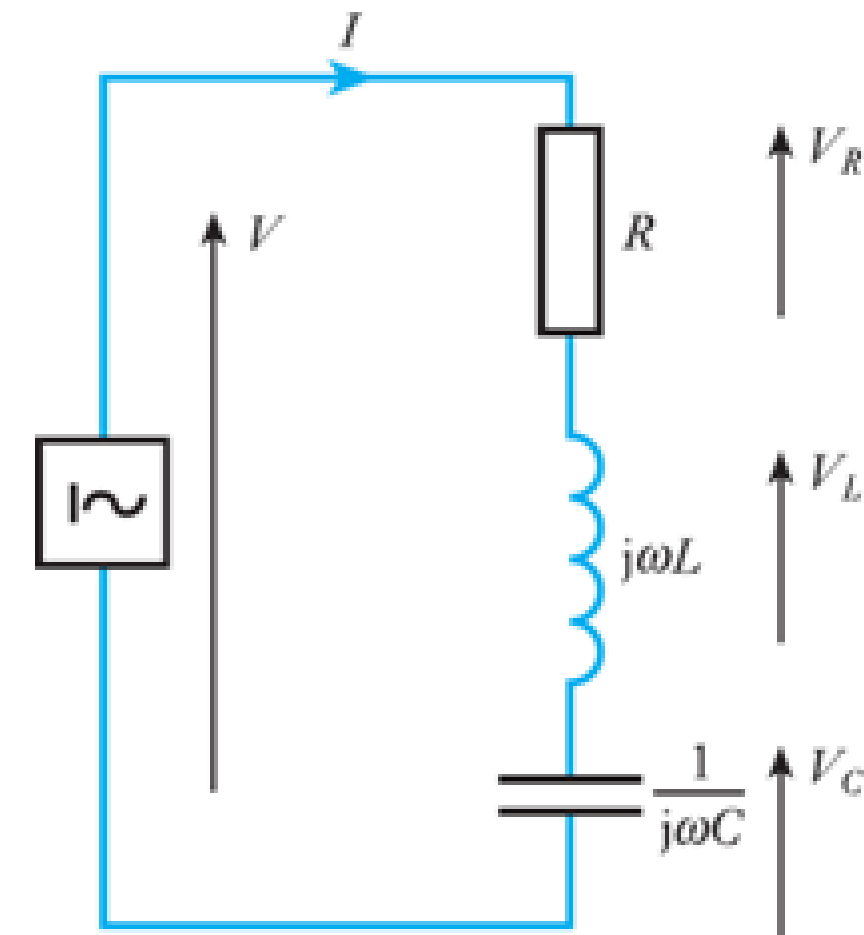
$$Q \left( \frac{\omega_1}{\omega_r} - \frac{\omega_r}{\omega_1} \right) = -1$$






# Bandwidth and Half Power Frequencies

- The half-power frequencies  $\omega_2$  and  $\omega_1$  are obtained as,

$$\omega_2 = \frac{\omega_r}{2Q} + \omega_r \sqrt{1 + \frac{1}{4Q^2}}$$
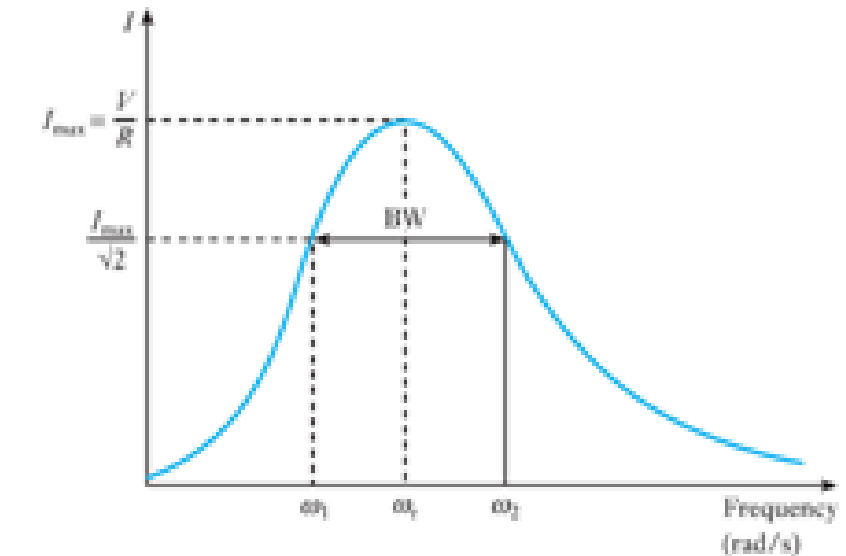
$$\omega_1 = \frac{-\omega_r}{2Q} + \omega_r \sqrt{1 + \frac{1}{4Q^2}}$$




- The bandwidth is obtained as:

$$BW = \omega_2 - \omega_1 = \frac{\omega_r}{Q} \text{ i.e. Bandwidth} = \frac{\text{Resonant frequency}}{Q \text{ factor}}$$

- Resonant frequency in terms of  $\omega_2$  and  $\omega_1$ , is expressed as:

$$\omega_r = \sqrt{\omega_1 \omega_2}$$

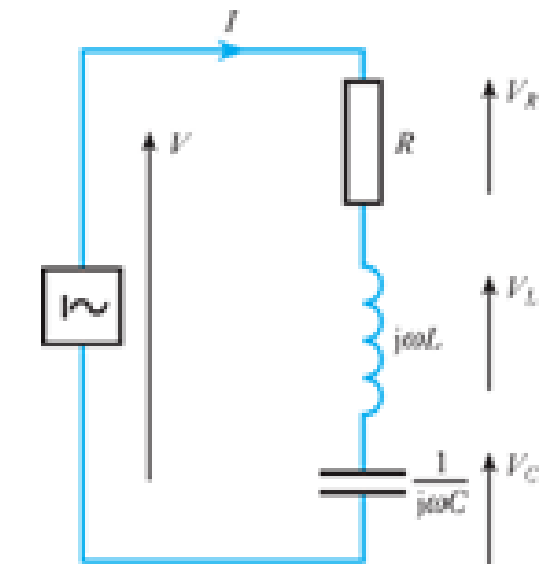




## Bandwidth and Half Power Frequencies

The bandwidth is also expressed as:

$$\omega_2 - \omega_1 = \frac{\omega_r}{Q} \Rightarrow \omega_2 - \omega_1 = \frac{R}{L} \text{ rad/s}$$

(or)
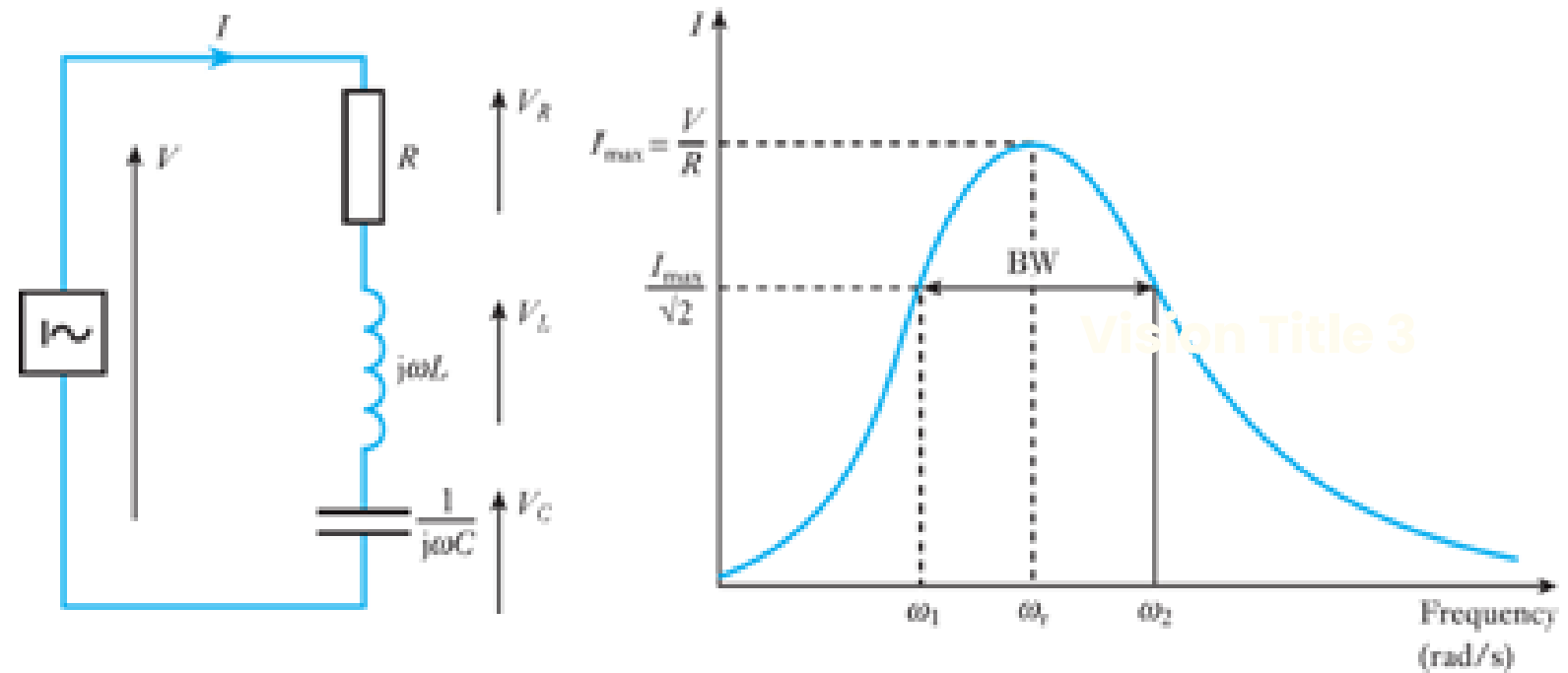
$$f_2 - f_1 = \frac{R}{2\pi L} \text{ Hz}$$



For  $Q \gg 1$ ,

$$\omega_r - \omega \approx \frac{BW}{2} \Rightarrow \omega = \omega_r - \frac{BW}{2} \Rightarrow \omega = \omega_r - \frac{R}{2L} \text{ rad/s}$$

$$\omega_2 - \omega \approx \frac{BW}{2} \Rightarrow \omega = \omega_2 + \frac{BW}{2} \Rightarrow \omega = \omega_2 + \frac{R}{2L} \text{ rad/s}$$