



# **SNS COLLEGE OF TECHNOLOGY**

## **(AN AUTONOMOUS INSTITUTION)**

Approved by AICTE & Affiliated to Anna University  
Accredited by NBA & Accredited by NAAC with 'A+' Grade,  
Recognized by UGC saravanampatti (post), Coimbatore-641035.



## **Department of Biomedical Engineering**

**Course Name: 23BMT201 & Circuit Analysis**

**I Year : II Semester**

**Unit V – RESONANCE CIRCUITS & COUPLED CIRCUITS**

**Topic : Parallel Resonance**




## Resonance in Parallel RLC Circuit

- The supply voltage:  $V = IZ$  where  $Z$  is the net impedance of the three parallel branches.
- In parallel circuits, it is simpler to consider the total admittance  $Y$  of the three branches. Thus,

$$V = IZ = \frac{I}{Y}$$

where
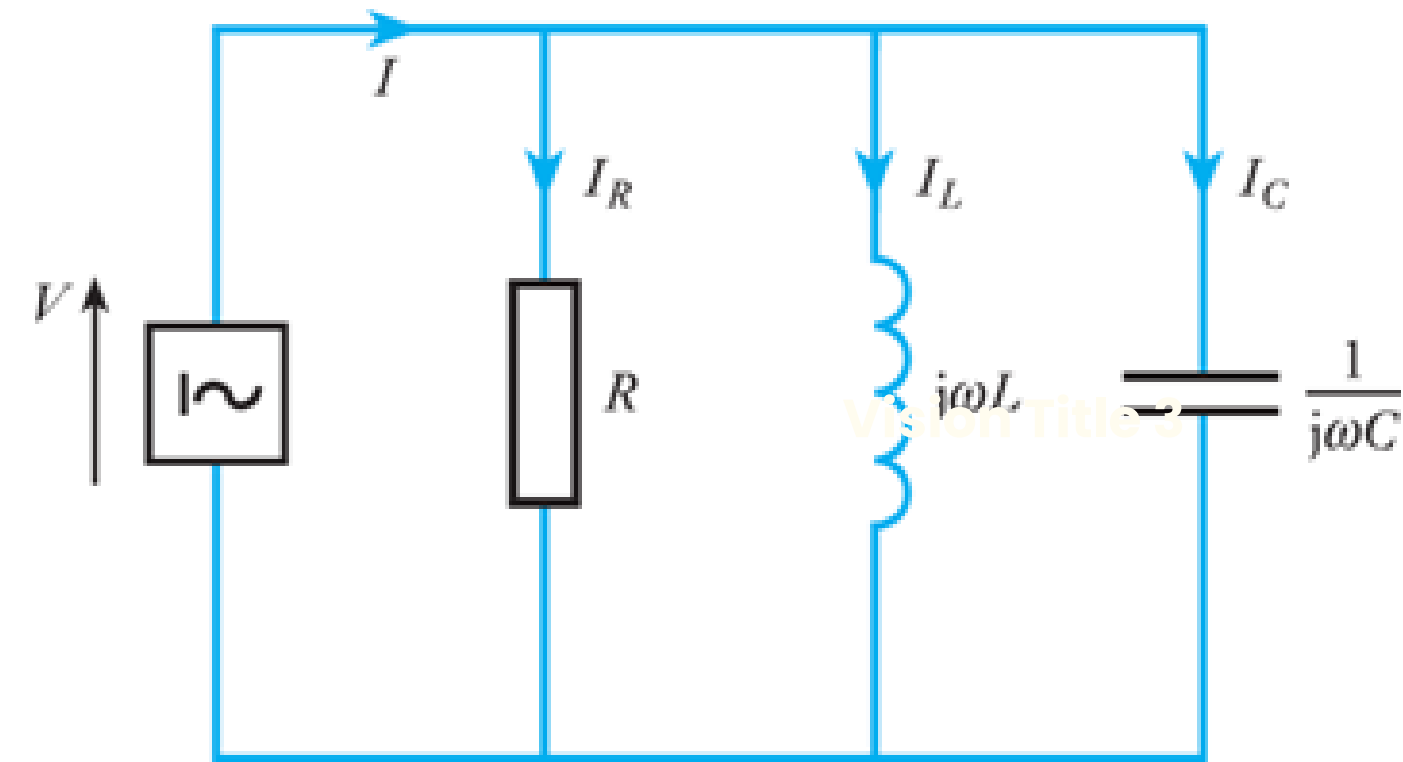
$$Y = G + \frac{1}{j\omega L} + j\omega C = G - \frac{j}{\omega L} + j\omega C = G + j\left(\omega C - \frac{1}{\omega L}\right)$$






## Resonance in Parallel RLC Circuit

- At resonance ( $\omega = \omega_r$ ), the net susceptance is zero.

i.e. 
$$\left( \omega C - \frac{1}{\omega L} \right) = 0$$

- Therefore, the resonant frequency ( $\omega_r$ ):
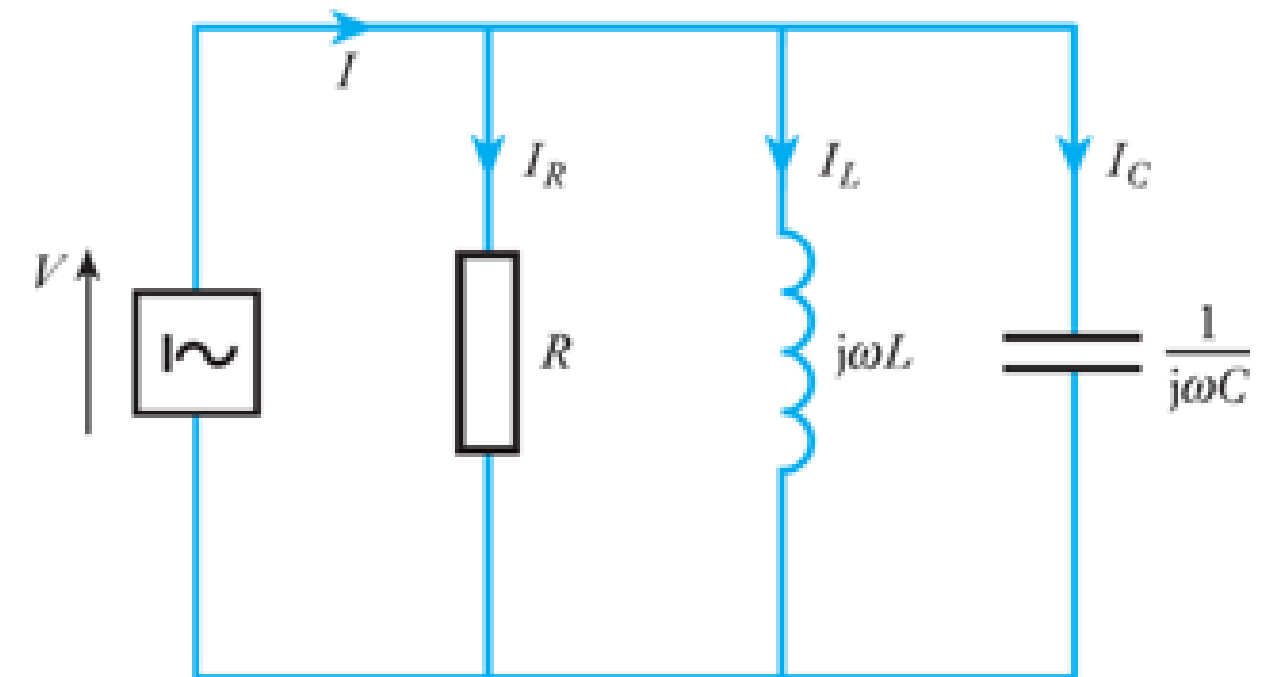
$$\omega_r = \frac{1}{\sqrt{LC}} \text{ rad/s}$$



- At the resonant frequency,  $Y = G = 1/R$ , the conductance of the parallel resistance, and  $I = VG$ .



## Current through Resistance


- The supply voltage magnitude:

$$|V| = \frac{|I|}{\sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}}$$

- At resonance,  $\omega = \omega_r$ ,

$$|V| = \frac{|I|}{\sqrt{\frac{1}{R^2} + (0)^2}} \Rightarrow |V| = |I| \times R$$

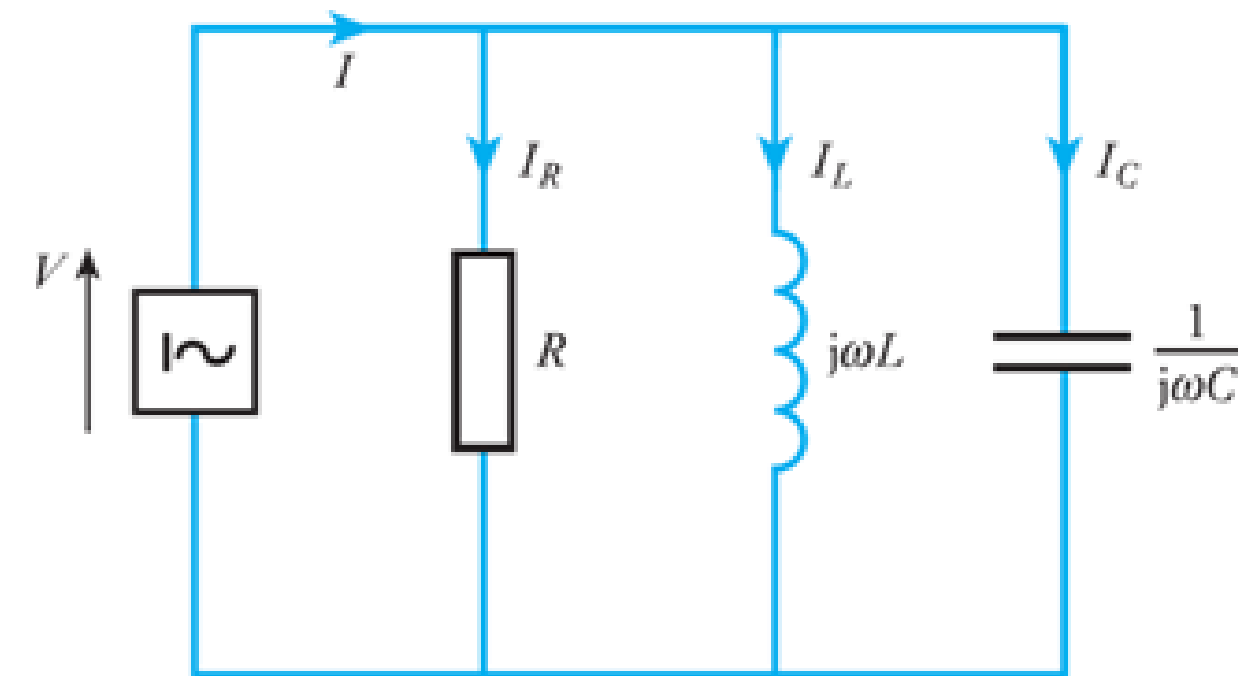- Current through the resistance at  $\omega_r$ :  $I_R = \frac{V_R}{R} = \frac{V}{R} = \frac{I \times R}{R} \Rightarrow I_R = I$



The three-branch parallel resonant circuit



# Current Magnification

- Magnitude of current through inductor at  $\omega_r$ :


$$|I_L| = \frac{V}{X_L} = \frac{I \times R}{\omega_r L} = \left( \frac{R}{\omega_r L} \right) \times I = Q \times I$$

- Magnitude of current through capacitor at  $\omega_r$ :

$$|I_C| = \frac{V}{X_C} = \frac{I \times R}{1/\omega_r C} = (\omega_r CR) \times I = Q \times I$$

where  $Q$  is the current magnification i.e.,
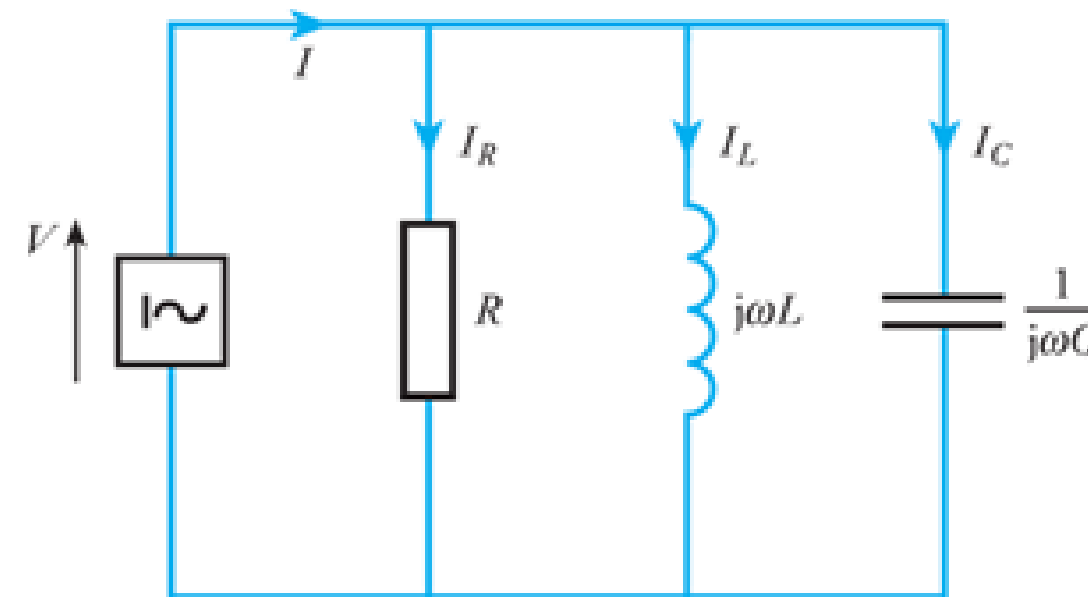
$$Q = \left( \frac{R}{\omega_r L} \right) = (\omega_r CR)$$



The three-branch parallel resonant circuit




## Current Magnification

Current magnification  $Q$  is also expressed in terms of inductive or capacitive susceptance ( $B$ ), inductive or capacitive reactance ( $X$ ) and conductance ( $G$ ) :

$$Q = \left( \frac{1}{\omega_r L G} \right) = \left( \frac{\omega_r C}{G} \right) = \left( \frac{B}{G} \right) = \left( \frac{R}{X} \right)$$

By substituting  $\omega_r = 1/\sqrt{LC}$  in  $Q$  :
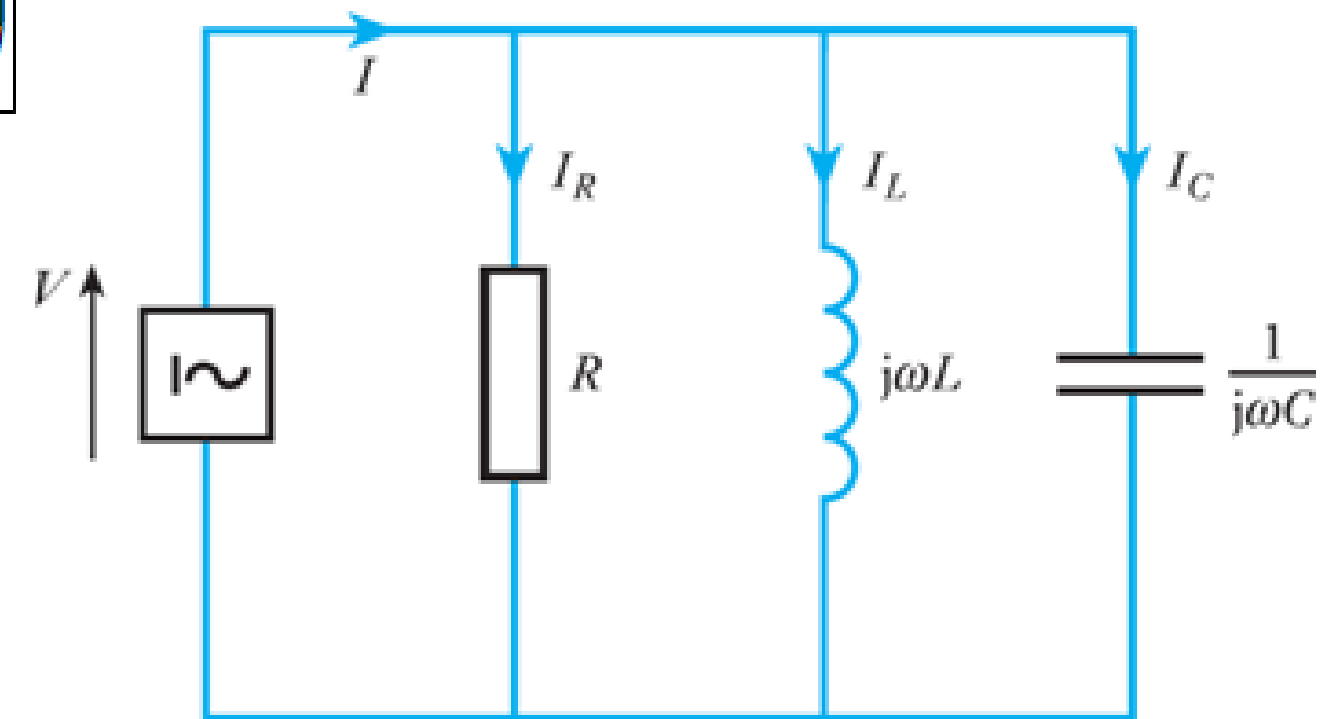
$$Q = \frac{1}{G} \sqrt{\frac{C}{L}} = R \sqrt{\frac{C}{L}}$$



The three-branch parallel resonant circuit




## Bandwidth and Half Power Frequencies

The parallel  $RLC$  circuit is the dual of the series  $RLC$  circuit. Therefore, by replacing  $R$ ,  $L$ , and  $C$  in the expressions for the series circuit with  $1/R$ ,  $C$ , and  $L$  respectively, we obtain for the parallel circuit, the  $Y_{\min}/2^{1/2}$  frequencies:

$$\omega_1 = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \quad \omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

Vision Title 3

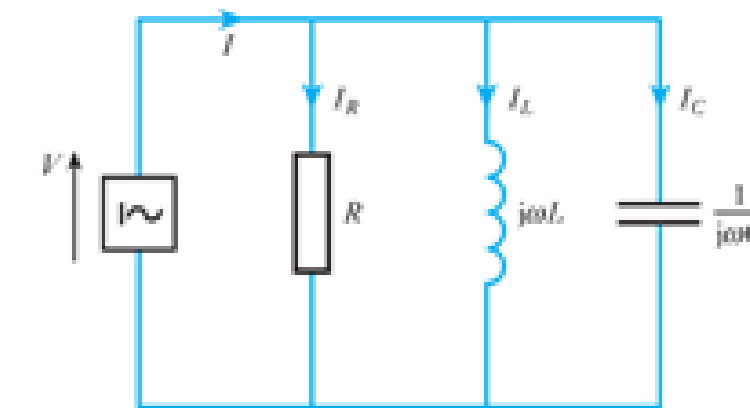- **Bandwidth:**  $BW = \omega_2 - \omega_1 = \frac{1}{RC}$



- **Relation between BW and Q:**  $Q = \frac{\omega_r}{BW} = \omega_r RC = \frac{R}{\omega_r L}$



# Bandwidth and Half Power Frequencies

The half-power frequencies in terms of quality factor:


$$\omega_1 = \omega_r \sqrt{1 + \left(\frac{1}{2Q}\right)^2} - \frac{\omega_r}{2Q}$$

$$\omega_2 = \omega_r \sqrt{1 + \left(\frac{1}{2Q}\right)^2} + \frac{\omega_r}{2Q}$$

For  $Q \gg 1$ ,

$$\omega_r - \omega_1 = \frac{BW}{2}$$

$$\omega_2 - \omega_r = \frac{BW}{2}$$

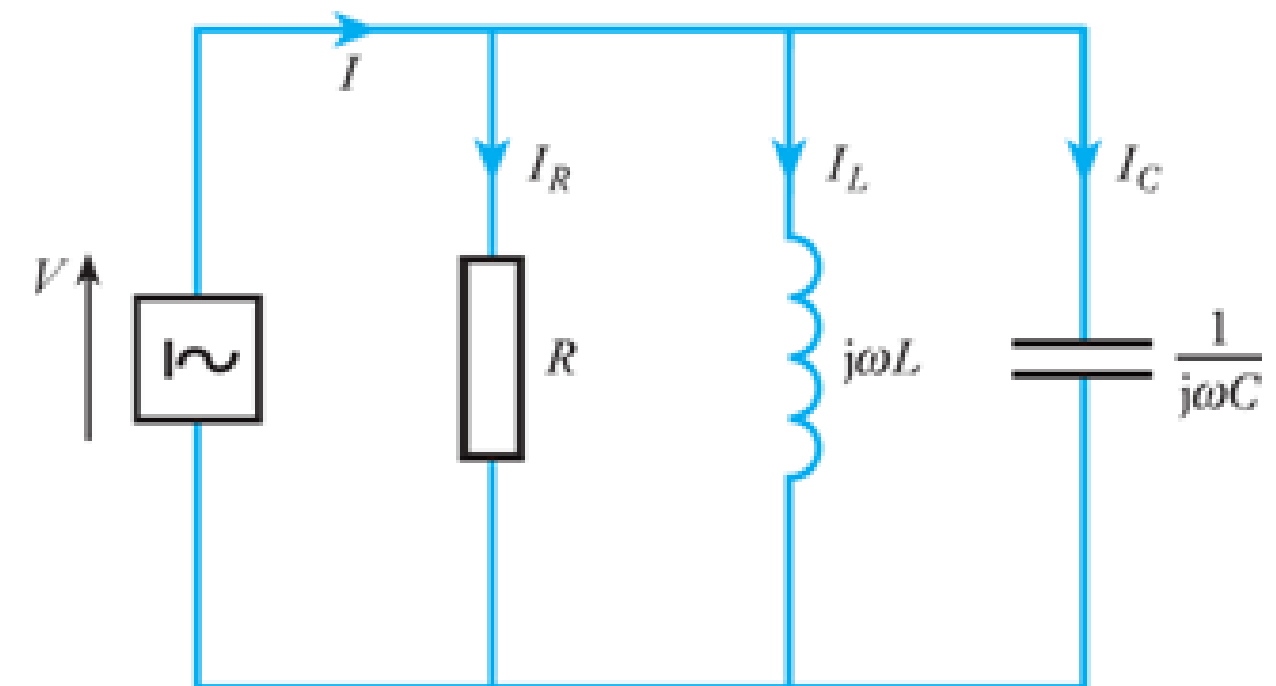

The three-branch parallel resonant circuit