



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A++’ Grade (III Cycle)

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

COURSE CODE & NAME: 23ECB202 LINEAR INTEGRATED CIRCUITS

II YEAR/IV SEMESTER

UNIT 1- OPAMP CHARACTERISTICS

TOPIC 1- INTRODUCTION OF OPERATIONAL AMPLIFIERS (Op-Amps)



OUTLINE

- What is an Op-Amp?
- Why Study Op-Amps?
- Anatomy of an Op-Amp (IC 741)
- Ideal vs. Practical Op-Amp Characteristics
- Op-Amp Configurations
- Applications of Op-Amps
- Real-Life Examples of Op-Amps
- Summary



What is an Op-Amp?

Definition:

- - An Operational Amplifier (Op-Amp) is an integrated circuit (IC) that can amplify weak electrical signals.
- - It has two inputs and one output.

Purpose:


- - Originally designed for mathematical operations like addition, subtraction, integration, and differentiation.

Basic Uses:

- - Amplifiers, filters, oscillators, and comparators.



What is an Op-Amp?

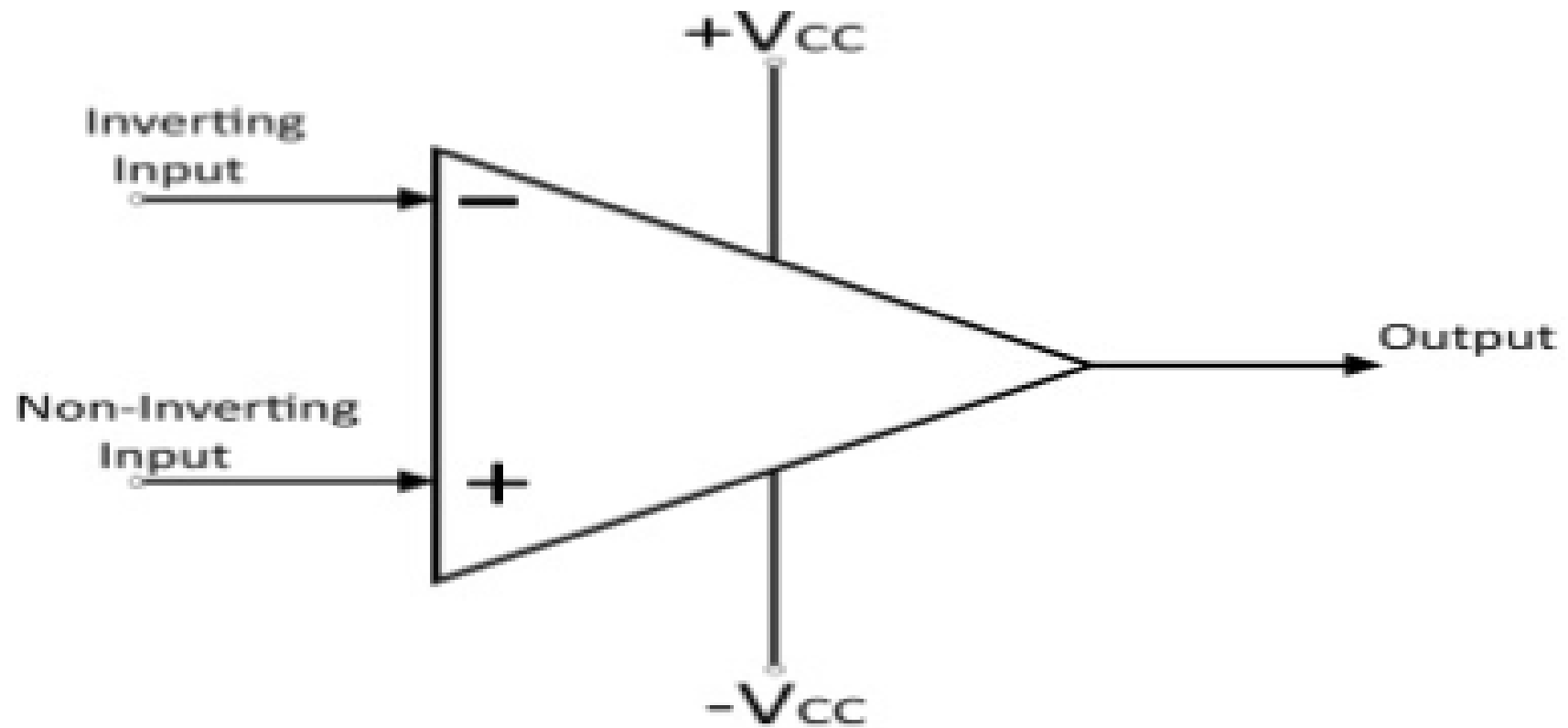



Why Study Op-Amps?

Key Reasons:

- - **Versatility:** Used in nearly all analog electronic devices.
- - **Foundation of Electronics:** Helps understand advanced analog and mixed-signal designs.
- - **Applications:** Found in audio systems, communication devices, and control systems.

Examples:

- - Audio amplifiers, ECG machines, and sensors.



Anatomy of an Op-Amp (IC 741)

Internal Block Diagram of IC 741:

- - Input Stage: Differential amplifier for high input impedance.
- - Gain Stage: Amplifies the signal further.
- - Output Stage: Provides low output impedance to drive loads.



Pin Configuration:

- - Power supply pins (V_+ and V_-).
- - Input pins (Inverting $-$ and Non-Inverting $+$).
- - Output pin.



Anatomy of an Op-Amp (IC 741)

Internal Block Diagram of IC 741:

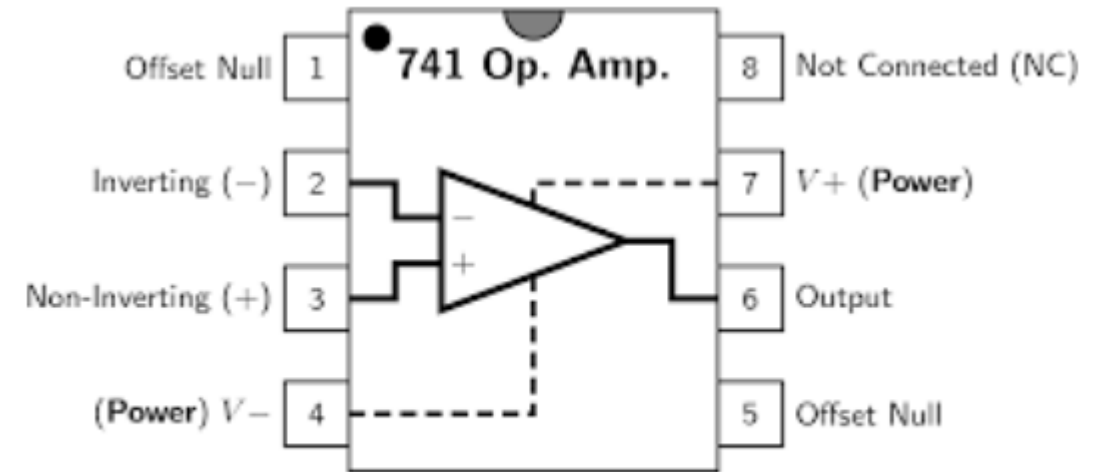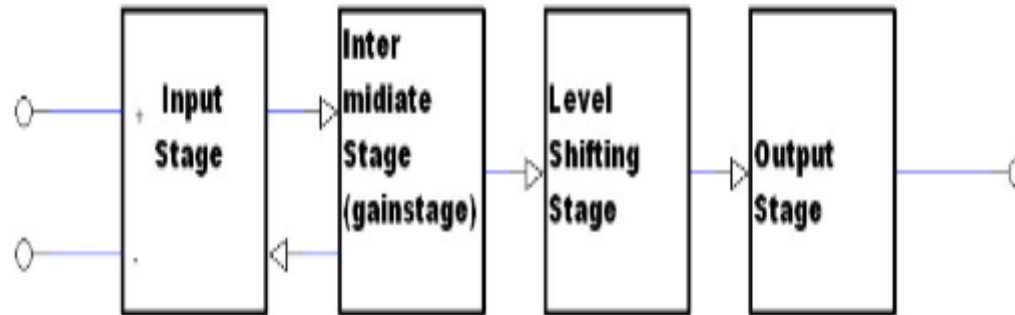

IC 741 Pin Diagram



Ideal vs. Practical Op-Amp Characteristics

Parameter	Ideal Op-Amp	Practical Op-Amp
Input Impedance	Infinite	High (~1 M Ω)
Output Impedance	Zero	Low (~100 Ω)
Open-Loop Gain	Infinite	Finite (100,000-1,000,000)
Bandwidth	Infinite	Limited (1 MHz typical for 741)
Slew Rate	Infinite	Limited (0.5 V/ μ s for 741)



Op-Amp Configurations



Two Main Configurations:

1. Open-Loop Configuration:

- Operates without feedback.
- Used in applications like comparators.

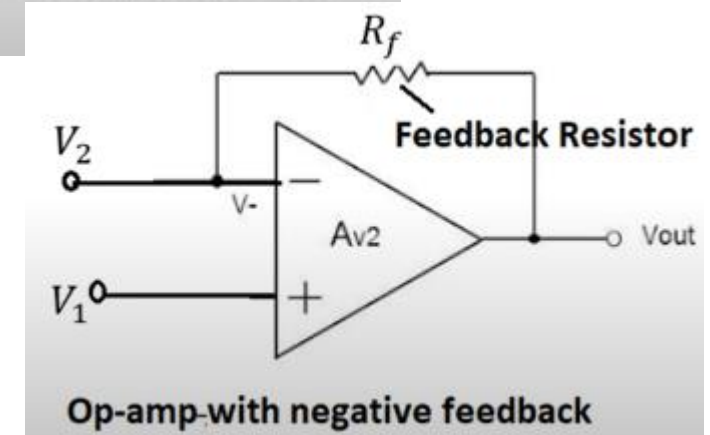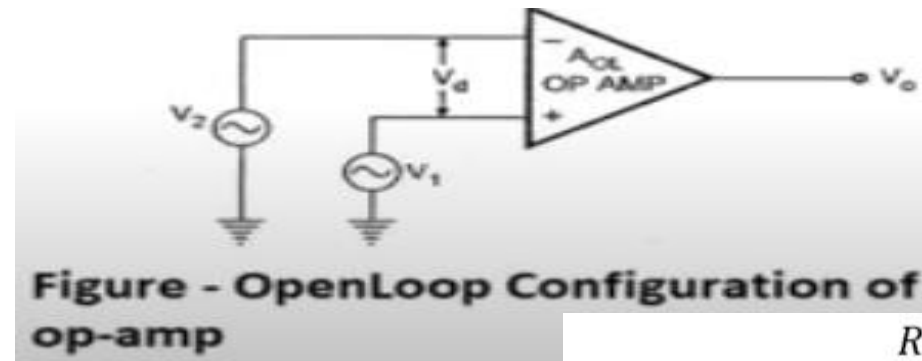2. Closed-Loop Configuration:

- Feedback is applied to control gain and improve stability.
- Used in amplifiers.












ACTIVITY




SOLVE IF YOU CAN

3	2	=	7
5	4	=	23
7	6	=	47
9	8	=	79
10	9	=	?

 +  +  = **60**

 +  = **26**

 +  = **15**

 +  ×  = **???**



Applications of Op-Amps

- Inverting Amplifier:
 - - Inverts and amplifies the input signal.
 - - Formula: $V_{out} = -(R_f/R_{in}) * V_{in}$

- Non-Inverting Amplifier:
 - - Amplifies the input without inverting it.
 - - Formula: $V_{out} = (1 + R_f/R_1) * V_{in}$.



Real-Life Examples of Op-Amps

Audio Amplifiers: Amplify microphone signals.

Filters: Remove noise in communication systems.

Voltage Comparators: Used in digital logic circuits.



ASSESSMENT

1. What does an Op-Amp do?

- a) Amplifies signals
- b) Reduces noise
- c) Converts AC to DC
- d) Stores energy

Correct Answer: **a) Amplifies signals**

2. Which of the following is an ideal Op-Amp characteristic?

- a) Infinite gain
- b) Zero output impedance
- c) Infinite input impedance
- d) All of the above

Correct Answer: **d) All of the above**

3. What is the gain formula for a non-inverting amplifier?

- a) Gain = $-R_f/R_1$
- b) Gain = $1 + (R_f/R_1)$
- c) Gain = V_{in}/V_{out}
- d) Gain = $1 - (R_f/R_1)$

Correct Answer: **b) Gain = $1 + (R_f/R_1)$**

4. In an Op-Amp, the term 'slew rate' refers to:

- a) The speed at which an Op-Amp operates
- b) The maximum rate of change of the output voltage
- c) The bandwidth of the amplifier
- d) The input impedance of the amplifier

Correct Answer: **b) The maximum rate of change of the output voltage**

5. What is the primary use of the IC 741 Op-Amp?

- a) Digital processing
- b) Signal amplification
- c) Voltage regulation
- d) Signal storage

Correct Answer: **b) Signal amplification**



SUMMARY

THANK YOU...