



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB202 – LINEAR INTEGRATED CIRCUITS

II YEAR/ III SEMESTER
1

UNIT 1 – OP AMP CHARACTERISTICS

TOPIC 1- 6 AC characteristics of Op Amp

2/22/2025



AC Characteristics




- Purpose of this circuit is to amplify a small **AC** input signal, such as an audio or radio frequency signal
- A small **AC** voltage is applied to the input, through a coupling capacitor
- Hence, such a circuit is useful only as an **AC amplifier**
- To amplify DC signals separate operational **amplifier** circuit is used
- For small signal sinusoidal applications the AC characteristics are
 1. Frequency response.
 2. Slew rate



Frequency response



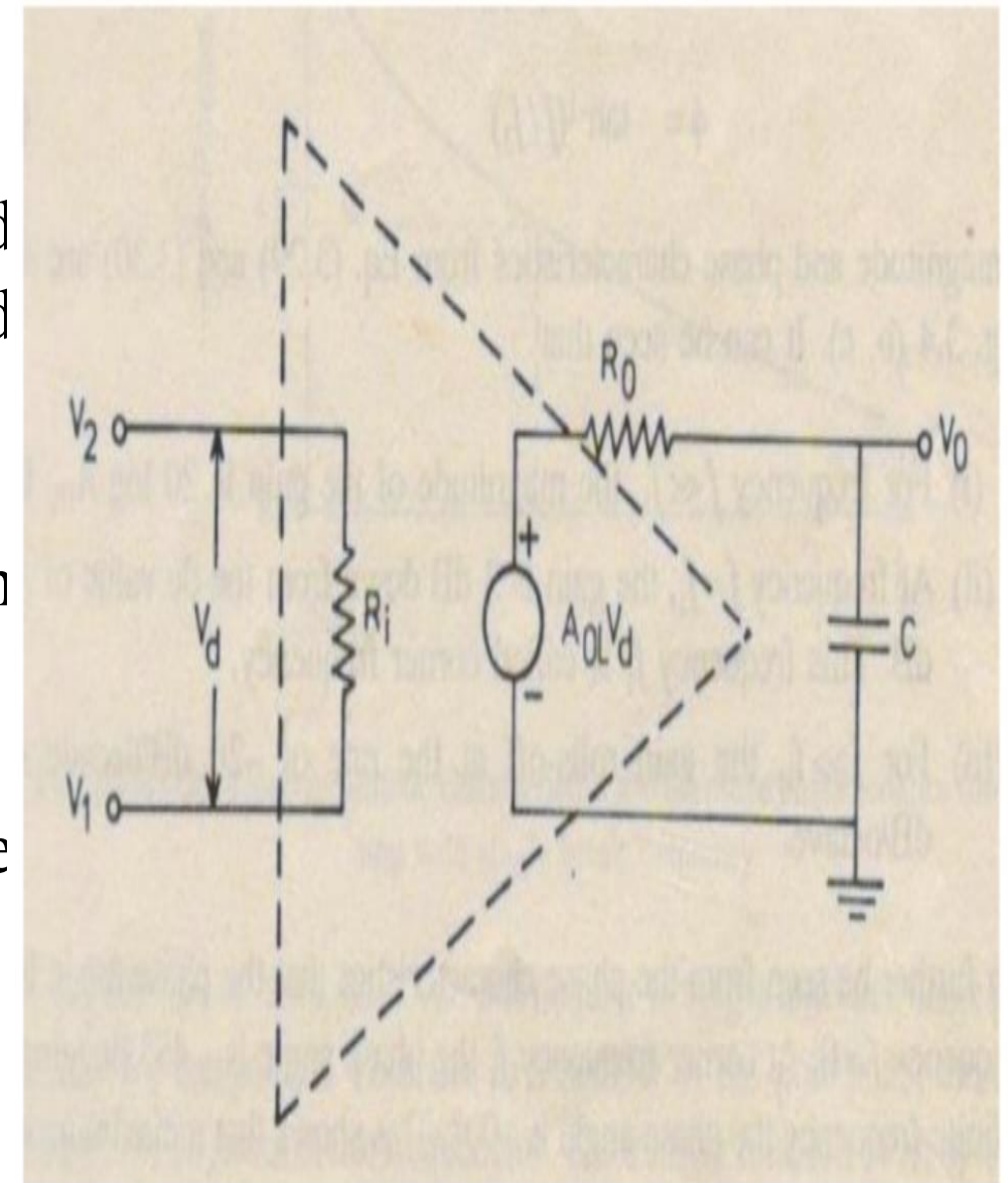- An ideal op-amp has infinite band width
- Its open loop gain is 90dB with d.c.signal and this gain should remain the same through audio and radio frequency
- But practically op-amp gain decreases at high frequency
- This is due to a capacitive component in the equivalent circuit of op-amp.




HIGH FREQUENCY MODEL OF OPAMP



Frequency response



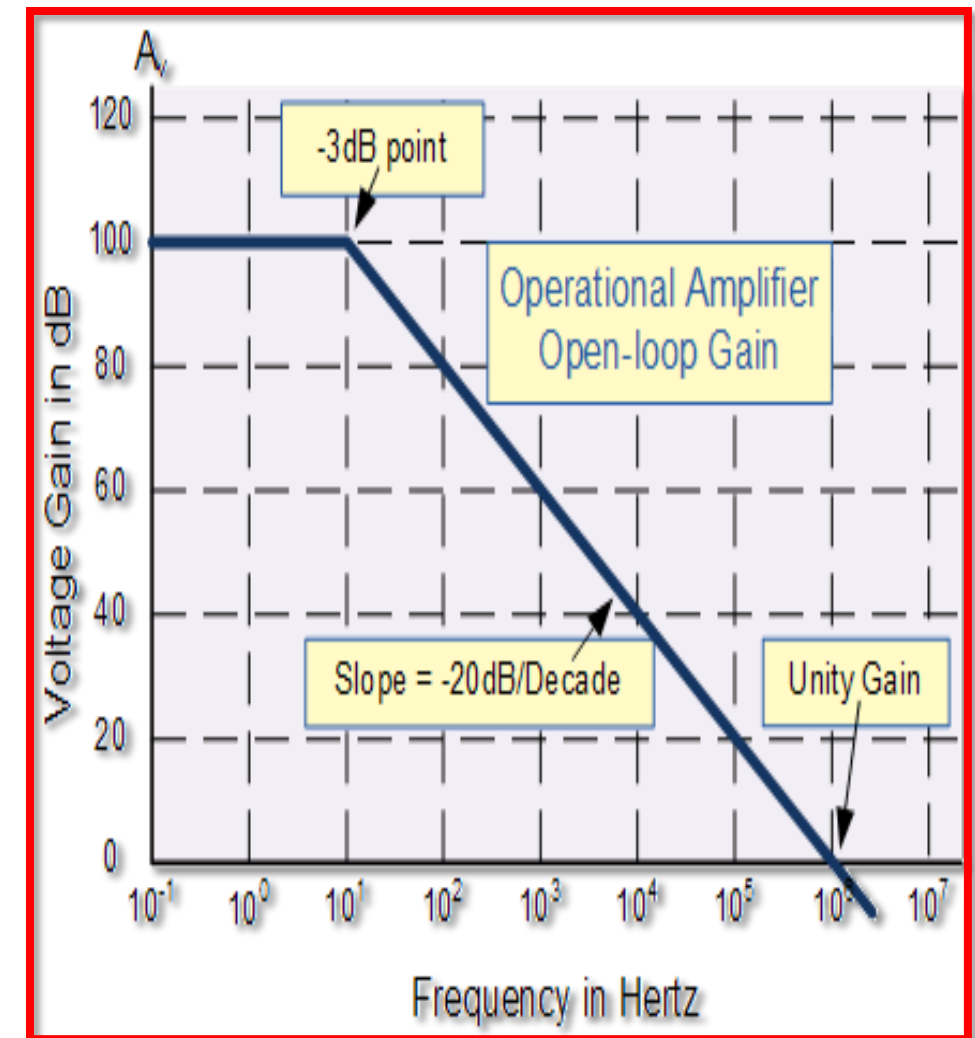- An ideal op-amp has infinite band width
- Its open loop gain is 90dB with d.c.signal and this gain should remain the same through audio and radio frequency
- But practically op-amp gain decreases at high frequency
- This is due to a capacitive component in the equivalent circuit of op-amp.





THANK YOU