



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **23ECB202 – LINEAR INTEGRATED CIRCUITS**

**II YEAR/ IV SEMESTER**

#### **UNIT 1 – OP AMP CHARACTERISTICS**

##### **TOPIC 1- 5 DC characteristics of Op Amp**

2/22/2025



# Why DC Characteristics?




- An ideal op- amp draws no current from the source and its response is also independent of temperature
- An real op-amp does not work this way
- Current is taken from the source into the op-amp inputs
- Also the inputs respond differently to current and voltage due to mismatch in transistors
- A real op-amp also shifts its operation with temperature
- In this case, these non- ideal dc characteristics that add error components to the dc output voltage



# DC Characteristics



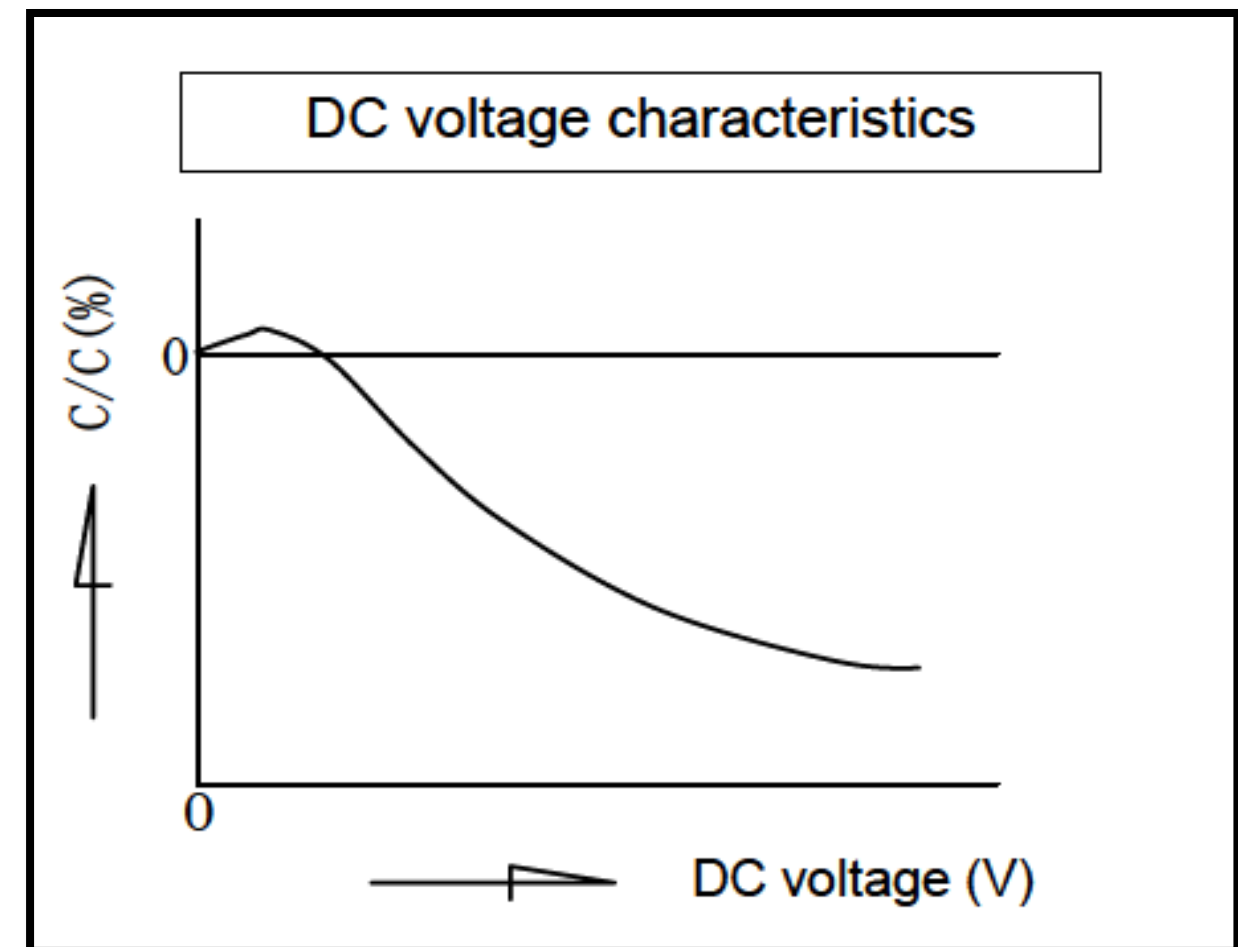1. Input bias current
2. Input offset current
3. Input offset voltage
4. Thermal drift






# Input bias current



- The op-amp's input is differential amplifier, which may be made of BJT or FET. In an ideal op-amp, we assumed that no current is drawn from the input terminals the base currents entering into the inverting and non-inverting terminals ( $I_{B-}$  &  $I_{B+}$  respectively)
- Even though both the transistors are identical,  $I_{B-}$  and  $I_{B+}$  are not exactly equal due to internal imbalance between the two inputs
- Input bias current and Inverting amplifier with bias currents



# Input bias current

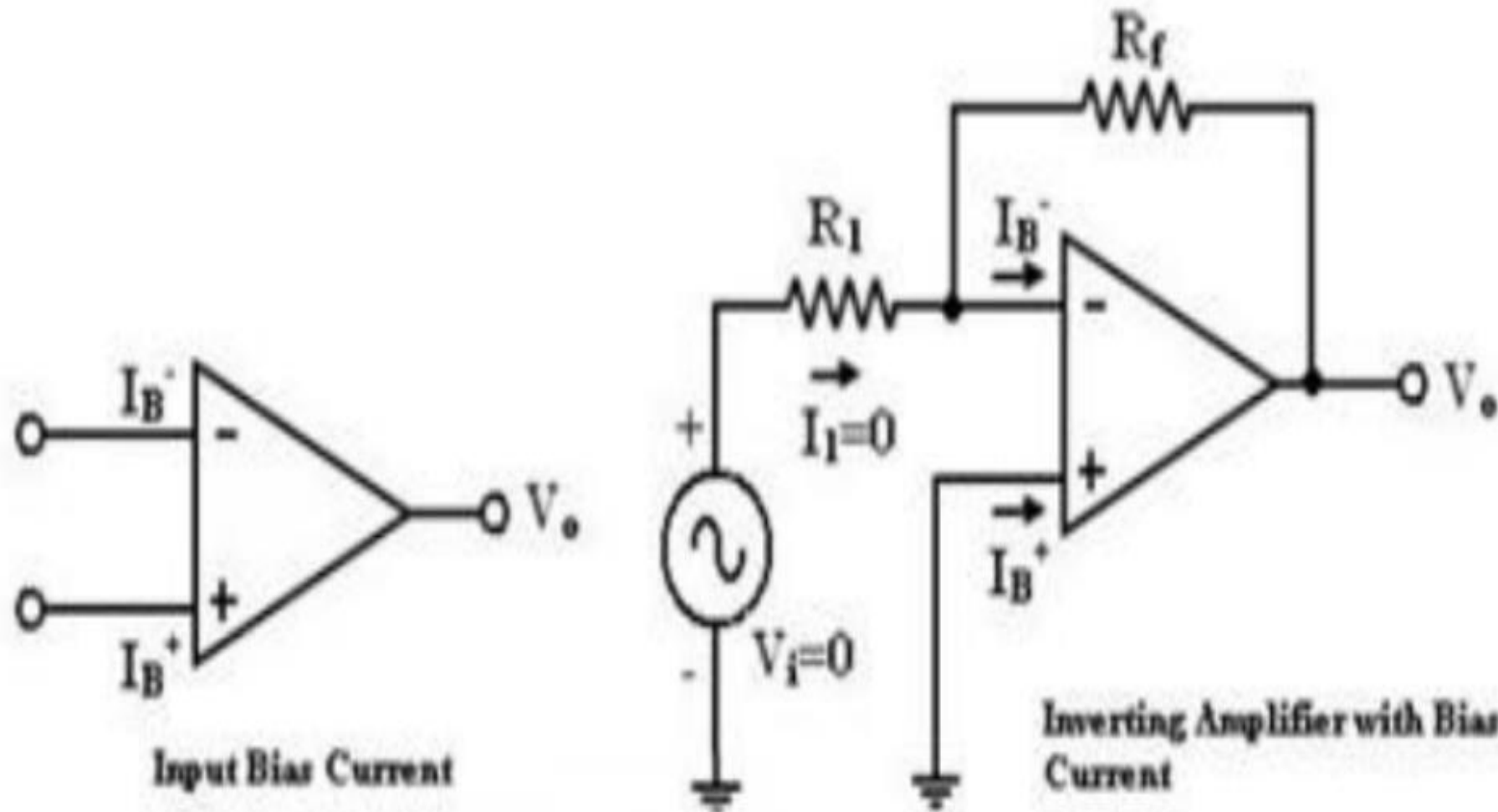


$$I_B = \frac{I_{b1} + I_{b2}}{2}$$


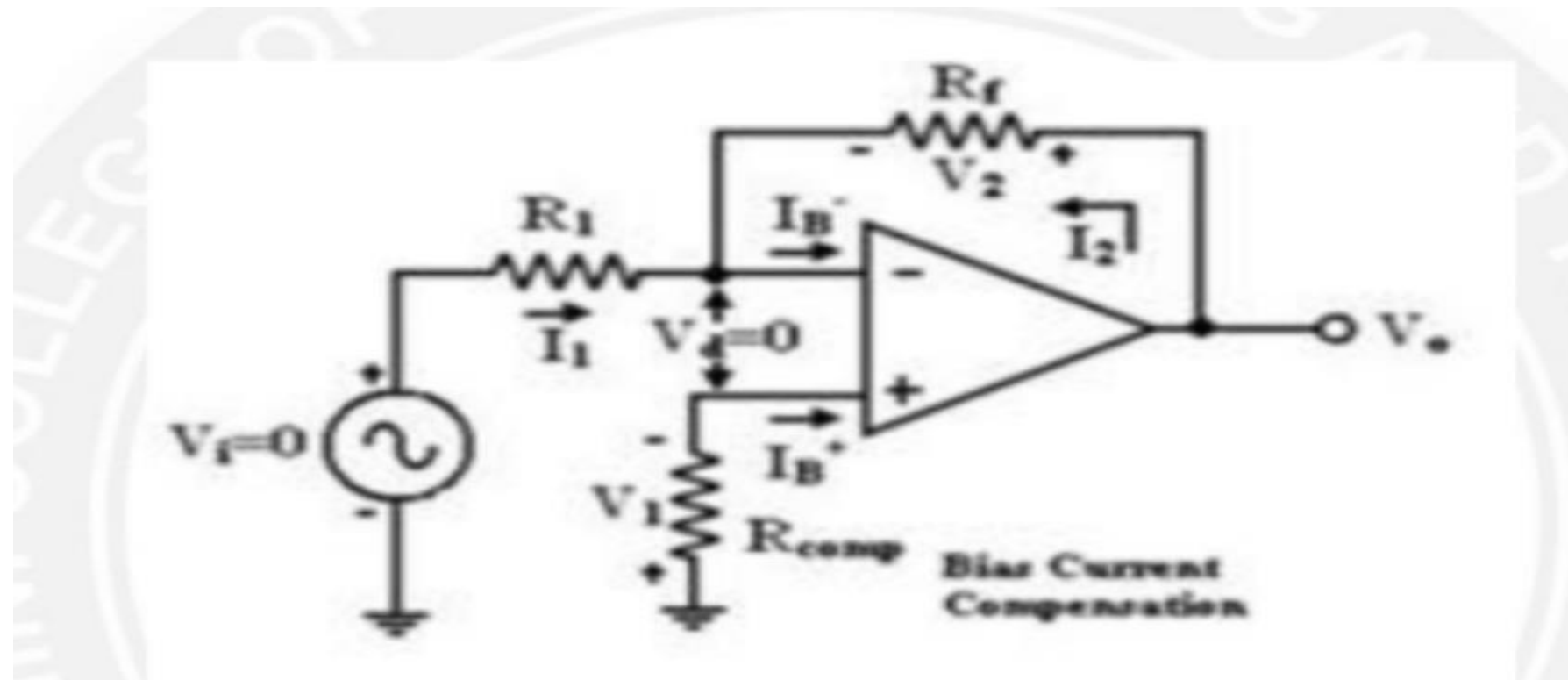
# Input bias current



- In application where the signal levels are measured in mV, this is totally unacceptable
- This can be compensated by a compensation resistor  $R_{comp}$  has been added between the non-inverting input terminal and ground







# Input offset current




- The input stage of the op-amp is dual input differential amplifier
- Hence the input currents of op-amp are the base currents of the transistors used in the input stage
- Due to transistor mismatch these currents differ
- The algebraic difference between the currents flowing into the two input terminals of the op-amp is called input offset current and denoted as  $I_{ios}$
- It is given by,

$$I_{ios} = |I_{b1} - I_{b2}|$$


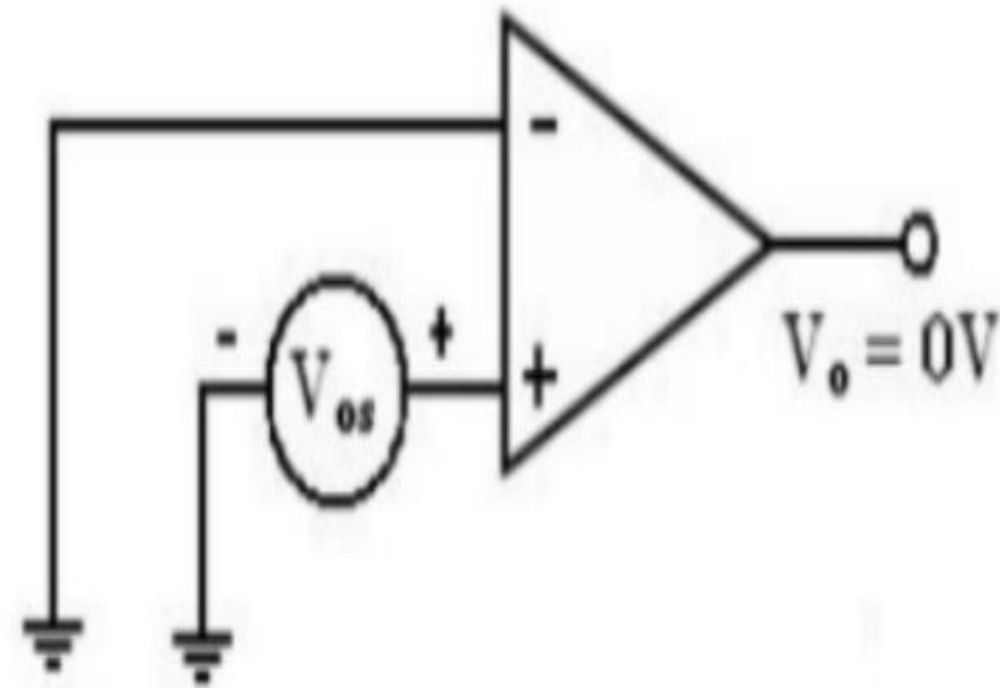
# Input Offset Voltage

- Input **offset voltage** is the differential **voltage** which is required to apply between the two terminals of the **op-amp** such that the **output** of the **op-amp** will become zero when no input is applied to the **op-amp**
- **Output offset voltage** is the multiplication of DC gain and the input **offset voltage**







# Thermal Drift



- **Thermal drift** is the changes in the normal operational behaviour of a device due to changes in ambient temperature
- **Drift** caused by internal heating of equipment during normal operation or by changes in external ambient temperature
- There are very few circuit techniques that can be used to minimize the effect of drift
- Careful printed circuit board layout must be equal be used to keep op-amps away from source of heat
- Forced air cooling may be used to stabilize the ambient temperature



**THANK YOU**