



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **23ECB202 – LINEAR INTEGRATED CIRCUITS**

II YEAR/ III SEMESTER  
1

#### **UNIT 1 – OP AMP CHARACTERISTICS**

**TOPIC 1- 8- Slew Rate & Frequency Compensation of Op Amp**




# Slew rate



- The slew rate is defined as the maximum rate of change of output voltage caused by a step input voltage.,

Specified in  $V/\mu s$

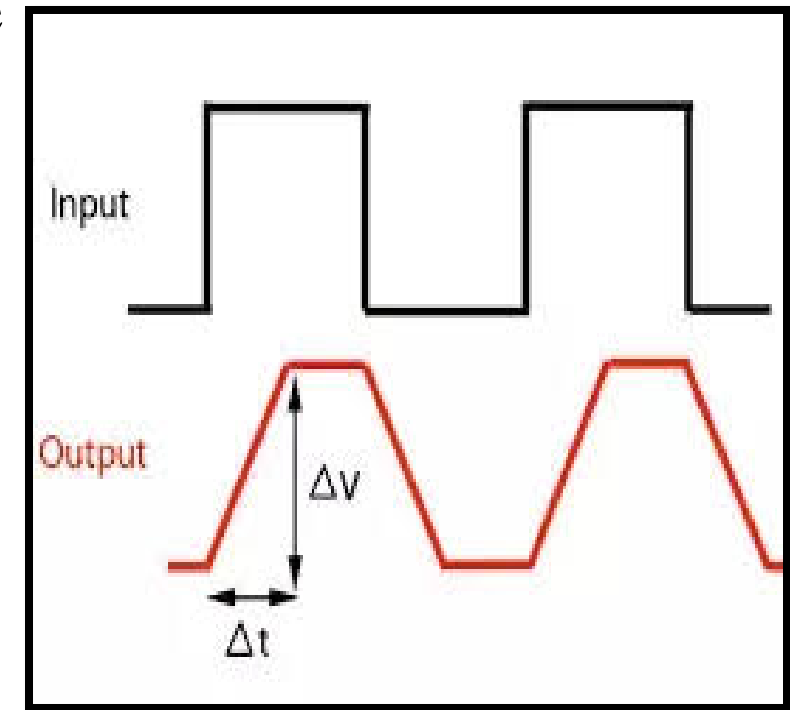eg : 1V/micro sec. slew rate denotes the output rises or falls by 1 volts in 1 micro seconds



- The rate at which the voltage across the capacitor  $dV_c/dt$  is given by

$$dV_c/dt = I/C, \text{ Slew rate } SR \ dV_c/dt|_{\max} = I_{\max}/C$$

- For IC741,  $I_{\max} = 15$  micro amps,  $C = 30$  Pico farad

$$\text{Slew rate} = 0.5V/\text{micro sec}$$



# Frequency Compensation of Op Amp



- The major challenge is to improve the stability of an op-amp in a wide bandwidth of applications
- The solution is to compensate the amplifier in terms of frequency response, by using a frequency compensation circuit across the operational amplifier
- The stability of an amplifier is highly dependent on different parameters



# Frequency Compensation of Op Amp



## Types of Op-Amp Frequency Compensation

- External Frequency Compensation in Op Amp
  1. Dominant pole Compensation
  2. Miller compensation
  
- Internal Frequency Compensation in Op Amp



# External Frequency Compensation in Op Amp



- External compensation techniques vary depending on the application, type of amplifier used and many other things
- The easiest way is to use out-of loop compensation technique or in-loop compensation technique
- Out of the loop compensation technique uses a simple resistor to isolate the capacitive load with the op-amp, lowering the capacitive loading of the op-amp
- The resistor typically varies from 10-50 Ohms but the increase in isolated resistor effects the op-amp bandwidth
- The bandwidth of the op-amp drastically reduced to a very low value. One of the popular ways of out of the loop frequency compensation techniques is to use Dominant pole compensation technique



# Dominant pole Compensation





- This technique uses a simple **RC network** connected across the output of the operational amplifier circuit
- This works great to overcome the instability issue
- The RC network creates a pole at unity or 0dB gain that dominates or cancels out other high-frequency poles effect
- The transfer function of the dominant pole configuration

$$A(s) = \frac{A \times \omega_1 \times \omega_2 \times \omega_3}{(s + \omega_1) \times (s + \omega_2) \times (s + \omega_3)}$$

Where,

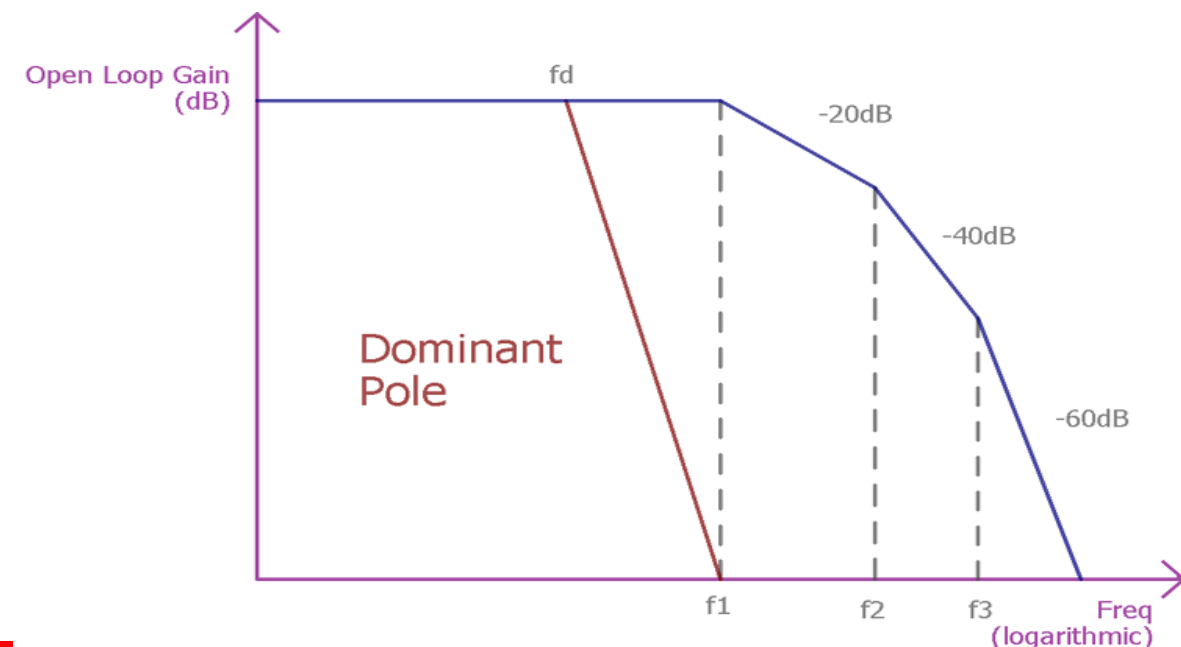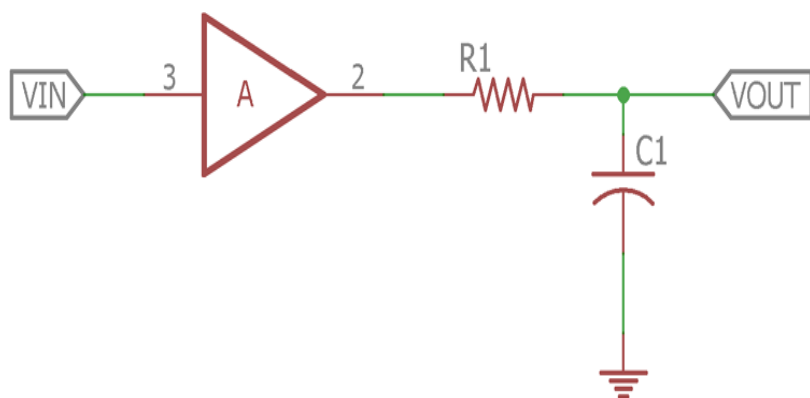- A(s) is the uncompensated transfer function
- A is the open-loop gain
- $\omega_1, \omega_2$ , and  $\omega_3$  are the frequencies where the gain roll-off at -20dB, -40dB, -60dB respectively
- The **Bode plot** below shows what happens if the dominant pole compensation technique is added across the op-amp output
- where  $f_d$  is the **dominant pole frequency**.





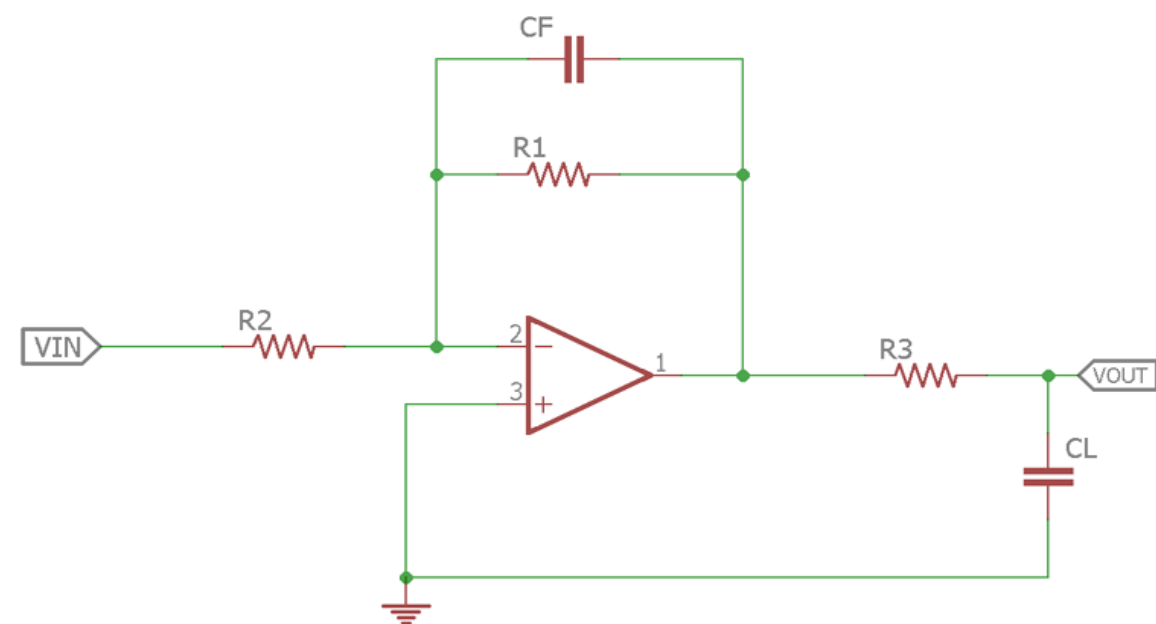
# Miller compensation



- Another effective compensation technique is the miller compensation technique and it is an in-loop compensation technique where a simple capacitor is used with or without load isolation resistor (Nulling resistor)
- a capacitor is connected in the feedback loop to compensate the op-amp frequency response
- also , a capacitor is connected to the feedback with a resistor across the output
- The circuit is a simple negative feedback amplifier with inverting gain dependent on R1 and R2
- The R3 is the null resistor and the CL is the capacitive load across the op-amp output
- CF is the feedback capacitor which is used for the compensation purposes
- The Capacitor and the resistor value depend on the type of amplifier stages, pole compensation, and the capacitive load





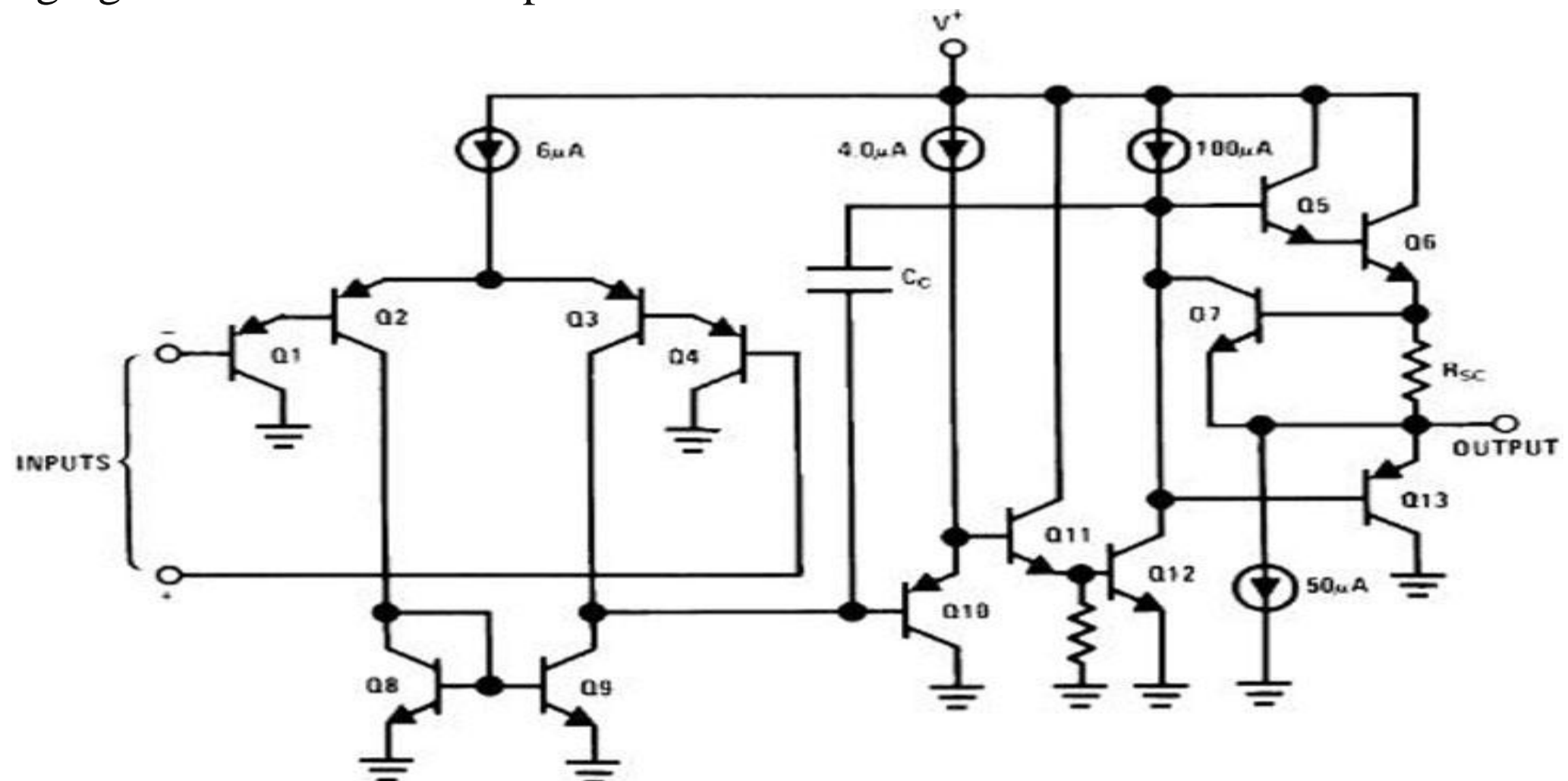
# Internal Frequency Compensation Techniques



- Modern operational amplifiers have internal compensation technique
- In the internal compensation technique, a small feedback capacitor is connected inside of the op-amp IC between the second stages Common emitter transistor
- For example, the below image is the internal diagram of popular op-amp LM358
- The  $C_c$  capacitor is connected across the  $Q_5$  and  $Q_{10}$ . It is the compensation Capacitor ( $C_c$ )
- This compensation capacitor improves the stability of the amplifier and as well as prevent the oscillation and ringing effect across the output







**THANK YOU**