



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade (III Cycle)
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB202 – LINEAR INTEGRATED CIRCUITS


II YEAR/ IV SEMESTER
1

UNIT 2 – APPLICATIONS OF OPERATIONAL AMPLIFIERS

TOPIC 2 – V to I and I to V convertor





Guess?????

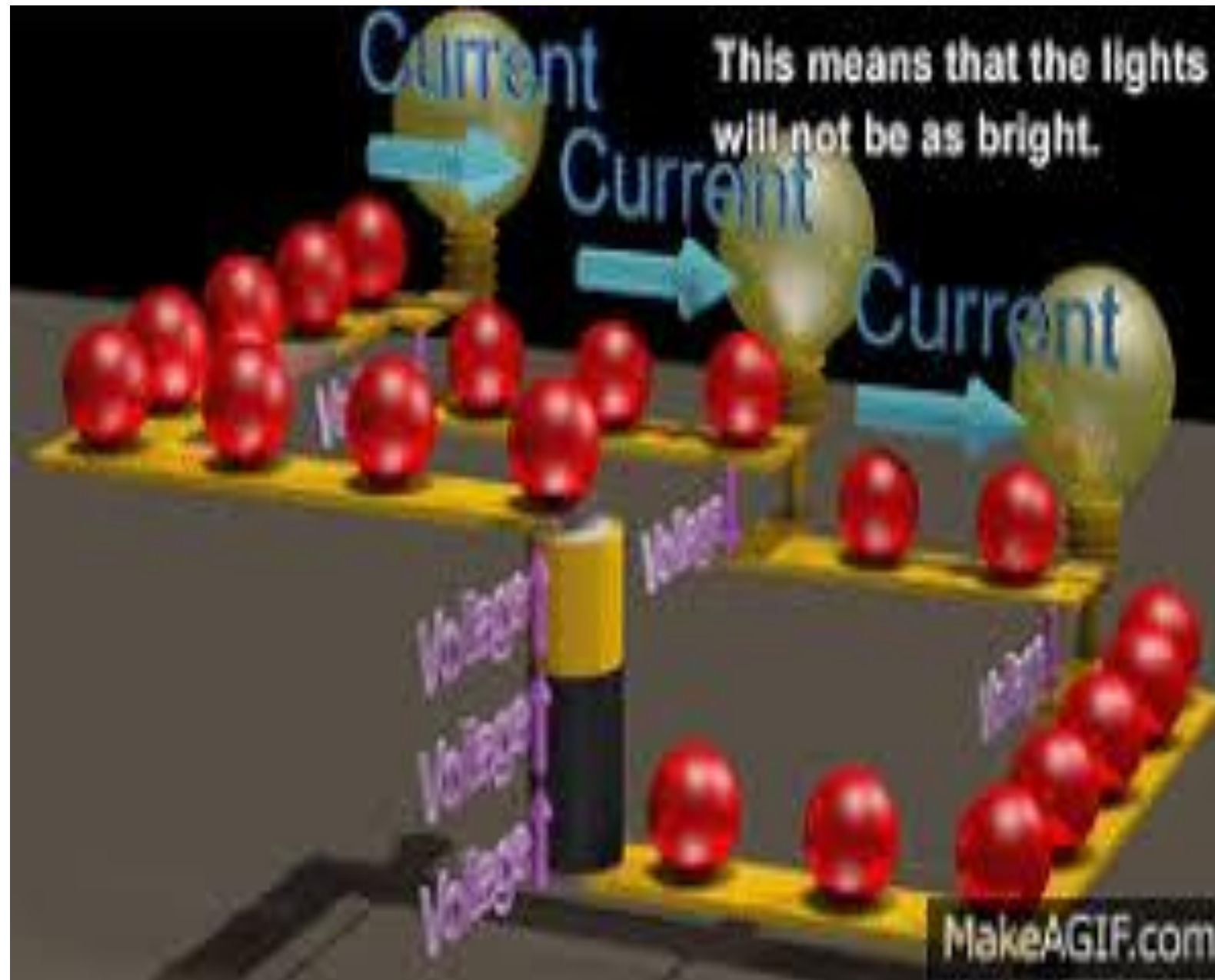



Why?

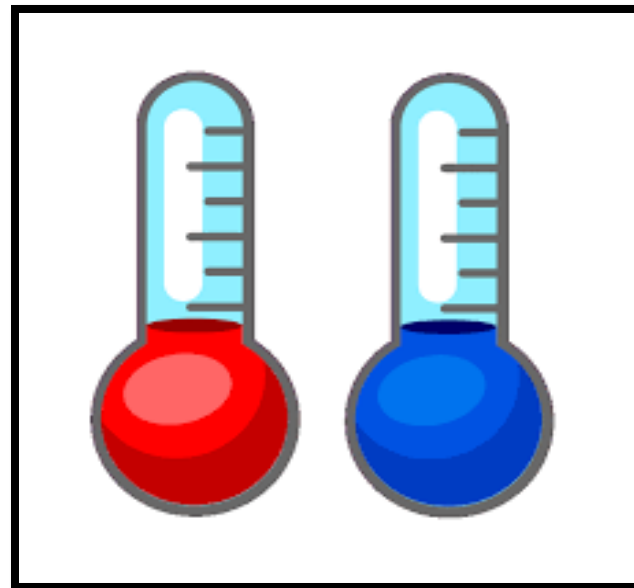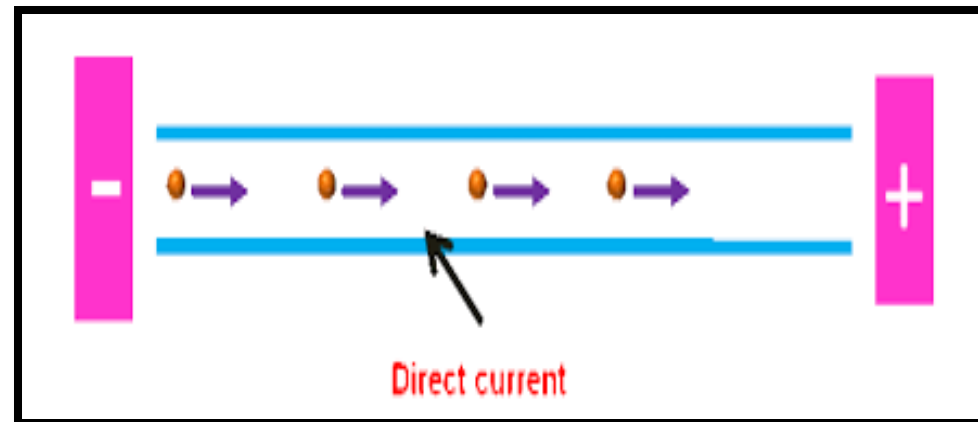


- In instrumentation circuitry, DC signals are often used as analog representations of physical measurements
- Temperature, pressure, flow, weight, and motion
- DC current signals will be constant throughout the circuit in series from the source to the load
- The current sensing instruments also have the advantage of less noise



Why?



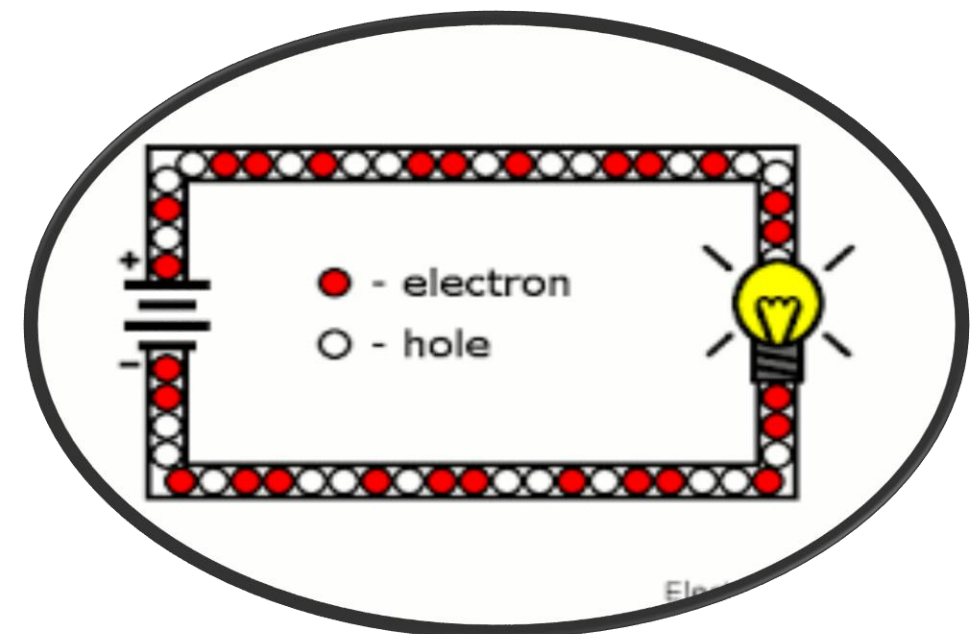- So sometimes it is essential to create current which is corresponding or proportional to a definite voltage.
- **Voltage to Current Converters** (also known as V to I converters) are used.
- It can simply change the carrier of electrical data from voltage to current.





Voltage to Current Converter



- ❑ A voltage to current (V-I) converter accepts as an input a voltage V_{in} and gives an output current of a certain value
- ❑ In general the relationship between the input voltage and the output current is

$$I_{out} = SV_{in}$$


Where S is the sensitivity or gain of the V-I converter



Voltage to Current Converter




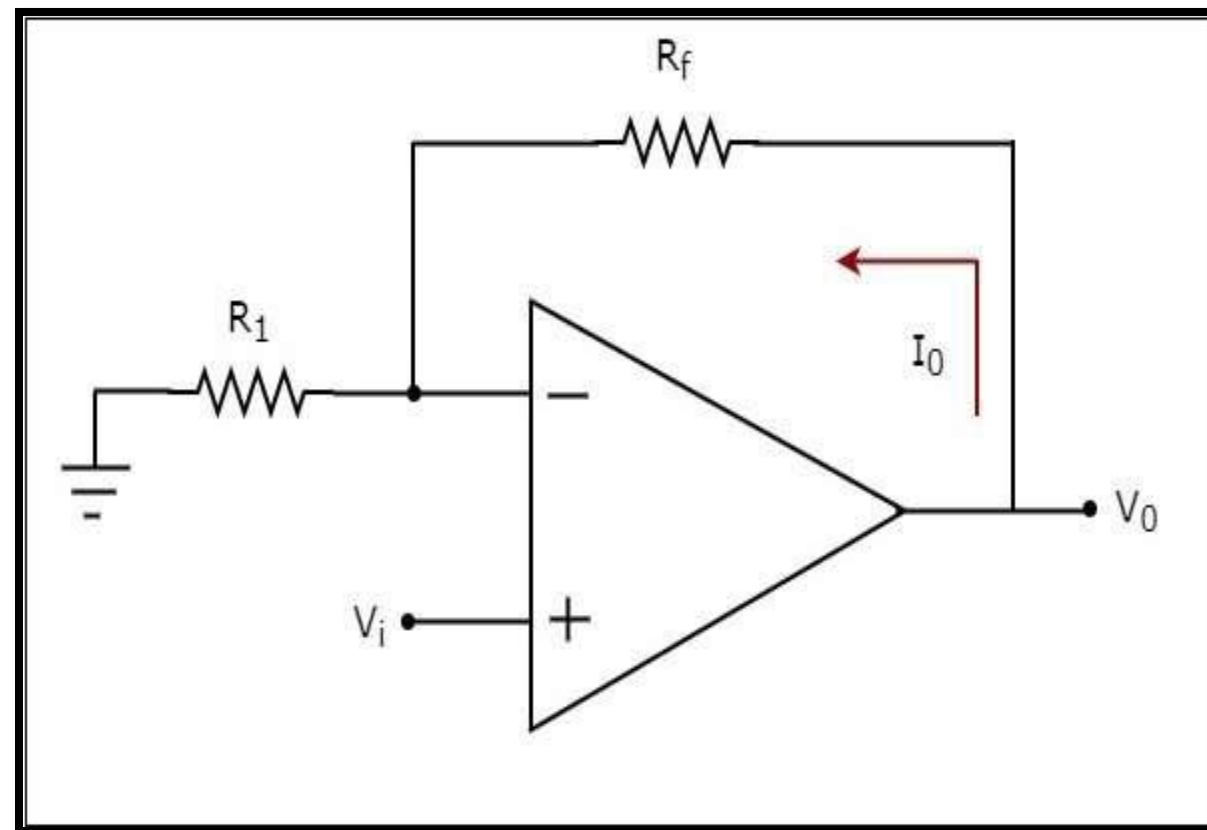- An op-amp based voltage to current converter produces an output current when a voltage is applied to its non-inverting terminal
- The **circuit diagram** of an op-amp based voltage to current converter is shown in the following figure





Activity

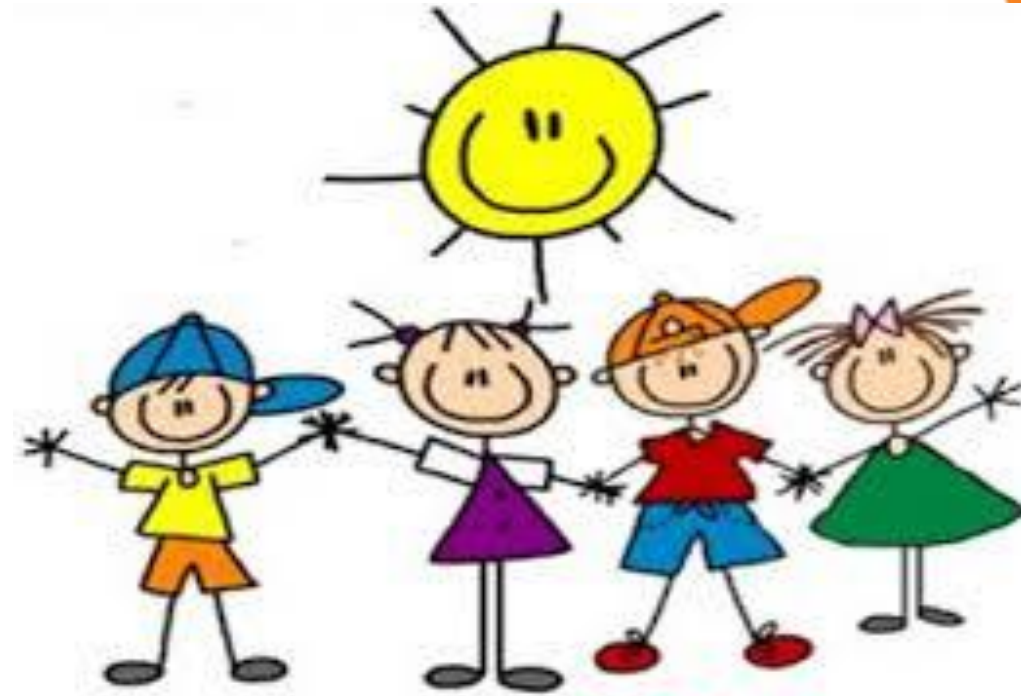

In class activity

$$\text{Green Circle} + \text{Green Circle} = 10$$

$$\text{Green Circle} \times \text{Yellow Square} + \text{Yellow Square} = 12$$

$$\text{Green Circle} \times \text{Yellow Square} - \text{Red Triangle} \times \text{Green Circle} = \text{Green Circle}$$

$$\text{Red Triangle} = ?$$



Voltage to Current Converter



- In the circuit shown above, an input voltage V_i is applied at the non-inverting input terminal of the op-amp
- According to the **virtual short concept**, the voltage at the inverting input terminal of an op-amp will be equal to the voltage at its non-inverting input terminal .
- So, the voltage at the inverting input terminal of the op-amp will be V_i
- The **nodal equation** at the inverting input terminal's node is

$$V_i / R_1 - I_0 = 0$$

$$I_0 = V_i / R_1$$



Voltage to Current Converter




➤ Thus, the **output current** I_0 of a voltage to current converter is the ratio of its input voltage V_i and resistance R_1

$$I_0 / V_i = R_1$$

- The above equation represents the ratio of the output current I_0 and the input voltage V_i & it is equal to the reciprocal of resistance R_1
- The ratio of the output current I_0 and the input voltage V_i is called as **Transconductance**.
- Gain of an voltage to current converter is the Transconductance and it is equal to the reciprocal of resistance R_1



Current to Voltage Converter

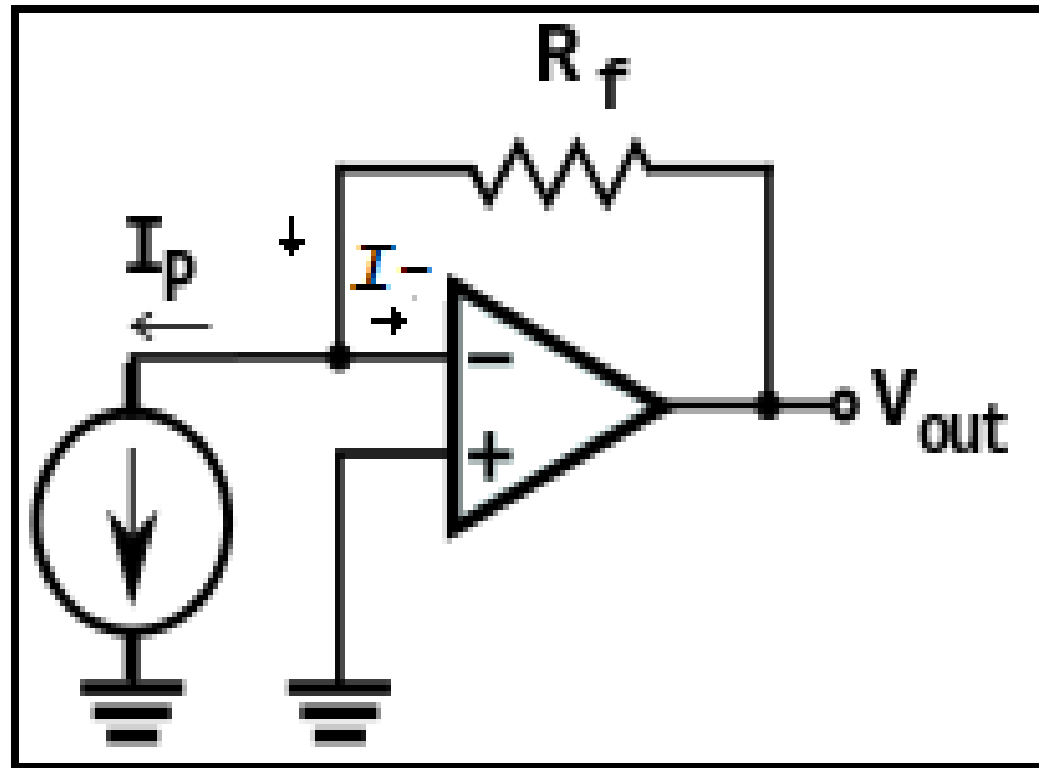

➤ A current to voltage converter will produce a voltage proportional to the given current.

➤ To analyse the current to voltage converter

➤ If apply KCL to the node at V- (the inverting input) and let the input current to the inverting input be I-, then

$$\square V_{out} - V / R_f = I_p + I$$



Current to Voltage Converter



The output is connected to V- through R_f

The opamp is in a negative feedback configuration

$$V_- = V_+ = 0$$

and assuming that I_- is 0 and simplifying

$$V_{out} = I_p R_f$$



Sensitivity



Sensitivity of the I – V converter:

1. The output voltage $V_0 = -R_F I_{in}$
2. The gain of this converter is equal to $-R_F$. The magnitude of the gain (i.e) is also called as sensitivity of I to V converter
3. The amount of change in output volt ΔV_0 for a given change in the input current ΔI_{in} is decide by the sensitivity of I-V converter
4. By keeping R_F variable, it is possible to vary the sensitivity as per the requirements



Assessment



1.State the need for V to I convertor



THANK YOU