

Department of Electrical and Electronics Engineering

ANALOG ELECTRONIC CIRCUITS / 19EET202

Important Questions (14 Marks)

UNIT I

1. Explain the structure and operation of PN junction diode with a neat sketch
2. Illustrate the difference between of PN diode and zenar diode. Discuss the RB operation of a zenar diode
3. Elaborate the operation of a full wave rectifier with a neat circuit and necessary waveforms
4. Discuss in detail the operation of (i) LED, (ii) Photo diode
5. Draw and explain with necessary circuit and waveform the working of clipper and clamper circuits
6. Describe the operation and application of PV cell

UNIT II

7. Describe the static input and output characteristics of a CE transistor with neat circuit diagram.
8. Explain the construction and working of FET with a neat sketch

9. Discuss with diagram, the structure and operation of MOSFET

10. Discuss with diagram, the structure and operation of SCR

11. Explain with necessary graph, the special application of UJT

12. Elaborate the structure of IGBT and also discuss its characteristics

UNIT III

13. Draw and explain with block diagram the IC fabrication process

14. Discuss in detail about photo-lithography process and Diffusion in manufacturing of monolithic IC

15. Illustrate the BJT fabrication process with relevant diagrams

16. Discuss how ICs are classified.

17. Draw and explain the working of seven segment display and LCD

18. Explain the purpose and operation of opto coupler devices

UNIT IV

19. List out different configurations of differential amplifier? Discuss with neat-labeled diagram for dual input, balanced output.

20. Describe in detail about transformer coupled class A amplifier

21. Evaluate the working of class B push pull amplifier

22. Discuss about multi stage amplifier and darling pair connection

23. Describe the working of Schmitt trigger using transistor.

24. With neat sketch describe the working of Astable multivibrator and find out the expression for time period and frequency of oscillation

UNIT V

25. State the advantages of negative feedback amplifier

26. Illustrate the with block diagrams, voltage series and current parallel feedback systems

27. Design and test the RC phase shift oscillator

28. Discuss with neat circuit diagram the working of colpitts oscillator

29. Discuss with neat circuit diagram the working of wien bridge oscillator

30. Explain with neat circuit diagram the working of crystal oscillator